

# INDIAN INSTITUTE OF TECHNOLOGY

DATE 9/08/16

EXPERIMENT No. 2

SHEET NO 12

OBJECTIVE:-

- (I) Verification of Maximum power theorem and Reciprocity theory.  
Verification of Maximum power theorem when the resistance and reactance of the load can be varied individually and separated.

APPARATUS REQUIRED:-


S.No.	Apparatus Name	Quantity	Range/Specifications
1.	AC Source	1	8V
2.	Resistors	2	100-200 $\Omega$
3.	Inductor	1	248mH.
4.	Variable Capacitor (Capacitance box)	1	upto 20 $\mu$ F
5.	Capacitors	1	2 $\mu$ F
		1	8 $\mu$ F
		1	10 $\mu$ F
		1	21.6 $\mu$ F.
6.	RLC-Multimeter	1	
7.	Multimeter	1	
8.	Connecting Wires		
9.	Rheostats	2	0-85 $\Omega$
		3	0-185 $\Omega$
		2	0-1180 $\Omega$ .

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO 13

## CIRCUIT DIAGRAM

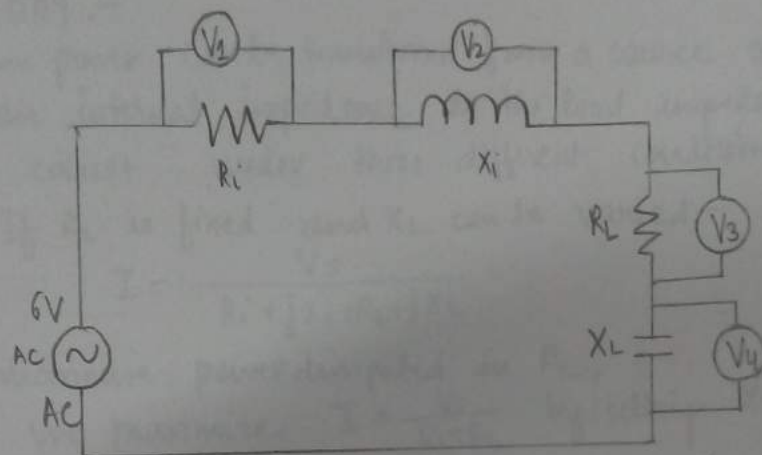



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 14

## THEORY:-

Maximum power can be transferred from a source of given voltage and an internal impedance to the load impedance  $Z_L$  in the circuit under three different conditions:-

- (a) If  $R_L$  is fixed and  $X_L$  can be varied:-

$$I = \frac{V_s}{R_i + jX_i + R_L + jX_L}$$

To maximise power dissipated in  $R_L$ ,

we maximize  $I = \frac{V_s}{R_i + R_L}$  by setting  $X_i = -X_L$

- (b) If  $X_L$  is fixed and  $R_L$  can be varied:-

$$P = |I|^2 R_L = \frac{V_s^2 R_L}{(R_i + R_L)^2 + (X_i + X_L)^2}$$

At max power

$$\frac{dP}{dR_L} = 0 \Rightarrow \frac{-1}{P^2} \frac{dP}{dR_L} = 0 \Rightarrow \frac{dP^2}{dR_L} = 0$$

$$\text{Hence, } \frac{d}{dR_L} \left\{ \frac{(R_i + R_L)^2 + (X_i + X_L)^2}{V_s^2 \times R_L} \right\} = 0$$

$$\Rightarrow \frac{1}{V_s^2} \left\{ \frac{-R_i^2}{R_L^2} + \frac{2R_i + 1}{R_L} \right\} + \frac{(X_i + X_L)^2}{V_s^2} \left( -\frac{1}{R_L^2} \right) = 0$$

$$\Rightarrow R_L = \sqrt{R_i^2 + (X_i + X_L)^2}$$

- (c) If both  $R_L$  and  $X_L$  are adjustable:-

Then both the above solutions are simultaneously valid.

Hence,  $X_i = -X_L$  and  $R_L = R_i$

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 15

## OBSERVATIONS:-

•  $L = 248 \text{ mH}$

•  $R_{in} = 60.3 \Omega$

•  $R_L = 100.2 \Omega$

• Expected value of  $C = \frac{1}{4\pi^2 f^2 L} = 40.86 \mu\text{F}$

•  $V_{in}/V_s = 8.81 \text{ V}$

•  $C_1 = 8.35 \mu\text{F}$

•  $C_2 = 10.2 \mu\text{F}$

•  $C_3 = 2.1 \mu\text{F}$

•  $C_4 = 20.2 \mu\text{F}$

TABLE-I

Sl. No.	C ( $\mu\text{F}$ )	$V_1$ (V)	$V_2$ (V)	$V_1, V_3$ (Volt <sup>2</sup> )	Max. Value ( $V_1 V_3$ ) (Volt <sup>2</sup> )
1.	10.3	2.158	3.666	<del>9.92</del> 7.911	
2.	11.4	2.271	$\approx 3.851$	8.746	
3.	12.4	2.360	4.000	9.44	
4.	13.5	2.420	4.100	<del>9.92</del> 9.92	
5.	14.6	2.448	4.153	<del>9.92</del> 10.166	
6.	15.6	2.452	4.167	10.217	
7.	16.7	2.458	4.168	10.245	
8.	<del>17.7</del> 17.7	2.440	4.127	10.069	
9.	18.7	2.449	4.102	10.025	
10.	19.8	2.421	4.091	9.904	
11.	20.8	2.408	4.067	9.793	
12.	21.8	2.38	4.06	9.663	
13.	28.7	2.255	3.821	8.616	
14.	29.7	2.226	3.790	8.436	

$10.24 \text{ Volt}^2$

at

$C = 16.7 \mu\text{F}$

$X_C = 190.60 \Omega$

Enter calculation?




Topic :

Graph-1 (variable C, fixed R)

Date :

Scale: X-axis  $\rightarrow 1 \text{ s.d.} = 0.2 \mu\text{F}$

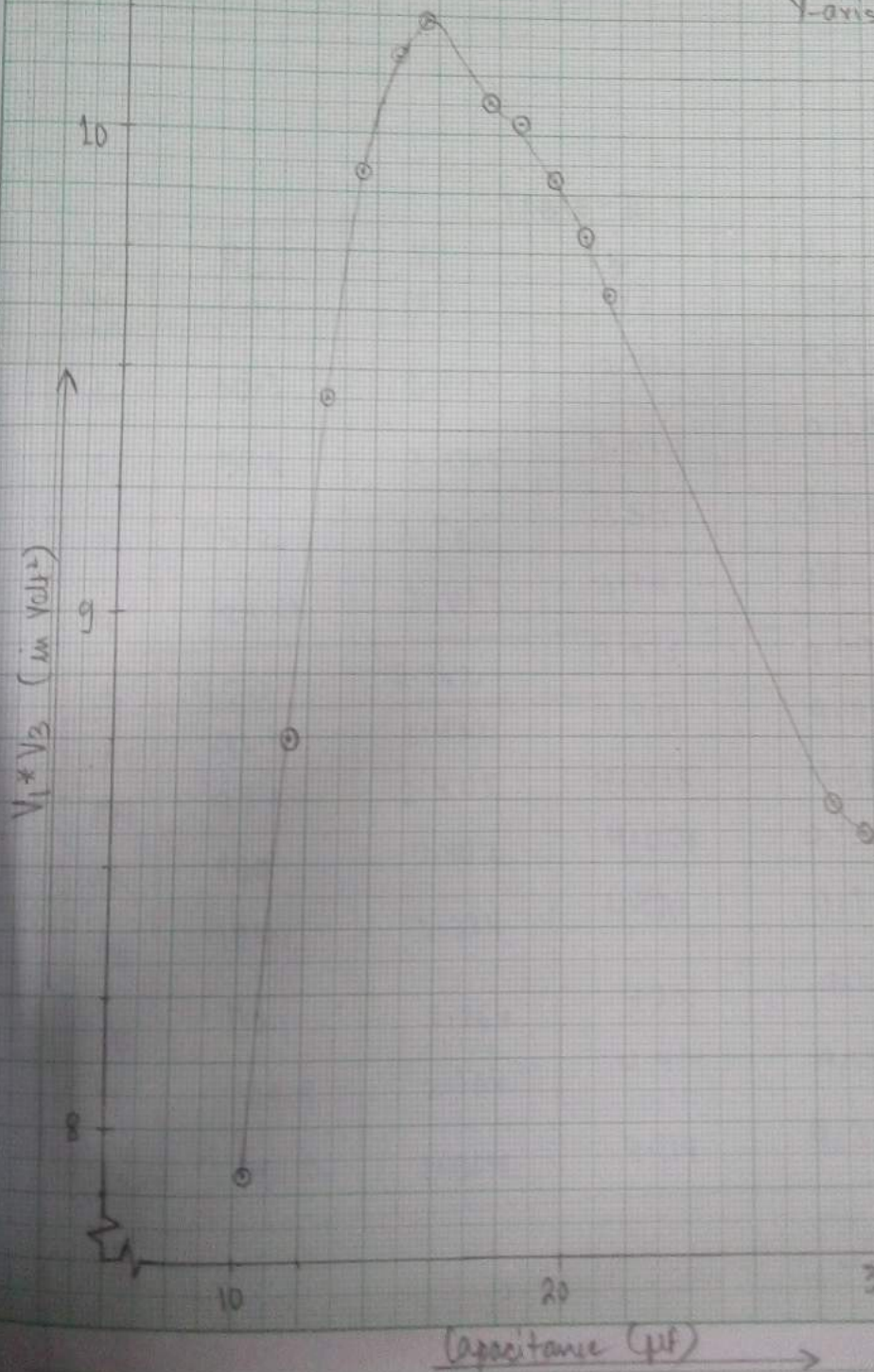Y-axis  $\rightarrow 1 \text{ s.d.} = 0.0125 \text{ V}^2$



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 16

TABLE-II

Sl. No.	$R_L$ ( $\Omega$ )	$V_1$ (V)	$V_{Z_0}$ (V)	$V_1 V_{Z_0}$ (V <sup>2</sup> )	Max. Value ( $V_1 V_{Z_0}$ ) (V <sup>2</sup> )
1.	50.3	3.263	2.750	8.973	<b>09.794</b> at $R_L = 95\Omega$
2.	59.8	3.045	3.060	9.318	
3.	75.2	2.763	3.53	9.706	
4.	85.0	2.607	3.741	9.750	
5.	95.0	2.462	3.978	9.794	
6.	96.5	2.442	3.977	9.712	
07	98.3	2.405	4.025	9.680	
08	99.9	2.402	4.054	9.738	
09	105.1	2.334	4.170	9.733	
10.	110.1	2.264	4.231	9.579	
11.	119.9	2.164	4.414	9.552	
12.	140.0	1.984	4.714	9.352	




Topic: Graph-2 (Variable R, fixed C)

Date: \_\_\_\_\_

Scale: X-axis  $\rightarrow 1\text{cm} = 0.5\Omega$

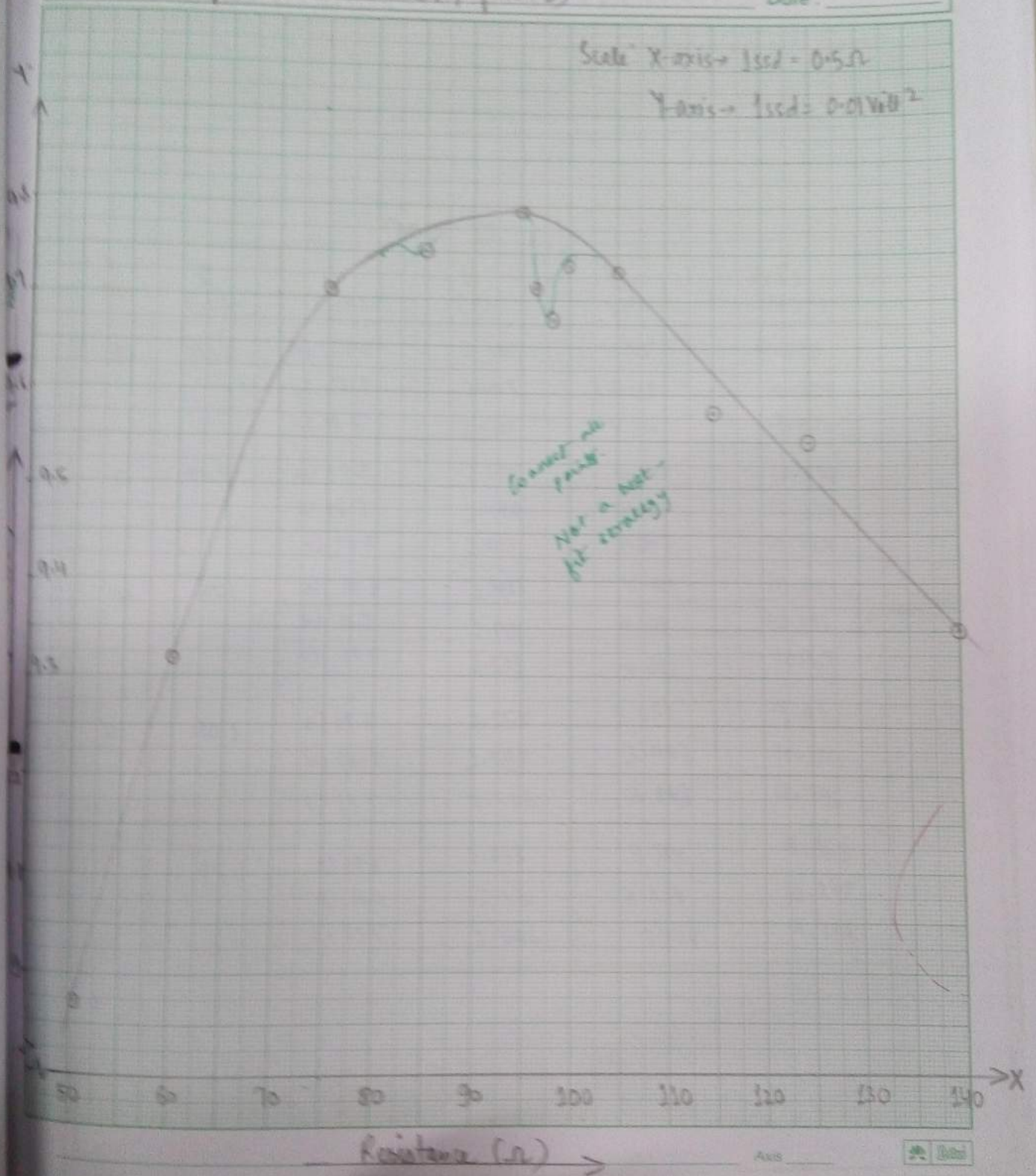Y-axis  $\rightarrow 1\text{cm} = 0.01\text{W}\Omega^2$



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 17

TABLE III

S. No.	R (Ω)	C (μF)	V <sub>1</sub> (V)	V <sub>3</sub> (V)	V <sub>1</sub> V <sub>3</sub> (V <sup>2</sup> )
1.	102.2	a) 14.8	2.382	4.145	9.873
		b) 16.7	2.427	4.218	10.237
		c) 18.5	2.570	4.136	9.802
2.	47.9	a) 14.8	2.458	4.097	10.070
		b) 16.7	2.498	4.155	10.379
		c) 18.5	2.471	4.097	10.124
3.	25.1	a) 14.8	2.488	4.025	10.014
		b) 16.7	2.544	4.104	10.441
		c) 18.5	2.503	4.022	10.067
4.	100.1	a) 14.8	2.555	3.883	9.921
		b) 16.7	2.588	3.957	10.241
		c) 18.5	2.536	3.863	9.796
5.	85.1	a) 14.8	2.633	3.784	9.963
		b) 16.7	2.672	3.854	10.298
		c) 18.5	2.606	3.749	9.769

← V<sub>1</sub> V<sub>3</sub> MAX



## DISCUSSION:-

### \* Verification of Maximum power theorem:-

#### 1. Sources of Error.

\* Contact resistance at joints and multimeter probes.

\* AC resistor of inductor (due to skin effect) was not added to the dc resistance we measured.

\* ~~Loose connections.~~

\* Measurement of inductor resistance:- We passed a dc current and measured the resistance across the inductor.

However, the method is not correct because ac circuit resistance differs from dc resistance because of proximity and skin effect, which are frequency dependent.

#### 2. Precautions:

\* The inductor should be kept at maximum distance from other circuit components as it may effect the power source or capacitance, resistance.

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 19

II Aim:-  
Verification of Reciprocity Theorem.

APPARATUS REQUIRED :-

S.No.	Apparatus Name	Quantity	Range / Specification
1.	Voltage Supply (AC)	1	
2.	Auto Transformer	1	270V-3A.
3.	Resistor (from Rheostat)	2	50 $\Omega$
		1	100 $\Omega$
		1	150 $\Omega$
		1	400 $\Omega$
4.	Ammeter	1	AC (MI)
5.	Multimeter/Voltmeter	1.	





# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 20

CIRCUIT DIAGRAM:-

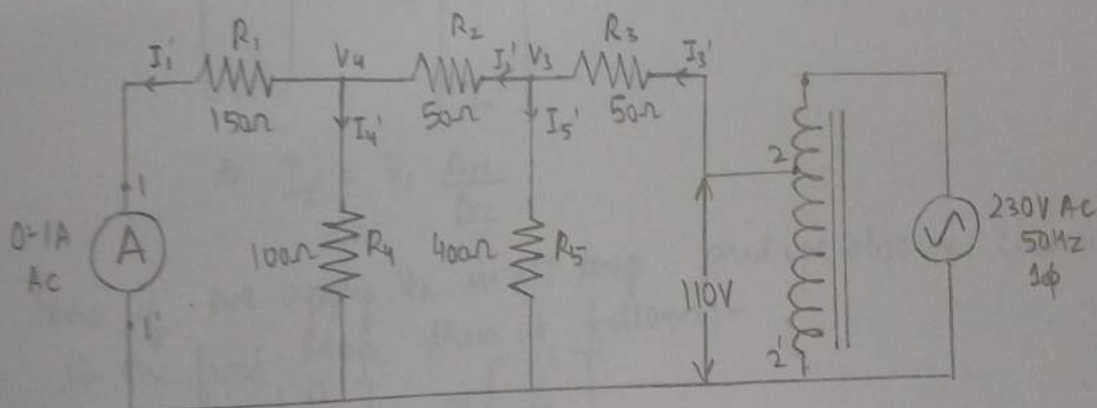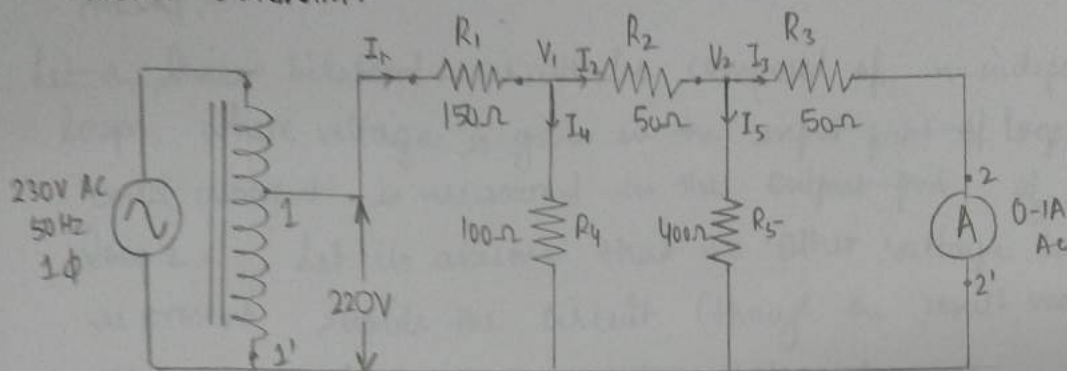

## THEORY:-

Let a linear bilateral circuit be composed of  $n$  independent loops, where voltage is given in the input port of loop 1 and current is measured in the output port of loop 2. Let us assume that no other voltage source is present inside the circuit (though the result would remain unchanged, and the additional voltages can be taken care of by superposition.) Hence it follows:-

$$\begin{bmatrix} V_1 \\ 0 \\ \vdots \\ 0 \end{bmatrix} = Z \begin{bmatrix} I_1 \\ I_2' \\ \vdots \\ I_n' \end{bmatrix}$$

$$\Rightarrow I_2' = V_1 \frac{\Delta_{12}}{\Delta Z}$$

Now if we apply  $V_2$  in 2nd loop and we observe current  $I_1$  in the first loop, then it follows:-

$$\begin{bmatrix} 0 \\ V_2 \\ \vdots \\ 0 \end{bmatrix} = Z \begin{bmatrix} I_1' \\ I_2 \\ \vdots \\ I_n \end{bmatrix}$$

$$\Rightarrow I_1' = V_2 \frac{\Delta_{21}}{\Delta Z}$$

Comparing,  $\frac{I_2'}{V_1} = \frac{I_1'}{V_2}$ . Thus the ratio of the response to the excitation is invariant to an interchange in position of excitation and response.



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 22

OBSERVATIONS:

$V_s(V)$	$I_3(A)$	$V_s/I_3(V/A)$	$V_{s'}(V)$	$I_{1'}(A)$	$V_{s'}/I_{1'}(V/A)$
201.3	0.485	415.05	100.2	0.25	400.8

$$\frac{V_s}{I_3} \approx \frac{V_{s'}}{I_{1'}}$$

Percentage error

$$= \frac{415.05 - 400.8}{415.05} \times 100 = 3.433\%$$



## DISCUSSION:-

### \* Verification of Reciprocity Theorem.

#### → Sources of Error:-

\* The multimeters' internal resistance, which needs to be added to the circuit across 1-1' at one time & across 2-2' in the other time. However, for reciprocity theorem to be valid, the circuit must be unchanged. Only the position of voltage source and current distribution should change. Thus the result is erroneous.

\* Resistance becomes large at any point of loose contact - eg. the probes of multimeter or any loose connection. Thus, unless the circuit is perfect, the distribution of resistance do not become exact.

#### → Branch Analysis:-

##### (i) First case.

$$V = 201.3V$$

$$\begin{aligned} R_{eq} &= 150 + (100 \parallel (50 + (400 \parallel 50))) \\ &= 150 + (100 \parallel (50 + \frac{8}{9} \times 50)) \\ &= 150 + (100 \parallel (\frac{17}{9} \times 50)) \\ &= 150 + 340\Omega \\ &= 198.57\Omega \end{aligned}$$

$$I_1 = \frac{V}{R_{eq}} = \frac{201.3}{198.57} = 1.01374A$$



DATE

SHEET NO 24

$$\therefore I_2 = I_1 \times \frac{100}{100 + \frac{17}{2} \times 50}$$

$$= 0.521 \text{ A}$$

$$\therefore I_3 = I_2 \times \frac{400}{450}$$

$$= 0.463 \text{ A} \rightarrow \text{Theoretical}$$

Practically Measured  $I_3 = 0.485 \text{ A}$ .

$$\therefore I_3 (\text{theoretical}) \approx I_3 (\text{practical})$$

(ii) Second case

$$V = 101.2 \text{ V}$$

$$R_{eq} = ((150 || 100) + 50) || 400 + 50$$

$$= (110 || 400) + 50$$

$$= 86.274 + 50$$

$$= 136.274$$

$$\therefore I_3' = \frac{V}{R_{eq}} = 0.74262 \text{ A}$$

$$\therefore I_2' = I_3' \times \frac{400}{510} = 0.58244 \text{ A}$$

$$\therefore I_1' = I_2' \times \frac{100}{250} = 0.233 \text{ A} \quad (\text{Theoretical})$$

$$I_1' (\text{practical}) = 0.250 \text{ A}$$

$$\therefore I_1' (\text{practical}) \approx I_1' (\text{theoretical})$$

$\frac{15}{219}$

# INDIAN INSTITUTE OF TECHNOLOGY

DATE 02/09/16

EXPERIMENT No. 3.

SHEET NO 25

## OBJECTIVE:-

To study Transient and frequency response of R-L-C series circuit.

## APPARATUS REQUIRED:-


S.No.	APPARATUS	QUANTITY	SPECIFICATIONS.
1.	FUNCTION GENERATOR	1	-
2.	Decade Resistance Box	1	Range: $2k\Omega$
3.	Inductor	1	<del>2k<math>\Omega</math></del>
4.	Capacitor	1	
5.	Cathode Ray Oscilloscope	1	




DATE

SHEET NO 26

CIRCUIT DIAGRAM:-

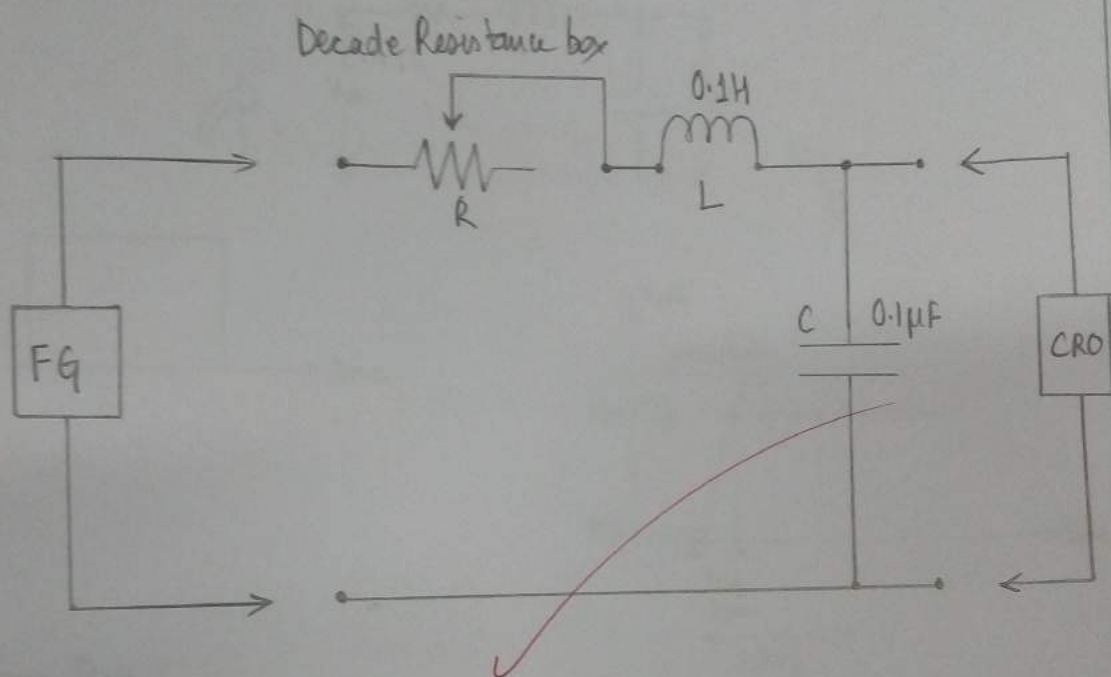

## THEORY :-

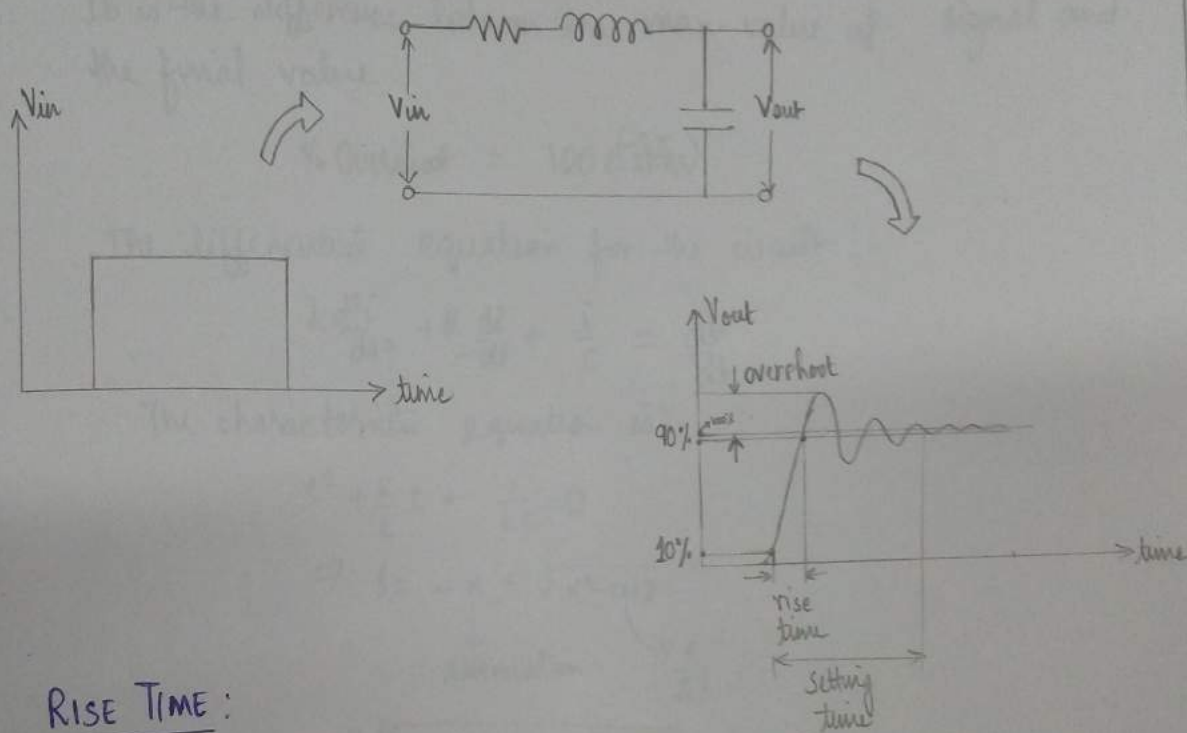

### RISE TIME :

It is the time taken by the signal to reach from 10% to 90% of its final value

$$\text{Rise time } t_r = \frac{1}{\omega_n \sqrt{1-\xi^2}} \left( \pi - \tan^{-1} \frac{\sqrt{1-\xi^2}}{\xi} \right)$$

### SETTING TIME :

It is the time taken by the signal to reach from 10% of its final value till it settles within 2% error band of its final value.

$$t_s = \frac{-\ln(\% \text{ of error band})}{\xi \omega_n}$$



### OVERSHOOT:

It is the difference between the max. value of signal and the final value.

$$\% \text{Overshoot} = 100 e^{\left(\frac{-\xi \pi}{\sqrt{1-\xi^2}}\right)}$$

The differential equation for the circuit :-

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = \frac{dv}{dt}$$

The characteristic equation is :-

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\Rightarrow s = -\underset{\substack{\downarrow \\ \text{attenuation}}}{d} \pm \sqrt{\alpha^2 - \omega_0^2}$$

$\searrow \frac{1}{\sqrt{LC}}$

$$\Rightarrow \xi = \frac{d}{\omega_0} = \frac{R}{2} \sqrt{\frac{C}{L}}$$

### GAIN:

$$\frac{V_c(j\omega)}{V_s(j\omega)} = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C} = \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\xi^2 \omega^2 \omega_0^2}} \angle \phi_c$$

$$\text{where } \tan \phi_c = \frac{-2\xi \omega \omega_0}{\omega_0^2 - \omega^2}$$

DATE

SHEET NO 28

## OVERSHOOT:

It is the difference between the max. value of signal and the final value.

$$\% \text{Overshoot} = 100 e^{\left(\frac{-\xi \pi}{\sqrt{1-\xi^2}}\right)}$$

The differential equation for the circuit :-

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = \frac{dv}{dt}$$

The characteristic equation is:-

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\Rightarrow s = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$\downarrow$  attenuation  $\searrow$   $\frac{1}{\sqrt{LC}}$

$$\Rightarrow \xi = \frac{d}{\omega_0} = \frac{R}{2} \sqrt{\frac{C}{L}}$$

## GAIN:

$$\frac{V_c(j\omega)}{V_s(j\omega)} = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C} = \frac{\omega^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\xi^2 \omega^2 \omega_0^2}} \angle \phi_c$$

where  $\angle \phi_c = \frac{-2\xi \omega \omega_0}{\omega_0^2 - \omega^2}$



DATE


SHEET NO 29

$$\frac{V_R(j\omega)}{V_S(j\omega)} = \frac{2\epsilon_y \omega_0 \omega}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\epsilon_y^2 \omega_0^2 \omega^2}} \angle \phi_R$$

where  $\phi_R = \pi - \tan^{-1} \left( \frac{2\epsilon_y \omega \omega_0}{\omega_0^2 - \omega^2} \right)$

$$\frac{V_L(j\omega)}{V_S(j\omega)} = \frac{\omega^2}{(\omega_0^2 - \omega^2)^2 + 4\epsilon_y^2 \omega^2 \omega_0^2} \angle \phi_L$$

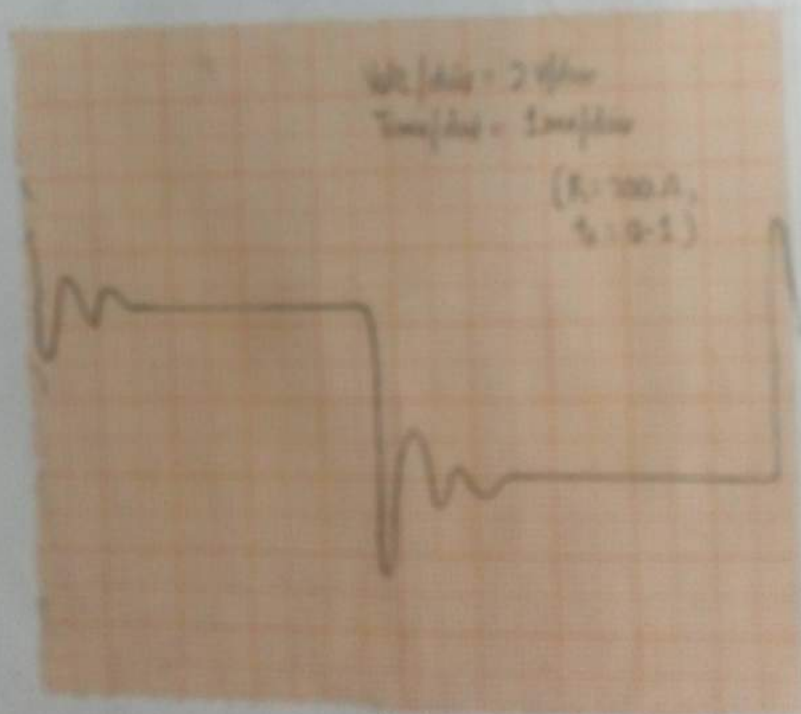where  $\phi_L = \pi - \tan^{-1} \left( \frac{2\epsilon_y \omega \omega_0}{\omega_0^2 - \omega^2} \right)$






$$\phi_1 = \frac{V_{in} \omega C}{1 + \omega^2 L^2 C^2}$$

$$\left( \frac{V_{in} \omega C}{1 + \omega^2 L^2 C^2} \right) \times 10^{-3} = \phi_1 \text{ mV}$$

$$\phi_2 = \frac{V_{in} \omega C}{1 + \omega^2 L^2 C^2}$$
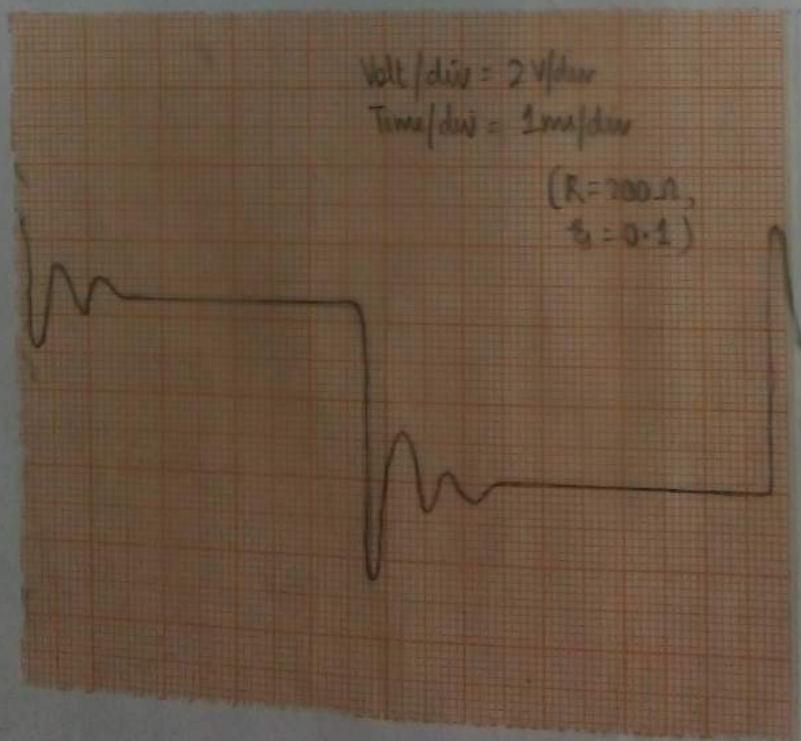
$$\left( \frac{V_{in} \omega C}{1 + \omega^2 L^2 C^2} \right) \times 10^{-3} = \phi_2 \text{ mV}$$



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 30

## OBSERVATIONS:-

$$C = 0.1 \mu F, \quad \alpha = 0.14$$

$$V_{\text{input}} = 2.06 \text{ V}$$

S.No.	$\xi$	$R$ (in $\Omega$ )	Voltage (in V)	Overshoot (in V)
1.	0.1	200	4.4	2.60
2.	0.2	400	4.4	1.80
3.	0.3	600	4.4	1.20
4.	0.5	1000	4.4	0.45
5.	0.7	1400	4.4	0.08
6.	0.8	1600	4.4	0.00

S.No	$\xi$	Theoretical % Overshoot	Actual % Overshoot
1.	0.1	72.92	59.09
2.	0.2	52.66	40.91
3.	0.3	37.23	27.27
4.	0.5	16.30	10.23
5.	0.7	4.60	1.82
6.	0.8	1.18	0



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 31


## FREQUENCY RESPONSE

$\beta = 0.5$ ,  $V_{in} = 4.6V$

S.No.	Frequency (in Hz)	$V_c$ (in V) ( $V_{out}$ )	Gain	Phase (in rad),
1.	50	4.6	1	0
2.	100	4.6	1	0
3.	300	4.6	1	0
4.	500	4.7	1.02	-0.377
5.	700	4.8	1.04	-0.528
6.	1000	5.2	1.13	-0.880
7.	1050	5.3	1.15	-0.923
8.	1100	5.4	1.17	-1.037
9.	1150	5.5	1.19	-1.084
10.	1200	5.4	1.17	-1.056
11.	1300	5.0	1.09	-1.225
12.	1400	4.5	0.98	-1.319
13.	1500	4.0	0.87	-1.508
14.	1700	3.5	0.76	-1.709
15.	2000	2.8	0.61	-2.011
16.	3000	1.2	0.26	-2.262
17.	4000	0.8	0.17	-3.016
18.	5000	0.4	0.09	-3.142


FREQUENCY RESPONSE

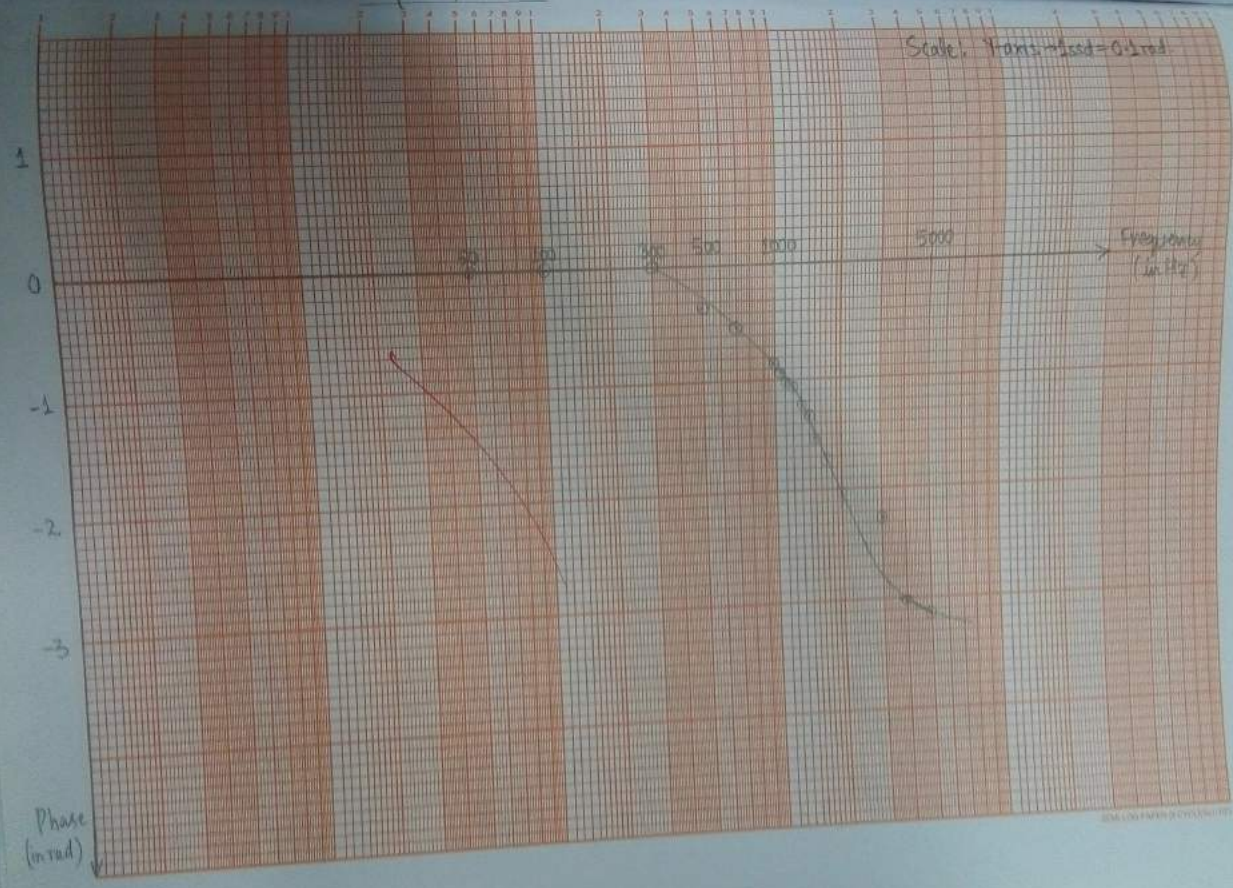Scale:  $V_{out}/V_{in} = 0.1 \text{ rad}$



Phase (in rad)



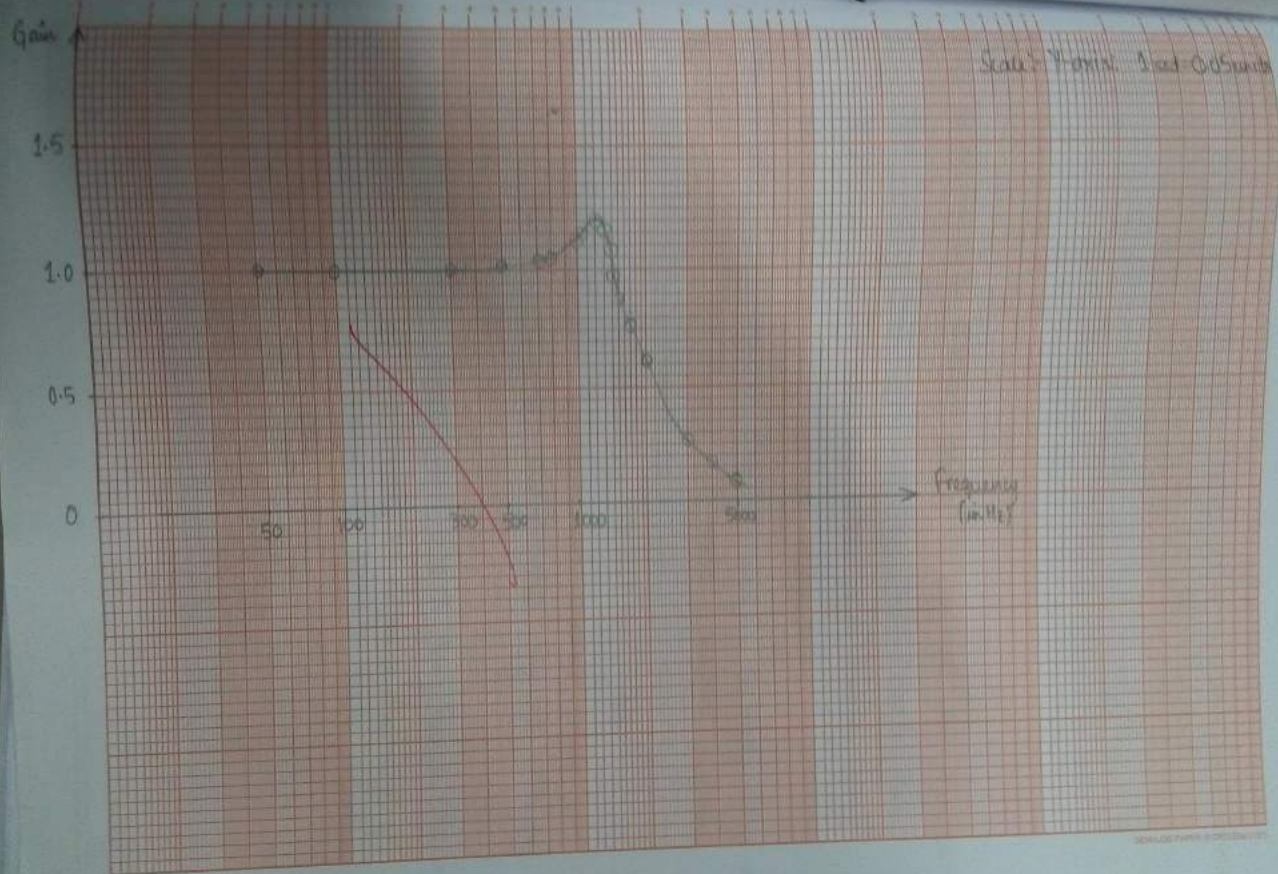

## DISCUSSION :

1. In the percentage overshoot part of the experiment, the theoretical and practical values may not have matched due to low precision in the instruments which might have been caused due to loose connections or user mishandlings.
2. The voltage across capacitor starts increasing from the supply voltage as we start from low frequency. It reaches a maxima and then asymptotically decreases to zero.

The theoretical value of maxima is  $115.47\%$  gain.

The theoretical value of freq. at which maxima occurs is  $\omega = 1.25 = 1125.39 \text{ Hz}$  and it tallies very well with the experimental values.

The phase angle decreases from  $0$  to  $-\pi$  going through  $-\pi/2$  at  $\omega = 1.25$  (Natural freq.). Experimentally we obtain a phase angle of  $-1.5$  radians at  $1.17$  radians at  $1300 \text{ Hz}$  &  $1700 \text{ Hz}$  respectively.

This confirms the predictions.

  
 20/11/20



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 32

## DISCUSSION :

\* In the percentage overshoot part of the experiment, the theoretical and practical values may not have matched due to loss of precision in the instruments which might have been caused due to loose connections or user mishandlings.

\* The voltage across capacitor starts increasing from the supply voltage as we start from low frequency. It reaches a maxima and then asymptotically decreases to zero.

The theoretical value of maxima is 115.47% gain.

The theoretical value of freq. at which maxima occurs is  $\omega \sqrt{1-2\xi^2} = 1125.39 \text{ Hz}$  and it tallies very well with the experimental values.

The phase angle decreases from 0 to  $-\pi$  going through  $-\pi/2$  at  $\omega \omega_0$  (Natural freq.). Experimentally we obtain a phase angle of  $-1.5$  radians  $-1.7$  radians at  $1500 \text{ Hz}$  &  $1700 \text{ Hz}$  respectively.

This confirms the predictions.

*[Signature]*  
20/7/20

P.R.E

P.R.E