

Module 4 : Pulse Circuits

1. a. Design an Astable Multivibrator using a 555-timer chip to operate at 30 KHz frequency with 50% duty cycle.
- b. Design a Monostable Multivibrator using a 555-timer chip for a positive (+) pulse width of 100 μ sec.