

**STUDIES ON ANALOG CIRCUITS USING OP-AMP:**

**AIM:** To study analog circuits using operational amplifiers.

**APPARATUS REQUIRED:**

- Printed circuit board
- DC power supply 12V
- AC signal generator
- Connecting wires
- Cathode Ray oscilloscope
- Multimeter.

**THEORY:**

Opamp stands for operational Amplifier.


It ideally has high input resistance and low output resistance. Thus, it takes less power from source due to high  $R_i$  and gives maximum power to external circuit due to low output resistance.

Hence it is more advantageous over BJT. in this domain. Also its gain is infinity (ideally) and thus it tends to reach maximum output value at less input voltages.

$I \rightarrow 0$  and thus,

$V^+$  is also called

virtual ground ( $V^+ \rightarrow 0$ )

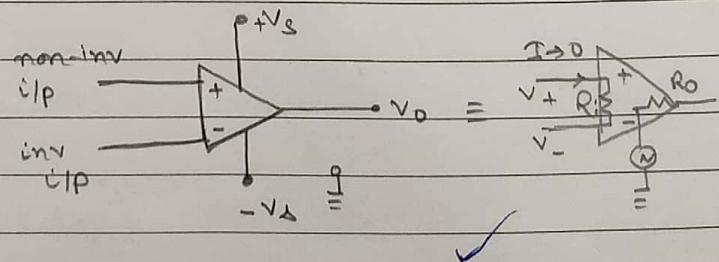

Teacher's Signature : \_\_\_\_\_

maximum voltage gap is the difference between  $V_{out\text{ (max)}}$  and  $V_s$ . For  $V_i = 12V$ ,  $V_{out\text{ (max)}}$  is generally  $\approx 9.5V$ .

The figure drawn in previous page shows opamp in open-loop circuit. It has uncontrolled gain. Thus, closed loop circuits are used to control gain.


→ Inverting amplifier

→ Non-inverting amplifier.

Inverting amplifier:


$$V_o = - \left( \frac{R_f}{R_i} \right) V_i$$

gain.

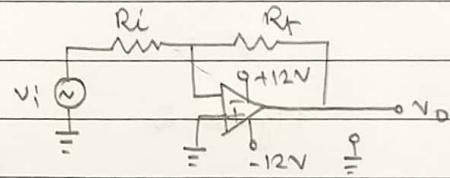

Non-inverting amplifier:
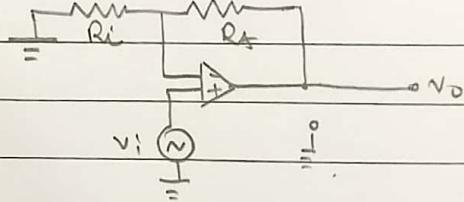
$$V_o = \left( 1 + \frac{R_f}{R_i} \right) V_i$$



The frequency responses of the two circuits are observed in this experiment.

Adder circuit is used to add a DC offset to a given  $V_i$ .

Integrator and differentiator circuits are used to manipulate input wave forms and give  $V_{out}$  according to equations:

$$V_{out} = - \left( 1/Rc \right) V_i dt + \text{const}$$

and

$$V_{out} = - R_i \times \frac{dV_{in}}{dt} \quad \text{respectively.}$$

## OBSERVATIONS AND CALCULATIONS :

I)  $V_4$  grounded (no-load voltages) :

Observed value at given terminals:

$$V_1 = 6.6V$$

$$V_2 = 3.35V$$

$$V_3 = 2.15V$$

-12V applied to  $V_4$ :

Observed value at given terminals:

$$V_1 = 1.12V$$

$$V_2 = -5.28V$$

$$V_3 = 7.66V$$

II) DC GAIN : (Inverting amplifier)


The OPAMP is set up in inverting configuration and bipolar supply is applied to power the opamp.

a)  $R_i^o = 10K\Omega$

| $R_f (K\Omega)$ | $V_{in}(V)$ | $V_{out}(V)$ | Observed gain<br>( $V_{out}/V_{in}$ ) | Theoretical gain<br>$(-R_f/R_i^o)$ |
|-----------------|-------------|--------------|---------------------------------------|------------------------------------|
| 10              | 0.850V      | - .850       | -1                                    | -1                                 |
| 27              | 0.848V      | - 2.29       | - 2.7                                 | - 2.7                              |
| 47              | 0.847V      | - 4.06       | - 4.793                               | - 4.7                              |
| 100             | 0.847V      | - 8.78       | - 10.366                              | - 10                               |

b) with  $R_i^o = 10K\Omega$  and  $R_f = 100K\Omega$ , we find voltage at inverting input (pin 2) is 15mV. This is negligible with respect to input and hence can be called virtual ground.

Teacher's Signature : \_\_\_\_\_

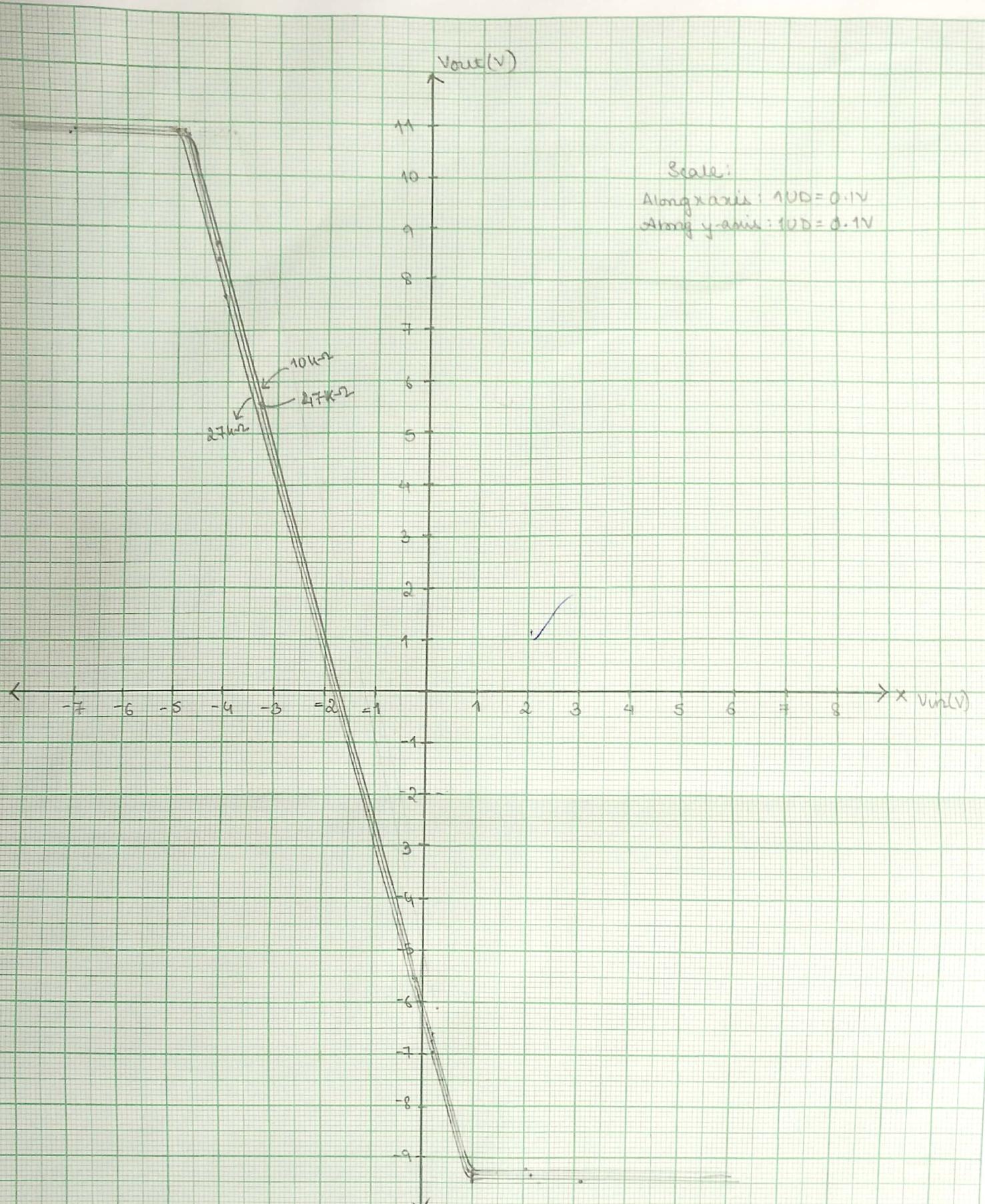

c) Calculation of input resistance :

Voltage across  $R_i$  ( $V_i$ ) = 0.856V,

and we have  $R_i = 10\text{ k}\Omega$ .

$$\text{Thus } I_i = \frac{0.856}{10 \times 10^3} \text{ A.}$$

$$\text{Now } R_{in} = \frac{V_{in}}{I_i} = \frac{0.847}{10 \times 10^3} \frac{10 \times 10^3 \times 0.847}{0.856} = 9.895 \text{ k}\Omega.$$

Thus we observe that  $R_{in}$  has a very close value to  $R_i$ .

$$R_f = 1\text{ k}\Omega$$

| $R_f (\text{k}\Omega)$ | $V_{in} (\text{V})$ | $V_{out} (\text{V})$ | $(-R_f/R_i) V_{in} (\text{V})$ |
|------------------------|---------------------|----------------------|--------------------------------|
| 10                     | 0.27                | -2.73                | -2.7                           |
| 27                     | 0.27                | -7.35                | -7.29                          |
| 47                     | 0.49                | -9.35                | -23.03                         |
| 100                    | 0.81                | -9.36                | -81.                           |

But, the OPAMP saturates when value of  $R_f \times V_{in}$  increases, since  $R_i$  is constant. It ceases to be linear after that. In this case, Opamp saturated with value of  $v_o = -9.37$ .

$$R_i = 10\text{ k}\Omega$$

| $R_f (\text{k}\Omega)$ | $V_{in} (\text{V})$ | $V_{out} (\text{V})$ | $(-R_f/R_i) V_{in} (\text{V})$ |
|------------------------|---------------------|----------------------|--------------------------------|
| 10                     | -4.24               | 4.22                 | 4.24                           |
| 27                     | -4.28               | 10.78                | 11.56                          |
| 47                     | -4.63               | 10.80                | 50.7621.761                    |
| 100                    | -4.94               | 10.84                | 49.4                           |

Teacher's Signature : \_\_\_\_\_


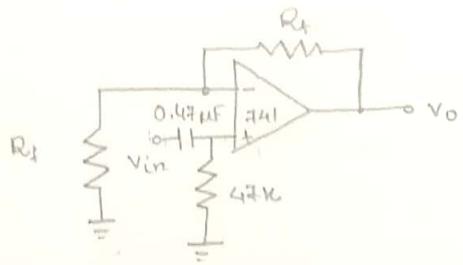


Figure-3

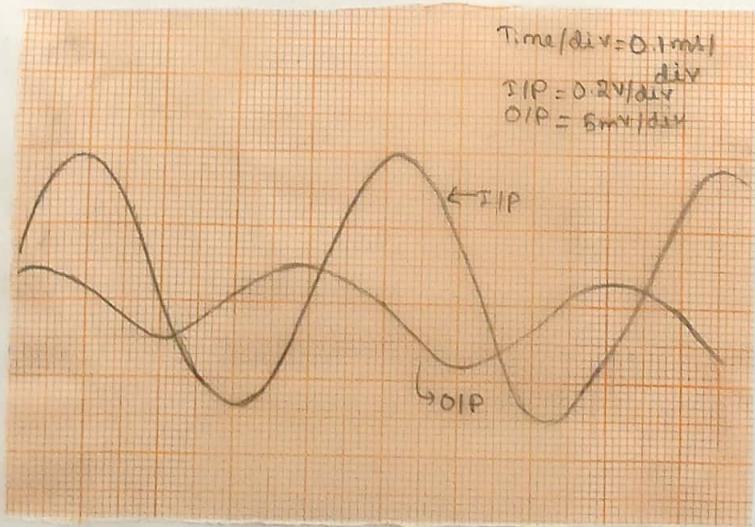

| $R_f$ ( $k\Omega$ ) | $V_{in}$ (V) | $V_{out}$ (V) | $(-R_f/R_i)V_{in}$ (V) |
|---------------------|--------------|---------------|------------------------|
| 10                  | -4.946.49    | 6.47          | 6.49                   |
| 27                  | -6.81        | 10.77         | 18.387                 |
| 47                  | -7.11        | 10.79         | 33.417                 |
| 100                 | -7.38        | 10.83         | 73.38                  |

As concluded from above two cases, voltage saturation level increased with increase in power supply voltage.

We also notice that Opamp saturates at  $V_o = 10.85$  V and -9.38 V.

### III) Non-Inverting Amplifier:

$A_i = 10 k\Omega$ ,  $R_f = 10 k\Omega$ . 1V p-p, 10KHz input is applied.


a) Gain :  $A_v = 1 + \frac{R_f}{R_i}$

| $R_f$ ( $k\Omega$ ) | $V_{out}$ (V p-p) | Expt gain<br>( $V_{out}/V_{in}$ ) | Theoretical gain<br>$(1 + \frac{R_f}{R_i})$ | % error |
|---------------------|-------------------|-----------------------------------|---|---------|
| 10                  | 2.23              | 2.23                              | 2   | 11.5%   |
| 27                  | 4.08              | 4.08                              | 3.7   | 10.2%   |
| 47                  | 6.48              | 6.48                              | 5.7   | 13.68%  |
| 100                 | 13.12             | 13.12                             | 11  | 10.2%   |

From the oscilloscope, we observe that output is not inverted.

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi \times 10^4 \times (0.47 \times 10^{-6})} = 33.862$$


frequency Response - I

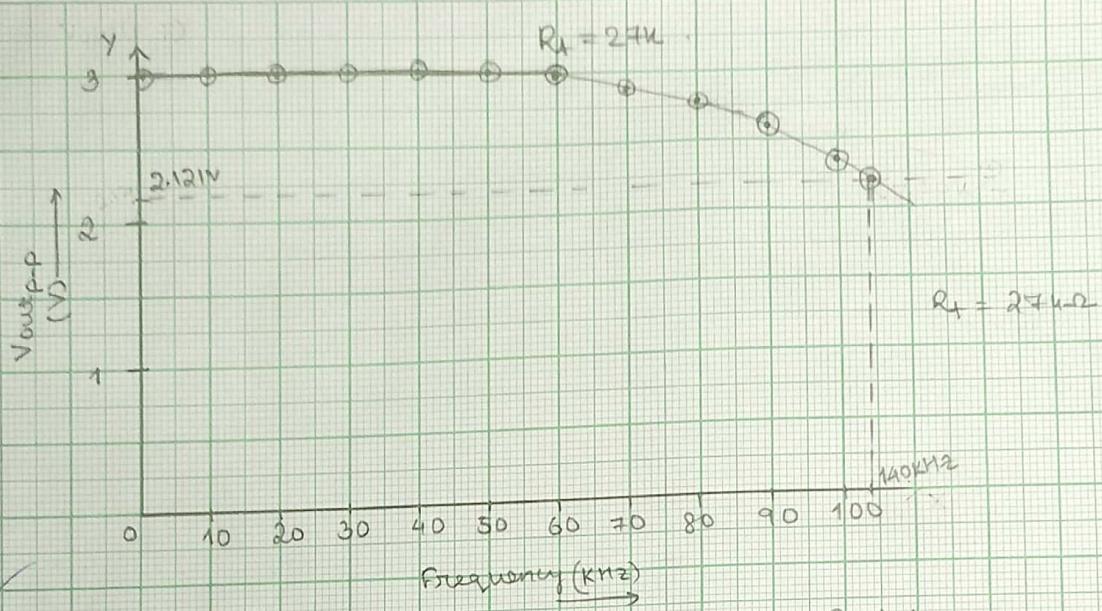

Scale:

Along x-axis  $\rightarrow 1\text{UD} = 1\text{kHz}$

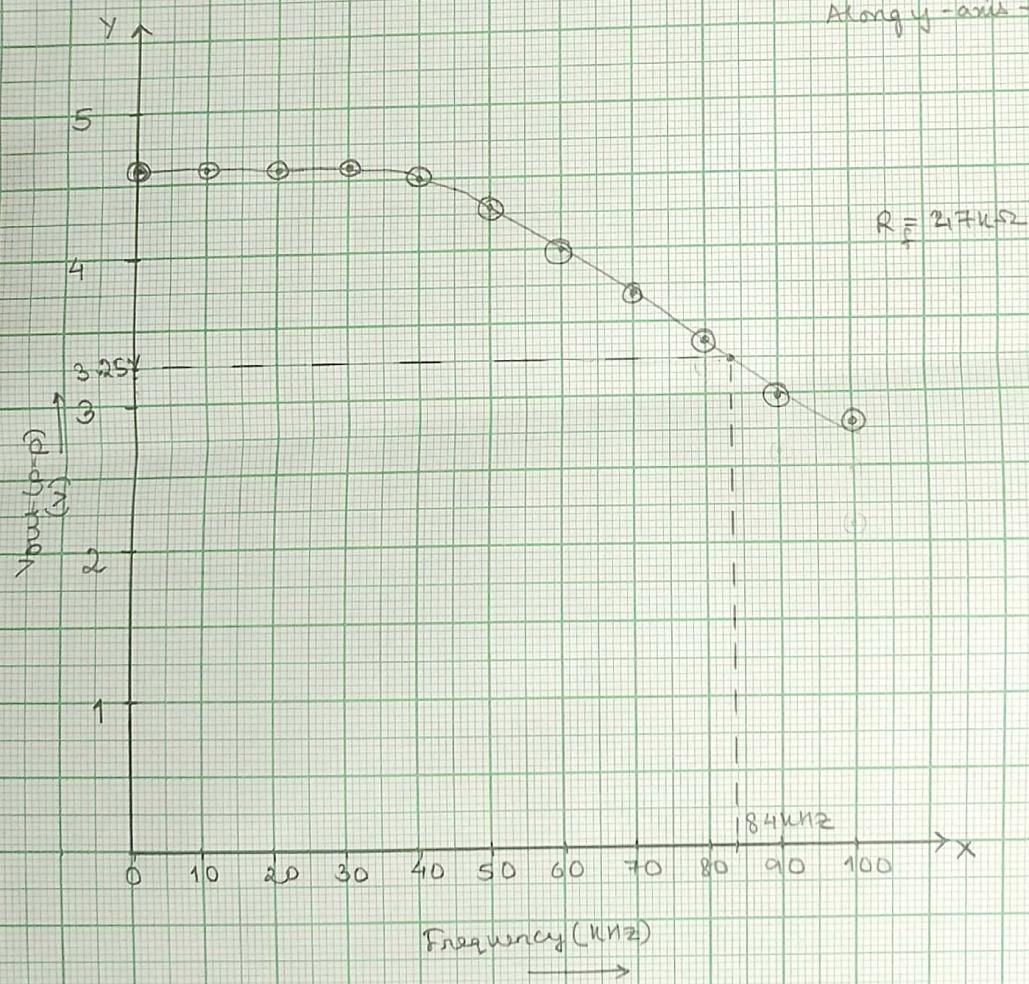Along y-axis  $\rightarrow 1\text{UD} = 0.05\text{V}$



Thus, value of capacitor impedance is negligible compared to values of resistors. Hence we consider them more-irrelevant for our gain calculations.


b) Frequency Response :

i)  $R_i = 10\text{k}\Omega$ ,  $R_f = 27\text{k}\Omega$ ,  $V_{in} = \frac{1}{15}\text{V (p-p)}$ .

| Frequency (kHz) | $V_{out\text{p-p}} (\text{v})$ | Gain ( $\text{V}_o/\text{V}_i$ ) |
|-----------------|--------------------------------|----------------------------------|
| 1               | 2.23                           | 4.43                             |
| 10              | 3                              | 4.43                             |
| 20              | 3                              | 3                                |
| 30              | 3                              | 3                                |
| 40              | 3                              | 3                                |
| 50              | 3                              | 3                                |
| 60              | 3                              | 3                                |
| 70              | 2.9                            | 2.9                              |
| 80              | 2.8                            | 2.8                              |
| 90              | 2.7                            | 2.7                              |
| 100             | 2.6                            | 2.6                              |

Teacher's Signature : \_\_\_\_\_

Frequency response : II

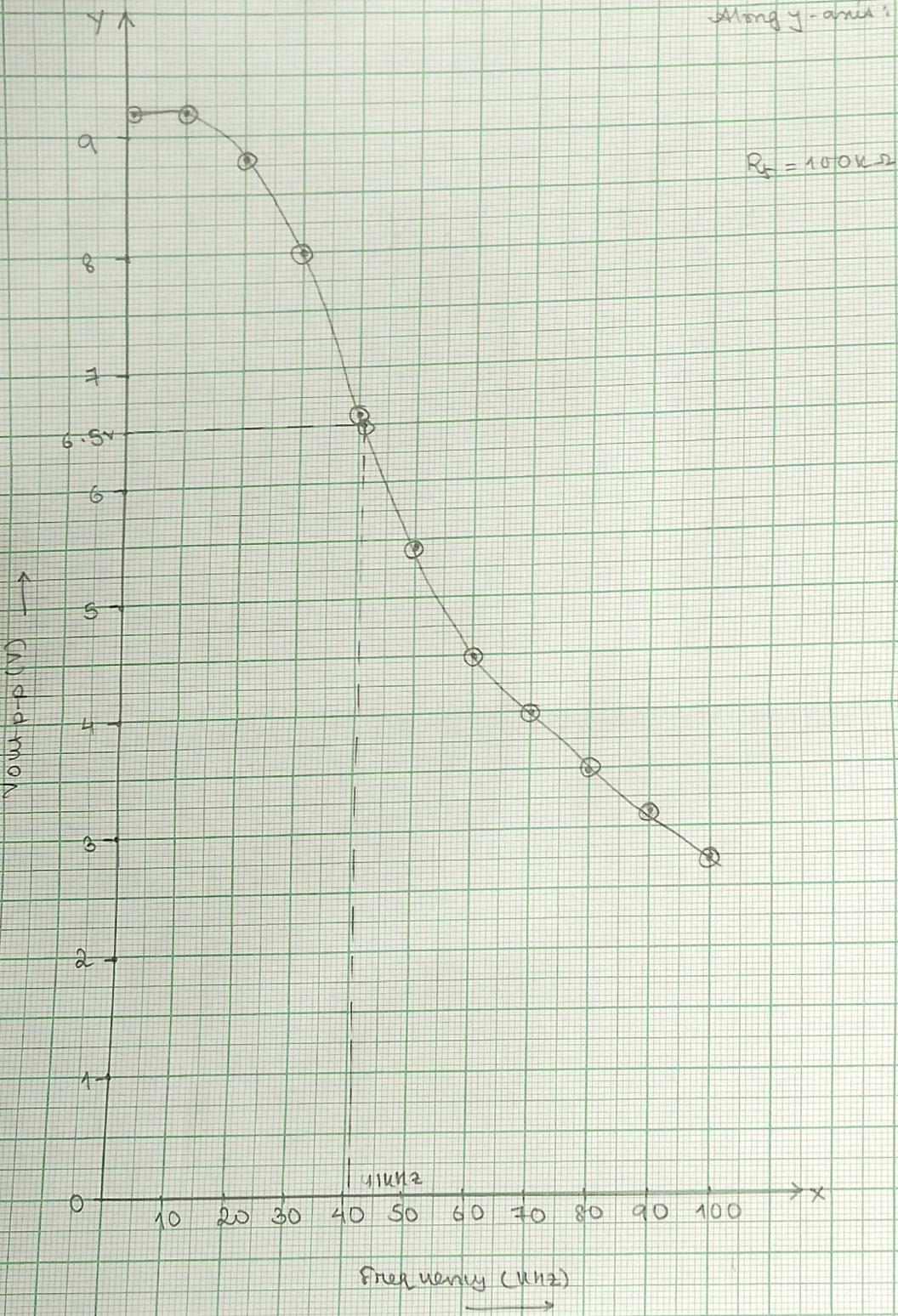

Scale:  
Along x-axis: 1 UD = 1 kHz  
Along y-axis: 1 UD = 0.05V

$$R_f = 100 \text{ k}\Omega$$

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

$$V_{out}(v) = \text{gain} (R_i = 1)$$

| Frequency | $R_f = 47\text{k}\Omega$ | $R_f = 100\text{k}\Omega$ |
|-----------|--------------------------|---------------------------|
| 1         | 4.6                      | 9.2                       |
| 10        | 4.6                      | 8.8                       |
| 20        | 4.6                      | 8                         |
| 30        | 4.6                      | 6.6                       |
| 40        | 4.5                      | 5.4                       |
| 50        | 4.3                      | 4.5                       |
| 60        | 4                        | 4                         |
| 70        | 3.7                      | 3.5                       |
| 80        | 3.4                      | 3.2                       |
| 90        | 3                        | 2.7                       |
| 100.      | 2.8                      | 2.3.                      |

$$R_i = 10\text{k}\Omega$$

$$R_f \quad \beta = \frac{R_i}{R_i + R_f} \quad \text{Gain}(A_f) \quad A_o = \frac{A_f}{1 - \beta A_f} \quad \text{B.W.} \quad \text{Gain} \times \text{B.W.}$$

$$27\text{k}\Omega \quad 0.27 \quad 2.121 \quad 4.96 \quad 140\text{kHz} \quad 296.94\text{kHz}$$

$$47\text{k}\Omega \quad 0.175 \quad 3.252 \quad 7.547 \quad 84\text{kHz} \quad 273.168$$

$$100\text{k}\Omega \quad 0.091 \quad 6.5044 \quad 15.94 \quad 41\text{kHz} \quad 266.5\text{kHz}$$

We measure B.W. by finding out frequency at which  $V_o = A_f$  (since  $R_i = 10$   $v_{in} = 1\text{V p-p}$ ), or by measuring from graph characteristics.

Teacher's Signature : \_\_\_\_\_

## IV Voltage follower :

$V_{in} = 1\text{V DC}$ .

No, inverting pin 2 is not at virtual ground.

| SL.NO. | $V_{in}$              | $V_{out}$ |
|--------|-----------------------|-----------|
| 1      | 1.112                 | 1.111     |
| 2      | <del>11.57</del> -7.8 | -7.78     |
| 3      | -5.32                 | -5.32     |
| 4      | 2.09                  | 2.08      |
| 5      | 3.41                  | 3.41      |

Thus, we observe that  $V_{out} = V_{in}$  at given  $V_{in}$  values.

The voltage divider system cannot provide  $V_{in}$  such that  $V_{out} \neq V_{in}$ . However for direct input of -12V and +12V supply, we get the following data:

$$\rightarrow V_{in}: 12.08 \} \text{maximum} \quad \rightarrow V_{in}: -12.03 \} \text{minimum}$$

$$V_{out}: 11.72 \quad V_{out}: -9.32,$$

## V) Adder:

$$V_1 = 2\text{V}, V_2 = 3\text{V}.$$

a) By theory,  $V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$ .

Observed value:  $V_1 = 1.53\text{V}$ ,  $V_2 = 2.53\text{V}$ .

$V_{out} = -3.96\text{V}$

Calculated value:  $-10 \left( \frac{1.53}{10} + \frac{2.53}{10} \right) = -4.06 \approx V_{out}(\text{observed})$ .



Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

b) Summing Amplifier :

$$V_1 = V_{in} = 1 \text{ V}_p-p \text{ at } 1 \text{ kHz.}$$

$$V_2 = V_{offset}.$$

| Sl. No. | V <sub>2</sub> (V) | V <sub>out</sub> (V <sub>p-p</sub> ) | DC offset (V) |            |
|---------|--------------------|--------------------------------------|---------------|------------|
|         |                    |                                      | Oscilloscope  | Multimeter |
| 1.      | 5.08               | 1.05                                 | + 5.37        | + 5.31     |
| 2.      | 2.72               | 1.07                                 | + 3           | 2.96       |
| 3.      | 1.84               | 1.09                                 | 1.8           | 1.92       |
| 4.      | 0.85               | 1.09                                 | 1             | 0.92       |
| 5.      | -4.27              | 1.11                                 | -5            | -4.97      |
| 6.      | -6.53              | 1.12                                 | -7            | -7.01      |

## VI Superposition :

| R <sub>f</sub> (kΩ) | V <sub>1</sub> (V) | V <sub>2</sub> (V) | Observed<br>V <sub>out</sub> (V) | Calculated<br>V <sub>out</sub> (V <sub>1</sub> +V <sub>2</sub> ) |
|---------------------|--------------------|--------------------|----------------------------------|--|
|                     | 3.12               | 0                  | -3.12                            | -3.12 + 4.09   |
| 10                  | 0                  | 2                  | 4.09                             | = 0.97   |
|                     | 3.08               | 1.98               | 0.87                             |  |
|                     | 3.2                | 0                  | -9.78                            | -9.78 + 10.98  |
| 47                  | 0                  | 2                  | 10.98                            | = 1.2  |
|                     | 3.08               | 1.98               | -3.31                            |  |
|                     | 3.2                | 0                  | -9.81                            | -9.81 + 11   |
| 100                 | 0                  | 2                  | 11                               | = 1.19   |
|                     | 3.08               | 1.98               | -9.26                            |  |

Thus, it does not hold for R<sub>f</sub> = 47 kΩ or 100 kΩ.

Teacher's Signature : \_\_\_\_\_

## b) Differential Amplifier:

$$V_{out} = V_2 \times \left[ \frac{R_3}{R_2 + R_3} \right] \left( 1 + \frac{R_f}{R_i} \right) - V_1 \left( \frac{R_f}{R_i} \right) \dots (i)$$

Also given,  $R_i = 10\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$ ,  $R_3 = 47\text{ k}\Omega$ .

$\therefore R_i = R_2$  and  $R_3 = R_f$ .  $\therefore$  from eqn (i), we have:

$$V_{out} = \frac{R_f}{R_i} (V_2 - V_1)$$

$R_f = 27\text{ k}\Omega$ :

OBSERVED VALUES :  $V_1 = 2.08\text{ V}$      $V_2 = 3.28\text{ V}$      $V_{out} = 4.32\text{ V}$

$$\text{THEORETICAL : } V_{out} = 3.28 \left( \frac{47}{57} \right) (1 + 2.7) - 2.08 (2.7)$$

$$= 4.39\text{ V}$$

$R_f = 47\text{ k}\Omega$ :

OBSERVED VALUES :  $V_1 = 2.06\text{ V}$      $V_2 = 3.28\text{ V}$      $V_3 = 5.6\text{ V}$ .

$$\text{THEORETICAL : } V_{out} = (3.28 - 2.06) \times \frac{R_f}{R_i}$$

$$= 5.734\text{ V}$$

## VII Integrator : sine wave :

5kHz sine-wave of 1V p-p is applied and it is traced from CRO.


$$V_{out} = -(RC) V_{in} dt + \text{const.}$$

$$= - \left( \frac{1}{100 \times 10^3 \times 47 \times 10^{-8}} \right) \frac{0.5 \times Y}{5 \times 10^6} =$$

$$\text{Theoretical gain} =$$

$$\text{Observed gain} =$$

Teacher's Signature : \_\_\_\_\_

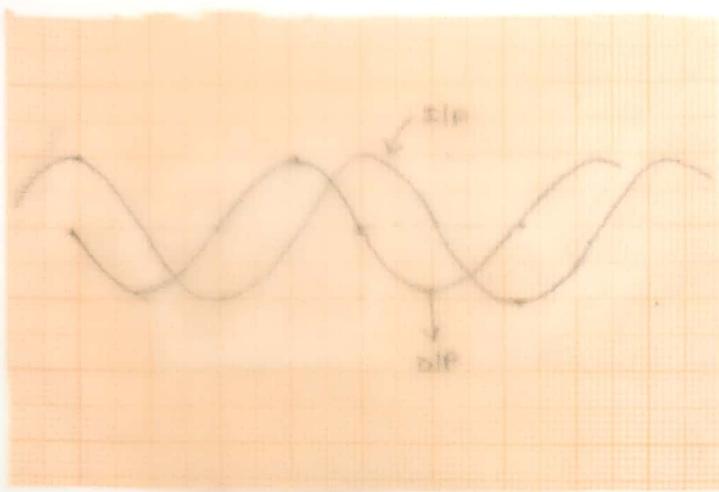


Sinewave:

$$T/div = 50\text{ }\mu\text{s/div}$$

$$T/P = 0.4\text{ V/div}$$

$$O/P = 5\text{ mV/div}$$

$$f = 5\text{ kHz}$$

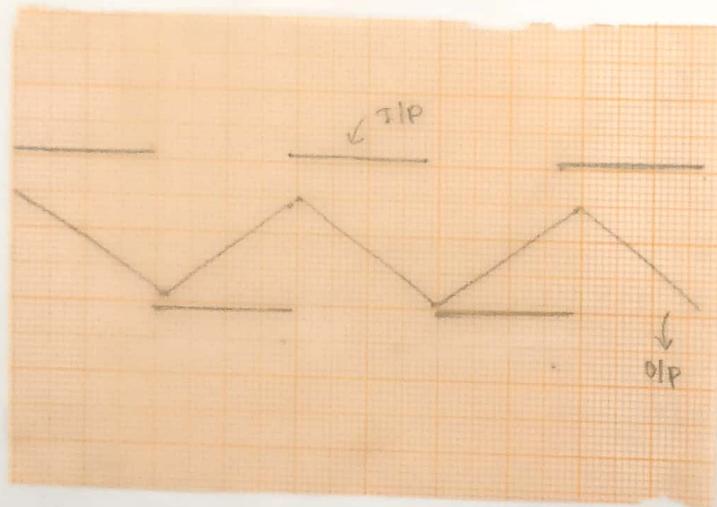

Squarewave:

$$Time/div = 50\text{ }\mu\text{s/div}$$

$$T/P = 0.5\text{ V/div}$$

$$O/P = 20\text{ mV/div}$$

$$f = 5\text{ kHz}$$

✓

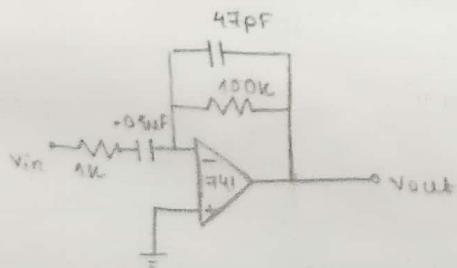


Figure-2

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

**Square wave :**

5 kHz square wave of 1Vp-p is applied.

$$V_{out} (\text{Theoretical}) = - \left( \frac{1}{100 \times 10^3 \times 47 \times 10^{-6}} \right) \frac{0.5 \times 1}{5 \times 10^3} = 21mV$$

observed  $V_{out} = 52mV$

$$V_{in} = 1Vp-p$$

| SL.NO. | Sine wave :     |                 | Square wave :   |                |
|--------|-----------------|-----------------|-----------------|----------------|
|        | Frequency (kHz) | $V_{out}$ (mV)  | Frequency (kHz) | $V_{out}$ (mV) |
| 1      | 1.01            | 50              | 1               | 52             |
| 2      | 2.0             | 30              | 1.5             | 38             |
| 3      | 3.5             | 15              | 2.31            | 24             |
| 4      | 4.19            | 9               | 2.87            | 20             |
| 5      | 5.82            | 9               | 3.9             | 15             |
| 6      | 7.5             | 7               | 5.23            | 12             |
| 7      | 8.91            | 6               | 7.28            | 8              |
| 8.     | 10.13           | 80 <del>5</del> | 10.13           | 5              |


**VIII Differentiator :****a) Square wave :**

0.2Vp-p, 1 kHz square wave is applied.


$$V_{out} = -RC \times (dV_{in}/dt)$$

cannot be calculated ( $dV_{in}/dt$ ) is not defined at edges.
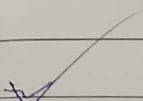
$$V_{out(\text{observed})} = 6.4V \text{ (overshoot)}$$



Teacher's Signature : \_\_\_\_\_

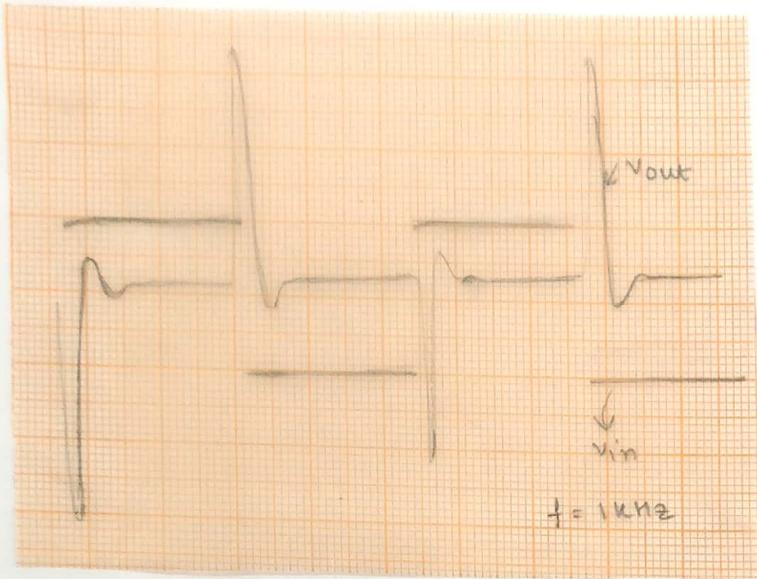


square wave :

Time 1 div =  $0.2 \text{ ms}/\text{div}$

T/P =  $0.1 \text{ V}/\text{div}$

O/P =  $2 \text{ V}/\text{div}$ .

✓

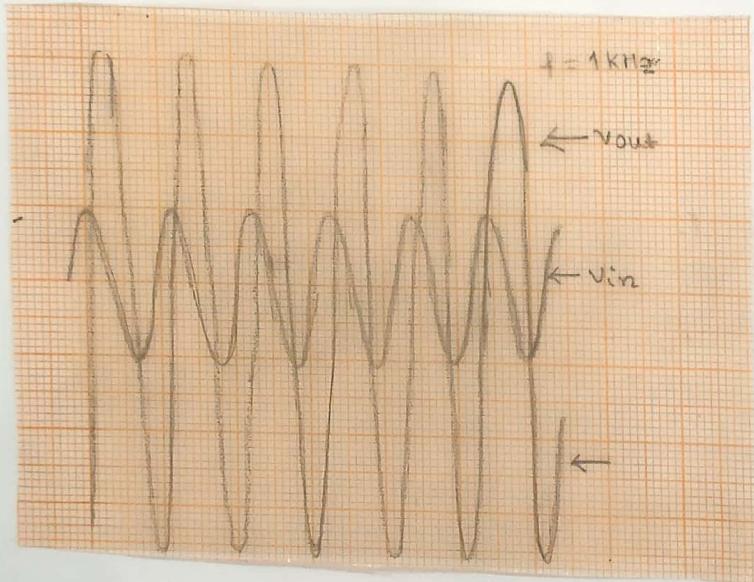


sine wave :

Time 1 div =  $1 \text{ ms}/\text{div}$ ,

T/P =  $0.1 \text{ V}/\text{div}$

O/P =  $0.1 \text{ V}/\text{div}$

✓

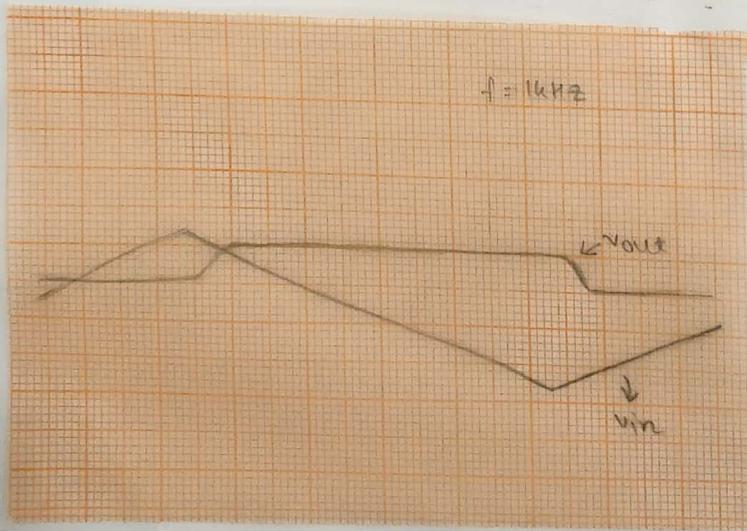

triangular wave:

Time 1 div =  $0.1 \text{ ms}/\text{div}$ .

T/P =  $0.1 \text{ V}/\text{div}$

O/P =  $1 \text{ V}/\text{div}$ .

✓

Sine wave :

0.2 V p-p is applied at 1 kHz.

$$V_{out} (\text{calculated}) = 1.663 \text{ V}$$

$$V_{out} (\text{observed}) = 1.32 \text{ V}$$

Triangular wave :


0.2 V p-p is applied at 1 kHz.

$V_{out} (\text{calculated})$  vary from  $\frac{\text{max}}{\text{min}}$  to  $\frac{\text{min}}{\text{max}}$  with change at max/min of triangular wave and constant otherwise.

$$V_{out} (\text{observed}) = 0.8 \text{ V}$$

Frequency Response :

| Sl.No. | Sine wave       |               | Square wave:    |               | Triangular wave: |               |
|--------|-----------------|---------------|-----------------|---------------|------------------|---------------|
|        | frequency (kHz) | $V_{out}$ (V) | frequency (kHz) | $V_{out}$ (V) | frequency (kHz)  | $V_{out}$ (V) |
| 1      | 1 kHz           | 1.32          | 1.02            | 6.4           | 1.017            | 0.8           |
| 2      | 2               | 2.65          | 2.34            | 6.4           | 2.06             | 2             |
| 3      | 3               | 3.2           | 3.15            | 6.4           | 3.02             | 3             |
| 4      | 4               | 5.3           | 4.48            | 7             | 5.01             | 5             |
| 5      | 5               | 7.7           | 6.65            | 7.2           | 6.97             | 7             |
| 6      | 6               | 8.2           | 8.34            | 7.4           | 8.95             | 9             |
| 7      | 7               | 9.2           | 10.0            | 6.6           | 10.74            | 9.2           |
| 8      | 8               | 10.4          |                 |               | 13.01            | 8.2           |
| 9      | 9               | 11            |                 |               |                  |               |
| 10     | 10              | 11.2          |                 |               |                  |               |

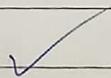

## DISCUSSION :

Swastika Datta  
(16CS10060)

Firstly a voltage divider was configured on the board. Then the opamp was set up in inverting configuration and  $V_{out\ (observed)}$  was compared with  $V_{out\ (calculated)} = -\frac{R_f}{R_i} V_i$ . The point of saturation of opamp was noted and graph was drawn. The effect of change of  $R_f$  and  $V_i$  was also observed.

Then the amplifier was set up in non-inverting configuration. The  $V_{out\ (calculated)} = \left(1 + \frac{R_f}{R_i}\right) V_i$  was calculated and compared to  $V_{out\ (observed)}$ . Higher current gain tends to 'roll-off' moreover since gain  $\times$  bandwidth remains constant for given setup and varying  $R_f$ .  $A_o$  was measured using observed value of  $A_f$ .

Voltage follower is used as a buffer amplifier to connect high-impedance source to low impedance load. We also observed that  $V_{in} \approx V_{out}$  and ground conditions of pin 2.

In addition,  $V_2 = V_{offset}$ , and we used formula:

$$V_o = R_f \left[ 2 \frac{V_i}{R_i} \right]$$

to calculate theoretical  $V_o$  and compare with observed  $V_o$ .

We then observed the applicability of superposition theorem on the circuit. It seems to be valid for higher values of  $R_f$  when amplifier gets in saturation mode.

Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

In differential amplifier, we calculated  $V_{out}$  using simplified formula :  $\frac{(R_f)}{R_u} (V_2 - V_1)$  and compared it with observed  $V_o$ .

In integrator circuit, we traced the waveforms of corresponding I/P O/P signals for square wave and sine wave.

$$V_{out} = -\frac{1}{RC} \int v_{in} dt + \text{const.}$$

This was compared to observed values. Also frequency response of both square wave and sine waves were recorded.

Again for differential circuit, we supply 0.2 Vpp input to sine wave, square waves and triangular waves respectively.

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

Square waves and triangular waves are not differentiable at points and that has been observed in corresponding O/P waveforms in CRO. Also, we noticed 90° phase shift between I/P and O/P waveform for sine waves in both integrator and differentiator circuits.

✓  
 10  
 10 ~~kbb~~

Teacher's Signature : \_\_\_\_\_



Discussion:-

By Chelsi Rathya

16CS10013

- An operational amplifier is a DC coupled high gain electronic voltage amplifier with a differential input and usually a single ended output.
- In voltage divider circuit, we observed slightly lesser value when it is connected to required load due to loading effect.
- In inverting part we got values close to theoretical values and when  $R_i = 10K\Omega$ ,  $R_f = 100K\Omega$  we observed that voltage at inverting pin 2 to be 0, i.e., virtual ground condition.
- As we increased power supply values, we observed saturation voltage level has increased.
- At high frequency, capacitor acted as short circuit.
- In adder circuit, the result we obtained on addition was slightly different from estimated value.
- While increasing frequency, current gain begins to roll off sooner and for higher values of  $R_f$ , higher gain was observed. Thus bandwidth decreases with increasing  $R_f$  &  $A_o$  increases with increasing  $R_f$ .

Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

- Superposition theorem was found only true for small  $R_f$ . For larger  $R_f$ , linear option is not valid as amplifier come in saturation mode.
- In differential amplification part we observed  $V_{out}$  was directly proportional to difference of inputs.

✓ ~~9.5~~ ~~10~~ jbf

Teacher's Signature : \_\_\_\_\_