

Tutorial Sheet 3 (Transient)

1. The switch in the circuit of Fig.1 is closed at $t = 0$. Before that the circuit was in steady state. Assuming that the inductance is ideal, find the current through the inductor at $t = 10$ s.

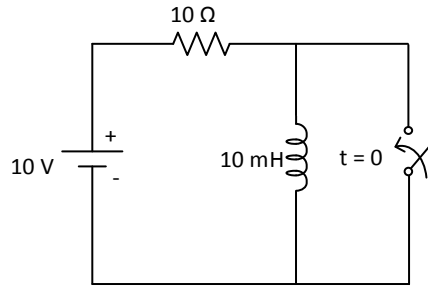


Fig. 1

2. The switch in Fig.2 was in open condition for a long time and closed at time $t = 0$. Find current i_{AB} as function of time thereafter.

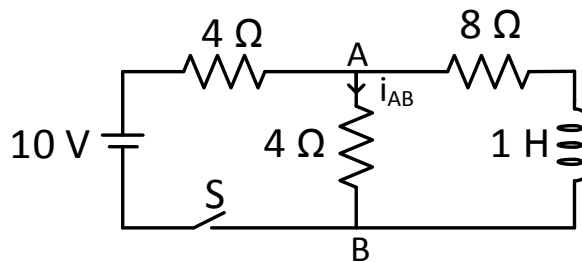


Fig. 2

3. The circuit in Fig.3 was in steady-state for $t < 0$, and the switch is opened at $t = 0$. Find the voltage V_x at $t = 100 \mu\text{s}$.

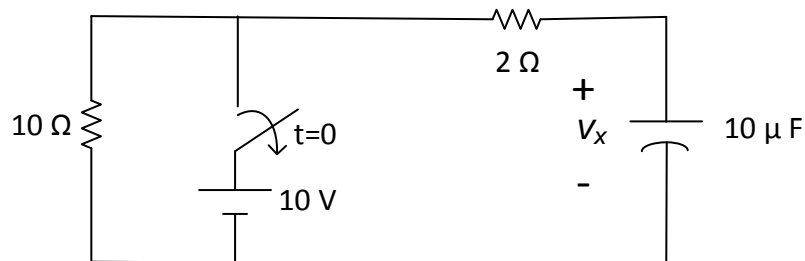


Fig. 3

4. The circuit in Fig.4 was in steady-state for $t < 0$, and the switch is closed at $t = 0$. Find the values of i_L , i_1 and i_2 at $t = 20$ sec.

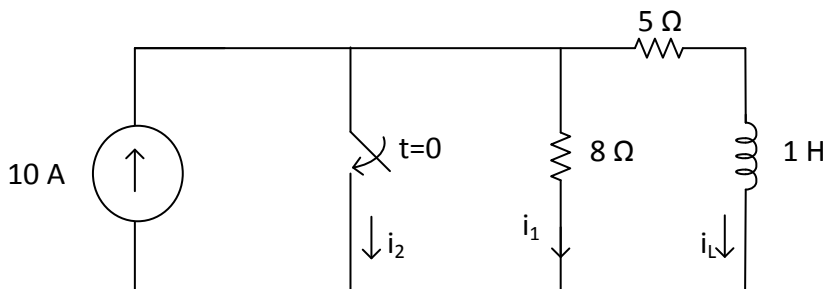


Fig. 4

5. The circuit in Fig.5 was in steady-state for $t < 0$, and the position of the switch is changed at $t = 0$. Find the capacitor voltage $V_c(t)$ and the current $i(t)$ in the $100\ \Omega$ resistor for all time.

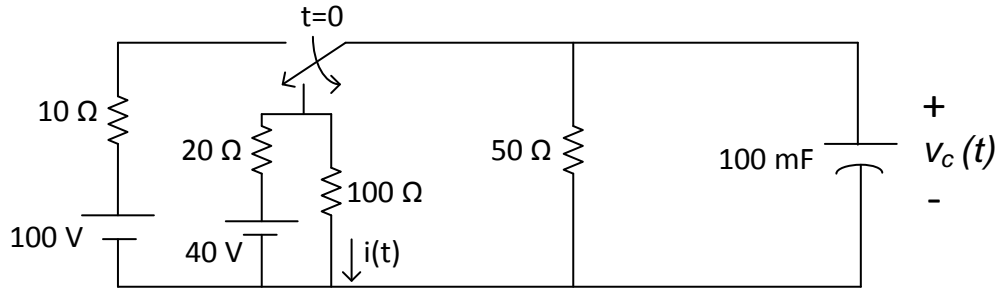


Fig. 5

6. In the circuit of Fig.6, the switch was open and the circuit was operating at steady state. At $t=0$, the switch is closed. Derive the expression for inductor current $i(t)$ for $t > 0$.

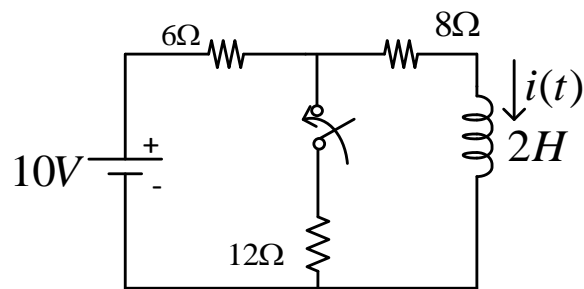


Fig. 6

7. In the circuit of Fig.7, the switch was open and the circuit was operating at steady state. At $t=0$, the switch is closed. Obtain the expression for inductor current $I_L(t)$ for $t > 0$.

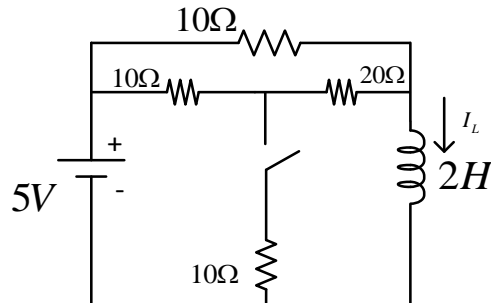


Fig. 7

8. The circuit in Fig.8 was in steady state and the switch S was open. At $t=0$, and the switch is closed. Find the expression of the current $i(t)$ through the inductor of 2 H for $t > 0$.

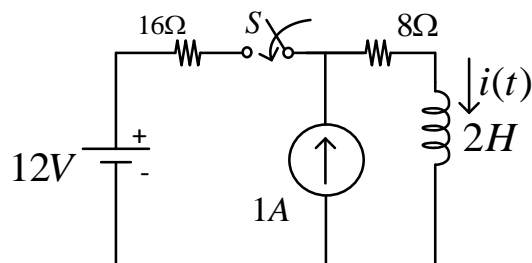


Fig. 8

9. The circuit in Fig.9 was in steady state and the switch S was open. At $t=0$, and the switch is closed. Find the expression of the current $i_c(t)$ through the capacitor for $t>0$.

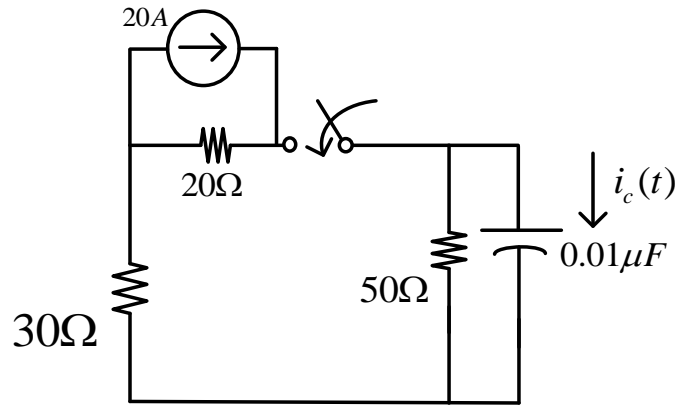


Fig. 9

10. The network in Fig.10 was at steady-state and the switch was open. Obtain the expression of the current $i(t)$ for $t>0$ when an AC voltage source $v(t) = V \sin \omega t$ is connected at $t=0$.

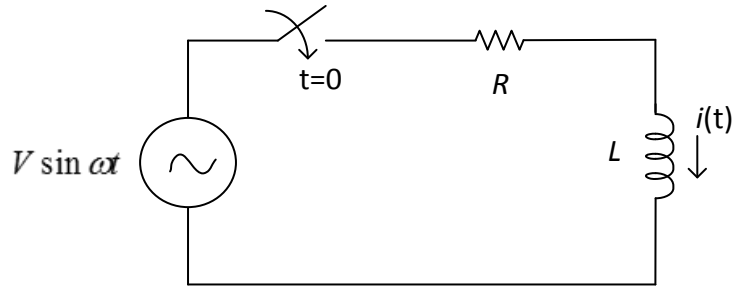


Fig. 10

11. In the circuit shown in Fig.11, assume that, initially the switch is not connected to either A or B terminal and the capacitor voltage is zero. At $t=0$ sec, the switch is connected to A terminal. Then, at $t=1$ s, the switch is disconnected from A terminal and connected to B terminal. Calculate $V_C(0+)$, $\frac{dV_C(0+)}{dt}$, $V_C(1-)$, $\frac{dV_C(1-)}{dt}$ and $V_C(1+)$, $\frac{dV_C(1+)}{dt}$ and $V_C(+\infty)$. Also, calculate the value of $V_C(t)$ at 2s.

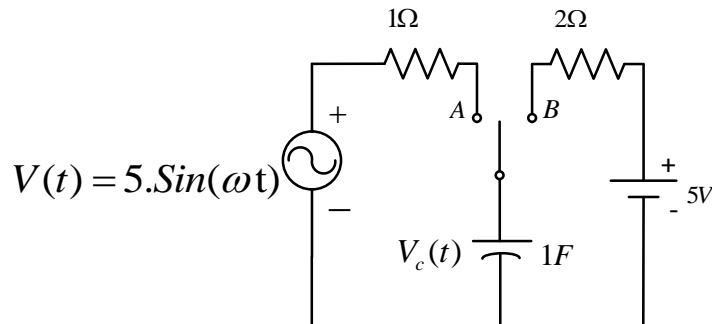


Fig. 11