

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

EXPERIMENT-5

SHEET NO.

## PART-1

### OBJECTIVE:-

To determine  $Y, Z$  and ABCD parameters of single and cascaded two port networks experimentally and verify their interrelation ships.

### APPARATUS REQUIRED:-


S.No.	APPARATUS NAME	QUANTITY
1.	Two Port Networks	2 (M, N)
2.	Multimeter	1
3.	12V DC Supply	1
4.	Connecting wires	-

# INDIAN INSTITUTE OF TECHNOLOGY



DATE

SHEET NO.

CIRCUIT DIAGRAMS:-

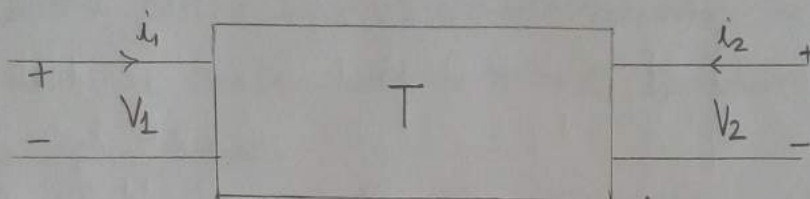

$$T = T_M \text{ or } T = T_N.$$

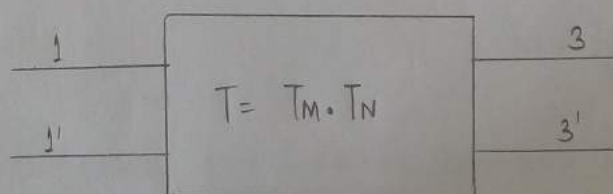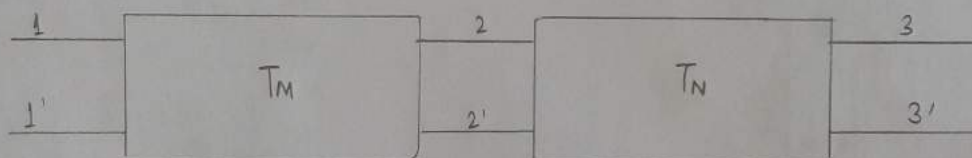

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

## THEORY:-

Consider a passive 2-port (4 Terminal) network. The voltages  $V_1, V_2$  and currents  $I_1, I_2$  can be related in terms of  $z$  parameters &  $y$  parameters as shown below:-

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

Where  $z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

Voltages & currents of port 1 can be represented in terms of those of port 2 as follows:-

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix} = T \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$-B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$-D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

## OBSERVATION TABLE

1-1' = Input

2-2' = Output.

Port	Conditions	$V_1$ (inv)	$I_1$ (mA)	$V_2$ (inv)	$I_2$ (mA)
M	O/p open	11.97	0.28	7.39	0
	O/p short	11.98	0.46	0	29
	I/p open	7.41	0	11.98	0.28
	I/p <del>short</del>	0	28	11.95	0.46
N	O/p open	11.97	0.33	4.013	0
	O/p short	11.96	0.38	0	12
	I/p open	3.97	0	11.93	0.33
	I/p short	0	13	11.97	0.37
MN	O/p open	11.97	0.35	1.43	0
	O/p short	11.98	0.36	0	4
	I/p open	1.41	0	11.98	0.35
	I/p short	0	4	11.98	0.35

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

CALCULATIONS:-

	M	N	MN
$Z_{11} = \frac{V_1}{I_1} \Big _{I_2=0}$	42.75 k $\Omega$	36.273 k $\Omega$	34.2 k $\Omega$
$Z_{12} = \frac{V_1}{I_2} \Big _{I_1=0}$	26.464 k $\Omega$	12.03 k $\Omega$	4.028 k $\Omega$
$Z_{21} = \frac{V_2}{I_1} \Big _{I_2=0}$	26.393 k $\Omega$	12.16 k $\Omega$	4.086 k $\Omega$
$Z_{22} = \frac{V_2}{I_2} \Big _{I_1=0}$	42.786 k $\Omega$	36.152 k $\Omega$	34.228 k $\Omega$
$Y_{11} = \frac{I_1}{V_1} \Big _{V_2=0}$	3.839 $\times 10^{-5}$ S	3.178 $\times 10^{-5}$ S	3.008 $\times 10^{-5}$ S
$Y_{12} = \frac{I_1}{V_2} \Big _{V_1=0}$	2.339 mS	1.086 mS	0.334 mS
$Y_{21} = \frac{I_2}{V_1} \Big _{V_2=0}$	2.421 mS	1.002 mS	0.334 mS
$Y_{22} = \frac{I_2}{V_2} \Big _{V_1=0}$	3.849 $\times 10^{-5}$ S	3.091 $\times 10^{-5}$ S	2.921 $\times 10^{-5}$ S
$A = \frac{V_1}{V_2} \Big _{I_2=0}$	1.6197	2.983	8.371
$B = -\frac{V_1}{I_2} \Big _{V_2=0}$	-413.103	-996.67	-2995
$C = \frac{I_1}{V_2} \Big _{I_2=0}$	3.789 $\times 10^{-5}$	8.223 $\times 10^{-5}$	2.448 $\times 10^{-4}$
$D = -\frac{I_1}{I_2} \Big _{V_2=0}$	-0.0159	-0.03167	-0.09

P.R.E.



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

REPORT :-

1. Theoretical relationships between  $y, z$  and ABCD parameters :-

$$\begin{aligned}
 [V] &= [Z][I] \quad \text{and} \quad [I] = [Y][V] \\
 \hookrightarrow [Z]^{-1}[V] &= [I] \quad \hookrightarrow [Y]^{-1}[I] = [V] \\
 \Downarrow & \quad \Downarrow \\
 [Y] &= [Z]^{-1} \quad \text{and} \quad [Z] = [Y]^{-1} \\
 [Z] &= \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \quad [Y] = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \\
 \Rightarrow \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} &= \frac{1}{|Z|} \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix} \Rightarrow \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \frac{1}{|Y|} \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix}
 \end{aligned}$$

$$* A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{\left. \frac{V_1}{I_1} \right|_{I_2=0}}{\left. \frac{V_2}{I_1} \right|_{I_2=0}} = \frac{z_{11}}{z_{21}} = \frac{-y_{22}}{y_{21}}$$

Similarly, theoretically we get :-

$$B = \frac{-1}{y_{21}} = \frac{|Z|}{z_{21}}$$

$$C = \frac{1}{z_{21}} = \frac{-|Y|}{y_{21}}$$

$$D = \frac{-y_{11}}{y_{21}} = \frac{z_{22}}{z_{21}}$$

For Port M :-

$$|Z| = |z_{11} z_{22} - z_{12} z_{21}| = 1130.637 \times 10^3$$

$$|Y| = |y_{11} y_{22} - y_{12} y_{21}| = 9.66 \times 10^{-6}$$

$$\bullet A = 1.6197, \quad \frac{z_{11}}{z_{21}} = \frac{42.75}{26.393} = 1.6197$$

$$\bullet B = -413.103, \quad \frac{-1}{y_{21}} = \frac{-1}{2.421 \times 10^{-3}} = -413.053$$

$$\bullet C = 3.789 \times 10^{-5}, \quad \frac{1}{z_{21}} = \frac{1}{26.393 \times 10^3} = 3.789 \times 10^{-5}$$

$$\bullet D = -0.0159, \quad \frac{-y_{11}}{y_{21}} = \frac{-(3.839 \times 10^{-5})}{(2.421 \times 10^{-3})} = -0.0159$$

Hence, verified

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

2. On connecting 2 networks M and N in cascade, transmission matrix of overall network is given as:  $T = T_M \cdot T_N$ .

We have,

$$T_M = \begin{bmatrix} 1.6197 & -413.103 \\ 3.789 \times 10^{-5} & -0.0159 \end{bmatrix}$$

$$T_N = \begin{bmatrix} 2.983 & -996.67 \\ 8.222 \times 10^{-5} & -0.03167 \end{bmatrix}$$

$$T = \begin{bmatrix} 8.371 & -2995 \\ 2.448 \times 10^{-4} & -0.09 \end{bmatrix}$$

$$T_M \cdot T_N = \begin{bmatrix} 4.7976 & -1601.223 \\ 1.117 \times 10^{-4} & -0.0373 \end{bmatrix}$$

3. Establish:  $AD - BC = 1$

Network	AD-BC
M	1.322
N	1.0266
MN	1.4927

Values are not so exact due to experimental errors.

Discrepancies/Precautions:-

- \* Avoid loose connections.
- \* Reading should be taken carefully.
- \* Avoid series connections of voltmeters & parallel connection ammeter.
- \* Power Supply should be switched off.
- \* Make connections acc to the circuit diagram.

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

EXPERIMENT - 5

SHEET NO.

## PART - 2

### OBJECTIVE:-

To determine the transient response of an RLC network in terms of the parameters  $\sigma$ ,  $\xi$ ,  $\omega$ ,  $\omega_n$  and initial conditions  $i_L(0^-)$ ,  $v_C(0^-)$ .

### APPARATUS REQUIRED:-


S.No.	APPARATUS NAME	QUANTITY	SPECIFICATIONS
1.	DC Voltage Source	2	12 V
		1	24 V
2.	Resistor	1	1 $\Omega$
		1	86 $\Omega$
		2	100 k $\Omega$
3.	Capacitor	1	20 $\mu$ F
4.	Inductor	1	20 mH
5.	Relay Switch	1	-




# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

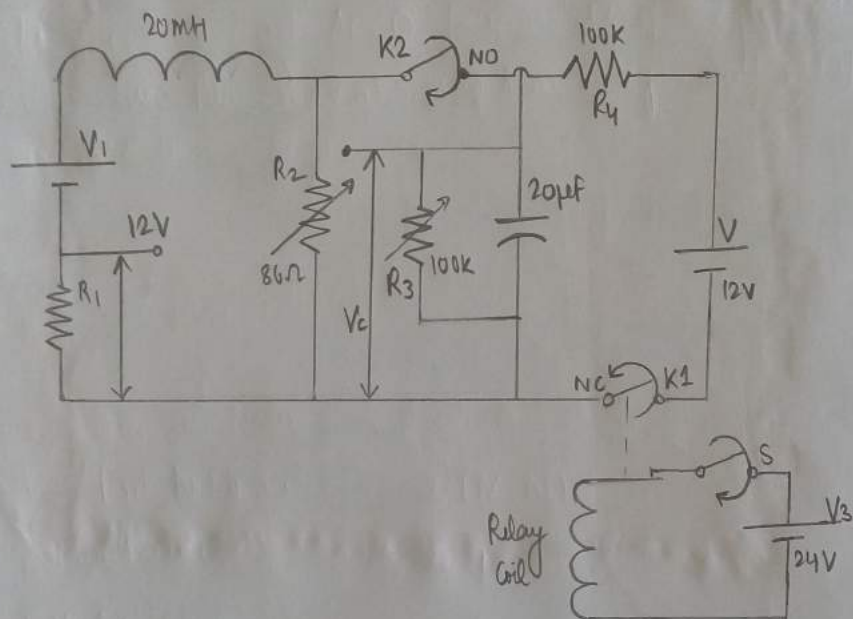

(R-C)

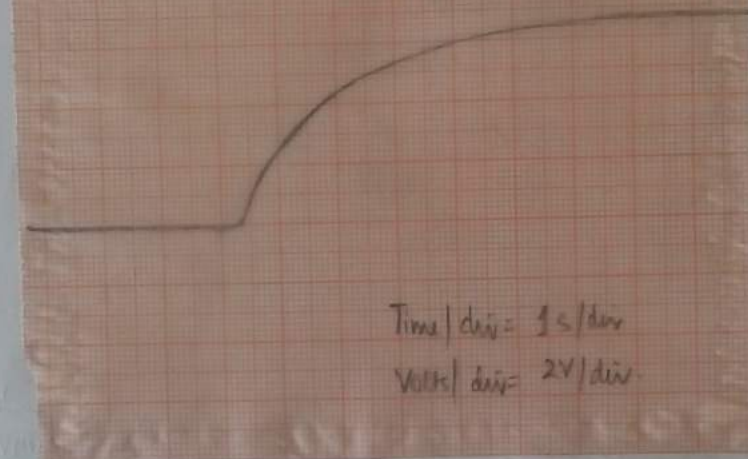

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

## REPORT :-


Determine initial conditions  $V_c(0^-)$  and  $V_c'(0^-)$

from circuit diagram we want to calculate the equivalent circuit and the initial conditions.

Use KCL and KVL,

We will get the differential equation indicating capacitance voltage as:-
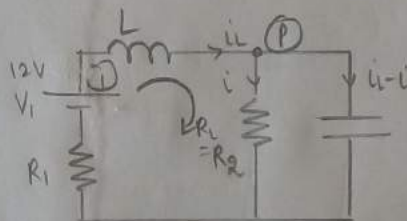
$$V_L = LC \frac{d^2 V_c(t)}{dt^2} + \frac{L}{R} \frac{d V_c(t)}{dt} + V_c(t)$$



Applying KVL at loop ①

$$V_1 - L \frac{di_L}{dt} - iR - i_L R_1 = 0 \quad \text{--- (1)}$$

Applying KCL at node P and KVL at loop ②

$$-iR + q_{1/C} = 0$$

$$V_c = iR \text{ or } q_{1/C} = iR$$

$$\Rightarrow \frac{i - i}{C} = R \frac{di}{dt}$$

$$\Rightarrow i = -RC \frac{di}{dt} + i_L \quad \text{--- (2)}$$

$$\Rightarrow \boxed{I_L = i + RC \frac{di}{dt}}$$



$$V = \frac{1}{C} \int i dt$$


$$V = \frac{1}{C} \int i dt \quad \text{--- (1)}$$

$$V = \frac{1}{C} \int i dt$$

$$V = \frac{1}{C} \int i dt$$

$$V = \frac{1}{C} \int i dt$$

Look to the graph of the current

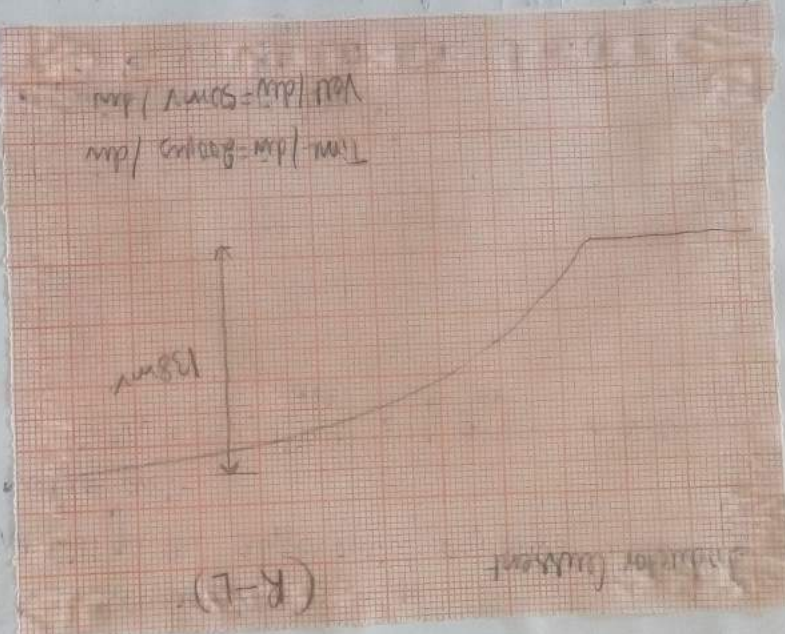

Report:-  
The graph shows the variation of voltage across the inductor with time. The voltage starts at zero and increases exponentially, reaching a steady state value of 100mV. This indicates that the inductor has reached its maximum energy storage capacity.

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

But  $i = \frac{V_c}{R}$  and  $\frac{di}{dt} = \frac{1}{R} \frac{dV_c}{dt}$  — (3)

$\Rightarrow \frac{di}{dt} = \frac{1}{R} \frac{dV_c}{dt} + C \frac{d^2 V_c}{dt^2}$  — (4)

Using (3), (4) and (1)

$V_1 - \frac{L}{R} \frac{dV_c}{dt} - LC \frac{d^2 V_c}{dt^2} - V_c - R_1 \left( \frac{V_c}{R} + C \frac{dV_c}{dt} \right) = 0$

Since  $R_1 \ll R$ ,  $R_1 \leq 1$ ,  $R_1 \left[ \frac{V_c}{R} + C \frac{dV_c}{dt} \right]$  can be neglected.

$\therefore V_1 = LC \frac{d^2 V_c(t)}{dt^2} + \frac{L}{R} \frac{dV_c(t)}{dt} + V_c(t)$  — (5)

Now current in  $R_3$  at  $t=0$  is  $\left\{ \frac{V_2}{(R_3+R_4)} \right\}$

Potential difference across  $R_3 = V_c(0^-) = \frac{R_3}{R_3+R_4} V_2$

$= \frac{V_2}{2} = 6V = V_c(0^-)$

Since voltage across capacitor does not change instantaneously,

So  $V_c(0^+) = V_c(0^-) = 6V$ .

$\therefore V_c'(0) = 0V$ .

For Inductor:

Current =  $i_L$

We have  $V_1 - L \frac{di}{dt} - i_L R_1 = V_c$

$\Rightarrow -L \frac{di_L}{dt} - R \frac{di_L}{dt} = \frac{dV_c}{dt}$

$$(2) \rightarrow \frac{V_0}{R} \left( 1 - \frac{e^{-t/\tau}}{1} \right) = \frac{V_0}{R} \left( 1 - e^{-t/\tau} \right)$$

$$(3) \rightarrow \frac{V_0}{R} \left( 1 - \frac{e^{-t/\tau}}{1} \right) = \frac{V_0}{R} \left( 1 - e^{-t/\tau} \right)$$

(1) time (2) (3) steady

(R-L-C)



$$V_0 = 10V, V = 10V, \tau = 0.2$$

$$V_0 = 10V, \tau = 0.2$$

$$V_0 = 10V, \tau = 0.2$$

$$V_0 = 10V, \tau = 0.2$$



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

Since  $C \frac{dv_c}{dt} = i_L - \frac{v_c}{R}$

$$\Rightarrow -L \frac{d^2 i_L}{dt^2} - R_1 \frac{di_L}{dt} = \frac{1}{C} \left[ i_L - \frac{1}{R} \left( V_1 - L \frac{di_L}{dt} - i_L R_1 \right) \right]$$

$$\Rightarrow \frac{V_1}{R} = LC \frac{d^2(i_L(t))}{dt^2} + \left( R_1 C + \frac{L}{R} \right) \frac{di_L}{dt} + \left( 1 + \frac{R_1}{R} \right) i_L$$

Since,  $R_1 C \ll \frac{L}{R}$  and  $\frac{R_1}{R} \ll 1$  these can be neglected.

$$\Rightarrow \frac{V_1}{R} = RLC \frac{d^2 i_L(t)}{dt^2} + L \frac{di_L}{dt} + R i_L \quad \text{--- (6)}$$

$$\Rightarrow i_L(0^-) = \frac{V_1}{R_1 + (R_2 || R_3)} = \frac{V_1}{1 + (86 || 100k)} = \frac{12}{86.93} = 138 \text{ mA}$$

Since current through inductor does not change instantaneously,

$$i_L(0^+) = i_L(0^-) = 138 \text{ mA. and } \frac{di_L(0)}{dt} = 0$$

These are the initial conditions for  $i_L(t)$ .

Solution for  $v_c(t)$ :- (from eqn (5):-)

$$V_1 = LC \frac{d^2 v_c(t)}{dt^2} + \frac{L}{R} \frac{dv_c(t)}{dt} + v_c(t).$$

Applying Laplace Transform:-

$$\frac{V_1(s)}{s} = LC [s^2 v_c(s) - s v_c(0) - v_c'(0)] + \frac{L}{R} [s v_c(s) - v_c(0)] + v_c(s)$$

Since  $v_c'(0) = 0$  and  $v_c(0) = 6$  (from part a)

$$\Rightarrow \frac{V_1}{s} = LC (s^2 v_c(s) - 6s) + \frac{L}{R} (s v_c(s) - 6) + v_c(s)$$

$$\Rightarrow v_c \left( 1 + \frac{Ls}{R} + LCs^2 \right) = \frac{V_1}{s} + 6sLC + \frac{6L}{R}$$

DATE

SHEET NO.

$$\Rightarrow V_c(s) = \frac{6RLCs^2 + 6Ls + V_1R}{RLC} \times \frac{1}{s\left(s^2 + \frac{s}{RC} + \frac{1}{LC}\right)}$$

Using Partial fraction,

$$V_c(s) = \frac{A}{s} + \frac{Bs+C}{s^2 + \frac{s}{RC} + \frac{1}{LC}} = \frac{(A+B)RLCs^2 + \left(\frac{A}{RC} + C\right)RLCs + AR}{RLCs\left(s^2 + \frac{s}{RC} + \frac{1}{LC}\right)}$$

$$= \frac{6RLCs^2 + 6Ls + V_1R}{RLCs\left(s^2 + \frac{s}{RC} + \frac{1}{LC}\right)}$$

$$\Rightarrow A+B=6, \quad \frac{A}{LC} = \frac{V_1}{LC}, \quad \frac{A}{RC} + C = \frac{6}{RC}$$

$$\Rightarrow A=V_1, \quad B=6-V_1, \quad C = \frac{6-V_1}{RC}$$

$$V_c(s) = \frac{A}{s} + \frac{Bs+C}{s^2 + \frac{s}{RC} + \frac{1}{LC}} = \frac{A}{s} + \frac{Bs+C}{\left(s + \frac{1}{2RC}\right)^2 + \left(\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}\right)^2}$$

Applying Inverse Laplace Transform:-

$$V_c(t) = L^{-1}[V_c(s)] = A + e^{-t/RC} \left[ B \cos\left(\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}} t\right) + \left(\frac{C - \frac{B}{2RC}}{\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}}\right) \sin\left(\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}} t\right) \right]$$

Substituting  $A, B, C$  and  $V_1 = 12V$ .

$$V_c(t) = \frac{12}{V_1} - 6e^{-t/RC} \left[ \cos\left(\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}} t\right) + \left[\frac{\frac{3}{R^2C} - \frac{1}{4}}{\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}}\right] \sin\left(\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}} t\right) \right]$$

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

Steady state solution (at  $t \rightarrow \infty$ )  $V_{css}(t) = 12V$ .

Transient Solution:-

$$V_{C_2}(t) = -6e^{-\frac{t}{RC}} \cos \omega t - \frac{3}{RC\omega} \sin \omega t e^{-\frac{t}{RC}}$$

$$\text{where } \omega^2 = \frac{1}{LC} - \frac{1}{4R^2C^2}$$

$$\text{And } R_1 = 5.86, R_2 = \frac{2.93}{RC\omega} = 1.094.$$

$$i_L(\max) = 0.14.$$

Finding Parameters:-

$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 20 \times 10^{-6}}} = \frac{\sqrt{10^9}}{20} \approx 1580 \text{ rad/s.}$$

$$\sigma = \frac{1}{2RC} = \frac{10^6}{2 \times 20 \times 85.9} = 291 \text{ rad/s.}$$

$$\xi = \frac{\sigma}{\omega_n} = 0.184$$

$$\omega = \omega_n \sqrt{1 - \xi^2} = 1580 \sqrt{1 - 0.084} = 1526.5 \text{ rad/s.}$$

$$k_1 = -6$$

$$k_2 = \frac{-3}{RC\omega} = 1.12$$

$$V_C(\max) = \frac{95.9}{86.9} \times 12 = 11.89V$$

→ Complete Solution for  $i_L$ :-

We have,

$$V_1 = RLC \frac{d^2 i_L(t)}{dt^2} + L \frac{di_L}{dt} + R i_L$$

$$\text{or } \frac{V_1}{R} = LC \frac{d^2 i_L}{dt^2} + \frac{L}{R} \frac{di_L}{dt} + i_L \quad \text{--- (7)}$$



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

Comparing (7) with eqn (5) & (6), we get:-

$$i_L(t) = A + e^{-\frac{t}{RC}} \left[ B \cos \omega t + \frac{G - B \frac{1}{2} RC}{\omega} \sin \omega t \right]$$

where  $\omega = \sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}$  and  $V_1 \rightarrow \frac{V_1}{R} C$

$$A = \frac{V_1}{R} = 0.14A \quad B = 6 - \frac{V_1}{R} = 5.86 \quad G = \frac{6 - \frac{V_1}{R}}{RC} = \frac{5.86}{RC}$$

So steady state solution  $i_{L,ss} = 0.14A$


Transient Solution:-

$$i_{L,t}(t) = 5.86 e^{-\frac{t}{RC}} \cos \omega t + \frac{2.93}{RC \omega} \sin \omega t$$

Since  $\omega^2 = \frac{1}{LC} - \frac{1}{4R^2C^2}$


Equivalent circuit in transfer domain and determination of input  $Z_L(s)$  and output  $Z_L(s)$ .

For inductor

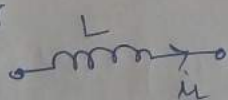


$$V_L = L \frac{di_L}{dt}$$

Transfer function

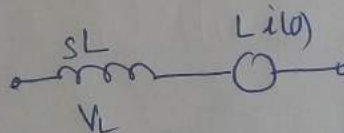

$$\frac{V_L(s)}{L} = s I_L(s) - I_L(0)$$

For capacitor,

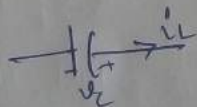

$$i_C = C \frac{dv_C}{dt}$$

Transform function



$$\frac{I_C}{C} = s V_L(s) - V_L(0)$$


$$\Rightarrow i_C(0) = 0.138A$$

$$V_C(0) = 6V$$

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

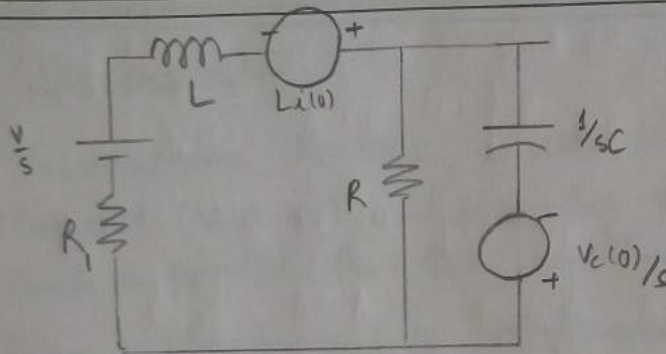

$$Z_{in} = (R_1 + sL) + (R \parallel \frac{1}{sC}) = R_1 + sL + \frac{R}{RCS + 1}$$

$$Z_o = \frac{1}{sC} \parallel R \parallel (R_1 + sL) = \frac{RR_1 + R sL}{RR_1 sC + s^2 RLC + R_1 + R_1 + sL}$$

In transfer domain apply Thevenin's theorem to determine current through inductor. Initial conditions are  $i(0) = 0.1A$   
 $C = 2\mu F$ ,  $V_c(0) = 5V$ ,  $L = 20mH$

$$V_{TH} = \frac{12}{s} + L \frac{di(0)}{dt} - \frac{V_c/s \times R}{R + \frac{1}{sC}}$$

$$R_{TH} = R_1 + R \parallel \frac{1}{sC} = R_1 + \frac{R}{1 + sRC}$$

$$i_L = \frac{V_{TH}}{R_{TH}} = \frac{\frac{12}{s} + L \frac{di(0)}{dt} - \frac{V_c(0)R}{RCS + 1}}{R_1 + \frac{R}{1 + sRC}}$$

$$= \frac{12}{s} + 2 \times 10^{-3} - \frac{5 \times 86 \times 20 \times 10^{-3}}{86 \times 5 \times 10^{-4} s + 1}$$

$$= \frac{12}{s} + \frac{86}{1.586 s + 1}$$



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO.

## DISCUSSION:-

- \* The resistance  $R_1 = 100k$  is used to create initial conditions for capacitor ( $V_C(0) = 6V$ ). and when relay is used, this resistance comes in parallel  $R_2 = 86\Omega$  and  $R_{eq} = 86\Omega$ .
- \* Relay coil has been used to simultaneously open and close two switches. So relay used to ~~determine~~ determine transient response with initial conditions.
- \* Current through conductor remains same before and after using relay (steady state value), current value only oscillates for a small duration ( $\sim 10ms$ ). then becomes steady state again. This current oscillates <sup>because</sup> between voltage <sup>across</sup> cap. ~~oscillates~~
- \* Without relay there is no oscillation in  $V_C$  because it has a large resistance in parallel ( $100k\Omega$ ) but after relay  $\rightarrow$  parallel ~~to~~ ( $86\Omega$ ). So as  $R$  decreases overshoot

## PRECAUTIONS:-

- \* Time scale of oscilloscope must be chosen wisely for transient to be observable.
- \* While measuring current by multimeter, it should be connected in series, not parallel.
- \* Triggering value must be added <sup>selected</sup> about half the steady value for better observation.
- \* All connections must be tight.



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO 0

Exp. No.	EXPERIMENT	PAGE NO.	DATE	Teacher's Signature.
1	Active Low Pass Filters	1-11	05/08/16	<i>[Signature]</i> 19.8.16
2	Verification of Max. Power Theorem and Reciprocity Theorem	12-24	19/08/16	<i>[Signature]</i> 21.9
3	To study Transient & freq response of RLC series ckt.	25-32	02/09/16	<i>[Signature]</i> 23/9/16
4	To find frequency response of Negative Impedance Converter Inverter ckt.	33-47	23/09/16	<i>[Signature]</i> 02.10.16
5	Determination of Fourier Coefficients and Analysis of non-linear elements.	48-59	14/10/16	
6.	Determination of parameters of a two port Network and to measure transient response of a RLC ckt.	60-76	28/10/16	

# INDIAN INSTITUTE OF TECHNOLOGY

DATE 05/08/16

EXPERIMENT No. 1

SHEET NO 1

## ACTIVE LOW PASS FILTERS

### OBJECTIVE:-

To familiarize with 2<sup>nd</sup> order Sallen Key active Low pass filters and to measure their frequency responses.

### APPARATUS REQUIRED:-

NAME	QUANTITY	SPECIFICATIONS
Breadboard	1	-
Function Generator	1	-
Cathode Ray Oscilloscope	1	-
Resistance	3	10k $\Omega$
Resistance	1	2.7k $\Omega$
Resistance	1	4.7k $\Omega$
Capacitor	2	1000pf
Operational amplifier - OPAMP	1	OPAMP-741




# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO 2

## CIRCUIT DIAGRAM

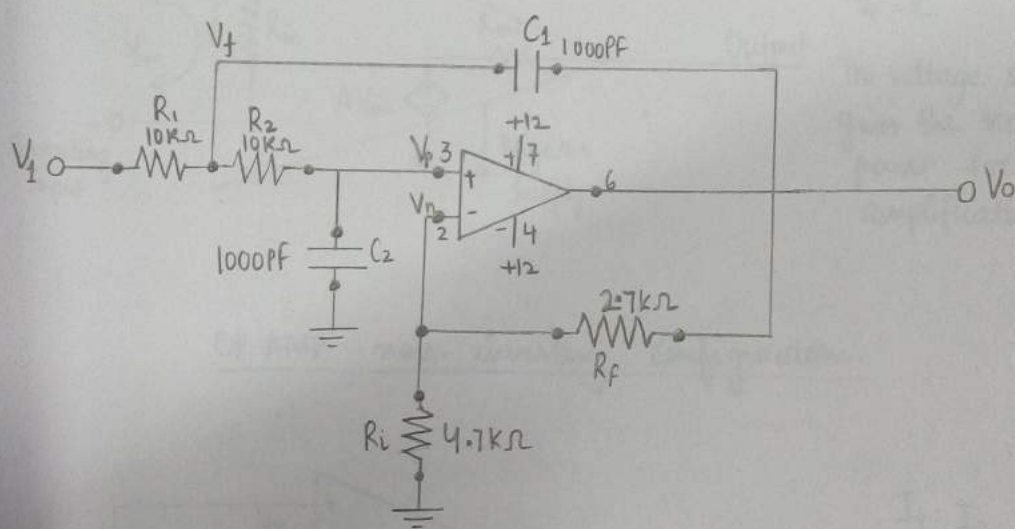




DATE

SHEET NO 3

## THEORY :-

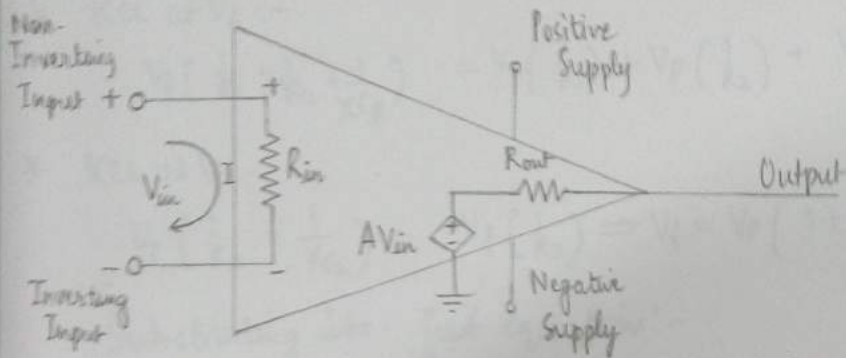


For ideal opamp

$$R_{in} \rightarrow \infty \text{ \& } I \rightarrow 0$$

$$V_+ = V_-$$

The voltage supply gives the necessary power for amplification.

## OP-AMP non-inverting configuration.

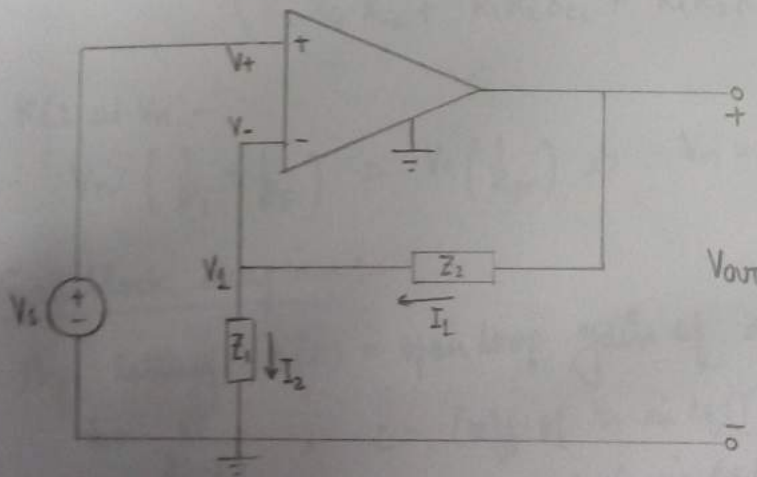

$$I_1 = I_2$$

$$\Rightarrow \frac{V_1}{Z_1} = \frac{V_{out} - V_1}{Z_2}$$

where  $V_s = V_+$

$$\Rightarrow V_{out} = \left(1 + \frac{Z_2}{Z_1}\right) V_1$$

For the generalized Sallen-Key circuit,

\* KCL at  $V_f$ :-

$$V_f \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{X_{C1}} \right) = V_i \left( \frac{1}{R_1} \right) + V_p \left( \frac{1}{R_2} \right) + V_o \left( \frac{1}{X_{C1}} \right)$$

\* KCL at  $V_p$ :-

$$V_p \left( \frac{1}{R_2} + \frac{1}{X_{C2}} \right) = V_f \left( \frac{1}{R_2} \right) \Rightarrow V_f = V_p \left( 1 + \frac{R_2}{X_{C2}} \right)$$

Substituting into first equation:-

$$V_p = V_i \left( \frac{R_2 X_{C1} X_{C2}}{R_2 X_{C1} X_{C2} + R_1 R_2 X_{C1} + R_1 R_2 X_{C2} + R_2^2 X_{C1} + R_2^2 R_1} \right) + V_o \left( \frac{R_1 R_2 X_{C2}}{R_2 X_{C1} X_{C2} + R_1 R_2 X_{C1} + R_1 R_2 X_{C2} + R_2^2 X_{C1} + R_2^2 R_1} \right) \quad (1)$$

\* KCL at  $V_n$ :-

$$V_n \left( \frac{1}{R_i} + \frac{1}{R_f} \right) = V_o \left( \frac{1}{R_f} \right) \Rightarrow V_n = V_o \left( \frac{R_i}{R_i + R_f} \right)$$

Gain block diagram:-

By letting  $a(f)$  = open loop gain of amplifier,

$$b = \frac{R_i}{R_i + R_f}, \quad c = \text{coeff. of } V_i \text{ in eq (1)},$$


$$D = \text{coeff. of } V_o \text{ in eq (1)}$$

and taking  $V_e = V_p - V_n$ , the generalized Sallen Key filter circuit can be represented in gain block.



DATE

SHEET NO 5

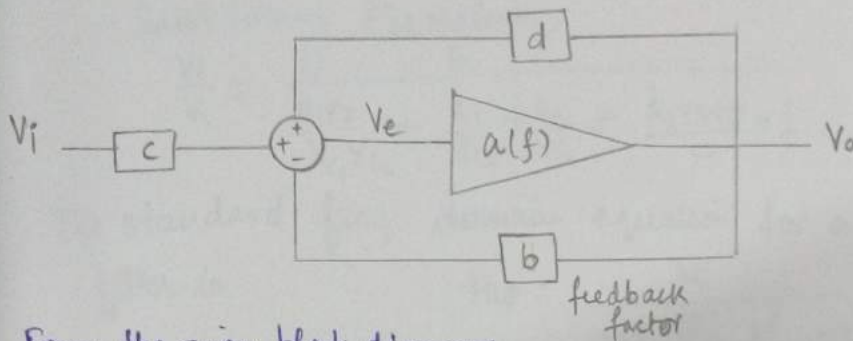

From the given block diagram,

$$V_o = a(f) V_e$$

$$(d-b) V_o = V_e - c V_i$$

$$\Rightarrow V_e = c V_i + d V_o - b V_o$$

Solving for the generalised transfer function

$$\frac{V_o}{V_i} = \left(\frac{c}{b}\right) \left[ \frac{1}{1 + \frac{1}{a(f)} \frac{d-b}{b}} \right]$$

Assuming  $a(f)b$  is very large over the frequency of operation,  $\frac{1}{a(f)b} \approx 0$ , the ideal transfer function from gain block analysis becomes

$$\frac{V_o}{V_i} = \left(\frac{c}{b}\right) \left[ \frac{1}{1 - d/b} \right]$$

By letting  $\frac{1}{b} \approx k$ ,  $c = \frac{N_1}{D}$  and  $d = \frac{N_2}{D}$ , where  $N_1, N_2$  and  $D$  are the numerators & denominator of the expression we derived in eq (1)

$$\frac{V_o}{V_i} = \left[ \frac{k}{\frac{D}{N_1} - k \frac{N_2}{N_1}} \right]$$



Substituting the values,

$$\frac{V_o}{V_i} = \frac{k}{\frac{R_1 R_2}{X_{C1} X_{C2}} + \frac{R_1}{X_{C2}} + \frac{R_2}{X_{C1}} + \frac{R_1(1-k)+1}{C}}$$

The standard freq. domain equation for a 2<sup>nd</sup> order low-pass filter is

$$H_{LP} = \frac{k}{-\left(\frac{f}{f_c}\right)^2 + j\frac{f}{Qf_c} + 1}$$

where  $f_c$  is the corner frequency (breakpoint between pass band & stop band) and  $Q$  is the quality factor.

- i)  $f \ll f_c \Rightarrow H_{LP} \approx k \rightarrow$  signal multiplied by gain factor  $k$ .
- ii)  $f = f_c \Rightarrow H_{LP} = -jkQ \rightarrow$  signals are phase shifted  $90^\circ$  and enhanced by  $Q$ -factor.
- iii)  $f \gg f_c \Rightarrow H_{LP} = -k\left(\frac{f_c}{f}\right)^2 \rightarrow$  signals are phase shifted by  $180^\circ$  and attenuated by sq. of frequency.

By putting  $R_1 = R_2 = R$  and  $X_{C1} = X_{C2} = \frac{1}{sC}$ , we get

$$\frac{V_o}{V_i} = \frac{k}{s^2 C^2 R^2 + sCR(3-k) + 1}$$

$$\text{where } k = 1 + \frac{R_f}{R_1}$$

Comparing  $\frac{V_o}{V_i} = \frac{k}{-\left(\frac{f}{f_c}\right)^2 + j\frac{f}{Qf_c} + 1}$


we get  $f_c = \frac{1}{2\pi RC}$  and  $Q = \frac{1}{3-k}$ .

$f = 159 \text{ kHz}$

Volt/div = 2V

Time/div = 0.1 ms


$V_{PP} = 7$

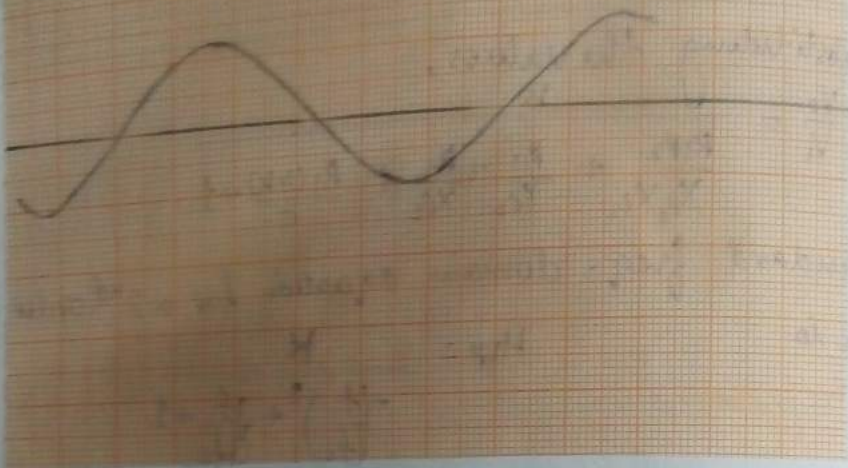

$f = 159 \text{ kHz}$

Volt/div = 2V

Time/div = 20 ps

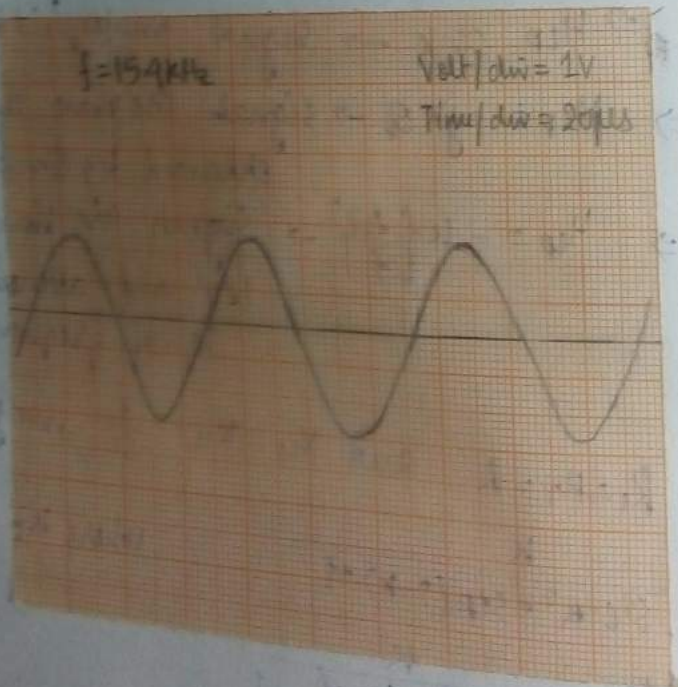

INDIAN I

TE

OBSERVATION

Input voltage

FREQUENCY (

- 0.1
- 0.2
- 0.3
- 0.5
- 1
- 1.59
- 3
- 6
- 8
- 10
- 15.9
- 25
- 30
- 31.8
- 50
- 80
- 100
- 120
- 159
- 200



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO 7

## OBSERVATION TABLE

Input Voltage = 3.0 V (P-P)



Original ckt ( $R_i = 4.7k\Omega$ )

S.No.	FREQUENCY (in KHz)	OUTPUT VOLTAGE (in V) (P-P)	$20 \log \left( \frac{V_{out}}{V_{in}} \right)$ (in dB)
1	0.1	4.6	3.713
2	0.2	4.6	3.713
3	0.3	4.6	3.713
4	0.5	4.6	3.713
5	1	4.6	3.713
6	1.59	4.6	3.713
7	3	4.6	3.713
8	6	4.5	3.522
9	8	4.4	3.327
10	10	4.1	2.713
11	15.9	2.9	-0.294
12	25	1.45	-6.315
13	30	1	-9.542
14	31.8	0.9	-10.457
15	50	0.36	-18.416
16	80	0.15	-26.021
17	100	0.096	-29.897
18	120	0.068	-32.892
19	159	0.04	-37.501
20	200	0.024	-41.938

8/11/16  
8/11/16

NEED



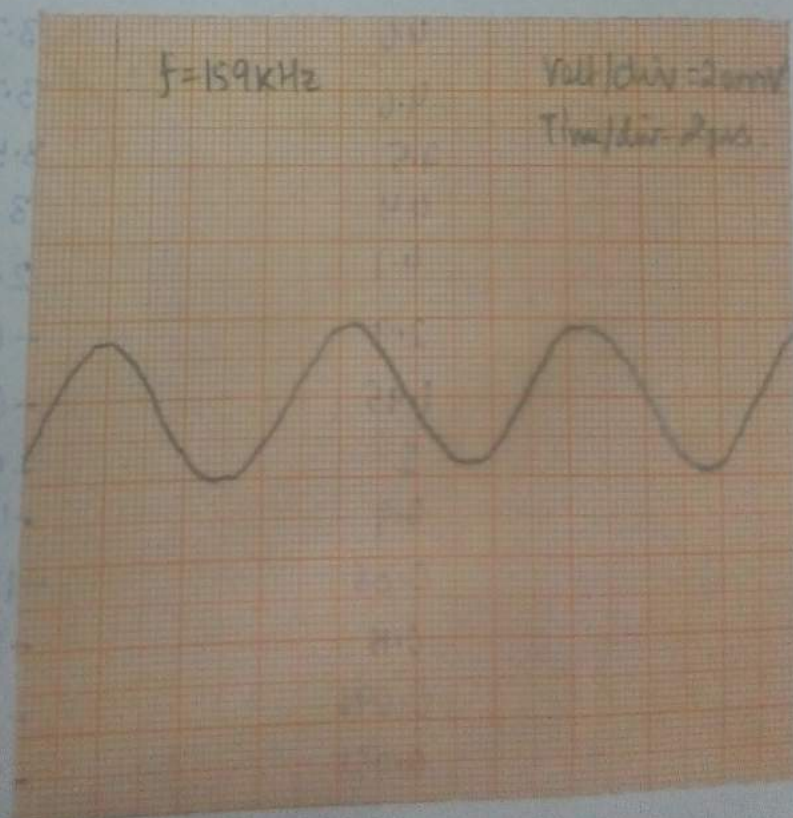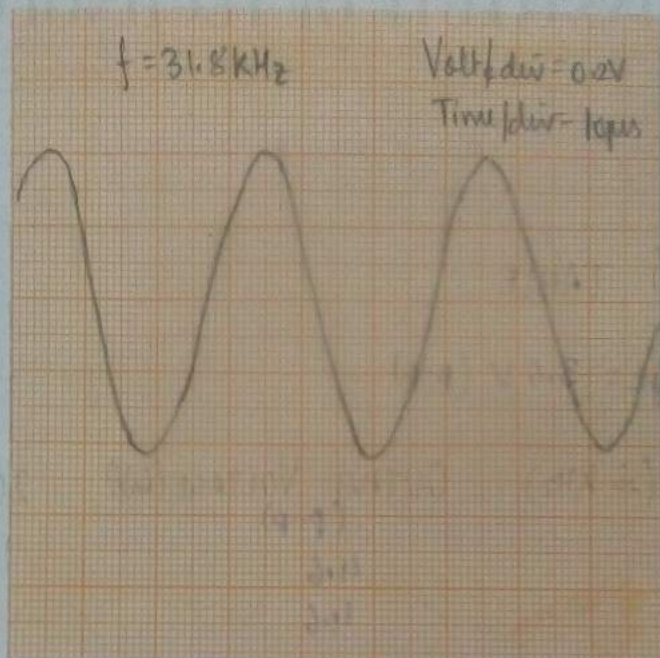

# Original Circuit

Frequency - (Hz)

Horizontal distance from 0dB to -3dB  
= 19.5 kHz

20 log (Vout/Vin) - in dB

10

0

-10

-20

-30

-40

REELUS

10




$f = 2\text{kHz}$

$(R_i = 4.7\text{k}\Omega)$

$V_{\text{div}} = 2\text{V}$

$T_{\text{div}} = 0.2\mu\text{s}$

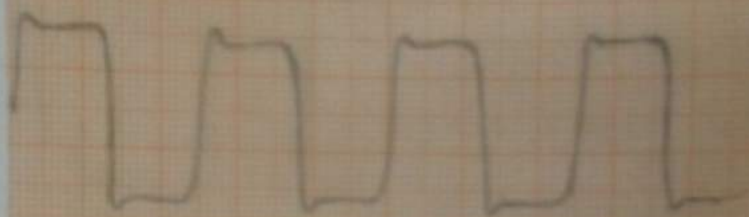



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO 8

## OBSERVATION TABLE

Input Voltage = 3.0V (p.p)

Modified Ckt (R1 = 10k $\Omega$ )


S.No.	FREQUENCY (in kHz)	OUTPUT VOLTAGE (in V) (p-p)	$20 \log(V_{out}/V_{in})$ (in dB)
1	0.1	3.7	1.822
2	0.2	3.7	1.822
3	0.5	3.7	1.822
4	1.59	3.7	1.822
5	3.5	3.6	1.584
6	5	3.5	1.339
7	7	3.3	0.828
8	8	3.2	0.560
9	10	3.0	0
10	12	2.6	-1.243
11	15.9	1.9	-3.967
12	17	1.7	-4.933
13	20	1.4	-6.620
14	25	1.0	-9.542
15	31.8 kHz	0.68	-12.892
16	50 kHz	0.28	-20.600
17	70 kHz	0.16	-25.460
18	120 kHz	0.056	-34.578
19	159 kHz	0.032	-39.439
20	200 kHz	0.021	-43.098

NEEDS



Frequency :- (in Hz)

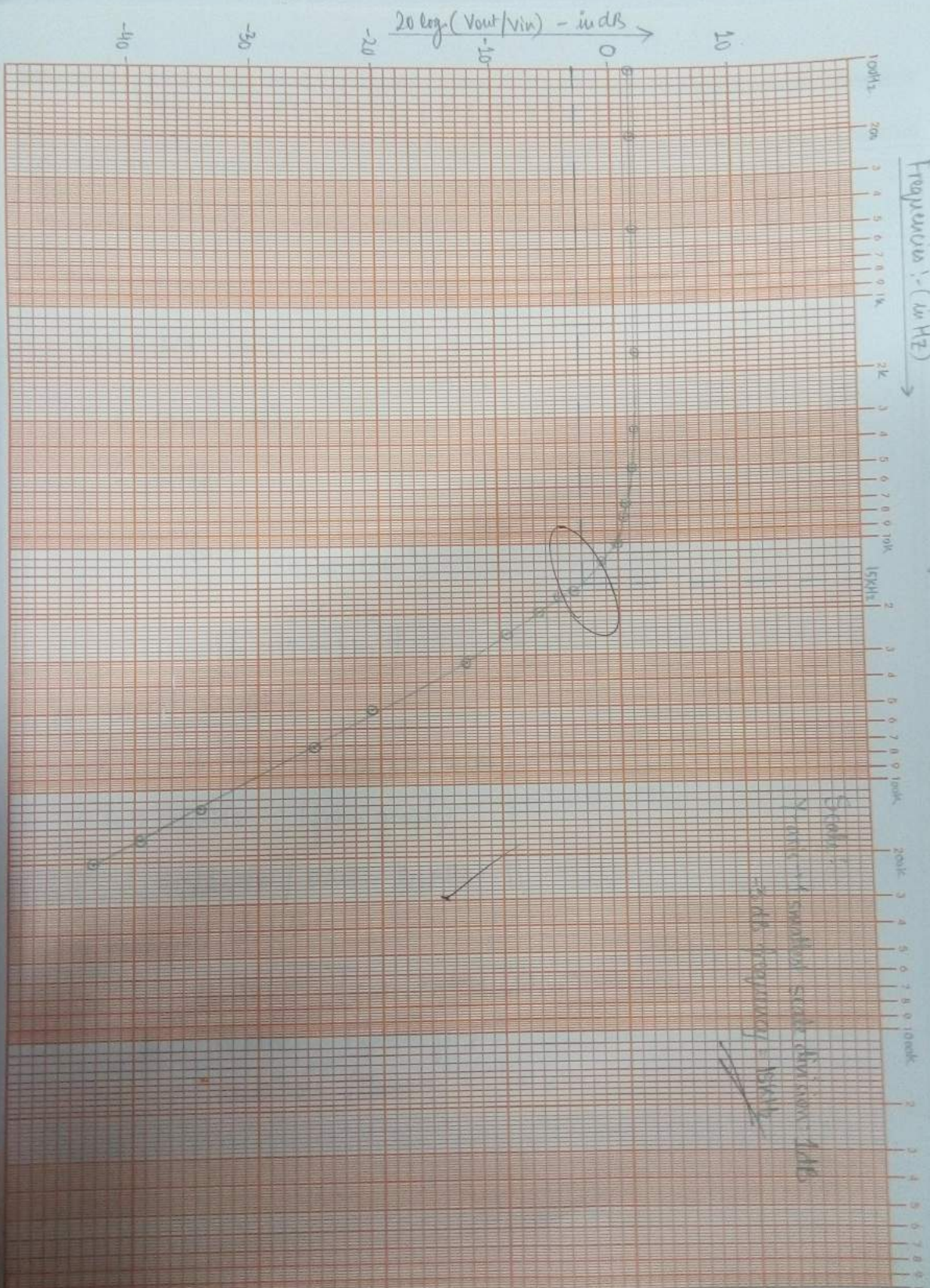Modified circuit (4.7K $\Omega$  replaced by 10K $\Omega$ )



Scale:

Peak to peak voltage = 10V

20 dB frequency = 10KHz



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 4

RESULT :-

Calculated value of  $f_0 = \frac{1}{2\pi RC}$

$$R = 10k\Omega = 10^4\Omega$$

$$C = 1000pF$$

$$\therefore f_0 = \frac{1}{2\pi(10^4)(10^{-9})} \text{ Hz}$$

$$= 15915.5 \text{ Hz}$$

$$f_0 = 15.9 \text{ kHz}$$

For normal circuit :-

$$f_0 = 15.9 \text{ kHz (calculated value)}$$

$$f_0 = 19.5 \text{ kHz (from graph)}$$

$$\therefore \text{deviation / error} = 3.6 \text{ kHz}$$

For modified circuit :-

$$f_0 = 15.9 \text{ kHz (calculated value)}$$

$$f_0 = 15 \text{ kHz (from graph)}$$

$$\therefore \text{deviation / Error} = 0.9 \text{ kHz}$$



# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO 10

DISCUSSION:-

Q1. Derive the expression for transfer function.


Ans. Transfer function:-  $\frac{V_o(s)}{V_i(s)} = \frac{k}{1 + (3-k)RCs + R^2C^2s^2}$ ,

$$k = 1 + \frac{R_f}{R_1}$$


This expression has already been derived in theory.

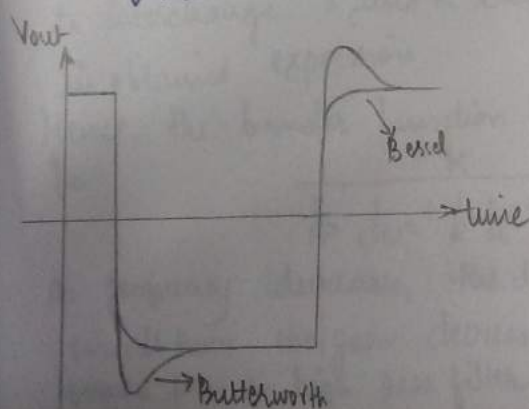Q2. Identify the type of filter in the modified ckt. Comment on its performance compared to Butterworth filter.

Ans. When we change the  $4.7k\Omega$  resistance with a  $10k\Omega$  resistance, the Q factor changes from 0.71 to 0.58, which is characteristic of a Bessel filter.



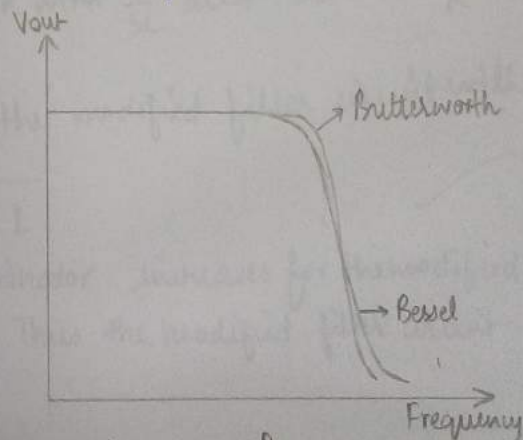Transient Response for a Square Wave form.



FREQUENCY RESPONSE

# INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO 11

Butterworth filter	Bessel filter.
(i) Q-factor = 0.71	(i) Q-factor = 0.58
(ii) It is <u>critically damped</u> .	(ii) It is <u>over damped</u> .
(iii) It has maximum pass band flatness, but it overshoots slightly in response to pulse input.	(iii) It has constant group delay, and no overshoot with pulse input.
(iv) Moderate rate of attenuation above $f_c$ .	(iv) Slow rate of attenuation above $f_c$ .

Q3. If you interchange  $R_1, R_2$  with  $C_1, C_2$  what type of filter characteristics would you get?

Ans. If the resistance & capacitor are interchanged, we need to interchange  $X_c$  and  $R$  i.e.  $R$  with  $\frac{1}{sC}$  and  $sC$  with  $\frac{1}{R}$  in obtained expression.

Hence, the transfer function for the modified filter circuit will be

$$\frac{K}{\frac{1}{R^2} \cdot \frac{1}{(sC)^2} + \frac{1}{R} \cdot \frac{1}{sC} (3-K) + 1}$$

As frequency decreases, the denominator increases for the modified circuit, hence the gain decreases. Thus the modified filter circuit would be a high pass filter.

M. 8.16

NEEDS