

GRAPH THEORY

1) The incidence matrix is given below as

Branches ① ② ③ ④ ⑤ ⑥ ⑦ ⑧

$$A = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \end{bmatrix}$$

Draw the oriented graph


2) The fundamental cut-set matrix is given below

$$Q = \begin{bmatrix} 1 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 & 0 & 1 & 0 \end{bmatrix}$$

Branch names ① ② ③ ④ ⑤ ⑥ ⑦


Draw the oriented graph.

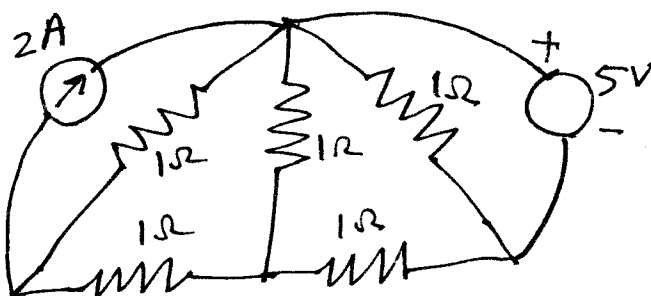3) For the network below draw the graph. Write ~~the~~ a tie-set matrix (after selecting a tree and identifying the loops). Then obtain the equilibrium equations / mesh equations using the tie set matrix. Solve the equations to get branch voltages and currents.




⦿ [Hint: Choose the branches of the tree cleverly]

4)

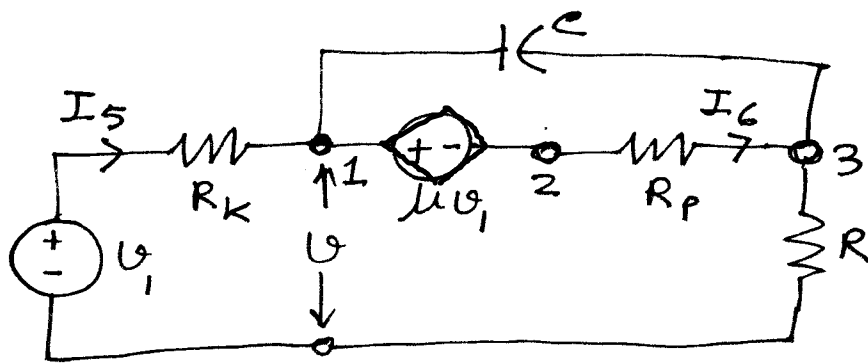


Draw the graph and find a tree. Determine the loop matrix B , branch impedance matrix Z and source voltage matrix V_s . Then write the loop equation. Solve for the current I_5 . Determine the driving point admittance I_5/U_1 .

5)

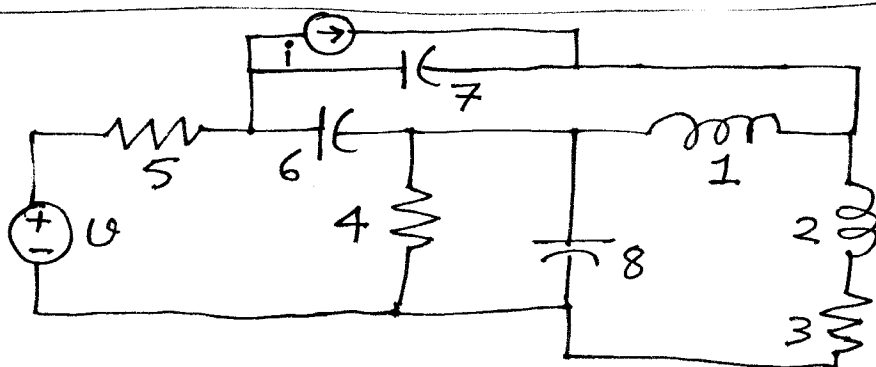

~~Numbers~~
Numbers in this diagram represent branch indices (Not the value of the impedances)

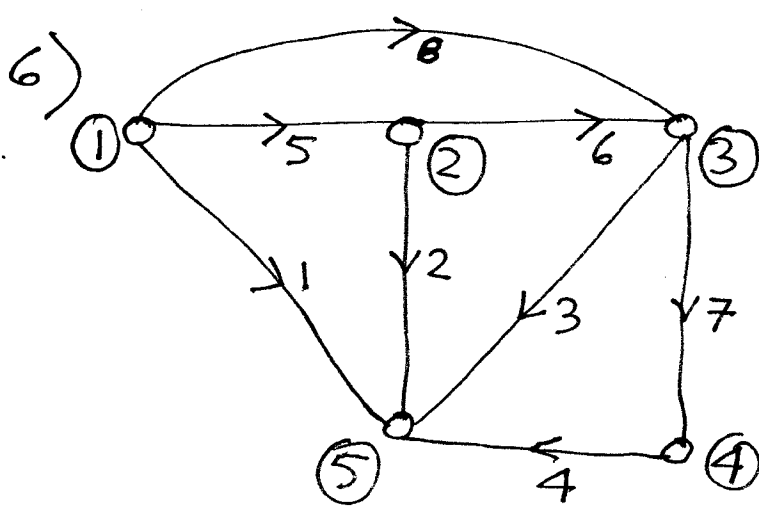Draw the directed graph. Choose a tree, write the cutset matrix, branch admittance matrix. Write the relation between twig and branch voltages. Write the KCL using the cutset matrix. Write the circuit equations / network equations using the cut set matrix. (You may use symbolic values for the resistances, inductances, capacitances)



Numbers inside circles are node numbers and numbers besides arrows are branch/edge number.

Write the incidence matrix of the graph and then express branch voltages in terms of node voltages. Write a loop matrix B and express branch currents in terms of the loop currents.