

INDIAN INSTITUTE OF TECHNOLOGY

DATE 23/09/16

EXPERIMENT NO. 6

SHEET NO. 33

OBJECTIVE:-

Experiment on 1-port Network : Negative Impedance Converter.
To find the frequency response of a simple Negative Impedance Converter.

APPARATUS:-


S.NO.	APPARATUS	QUANTITY	SPECIFICATION
1.	Cathode Ray Oscilloscope (CRO)	1	-
2.	Function generator	1	-
3.	Supply Source	1	+12V
4.	Resistor	3	10K Ω
5.	Capacitor	1	1nF
6.	Bread Board	1	-
7.	Op-Amp (Operational Amplifier)	1	IC-741

INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 34

CIRCUIT DIAGRAM:-

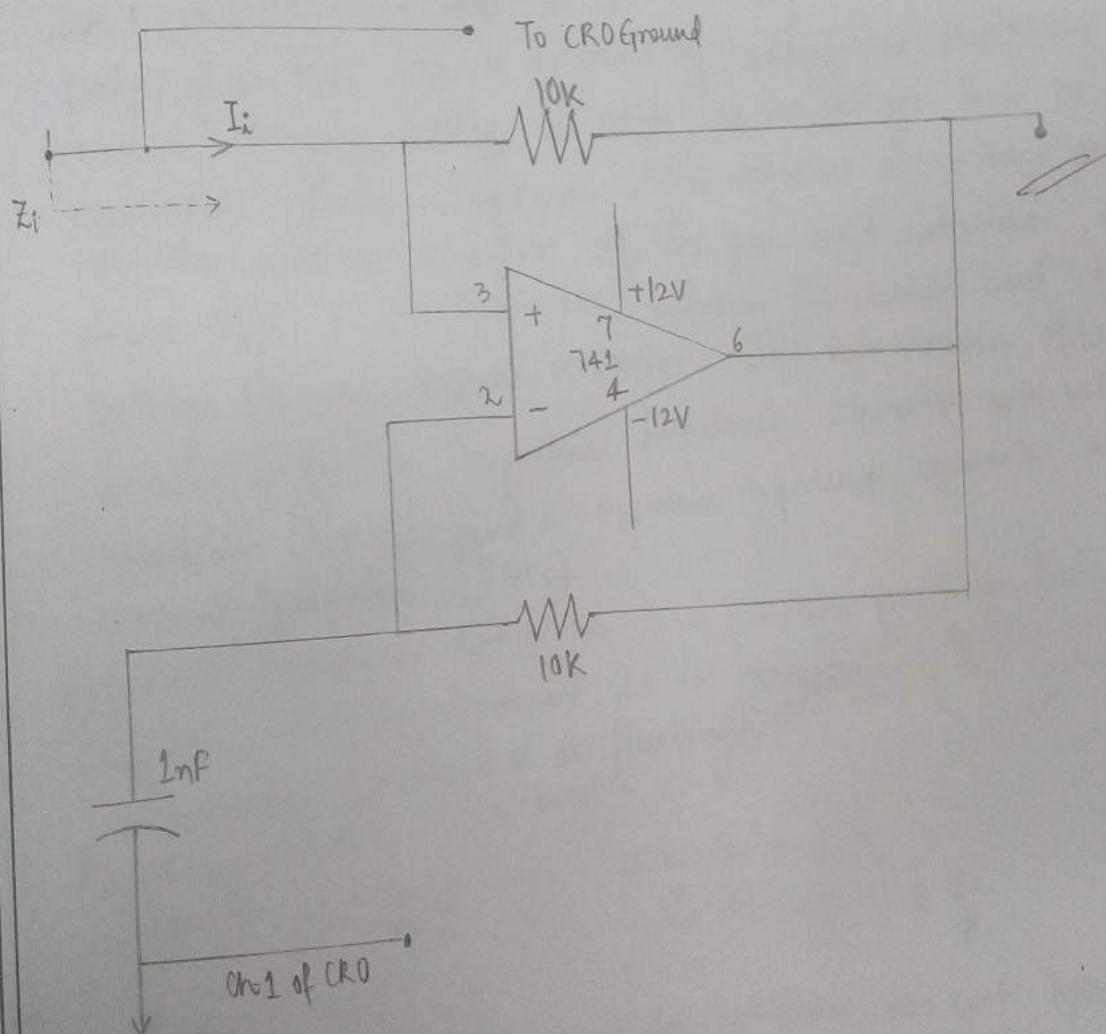

P.R.E.

THEORY :-

The negative impedance converter (NIC) is a one-port op-amp circuit acting as a negative load which injects energy into circuits in contrast to an ordinary load that consumes energy from them. This is achieved by adding or subtracting excessive varying voltage in series to the voltage drop across an equivalent positive impedance. This preserves the voltage polarity or the current direction of the port and introduces a phase shift or 180° (inversion) between the current and the voltage for any signal converter. The two versions obtained are accordingly a negative impedance converter with voltage inversion (VNIC) and a negative impedance converter with current inversion (INIC).

Negative impedance conversion is a function yielding (normally) impedance that is proportional to the negative of the given impedance (grounded or floating).

Assuming ideal equations:-

$$V_o = V_i \left[1 + \frac{Z_1}{Z_2} \right]$$

$$V_i Z_2 - V_o = I_1 I_2$$

$$\therefore Z_1 = \frac{V_i}{I_1} = -Z_2 \frac{Z_1}{Z_2}$$

$$\text{If } Z_2 = Z_1, Z_1 = -Z$$

For proper inversion there must be a path for each opamp input. A more negative than positive feedback which requires:-
 $Z/Z_1 > Z_s/Z_2$, where Z_s is the source impedance.

INDIAN INSTITUTE OF TECHNOLOGY

DATE


SHEET NO 36

OBSERVATION TABLE:-

$V_{input} = 1V_{pp}$

Capacitance = 1mf.

SNo.	Frequency (in kHz)	V_{out} (in volts)	V_{out}/V_{in}	$20 \log (V_{out}/V_{in})$	Phase (in degrees)
1	1	0.060	0.060	-24.44	87.9°
2	2	0.112	0.112	-15.02	88.5°
3	3	0.170	0.170	-15.39	70.3°
4	4	0.220	0.220	-13.15	65.4°
5	5	0.270	0.270	-11.37	62.7°
6	6	0.320	0.320	-9.90	57.5°
7	7	0.360	0.360	-8.87	51.1°
8	8	0.380	0.380	-8.40	47.5°
9	9	0.420	0.420	-7.54	45.6°
10	10	0.480	0.480	-6.38	38.7°
11	20	0.600	0.600	-4.44	19.5°
12	80	0.700	0.700	-3.09	0.01°
13	100	0.720	0.720	-2.85	0.006°
14	200	0.660	0.660	-3.61	0.008°
15	300	0.560	0.560	-5.04	0.008°
16	500	0.440	0.440	-7.13	0.02°

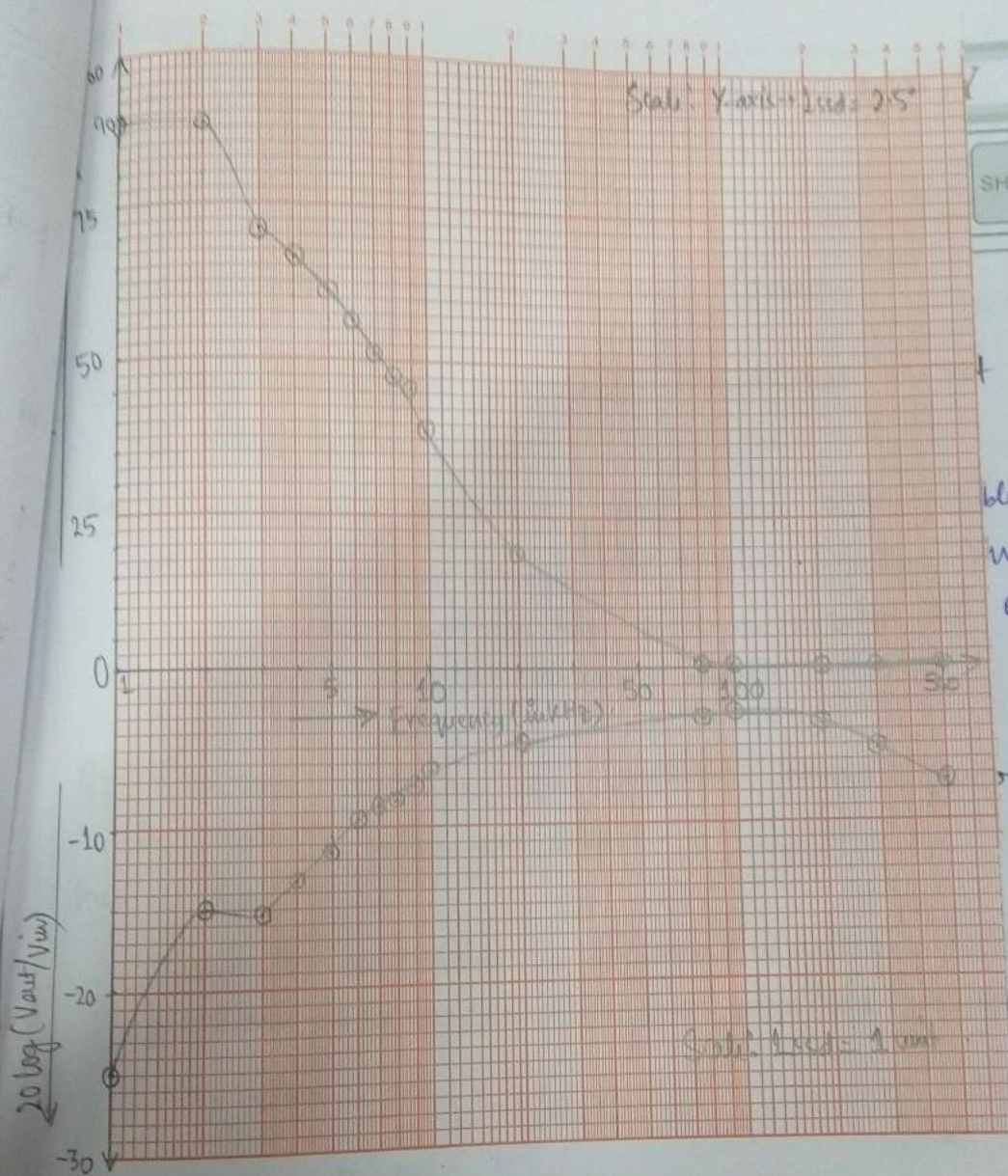

SHEET NO 37

+ possible

ble for
inverter (NIC)
op amp

or using

that is
d or (floating).

Scale: X-axis $\rightarrow 1 \text{ unit}$

$\rightarrow I$

$$4\pi^2 v^2 C$$

where v is the frequency when the voltage leads the current by 90° , then we get an inductance (L), whose value is given by

$$L = \frac{1}{4\pi^2 v^2 C}$$

\downarrow JWC

DISCUSSION: Negative Impedance Converter.

Q1. Why the negative impedance characteristics are not possible in all frequency range?

Ans. - The negative impedance characteristics aren't possible for all frequency ranges because the Negative Impedance Converter (NIC) circuit inverts impedances only at frequencies where the opamp open loop gain can be considered infinite.

Q2. Can you synthesize an inductor from a capacitor using the circuit? Justify your answer.

Ans. - Yes.

Since the circuit yields an impedance (normally grounded) that is proportional to the negative of the given impedance (grounded or floating).


So, when $|j\omega L| = |\frac{1}{j\omega C}|$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow L = \frac{1}{4\pi^2 \nu^2 C}$$

where ν is the frequency when the voltage leads the current by 90° , then we get an inductance (L), whose value is given by

$$L = \frac{1}{4\pi^2 \nu^2 C}$$

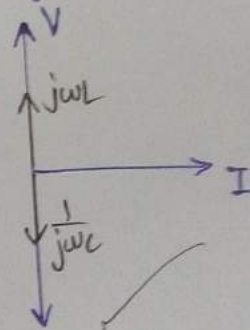

Q3. What could be the reasons for distortion of in the output voltage?

Ans. The distortion of the output voltage signal is due to the output non-linearity in the Negative Impedance Converter (NIC) circuit.

Q3. What could be the reasons for distortion of in the output voltage?

Ans. The distortion of the output voltage signal is due to the spurious non-linearity in the Negative Impedance Converter (NIC) circuit.

INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 38

Q3. What could be the reasons for distortion of in the output voltage?

Ans. The distortion of the output voltage signal is due to the opamp non-linearity in the Negative Impedance Converter (NIC) circuit.

INDIAN INSTITUTE OF TECHNOLOGY

SHEET NO. 39

OBJECTIVE :-


Study of the Gyrator circuit and its application in synthesizing inductors.

→ To find the frequency response of a Gyrator circuit.

APPARATUS :-

S.No.	APPARATUS	QUANTITY	SPECIFICATION
1.	Cathode Ray Oscilloscope (CRO)	1	-
2.	Function Generator	1	-
3.	Supply Source	1	12V
4.	Resistors	7	10k Ω
		1	1k Ω
5.	Capacitors	1	10nF
		1	220nF
		1	1 μ F
6.	Bread Board	1	-
7.	Op-amp (Operational Amplifier)	2	IC - 741

CIRCUIT DIAGRAM:-

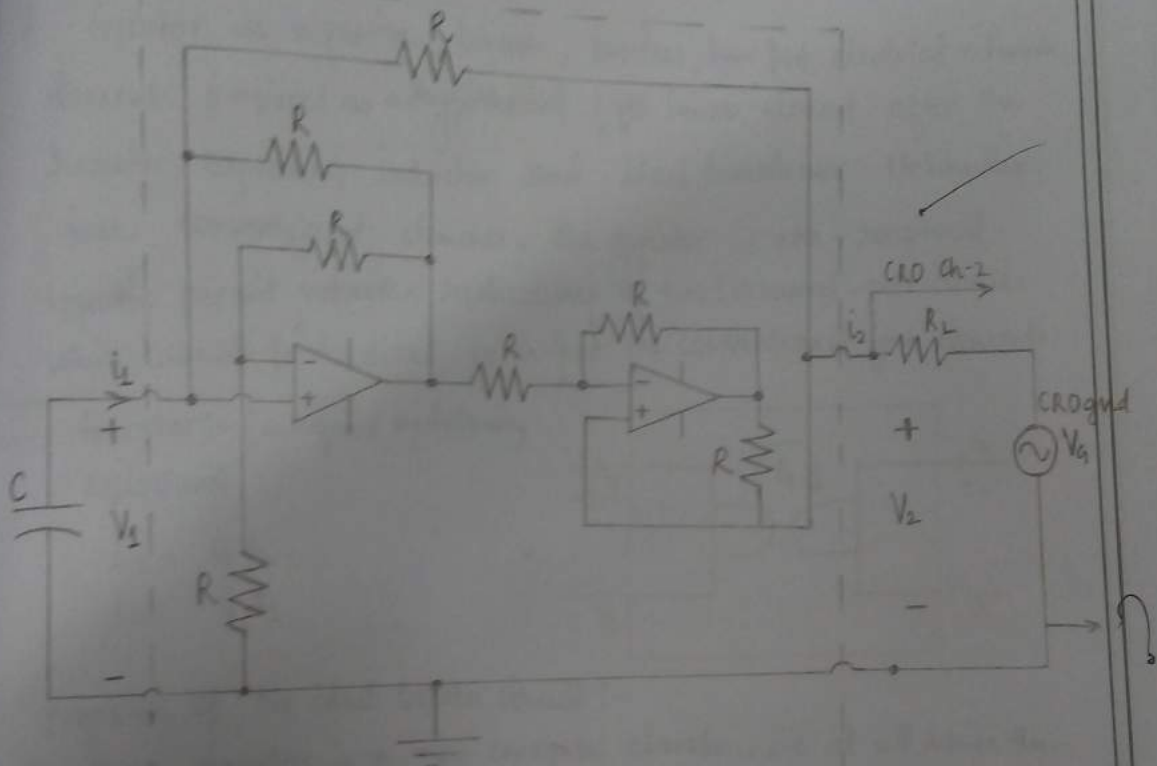


THEORY:-

A Gyration is a passive, linear, lossless, two port electrical network element proposed as a hypothetical fifth linear element after the resistor, capacitor, inductor and ideal transformer. Unlike the four conventional elements, the gyrator is non-reciprocal. Gyrator permit network realizations of two (or more) port devices which cannot be realized with just the conventional four elements.

Gyrator:- (is defined by following equations)

$$i_1 = G \cdot V_2$$

$$i_2 = -G \cdot V_1$$

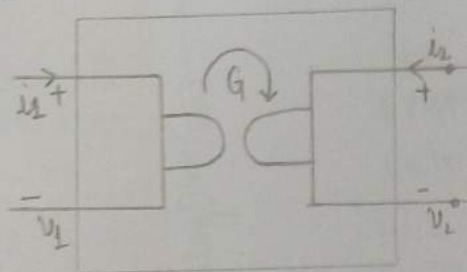


Properties of the ideal Gyrator circuit:-

1. The ideal gyrator is a non-energetic element, i.e. at all times the power delivered to the two port is identically zero.

2. Impedance gyration is given by:-

$$\frac{V_1}{i_1} = -\frac{1}{G^2} \frac{i_2}{V_2} \Rightarrow \frac{V_1}{i_1} = \frac{1}{G^2} \frac{1}{R_L}, \text{ where } R_L = \frac{V_2}{-i_2}$$

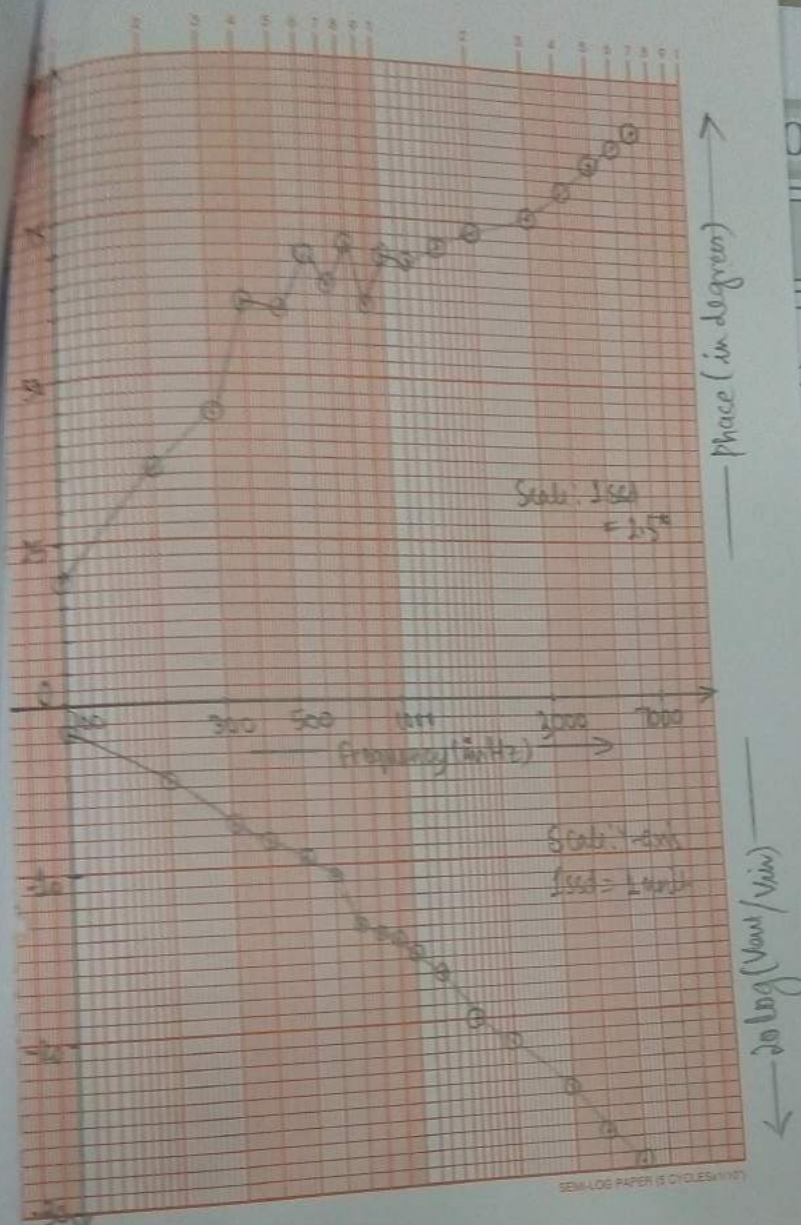3. Capacitor to Inductor Mutation property:- If the output port of an ideal gyrator is terminated with a capacitor, the input port behaves like an inductor. Thus, a gyrator is a useful element in the design of inductor less filters.



DIOLOGY

SHEET NO. 42

Phase
(in degrees)

19.07°

36.860

44.42°

62.73°

61.04°

68.59°

64.15°

71.15°

62.73°

69.63°

68.21°

71.32°

76.19°

80.02°

82.19°

85.23°

88.19°

89.23°

15.

4000

0.04

-27.9

16

5000

0.032

-29.9

17.

6000

0.028

-31.03

18.

7000

0.024

-32.3

INDIAN INSTITUTE OF TECHNOLOGY

SHEET NO. 42

OBSERVATION TABLE:-

$$V_{in} = 1V_{p-p}$$

$$C = 11.39 \mu F$$

S.No.	Frequency (in Hz)	V _{out} (in volts)	20 log(V _{out} /V _{in})	Phase (in degrees)
1.	100	0.84	-1.51	19.07°
2.	200	0.60	-4.4	36.86°
3.	300	0.44	-7.1	44.42°
4.	400	0.36	-8.8	62.73°
5.	500	0.32	-9.9	61.04°
6.	600	0.24	-10.75	68.59°
7.	700	0.20	-14	64.15°
8.	800	0.19	-14.4	71.15°
9.	900	0.18	-14.9	62.73°
10.	1000	0.16	-15.9	69.63°
11.	1200	0.14	-17.0	68.21°
12.	1500	0.10	-20.0	71.32°
13.	2000	0.08	-21.9	76.19°
14.	3000	0.06	-24.4	80.02°
15.	4000	0.04	-27.9	82.19°
16.	5000	0.032	-29.9	85.23°
17.	6000	0.028	-31.03	88.19°
18.	7000	0.024	-32.3	89.23°

P.R.E

P.R.E

INDIAN INSTITUTE OF TECHNOLOGY

SHEET NO. 43

$$V_{in} = 1V_{pp}$$

$$C = 95nF$$

S.No.	Frequency (in Hz)	V_{out} (in Volts)	$20 \log(V_{out}/V_{in})$	Phase (in degrees)
1.	100	0.18	-16.5	12.6°
2.	200	0.09	-20.9	18.0°
3.	300	0.06	-24.4	86.4°
4.	400	0.05	-26.0	85.3°
5.	500	0.036	-28.8	90°
6.	600	0.032	-29.8	86.1°
7.	700	0.028	-31.1	75.6°
8.	1000	0.019	-34.5	72.0°
9.	2000	0.010	-40.0	81.3°
10.	3000	0.005	-46.0	78.3°
11.	5000	0.002	-53.9	72.0°

P.R.E

P.R.E

$$V_{in} = 1V_{pp}$$

$$C = 1nF$$

No.	Frequency (in kHz)	V _{output} (in Volts)	$20 \log(V_{out}/V_{in})$	Phase (in degrees)
1.	1	0.016	-35.92	48.6°
2.	2	0.024	-32.40	56.4°
3.	3	0.034	-29.37	55.4°
4.	4	0.044	-27.13	59.9°
5.	5	0.054	-25.35	58.4°
6.	6	0.060	-24.44	53.1°
7.	7	0.068	-23.35	55.4°
8.	8	0.076	-22.38	47.5°
9.	9	0.080	-21.94	48.6°
10	10	0.088	-21.11	46.6°
11.	20	0.128	-17.86	34.5°
12.	50	0.170	-15.39	20.7°
13.	100	0.220	-19.15	21.3°
14.	500	0.230	-12.77	0

DISCUSSION: GYRATOR CIRCUIT:-

Q1. Why this circuit is named as a Gyrator circuit?

Ans - 'Gyrator' means to oscillate or vary, especially in a repetition pattern. This circuit is named Gyrator because of the following properties shown by the circuit:-


1. It reverses the polarity of the signal travelling in the backward direction (180° phase-shifts the backward travelling signal).
2. If one port of the circuit is terminated with a linear load, then the other part represents an impedance inversely proportional to that of the load.
3. It inverts the current-voltage characteristic of an electrical component or network.
4. In the case of linear elements, the impedance is also inverted.

In other words, a gyrator can make a capacitive circuit behave inductively, a series LC circuit behaves like a polarised rect, and so on. Hence, this circuit shows an oscillatory behaviour, so it is named as gyrator circuit.

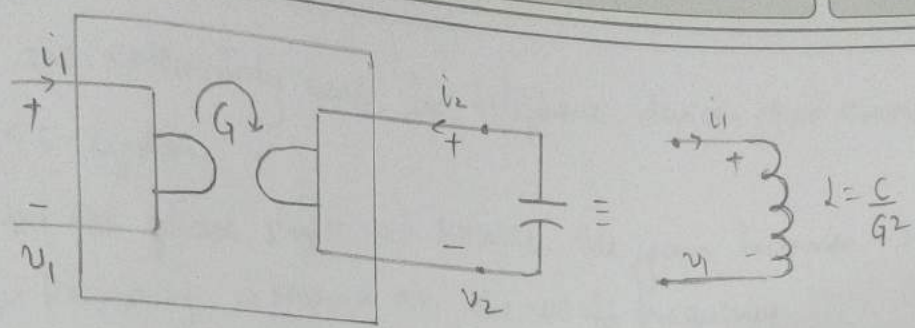Q2. Derive the expression:- $L = R^2 C$.

Ans - Applying Kirchhoff's loop law:-

$$V_1 = L \frac{di_1}{dt} = \left(\frac{C}{G^2} \right) \frac{di_1}{dt}$$



from the experimental ckt;
~~ckt~~

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/R \\ 1/R & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Gyrator : $G = 1/R$

$L = C/G^2$

$\Rightarrow \boxed{L = CR^2}$

Q3. What is the frequency when there is an exact 90° phase shift? Explain the reason of this behaviour.

Ans - At 50 kHz, the phase shift is around 90° . As the inductive impedance becomes very large at low frequency there is about 90° phase shift.

At low frequency, the capacitor gives a high impedance. When this is inverted, the inductance at low frequencies also become very large.

Amplifiers are extensively used in telephone devices that connect to POTS system.

At the 90° phase shift at 50 kHz, the gain becomes -3dB. This frequency is known as the cutoff frequency.

The 50 kHz frequency is the lower cutoff point of the amplifier circuit.

[Signature]

Gyrators are extensively used in telephone devices that connect the POTS system

* At the 90° phase shift at 50kHz , the gain becomes -3dB .
This frequency is known as the cutoff frequency.

The 50kHz frequency is the lower cutoff point of the gyrator circuit.

[Signature] 10.16

INDIAN INSTITUTE OF TECHNOLOGY

DATE 19/04/16

Experiment 4

SHEET NO 48

OBJECTIVE:-


(PART-1)


Experimental verification of fourier coefficients of a square wave signal using passive network.

APPARATUS REQUIRED:-

S.No.	APPARATUS NAME	QUANTITY	SPECIFICATIONS
1.	CRO	1	-
2.	Function Generator	1	-
3.	Resistor (10k)	1	-
4.	Inductor (10mH)	1	-
5.	Capacitor (100nF)	1	-

CIRCUIT DIAGRAM:-

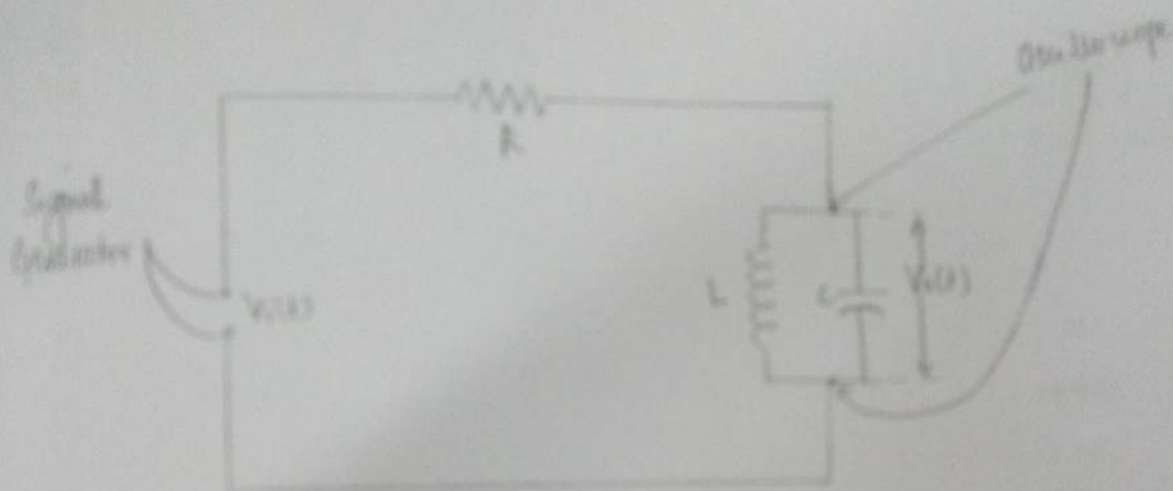

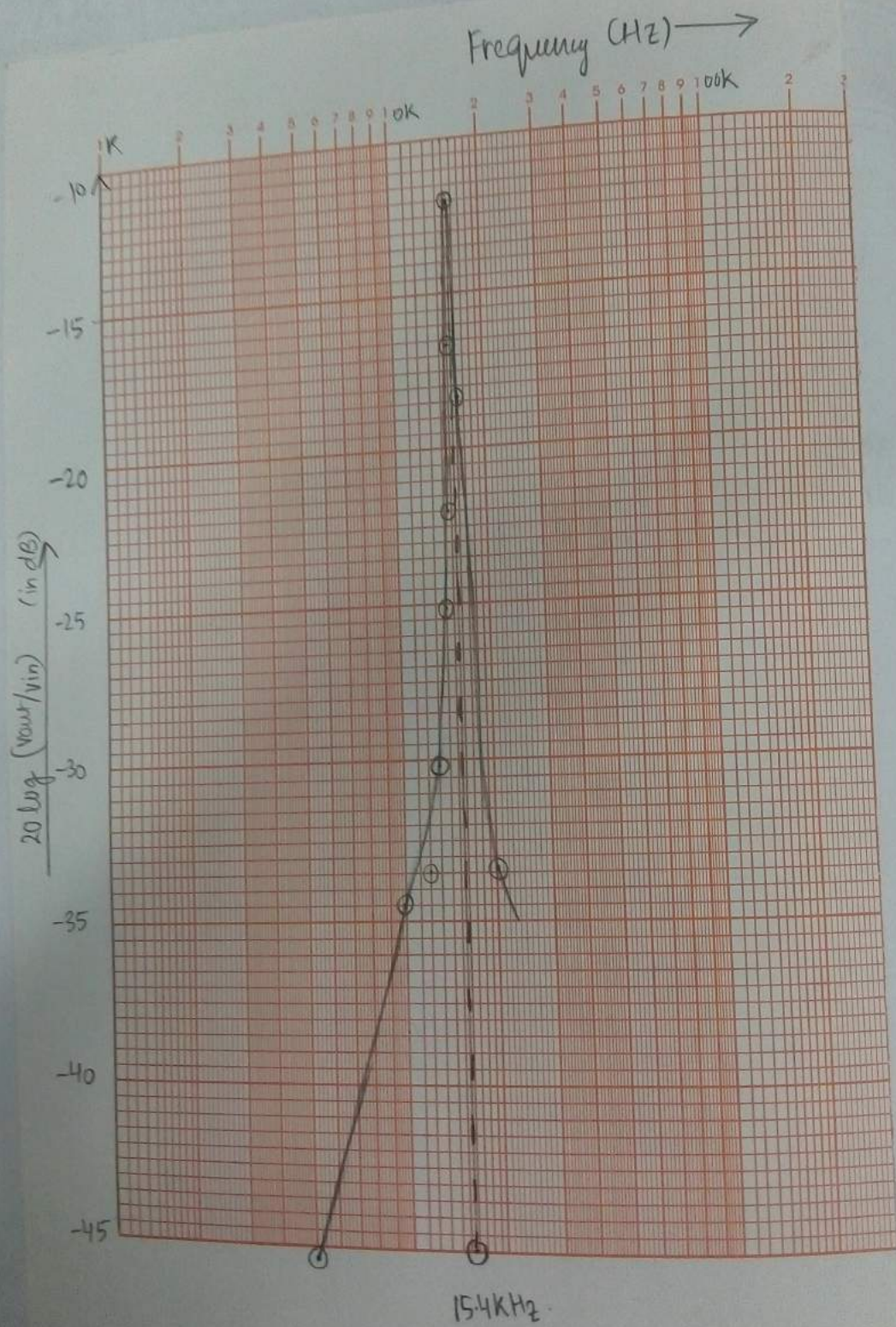

INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 50

OBSERVATIONS:-

Part I


$V_{in} = 3V_{pp}$

Sl. No.	Frequency (in Hz)	V_{out} (in V)	Gain = $\frac{V_{out}}{V_{in}}$	$20 \log \left(\frac{V_{out}}{V_{in}} \right)$ (in dB)
1	100	0	0	-
2	1k	0	0	-
3	5k	15mV	5×10^{-3}	-46.02
4	10k	36mV	0.0187	-34.56
5	12k	64mV	0.021	-73.556
6	13k	92mV	0.0307	-30.266
7	14k	0.16V	0.0533	-25.165
8	14.5k	0.24V	0.080	-21.940
9	15k	0.44V	0.1467	-16.6714
10	15.3k	0.60V	0.200	-13.980
11	15.4k	0.76V	0.2533	-11.927
12	15.5k	0.72V	0.240	-12.396
13	16k	0.36V	0.120	-18.42
14	20k	64mV	✓ 0.0213	-33.432

DATE

SHEET NO. 51

In s domain :

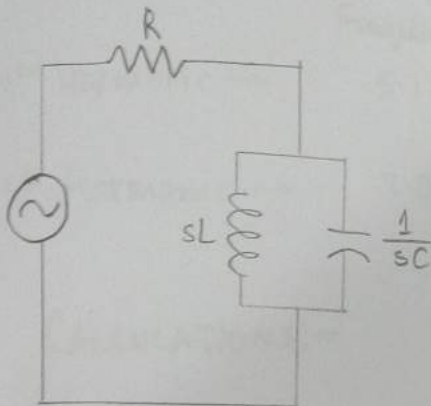

$$I(s) = \frac{V_{in}(s)}{R + (sL \parallel \frac{1}{sC})}$$

$$V_{out}(s) = (sL \parallel \frac{1}{sC}) \left\{ \frac{V_{in}(s)}{R + (sL \parallel \frac{1}{sC})} \right\}$$

Transfer function $G(s) = \frac{V_{out}(s)}{V_{in}(s)}$

$$G(s) = \frac{sL \parallel \frac{1}{sC}}{R + sL \parallel \frac{1}{sC}}$$

*Substituting $s = 2\pi f$, and LCR values, for max value :- $\frac{dG(s)}{ds} = 0$

$$\Rightarrow f = 15.91 \text{ kHz}$$

$$G(s) = \frac{s/Rc}{s^2 + (\frac{1}{RC})s + \frac{1}{LC}} \rightarrow \text{Band pass filter}$$

Part II

$R = 100 \text{ k}\Omega$ $V_{in} = 3.2 \text{ V}$

Sl. No.	L (in mH)	C (in nF)	V _{out} (p-p)	f _o (experimental)	f _c (theoretical)
1	10	10	2.08	15.42 kHz	15.92 kHz
2	10	12	1.96	14.1 kHz	14.53 kHz
3	12	10	2.16	14.09 kHz	14.53 kHz

INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 51

Part III

$V_{in} = 3V$ ~~5 kHz~~

	Frequency (in kHz)	V_o (in V)
3 rd Harmonic \rightarrow	5.13 kHz	0.68V
5 th Harmonic \rightarrow	3.09 kHz	0.44V

CALCULATIONS:-

Theoretically for a square wave:

$$\text{Square}(t) = \frac{4}{\pi} \sum_{k=1}^{\infty} \left[\sin(2\pi f_1 t) + \frac{1}{3} \sin(2\pi f_3 t) + \frac{1}{5} \sin(2\pi f_5 t) + \dots \right]$$

f_1 = Fundamental freq.

f_3 = 3rd Harmonic

f_5 = 5th Harmonic.

Fundamental coefficient (exp.) = 1.08V.

Theoretically, Fundamental $\rightarrow \frac{4}{\pi} \times 1.5 = 1.9V$ (for 3Vpp)

3rd Harmonic $\rightarrow 0.63V$

5th Harmonic $\rightarrow 0.38V$

INDIAN INSTITUTE OF TECHNOLOGY

DATE

SHEET NO. 91

(PART-2)

OBJECTIVE:-

Derivation of V-I characteristic of a diode. Model a non-linear circuit using diode as piecewise linear and then compare its theoretical and experimental transient response.



APPARATUS REQUIRED:-





S.No.	APPARATUS NAME	QUANTITY	SPECIFICATIONS
1.	Function Generator	1	-
2.	Diode	1	1N4148, 200mA, 100V
3.	Resistance	1	100 Ω
		1	1k Ω
4.	CRO	1	-
5.	Capacitance	1	1 μ F.

DATE

SHEET NO. 55

CIRCUIT DIAGRAM:-

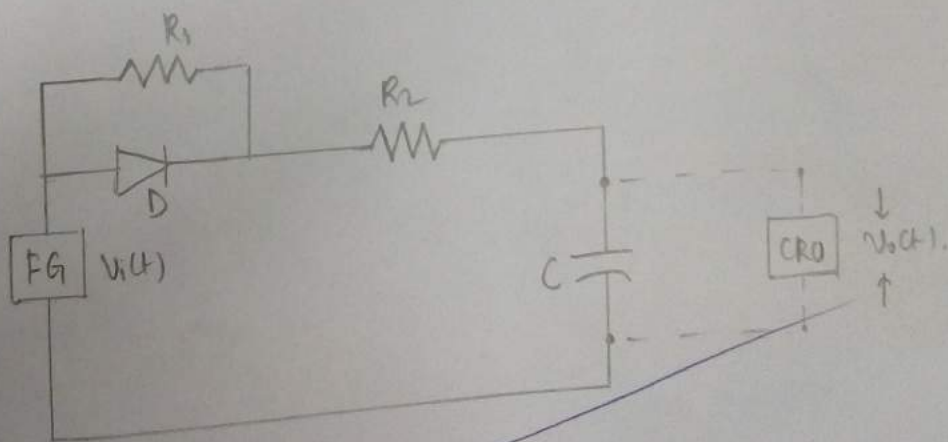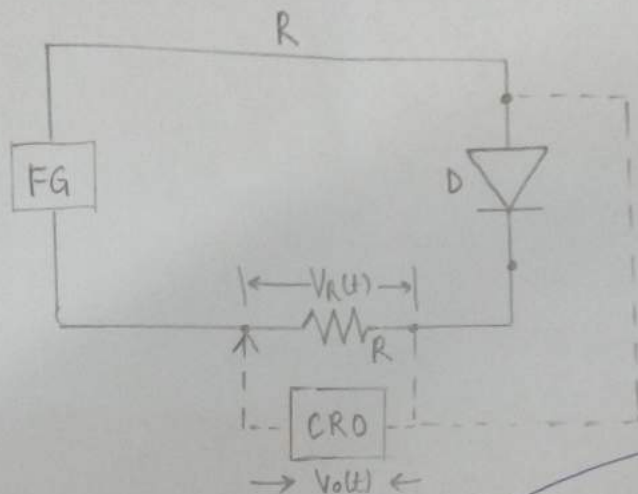

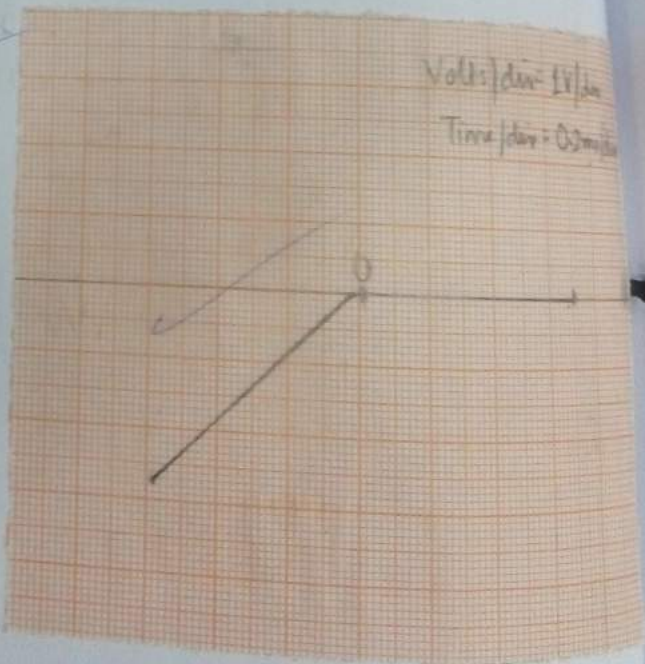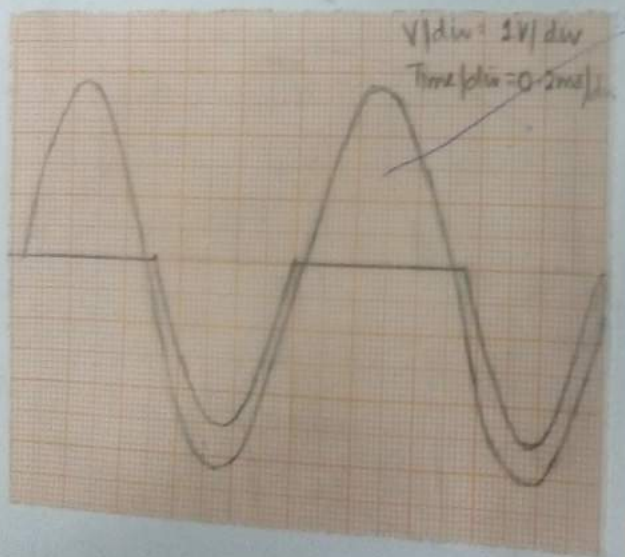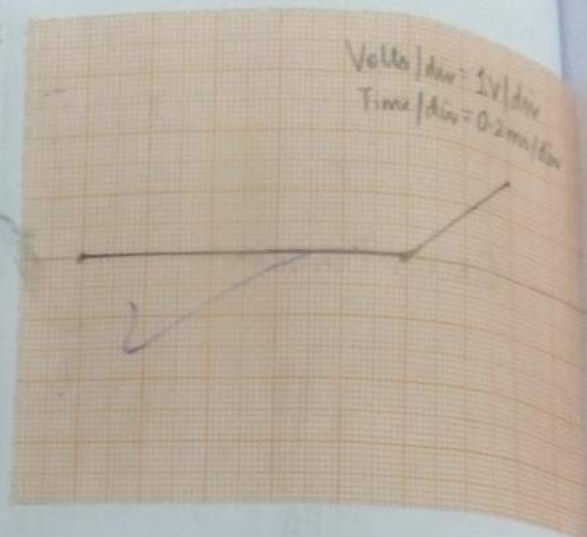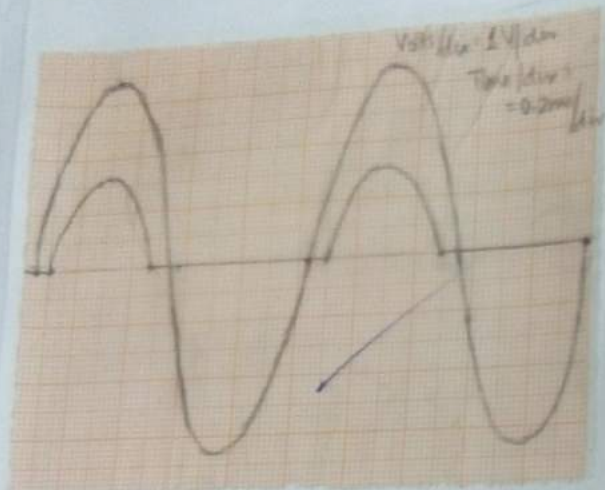

OBSERVATIONS:-

Part I

Forward Biased.

$$V_{in} = 3.98V$$

$$V_{out} = 3.60V$$

$$\text{Frequency} = 1kHz$$


Reverse Biased.

$$V_{in} = 3.46V$$


$$V_{out} = 3.30V$$




$$\text{Frequency} = 1kHz$$

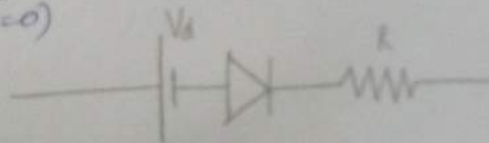As observed from V-I characteristics, the diode can be replaced by a voltage source with a resistance in series and an ideal diode.
($V_f = 0, \eta = 0$)



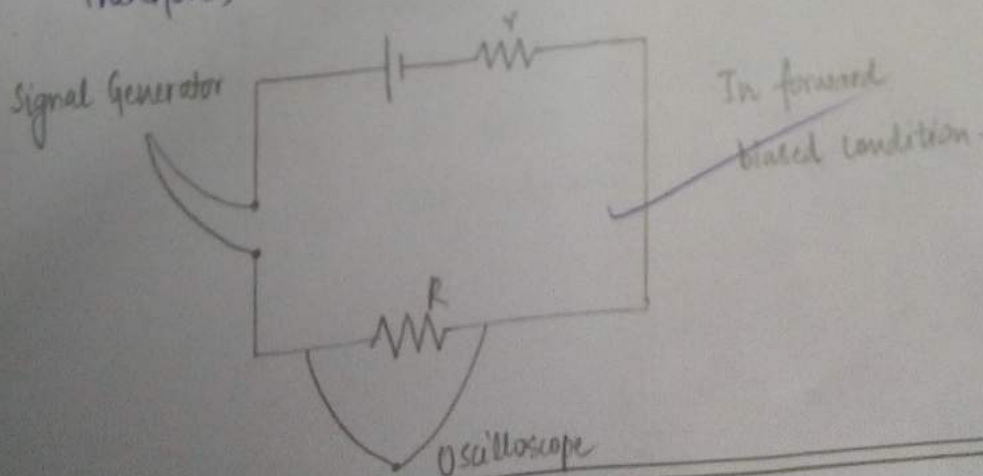This is the two segment piecewise linear model.
Therefore, the circuit becomes:-



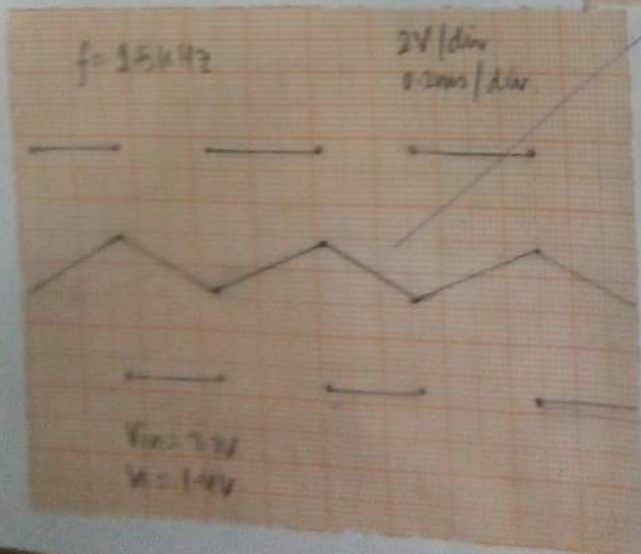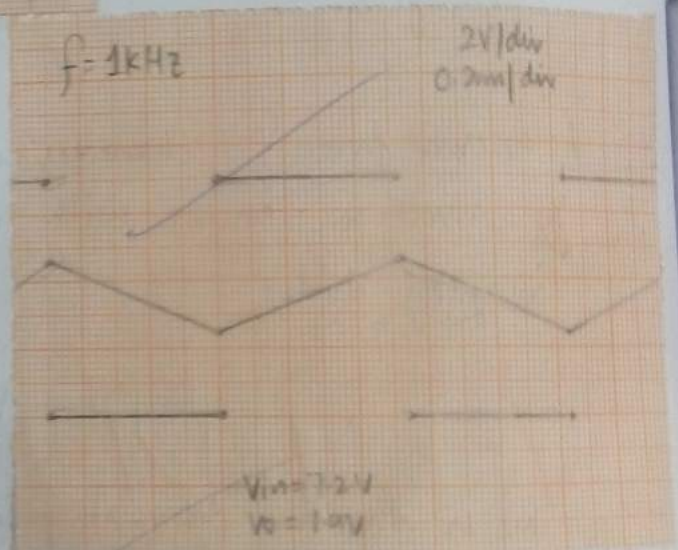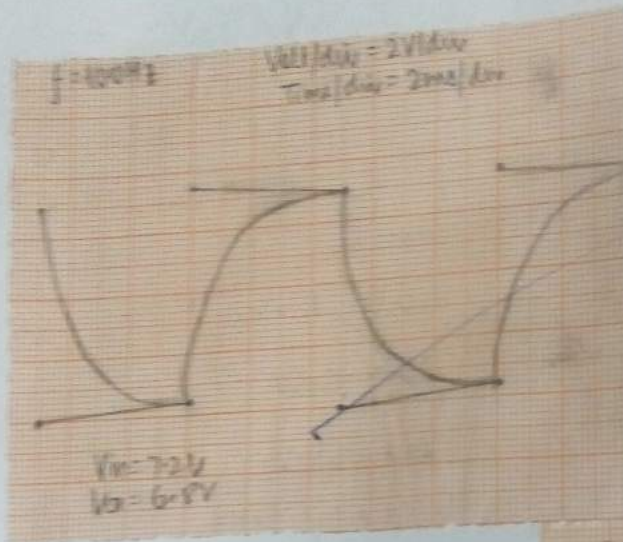

DATE

SHEET NO. 57


Part II

$$V_{in} = 7.20V$$

$$\text{Frequency} = 100\text{ Hz}$$

$$V_{out} = 6.80V$$

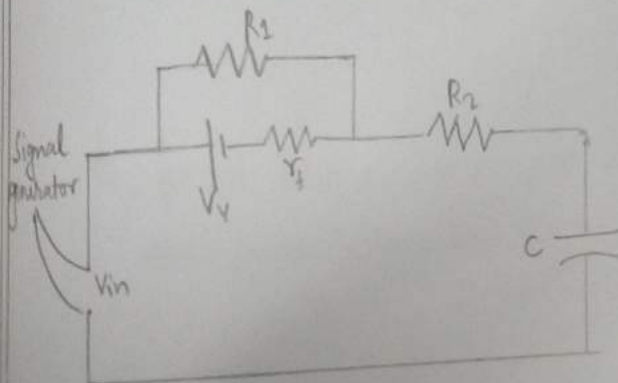Applying piecewise linear model :
(In forward biased condition)




When the capacitor reaches steady state, no current will flow through the circuit.

$$\Rightarrow \text{Voltage across } R_1 = V_f$$

$$\text{Voltage across } R_2 = 0$$


$$\text{Voltage across capacitor (in steady state)} = V - V_f = 6.80V$$

In reverse biased condition:-

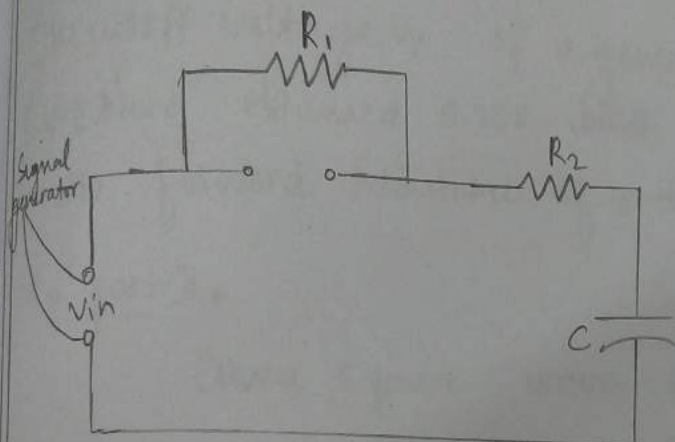

The diode is cutoff and the circuit simplifies to a capacitor in series with $R_1 + R_2$. When the capacitor reaches steady state, no current flows through the circuit.

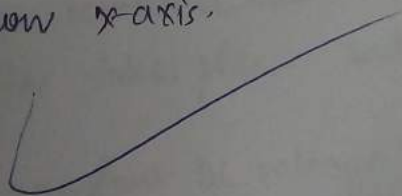The peak above x-axis is a bit smaller than the peak below x-axis.



DISCUSSION :-

The cutoff voltage V_f of a general silicon diode is 0.7V. We have obtained 0.76V which is nearly equal. In general the forward resistance of a diode is very low.

In part II,

Given square wave is applied

$$x(t) = \begin{cases} A & 0 \leq t \leq T/2 \\ -A & T/2 \leq t \leq T \end{cases}$$

In $0 \leq t \leq T/2$, a constant DC voltage of A is applied, the circuit consists of a resistance and capacitor in series. Therefore charging of capacitor takes place and we get a transient response.

In $T/2 \leq t \leq T$, a constant DC voltage of $-A$ is applied and diode gets into the rev. biased mode because of the negative voltage applied. Hence, this also turns out to be a transient because of the resistor and capacitor.

The time constant in both cases are different as in the first case i.e. $0 \leq t \leq T/2$ the forward resistance r_f acts parallel to R_1 , whereas in 2nd case i.e. $T/2 \leq t \leq T$ the diode ckt is cut and there is no r_f , only R_1 & R_2 in series.

$$\tau_1 = (R_2 + R_1 || R_f) C$$

$$\tau_2 = (R_2 + R_1) C$$

Jal
28/10/16