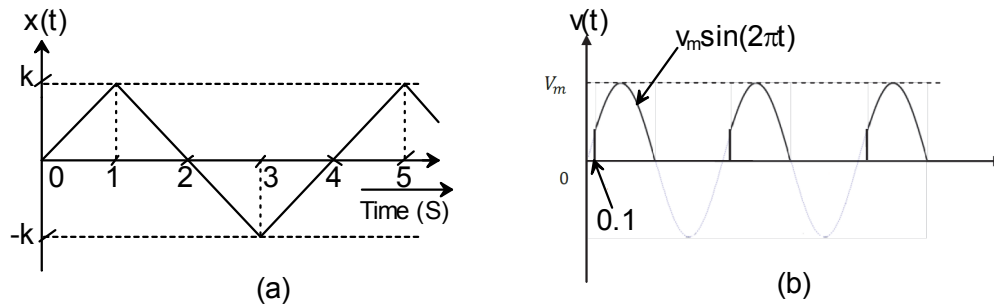


## Tutorial Sheet 2: Single Phase AC Networks


**Q1.** (a) Calculate the (i) rms value, (ii) average value, (iii) form factor and (iv) peak factor of the signal  $x(t)$  as shown in Fig 1(a).

(b) The waveform of the Fig. 1(b) is derived from a sine function and has zero value when the sine function is negative and also from  $t=0$  to  $t=0.1$  and for the corresponding interval of each period. Find the rms value and the average value of this waveform.




**Fig. 1**

**Q2.** For the circuit of Fig. 2, calculate  $I_2$ ,  $I_3$ ,  $V_1$  and  $V_2$ . Draw suitable phasor diagrams to represent them. Calculate the active and reactive powers absorbed by each parallel branch and also the active and reactive power supplied by the current source.

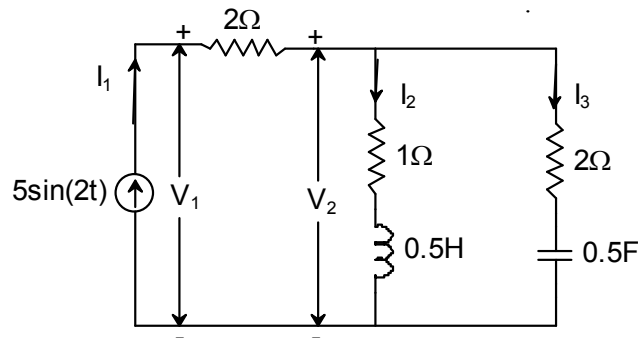

**Fig. 2**


**Q3.** (a) In the circuit shown in Fig. 3, the magnitudes of  $V_L$  and  $V_C$  are twice that of  $V_R$ . Calculate the inductance of the coil.

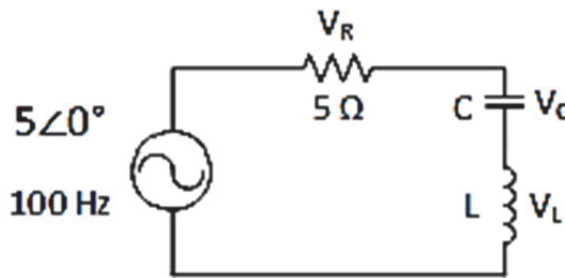

**Fig. 3**


**Q4.** Draw the phasor diagram for current in the circuit,  $V_{AB}$  and  $V_{AC}$ , when 200 V, 50 Hz source is connected across the circuit shown in Fig. 4. Indicate the angles and magnitudes in the diagram with supply voltage as reference.

- Calculate the reactive power drawn by the circuit.
- Find the value of capacitance to be connected in parallel across the circuit to raise the overall power factor of the combination to unity.
- Calculate the current and real power drawn by the combination.

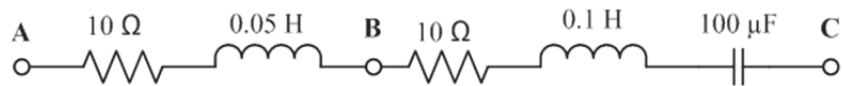


**Fig. 4**

**Q5.** Calculate the current through the  $j5\Omega$  impedance of Fig. 5 using (a) Mesh Analysis, (b) Nodal Analysis and (c) Superposition theorem.

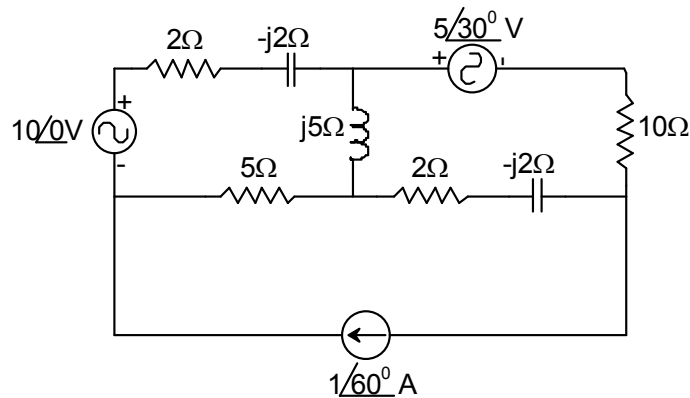


**Fig. 5**

**Q6.** Find  $I_L$  and the voltage across the current source in Fig. 6 using (a) Thevenin's theorem (b) Norton's theorem

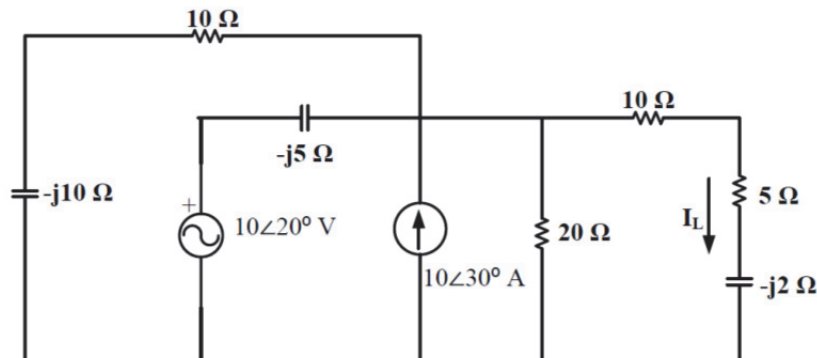


**Fig. 6**

**Q7.** If  $G_2$  of Fig. 7 supplies 5 kW at 0.707 pf lagging, find amount of power supplied by  $G_1$  with pf.

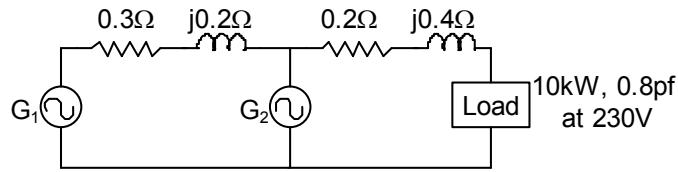

**Fig. 7**


**Q8.** Assuming both the voltage sources are in phase, the value of  $R$  for which maximum power is transferred from circuit A to circuit B in Fig. 8 is

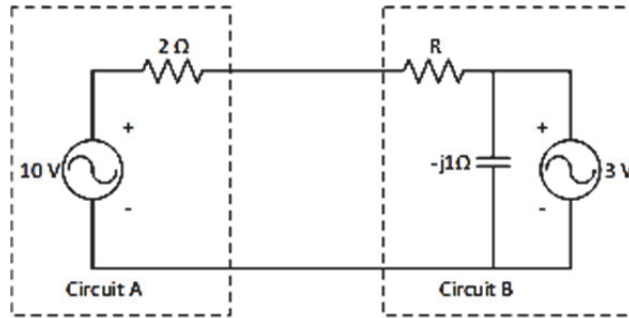

**Fig. 8**

**Q9.** (a) A single phase, 100V, 50Hz source supplies a single phase load having impedance of  $10\Omega$  and power factor of 0.8 (lag) through a line of impedance  $Z_{\text{line}} = (2+j6)\Omega$ , as shown in Fig. 9. A pure capacitor is connected in parallel (shunt) with the load. Two voltmeters,  $V_1$  and  $V_2$ , are connected at the source and load terminals respectively as shown in the figure. Find the minimum value of the capacitance ( $C_{\text{sh}}$ ) such that the readings of the two voltmeters are exactly same. Find the load current ( $\bar{I}_L$ ) and the source current ( $\bar{I}_S$ ) under this condition.

(b) Taking the source voltage as the reference, draw a phasor diagram showing the load terminal voltage, source current, load current and the current into the capacitor ( $\bar{I}_C$ ).

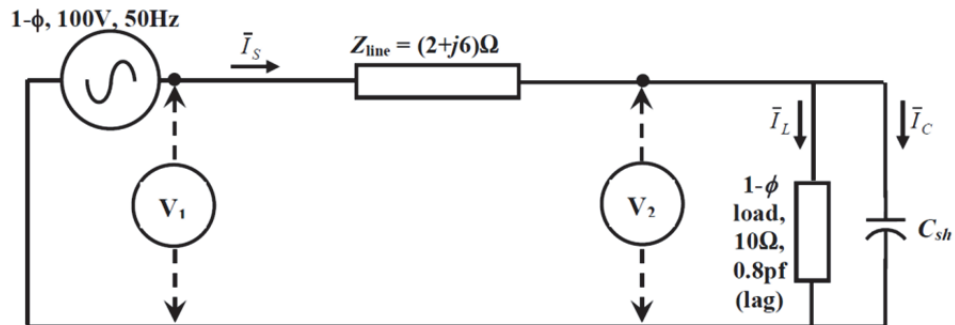

**Fig. 9**