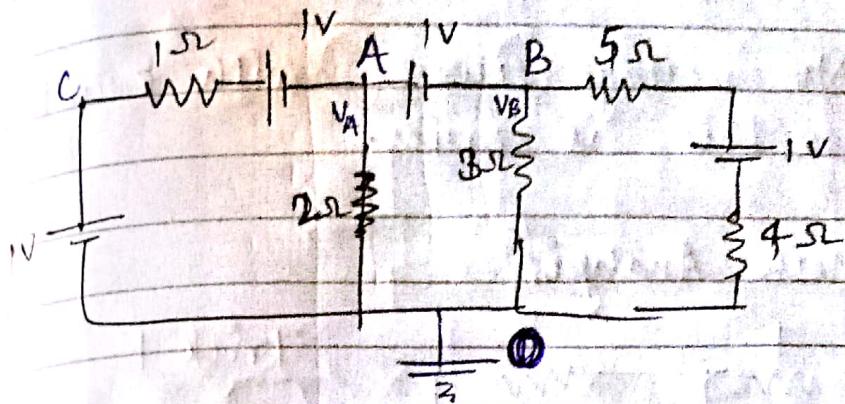


Network Theorems.

Nodal analysis,
KCL for node A,

$$\frac{V_A}{1} + \cancel{\frac{V_A}{2}} + \cancel{\frac{V_A - 1}{3}} = \frac{V_A + 1 - V_C}{1} + \frac{V_A - 1}{0}$$

(Absent ...)

Trick-1

Consider A & B together,


$$V_A = V_B + 1$$

Joint KCL for 'A' & 'B':

$$I_{CA} + I_{OA} + I_{OB} + I_{DB} = 0$$


$$\frac{V_A}{1} + \frac{V_A}{2} + \frac{V_B}{3} + \frac{V_B - 1}{4} = 0$$

Trick-2

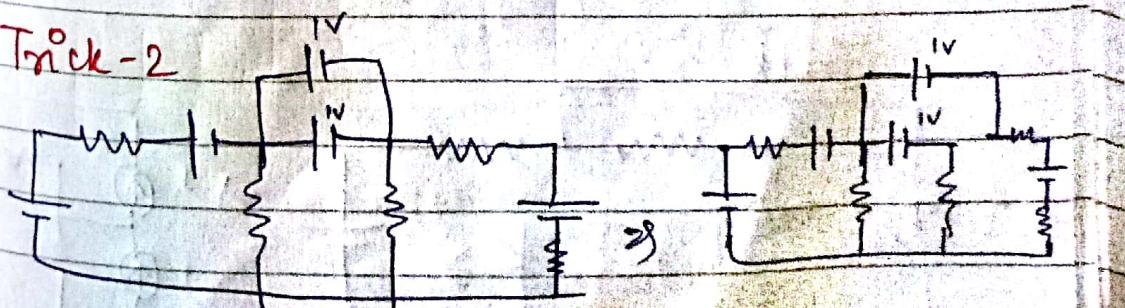

No voltage source with zero impedance so this is easier.


→ Mesh Analysis

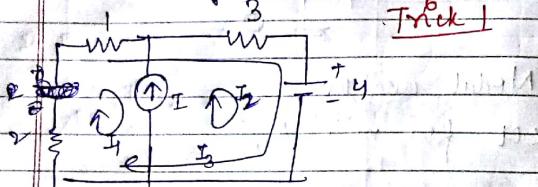

Outer loop \Rightarrow 1 eq.


$$I_2 - I_1 = I$$

Trick 2

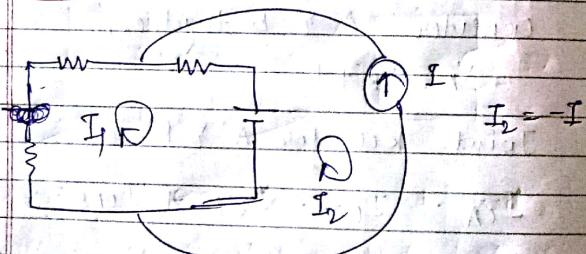

Write mesh for I_1 .


Trick-3

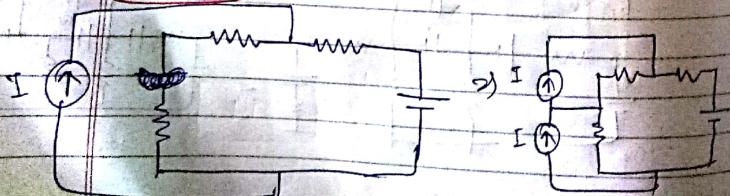

convert current \Rightarrow voltage source.


This is so simple that Trick 3 is not necessary but trick 3 is valid.

Substitution Th.

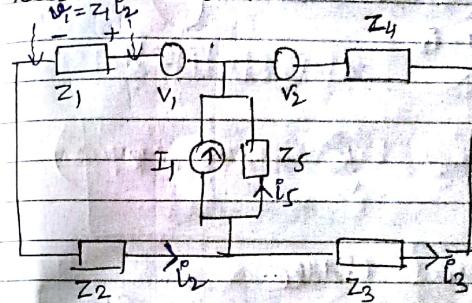

Suppose ckt is solved.


Substitution with voltage source.

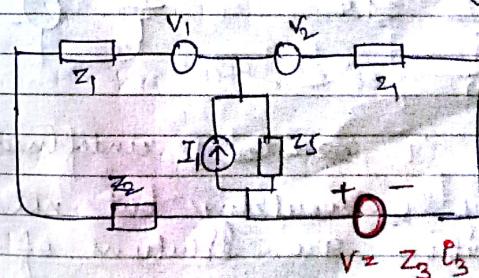

To prove : ① KCL


② KVL

③ $V_K = Z_K i_K$

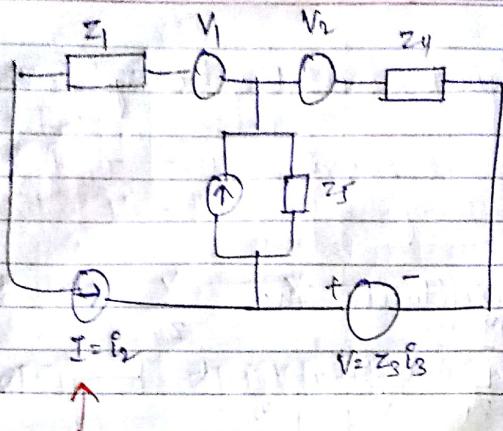

(Replaced by current source)



* Advanced Riddle:

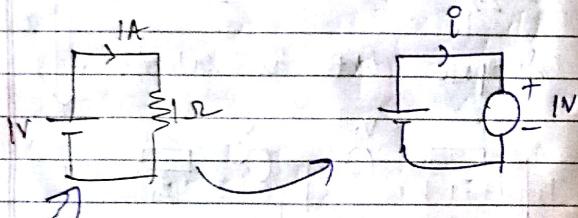

i is undefined, it may be something but not of all solutions are solutions of,

compensation thro.

use Prev. ckt.

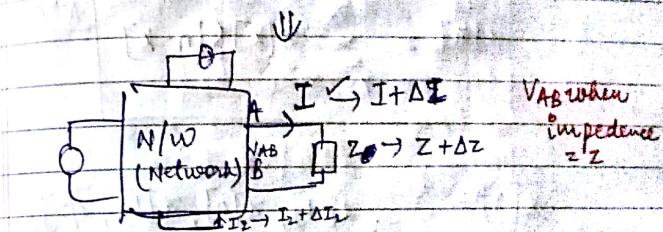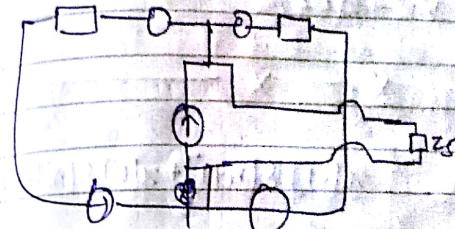

Suppose N/W is solved once.

Modify $Z \rightarrow Z + \Delta Z$
 $I \rightarrow I + \Delta I$


Task: To find

$$\textcircled{1} \quad I + \Delta I = ?$$

$$\textcircled{2} \quad I_2 + \Delta I_2 = ?$$




Answer 1 by solve again.

" 2 by use compensation thro."


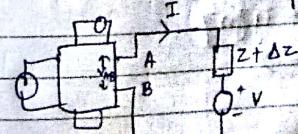


* Network theorems.

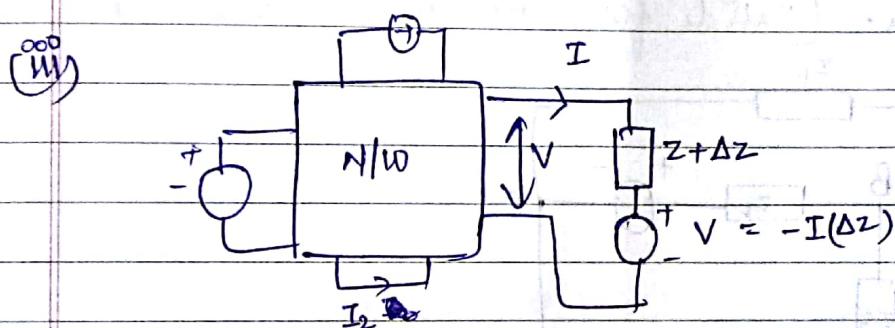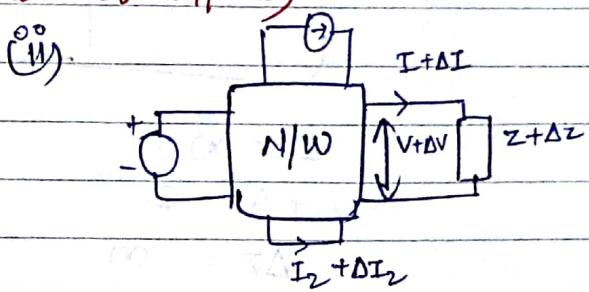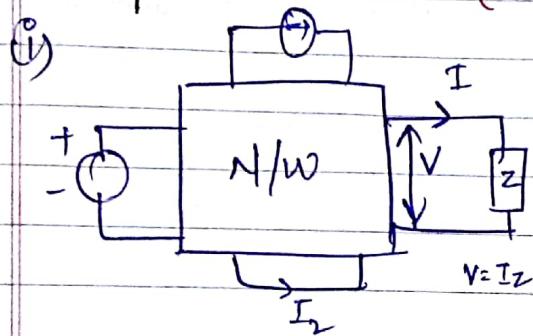① Compensation th. (Only for linear N/Ws)



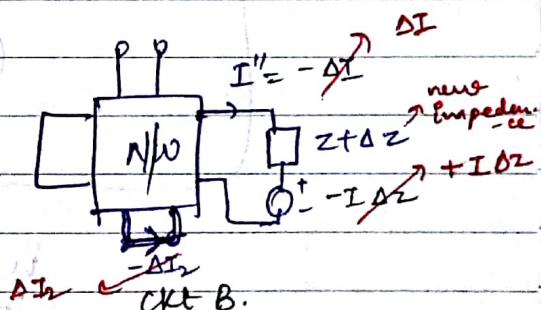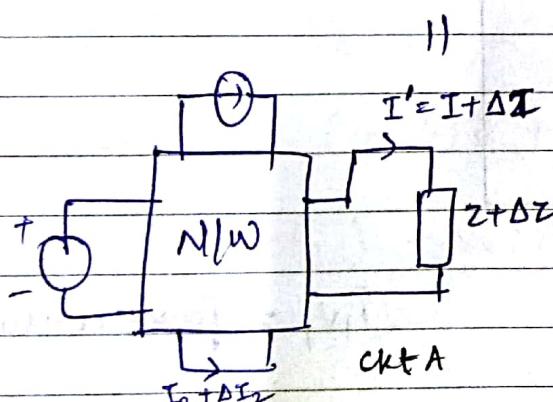We used
compensating
source &
change in
impedance.



$$I' + I'' = I$$


$$\Rightarrow I'' = -\Delta I$$

To get ΔI , Just solve
ckt B

To get ΔI_2 , Just solve
ckt. B

~~H.W.~~

Q.

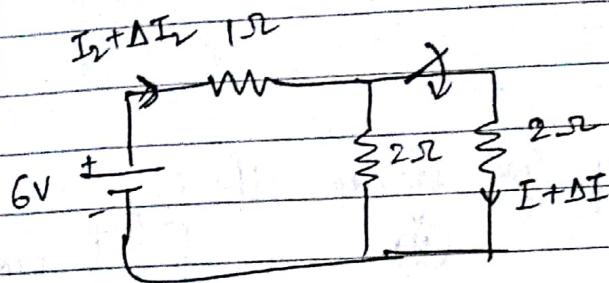

find ΔI & ΔI_2
using compensation th.


use compensating I-
source & change in
admittance.

$$Z = \infty$$


$$Z + \Delta Z = 2$$

$$\Delta Z = -\infty$$

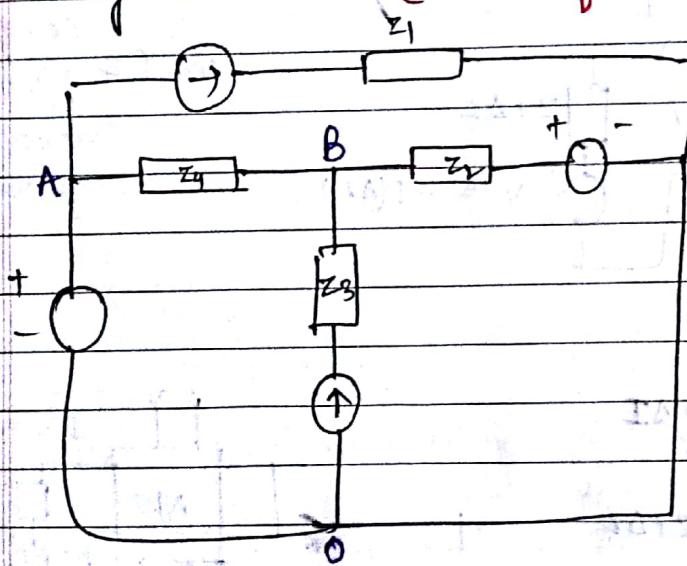* Tellegen's th. (Valid for nonlinear ckt. also)





$P_i V_i$ = Power consumed

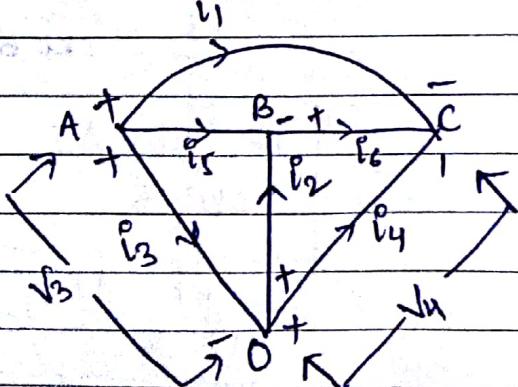

$$\sum_{k=1}^6 P_k V_k = 0$$

{all branches}

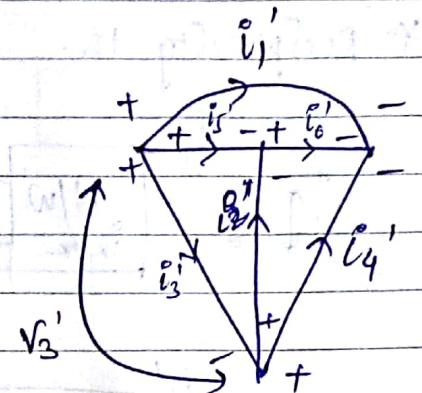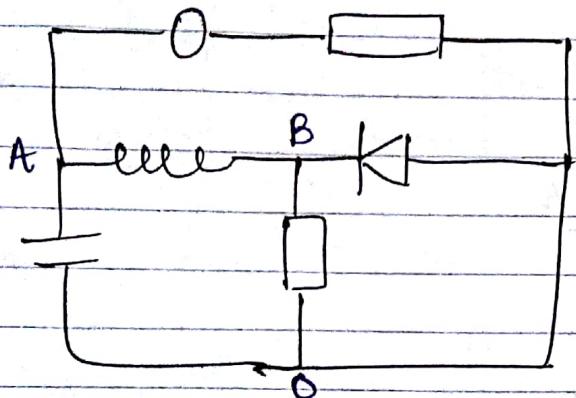Now, if the topology is same but elements
are diff. for a ckt.



Theorem says,

$$\sum_k \rho_k v_k' = 0$$

$$\sum_k i_k' v_k = 0$$

$$\sum_k v_k i_k' = 0$$

$$\Rightarrow V_{OB} i_2' + V_{AC} i_1' + V_{AB} i_5' + V_{BC} i_6' + V_{AO} i_3' + V_{OC} i_4'$$

$$= (V_O - V_B) i_2' + (V_A - V_C) i_1' + (V_A - V_B) i_5' + (V_B - V_C) i_6' + (V_A - V_O) i_3' + (V_O - V_C) i_4'$$

$$= V_O (i_2' + i_4' - i_3') + V_A (i_1' + i_5' + i_3') + V_B (-) + V_C (-)$$

$$= 0$$

$$\sum k v_k i_k' = 0$$



$$\sum k v_k' i_k = 0$$

* Substitution.

A slight modification will make it cope with nonlinearity

Q Is Telegence valid ^{only} for linear N/W?
NO (as $V = IR$ not used)

* Reciprocity th.

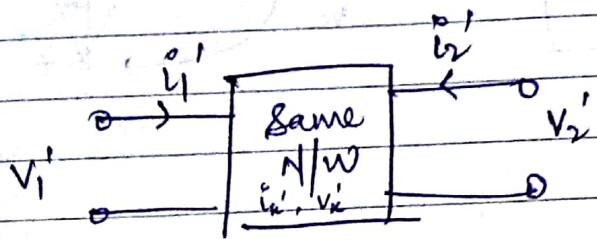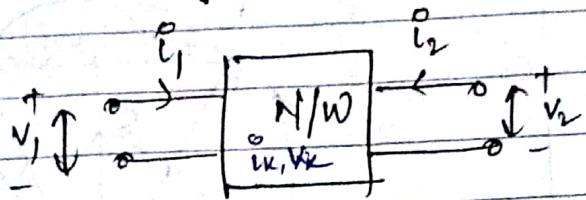

$$\sum_{k=1,2} \rho_k v_k = 0$$

$$\Rightarrow i_1 v_1 + i_2 v_2 + \sum_k \rho_k v_k = 0$$


$$\sum_k \rho'_k v'_k = 0$$

$$\Rightarrow i'_1 v_1 + i'_2 v_2 + \sum_k \rho'_k v'_k = 0$$


New conditions

① N/W is linear ($V = IZ$)

② N/W is passive. (No energy source)

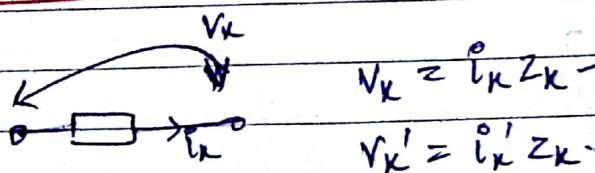
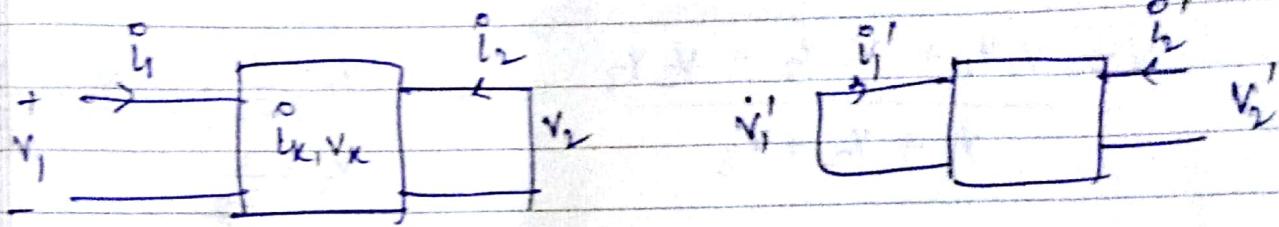
$$\Rightarrow i_1 v_1 + i_2 v_2 = i'_1 v'_1 + i'_2 v'_2$$



$$\Rightarrow i_2 V_2' = i_1' V_1$$

$$\Rightarrow \boxed{\frac{i_2}{V_1} = \frac{i_1'}{V_2'}}$$

$$\Rightarrow \left(\frac{O/P}{I/P} \right)_{N/W_1} = \left(\frac{O/P}{I/P} \right)_{N/W_2}$$



~~H.W.~~

Q. Consider,

I/P = current source


O/P = Voltage measured with voltmeter by open circuiting the O/P port.

* Millman's th.

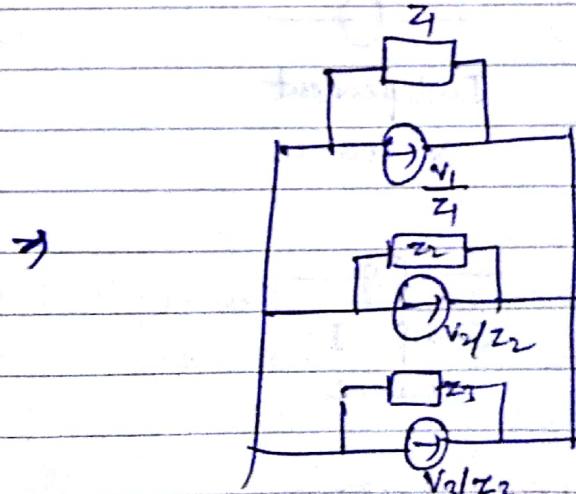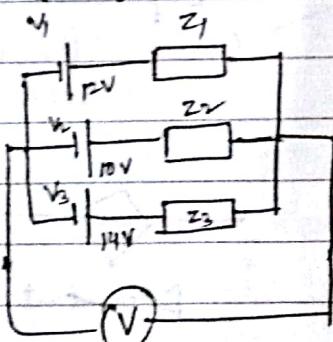


$$\frac{V_1 + V_2 + V_3}{z_1}$$

$$= \frac{1}{z_1 + z_2 + z_3}$$


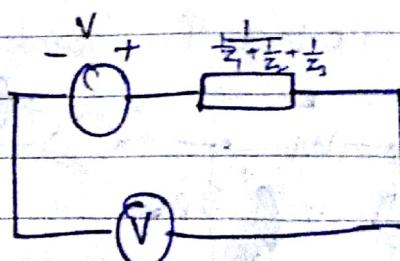


$$V = \frac{V_2}{z_1} + \frac{V_2}{z_2} + \frac{V_3}{z_3}$$



$$V = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3} ; \quad Y_1 = \frac{1}{Z_1}, \quad Y_2 = \frac{1}{Z_2}, \quad Y_3 = \frac{1}{Z_3}$$

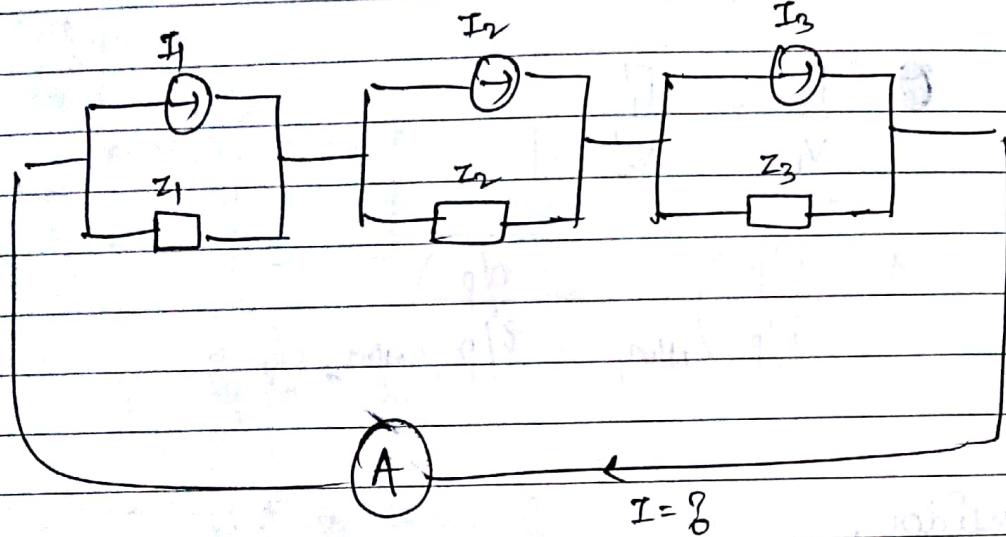~~H.W.~~

* Dependent sources:

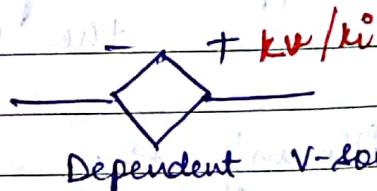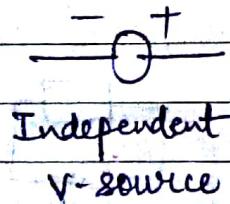



- Only Linear dependency is followed.

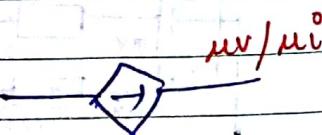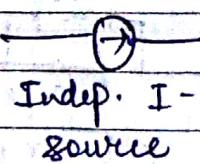



$k = \text{const.}$

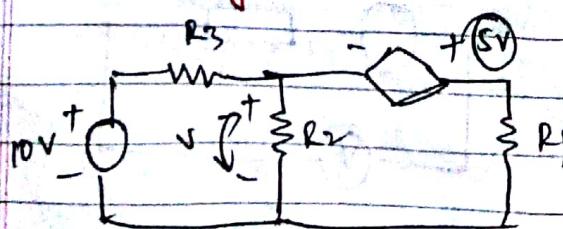$V = \text{Voltage in some other branch.}$



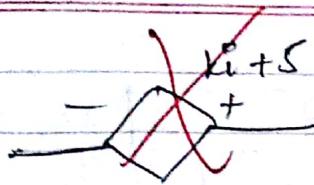

Not allowed.

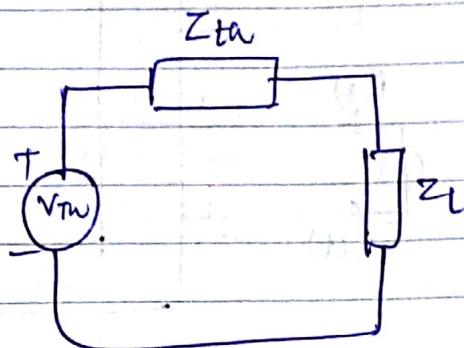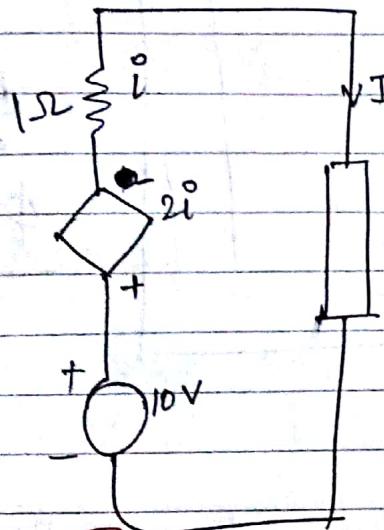


$$V_{Th} = 10 \text{ V} \quad (\because i=0)$$

Assume
 $Z_{Th} = 1\Omega$

$$I_L = \frac{10}{1+1} = 5 \quad X$$

$$10 - 2i - i - i = 0$$

$$i = 2.5$$


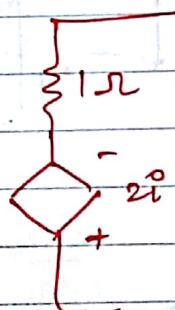


Note: Never remove dependent sources while applying Thévenin's th., superposition th. etc.

* Mutual Inductance & transformer.




$$\frac{di(t)}{dt} = \text{fve}$$

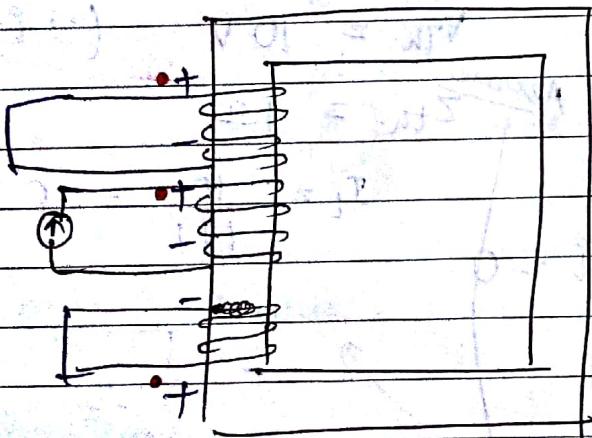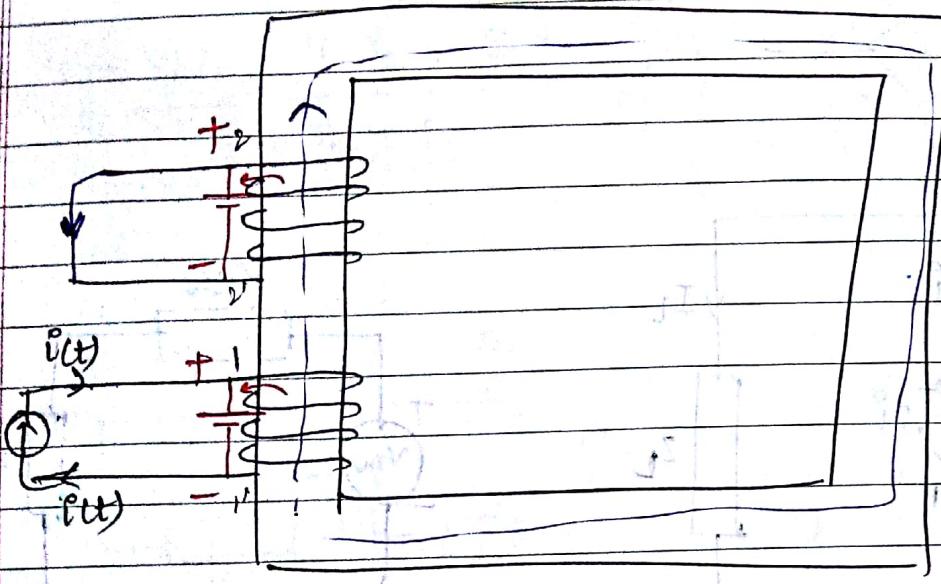Dot convention


→ All +ve or All -ve together.

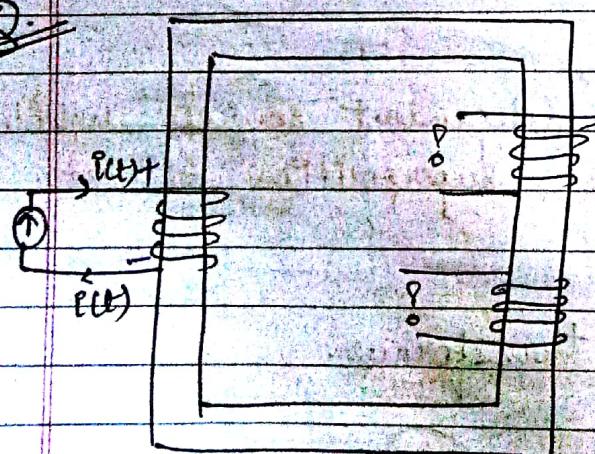→ If current enters coils, through dots the flux generated are all in the same direction.



$$\frac{di}{dt} = +ve$$

* Energy stored in coils.

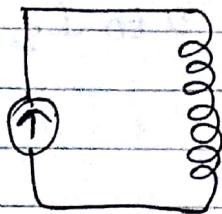

$$E = \frac{1}{2} L I^2$$


* Definitions.

$$(1) L = \frac{\text{flux}}{I} = \frac{N\phi}{I} \quad \text{or} \quad L = \frac{V}{(di/dt)}$$

$$V = \frac{d\phi}{dt}$$

$$V = N \frac{d\phi}{dt} = \frac{d\phi}{dt}$$

flux linkage $\rightarrow \psi = N\phi$

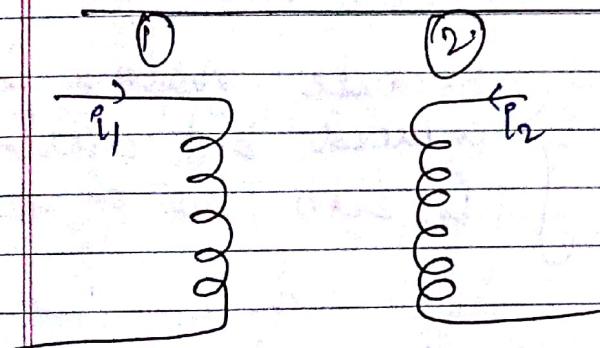


$$\phi_{21} = M_{21} I_1$$

\uparrow
Mutual Inductance

$$\phi_{12} = M_{12} I_2$$

$$V_1 = M_{12} \frac{dI_2}{dt} \quad ; \quad V_2 = M_{21} \frac{dI_1}{dt}$$

* Energy in pair of coils.

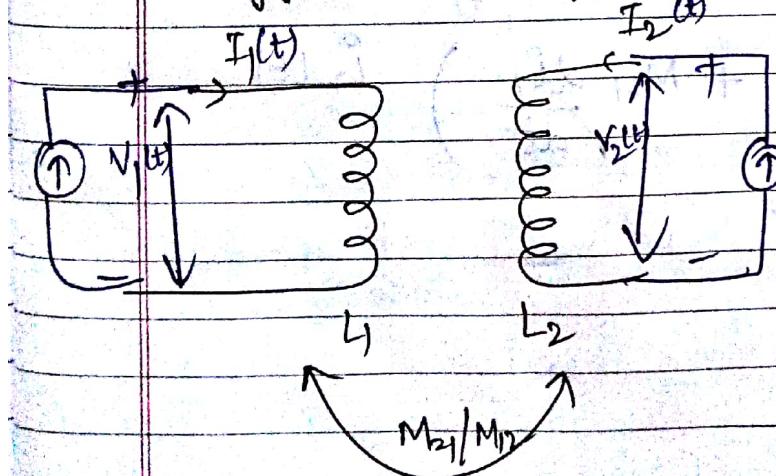

At any instant, 't'

$$P(t) = V_1(t) I_1(t) + V_2(t) I_2(t)$$

func. of
 I_1, I_2

func. of
 I_1, I_2

For simplicity of calculation, I shall first increase I_1 from 0 to I_1 & then keeping I_1 const. increase I_2 from 0 to I_2

Phase 1

$$I_2 = 0$$

Power in coil 1

$$\int P_1(t) dt = \int V_1 i_1(t) dt$$

$$= \int L_1 \frac{di_1}{dt} \cdot i_1(t) dt$$

$$E_1 = \frac{1}{2} L_1 i_1^2$$

$$E_2 = 0$$

} Because voltage is induced but current is zero, so $E_2 = 0$.

Phase 2

$$i_1(t) = I_1 = \text{const.}$$

Power in coil 2

$$P_2(t) = V_2(t) i_2(t)$$

$$= \left(L_2 \frac{di_2}{dt} + M_{21} \frac{di_1}{dt} \right) i_2(t)$$

$$E_2(t) = \frac{1}{2} L_2 i_2^2$$

Power in coil 1,

$$P_1(t) = V_1(t) I_1$$

$$= M_{12} \frac{di_2}{dt} \cdot I_1$$

$$= M_{12} I_1 I_2$$

$$\text{Total energy} = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{12} I_1 I_2$$

If we would have done this in oppo. order then we would have got,

$$E_{\text{Total}} = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{21} I_1 I_2$$


$$\therefore [M_{12} = M_{21}]$$

$$E \geq \frac{1}{2} \left[(\sqrt{L_1} I_1 - \sqrt{L_2} I_2)^2 + 2(\sqrt{L_1 L_2} + M) I_1 I_2 \right]$$

$$\approx \\ > 0$$


$$M > -\sqrt{L_1 L_2}$$

e.g.

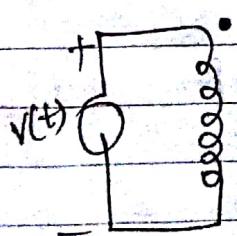


$$t = t_0$$

$$V(t) > 0$$

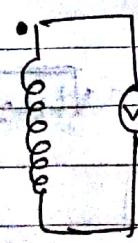


$$V > 0$$

Voltmeter reading

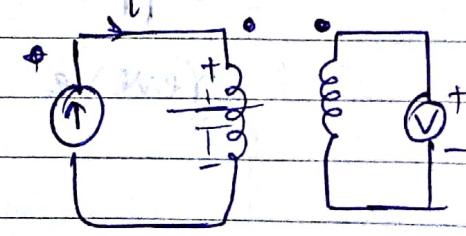

$$\frac{di}{dt} > 0 \Rightarrow V > 0$$
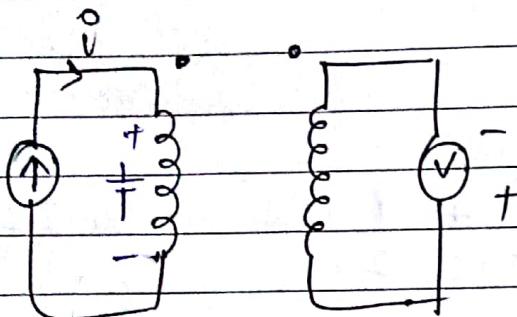
$$M_{21} = \frac{V}{\frac{di^o}{dt}} > 0$$




$$\frac{di^o}{dt} > 0 \Rightarrow V < 0$$

$$M_{21} = \frac{V}{\frac{di^o}{dt}} < 0$$

* Energy in a pair of coils:
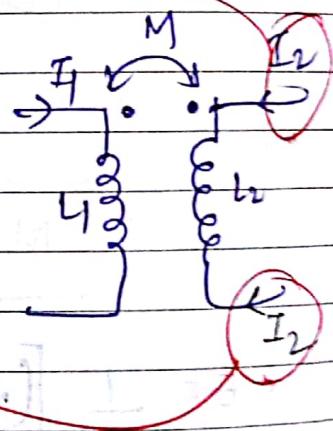
$$E = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 - M I_1 I_2$$



$$= \frac{1}{2} [(\sqrt{L_1} I_1 - \sqrt{L_2} I_2)^2 + 2\sqrt{L_1} I_1 I_2 + M I_1 I_2]$$

$$M + \sqrt{L_1 L_2} > 0$$

$$M > -\sqrt{L_1 L_2}$$

Suppose $M = \sqrt{L_1 L_2} + p$

Reverse polarity $M = -\sqrt{L_1 L_2} - p$


$$|M| \leq \sqrt{L_1 L_2}$$

Not possible if $p > 0$
 $\Rightarrow p = 0$


Defⁿ

$$\frac{M}{\sqrt{L_1 L_2}} := k \leq 1$$

↑
coeff. of mutual inductance.

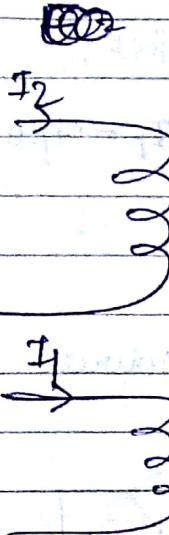If $I_1 > 0$ & $I_2 > 0$ 
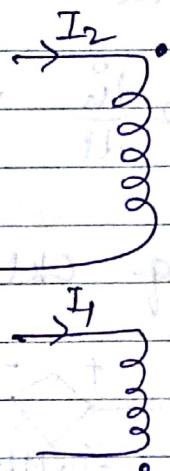
$$E = E_1 + E_2 + \text{coupling energy}$$




$$E = E_1 + E_2 - \text{coupling energy}$$

Very close

$$\Rightarrow M \approx \sqrt{L_1 L_2}$$



$$|M| = \sqrt{L_1 L_2}$$

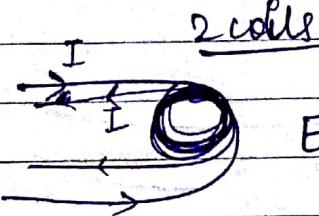


$$I_1 = I, I_2 = -I, M = \sqrt{L_1 L_2}$$

$$E = \frac{1}{2} L I^2 + \frac{1}{2} L I^2 + \sqrt{L_1 L_2} I^2$$

$$LI^2 - LI^2 = 0$$

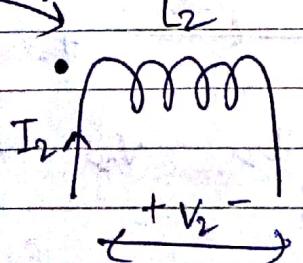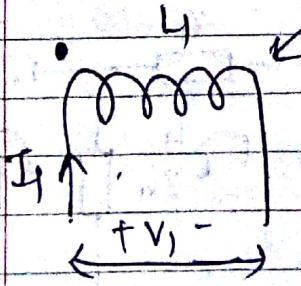Magnitude of mutual ind. = $M > 0$ 

$$V_1 = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$

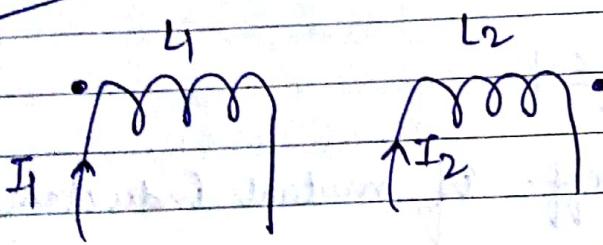Same

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$


$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

$$I_1 = i_1 e^{j\omega t}$$

$$I_2 = i_2 e^{j\omega t}$$

$$\Rightarrow V_1 = L_1 j\omega i_1 - M j\omega i_2$$

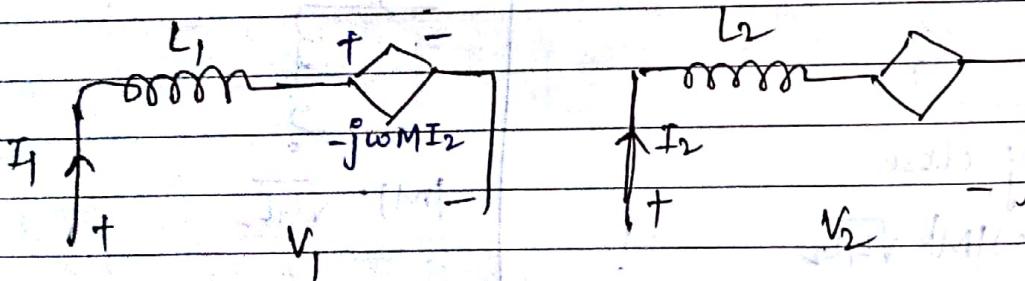* Draw an eq. ckt. with dependent sources



No coupling


$$V_1 = j\omega L_1 I_1 - j\omega M I_2$$

as V₁ should be

$$L_1 j\omega I_1 - M j\omega I_2$$

Same

we get V_{dependent source} = -jωMI₂

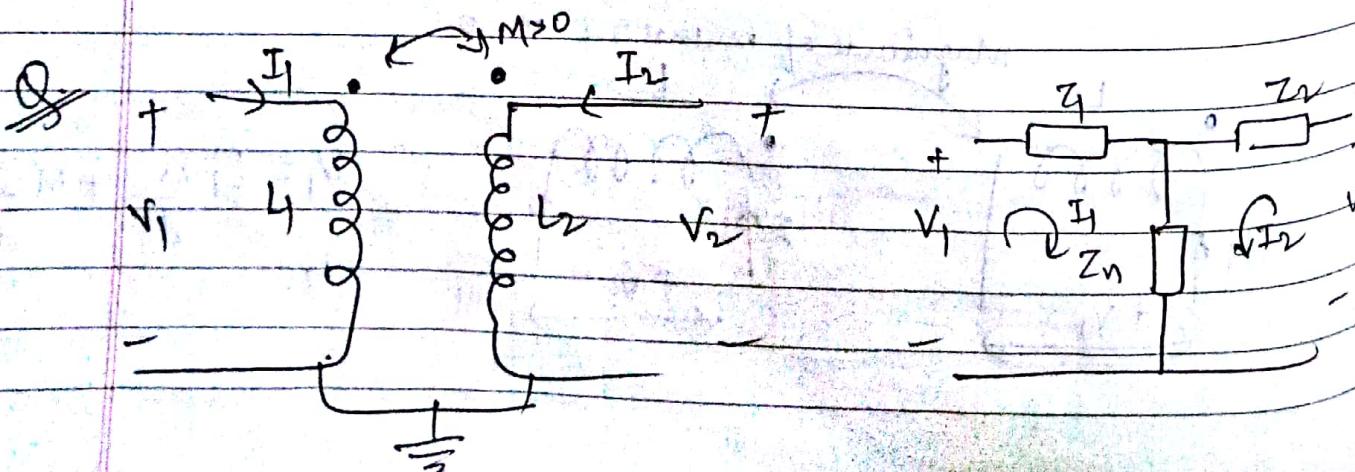

$$N_i = R\phi \quad ; \quad N_i^o = MMF$$

R = Reluctance.

classmate

Date _____

Page _____

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$


Find Z_1, Z_2, Z_n
for these circuits
to be equivalent.

$$Z_1 = j\omega L_1 - j\omega M$$

$$Z_2 = j\omega L_2 - j\omega M$$

$$Z_n = j\omega M$$

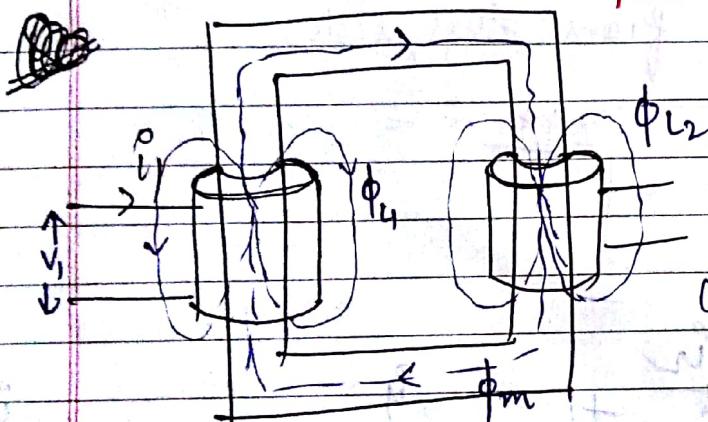for Ideal transformer, $\phi_{L1} = 0$
(No leakage) $\phi_{L2} = 0$



To find an expression
for L_1, L_2 . In terms of M .

$$(due to i_1) V_1 = \frac{d\phi_1}{dt} = \frac{d(N_1 \phi_1)}{dt}$$

$$= \frac{d}{dt} N_1 (\phi_m + \phi_{L1})$$

$$= \frac{N_1}{dt} \left(\frac{N_1 i_1}{R} + \frac{N_1 i_1}{Ra} \right)$$

$$(due to i_2) V_2 = \frac{d N_2 (\phi_m)}{dt} = \frac{d}{dt} \left(\frac{(N_1 i_1)}{R} \right) N_2$$

$$M_{21} = \frac{V_2}{\frac{di_2}{dt}} = \frac{N_1 N_2}{R} = M$$

$$L_1 = \frac{V_1}{\frac{di_1}{dt}} = \frac{N_1^2}{R} + \frac{N_1^2}{Ra}$$

$$L_1 = \frac{N_1}{N_2} \cdot \frac{N_1 N_2}{R} + \frac{N_1 N_1}{Ra} \rightarrow \text{Reluctance of air.}$$

$$L_1 = \frac{N_1}{N_2} M + L_{u1} = aM + L_{u1}$$



↑ Turns. Ratio

$$\therefore L_1 = aM + L_{u1}$$

~~XXX~~

Now, by exciting from other side,
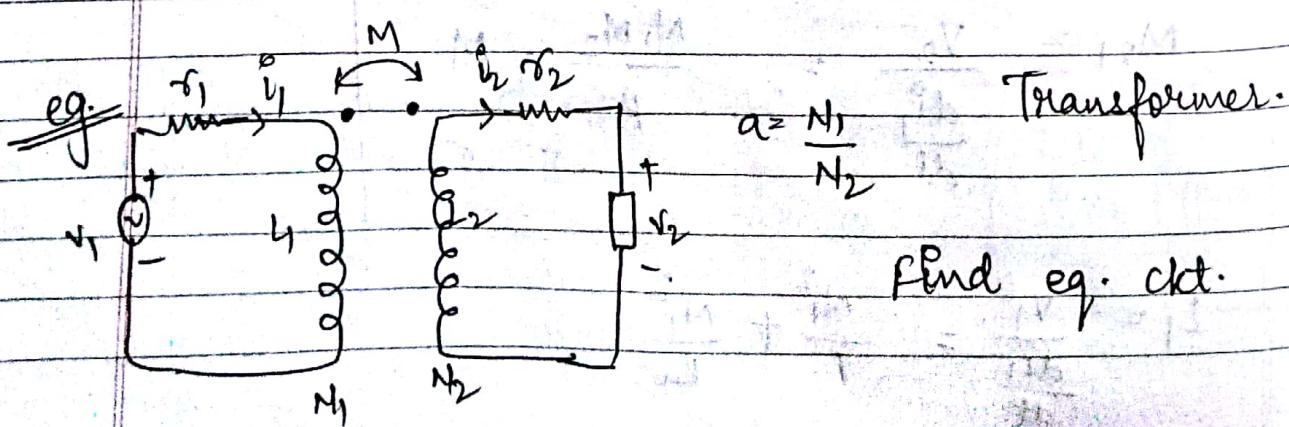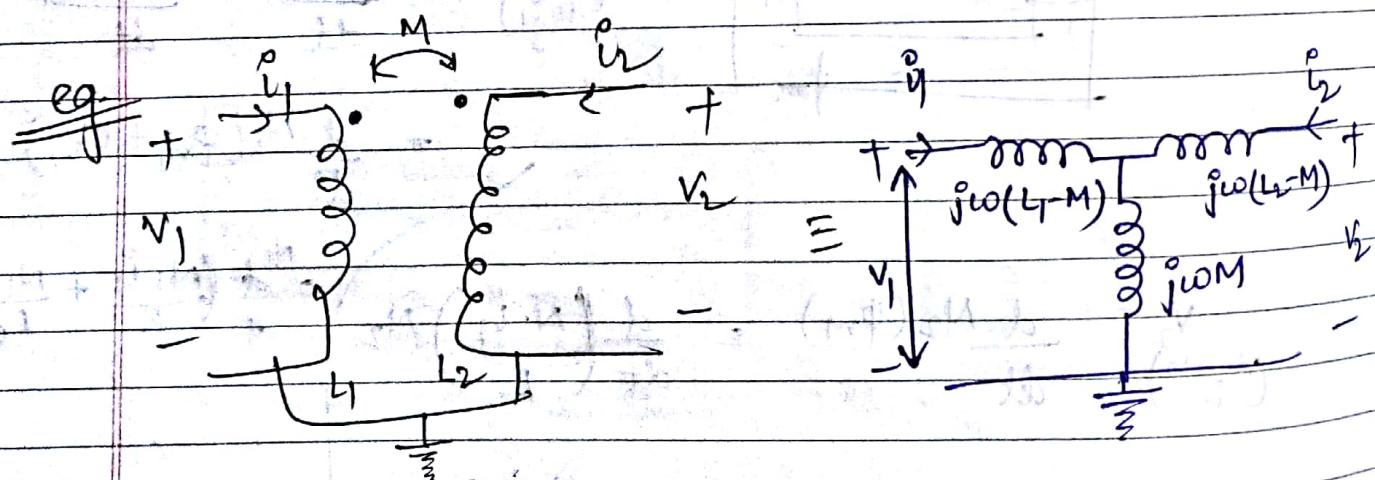
$$L_2 = \frac{M}{a} + L_{u2} \quad \boxed{\text{XXX}}$$



$$a = \frac{N_1}{N_2}$$

Transformer.

Find eq. ckt.

$$V_1 = i_1 r_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = -i_2 r_2 - L_2 \frac{di_2}{dt}$$

$$+ M \frac{di_1}{dt}$$

why "plus"
as current in
coil 1 enters
dot $\Rightarrow + M \frac{di_1}{dt}$
coil 2 ~~goes~~
dot = +ve voltage

$$V_2 = \frac{V_1}{a}$$

$$l_2 = l_1 a$$

$$V_2 a := V_2' \quad \text{defined as}$$

Just to bring the voltages on both sides to a similar range.

$$\frac{i_2}{a} = i_2' \rightarrow$$

$$\therefore aV_2 = a^2 \left(-\frac{i_2}{a} \right) r_2 + a^2 L_2 \frac{d}{dt} \left(-\frac{i_2}{a} \right) + aM \frac{di_1}{dt}$$

Put the value of L_1 & L_2 ($L_1 = aM + L_1$
 $L_2 = \frac{M}{a} + L_2$)




$$① V_1 = i_1 r_1 + aM \frac{di_1}{dt} + L_1 \frac{di_1}{dt} + aM \frac{d}{dt} \left(-\frac{i_2}{a} \right)$$

$$② aV_2 = a^2 \left(-\frac{i_2}{a} \right) r_2 + a^2 \frac{d}{dt} \left(\frac{M}{a} \frac{d(-i_2)}{dt} \right) + a^2 L_2 \frac{d}{dt} \left(-\frac{i_2}{a} \right) \\ + aM \frac{di_1}{dt}$$


$$\Rightarrow aV_2 = \left(\frac{-i_2}{a}\right) r_2 a^2 + a^2 L_{t2} \frac{d}{dt} \left(\frac{-i_2}{a}\right) + aM \frac{d}{dt} \left(\frac{i_1}{a}\right)$$

$$+ aM \frac{d}{dt} i_1$$

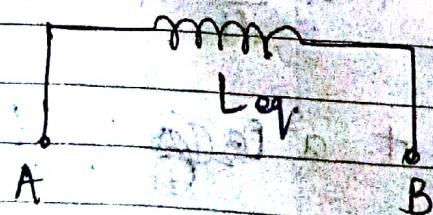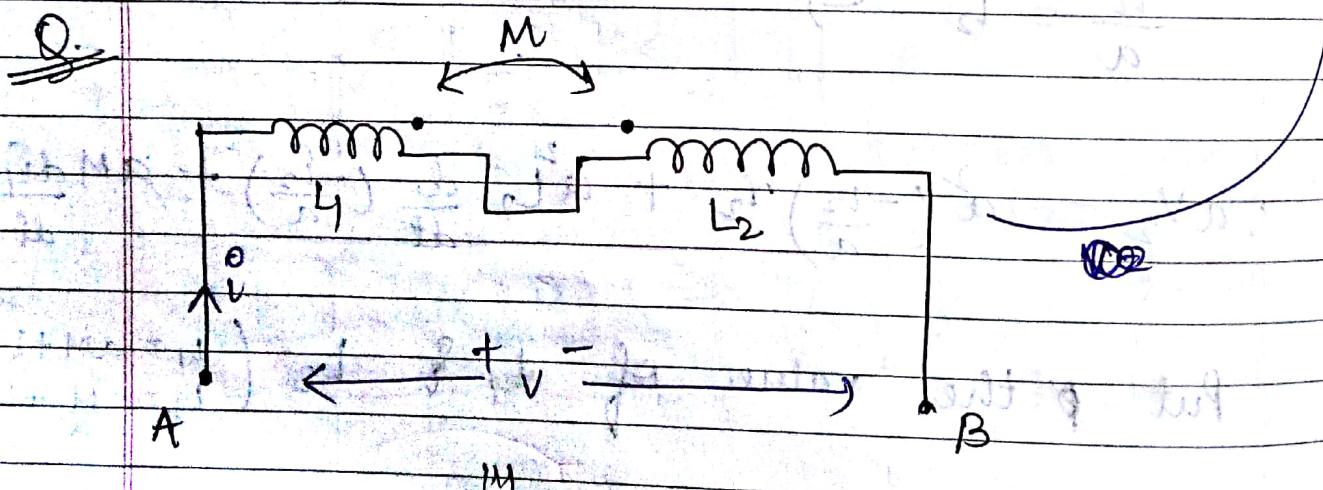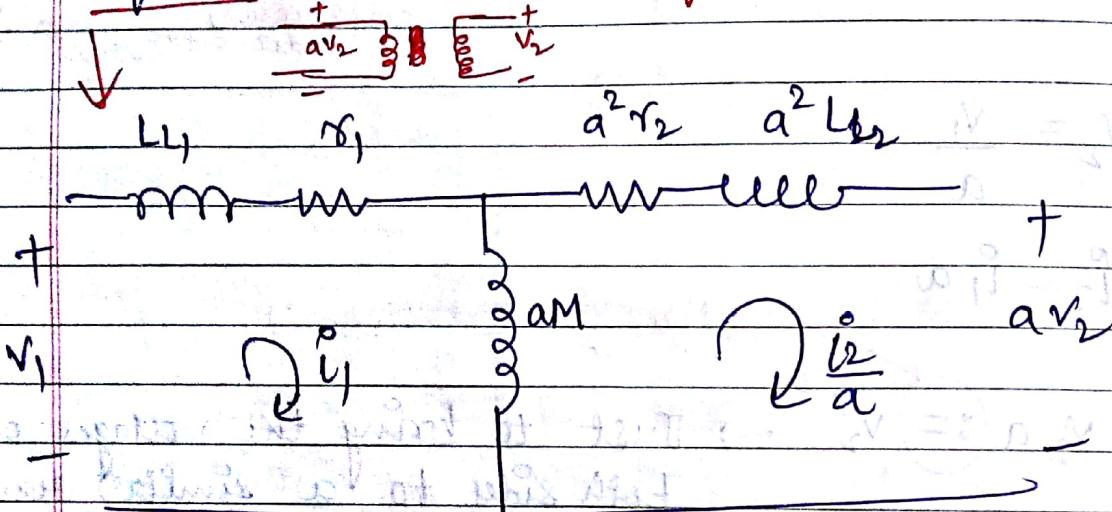Eq. ckt. + Ideal transformer = Complete eq. ckt.



~~Q. Q. Q. Q. Q.~~

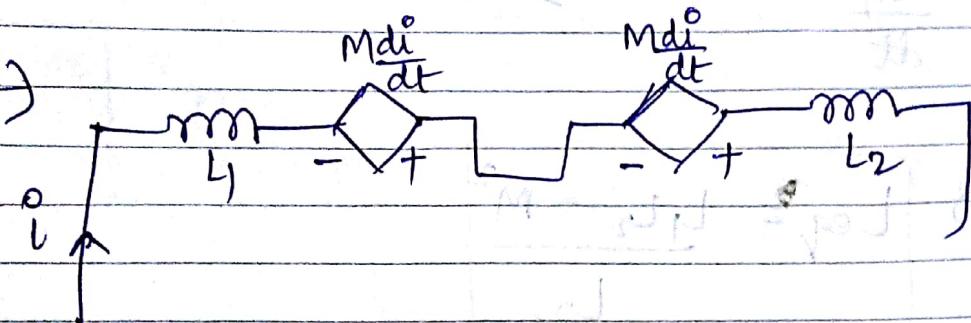


$$V_\theta = L_1 \frac{di}{dt} - M \frac{di}{dt} - M \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$= (L_1 + L_2 - 2M) \frac{di}{dt}$$


$$= \text{Leg. } \frac{di}{dt}$$
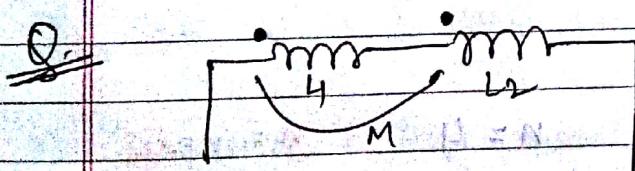
$$\Rightarrow \boxed{\text{Leg.} = L_1 + L_2 - 2M}$$



$$\boxed{\text{Leg.} = L_1 + L_2 + 2M}$$

~~Q.~~

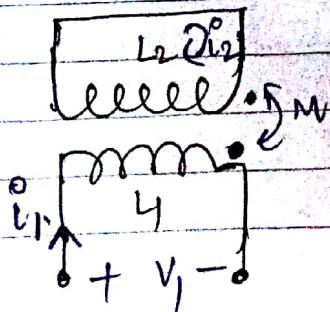

Find eq. Inductance.

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$



$$0 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} \Rightarrow \frac{M}{L_2} \frac{di_1}{dt} = \frac{di_2}{dt}$$

$$\frac{M}{\frac{dI_1}{dt}} = L_1 - \frac{M^2}{L_2}$$

$\Rightarrow L_{eq} = \frac{L_1 L_2 - M^2}{L_2}$

* Graph Theory.


* Key Points.

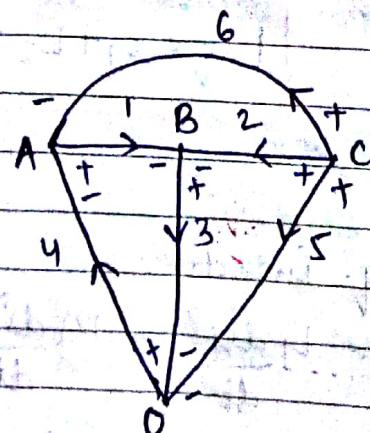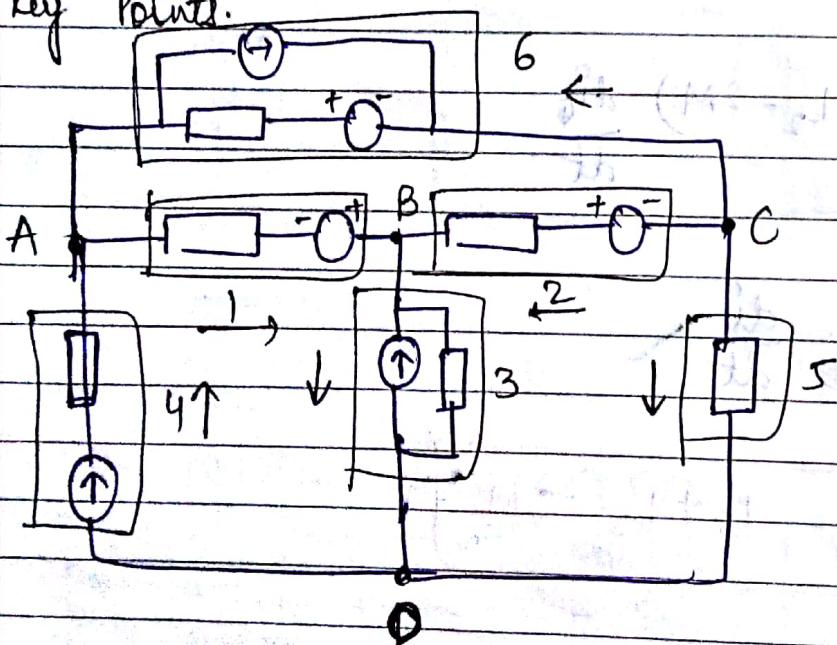

$$n = 4 \quad n = \text{nodes}$$

$$e = 6 \quad e = \text{edges.}$$


* TREE (Spanning tree)

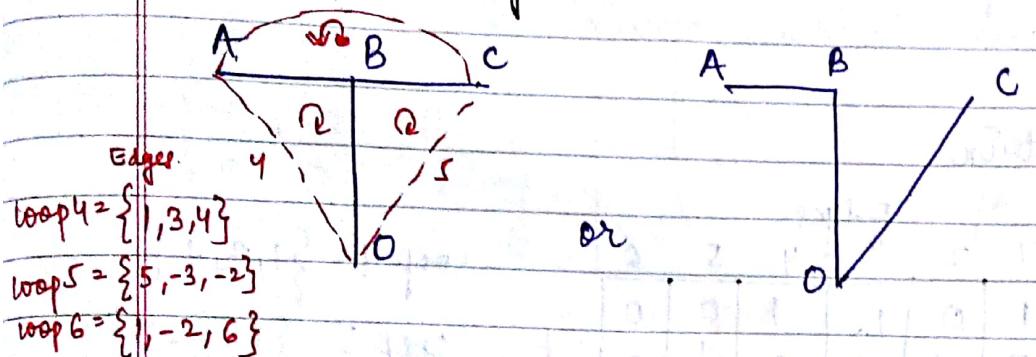

→ Is TREE Unique? (N.O.)

→ How many branches should a tree contain? n-1

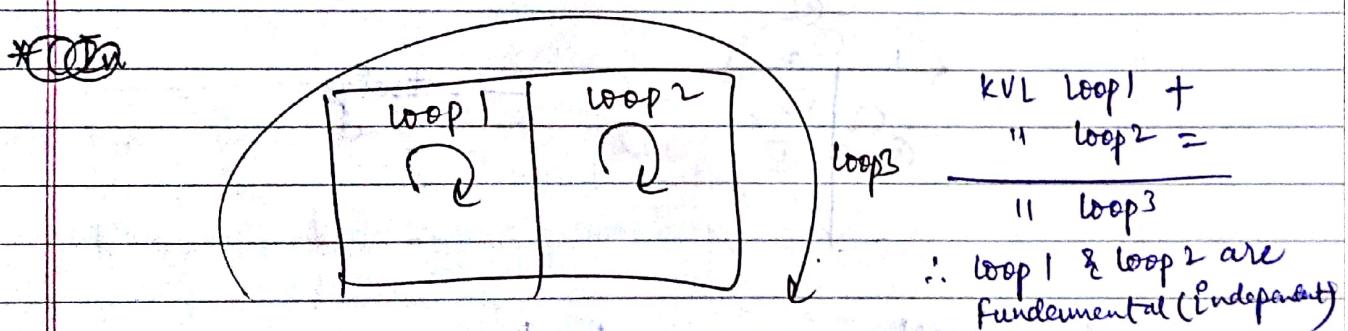→ # loops formed ~~if we join nodes~~ → e - (n-1)
Fundamental
 ↴ (Independent)



OR loop₁ & loop₃ are funda (Independent)

* Incidence Matrix

	1	2	3	4	5	6		
Nodes	A	1	0	0	-1	0	-1	$[A]$
	B	-1	-1	1	0	0	0	
	C	0	1	0	0	1	1	
	D	0	0	-1	1	-1	0	

All rows are linearly independent.

1 → current coming out of that node
 -1 → " going in
 0 → NO Relation.

Remove any 1 row
 ⇒ "Reduced Incidence Matrix".


* Loop Matrix

Independent loops	Edges						$\text{loop } 4 = \{1, 3, 4\}$ $\text{loop } 5 = \{5, -3, -2\}$ $\text{loop } 6 = \{1, -2, 6\}$
	1	2	3	4	5	6	
	4	1	0	1	1	0	
	5	0	-1	-1	0	1	
	6	1	-1	0	0	0	

twigs links.

1 ⇒ current aligned to assumed direction
 -1 ⇒ " not " " "
 0 ⇒ No Relation.

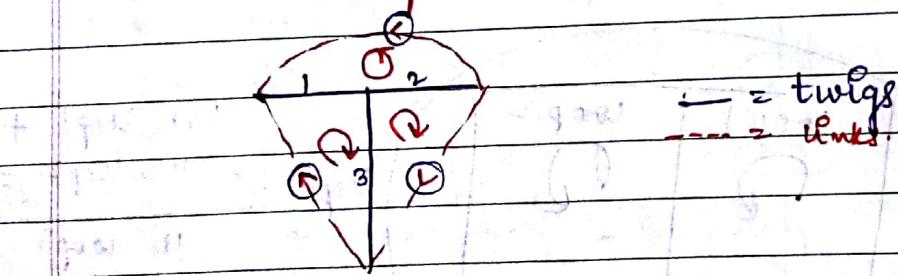* This direction of loop is direction of edges added.



V_{ek} = voltage across edge k

V_{nk} = voltage across at node n_k

i_{ek} = current in edge k

* Relation betⁿ node & edge voltages.

$$A^T \begin{bmatrix} V_{nA} \\ V_{nB} \\ V_{nC} \\ V_{nD} \end{bmatrix} = \begin{bmatrix} ? \\ ? \\ ? \\ ? \end{bmatrix}$$

$$2) \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ 0 & 1 & 0 & -1 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & 1 & -1 \\ -1 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \\ v_{n3} \\ v_{n4} \\ v_{n5} \end{bmatrix} = \begin{bmatrix} v_{e_1} \\ v_{e_2} \\ v_{e_3} \\ v_{e_4} \\ v_{e_5} \\ v_{e_6} \end{bmatrix}$$

(1)

$\therefore \begin{bmatrix} v_{e_1} \\ v_{e_2} \\ v_{e_3} \\ v_{e_4} \\ v_{e_5} \\ v_{e_6} \end{bmatrix} = A^T \begin{bmatrix} v_{n1} \\ v_{n2} \\ v_{n3} \\ v_{n4} \\ v_{n5} \end{bmatrix}$

~~***~~

$$A \begin{bmatrix} i_{e_1} \\ i_{e_2} \\ \vdots \\ i_{e_6} \end{bmatrix} = [?]$$

(2)

$$A \begin{bmatrix} i_{e_1} \\ i_{e_2} \\ \vdots \\ i_{e_6} \end{bmatrix} = 0 \quad \boxed{\text{KCL}}$$

~~***~~

check if $B \begin{bmatrix} v_{e_1} \\ v_{e_2} \\ \vdots \\ v_{e_6} \end{bmatrix} = 0$

(3)

$$B \begin{bmatrix} v_{e_1} \\ v_{e_2} \\ \vdots \\ v_{e_6} \end{bmatrix} = 0 \quad \boxed{\text{KVL}}$$


* Relation betⁿ branch & loop currents.

$$B^T \begin{bmatrix} i_{b4} \\ i_{b5} \\ i_{b6} \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 & 1 \\ 0 & -1 & -1 \\ 1 & -1 & 0 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{b4} \\ i_{b5} \\ i_{b6} \end{bmatrix} = \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix}$$

(4.) B^T [Loop currents] = [edge current]

* Cut Set

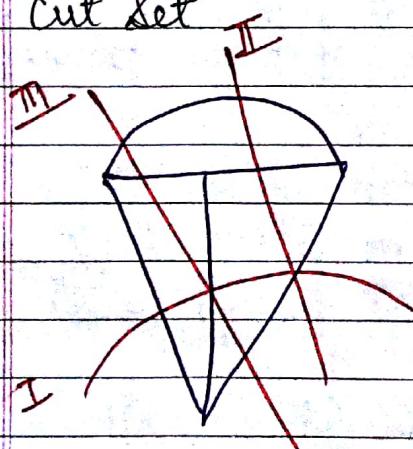


Edges

$$I = \{4, 3, 5\}$$

$$II = \{6, 2, 5\}$$

$$III = \{6, 1, 3, 5\}$$

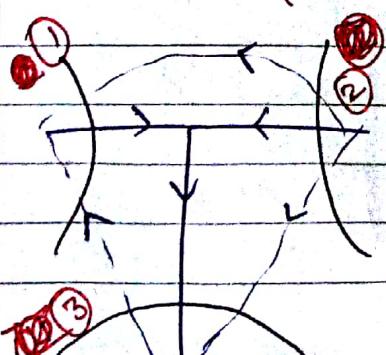

fundamental cut \Rightarrow cuts which passes through only one twig.

$\hookrightarrow (n-1)$ (No. of twigs)

$$i = \{1, 6, 4\}$$

'+' for 'i' direcⁿ oppo. to branch/twig
'k' for kth cut.

$$2 = \{6, 2, 5\}$$

$$3 = \{5, 3, -4\}$$


	1	2	3	Edges	4	5	6	
cut	1	1	0	0	-1	0	-1	= [B]
2	0	0	1	0	0	1	1	
3	0	0	1	-1	1	1	0	

$$\cancel{Q} \quad \cancel{B} \begin{bmatrix} \overset{0}{l_{e_1}} \\ \overset{0}{l_{e_2}} \\ \vdots \\ \overset{0}{l_{e_6}} \end{bmatrix} = \cancel{0} \quad l_{e_1} - l_{e_4} - \overset{0}{l_{e_6}} = 0$$

$$\textcircled{3.} \quad \boxed{\cancel{B} \begin{bmatrix} l_{e_1} \\ l_{e_2} \\ \vdots \\ l_{e_6} \end{bmatrix} = 0} \quad \text{ACK}$$

General representation of any branch:


$$Y_K = \frac{1}{Z_K}$$

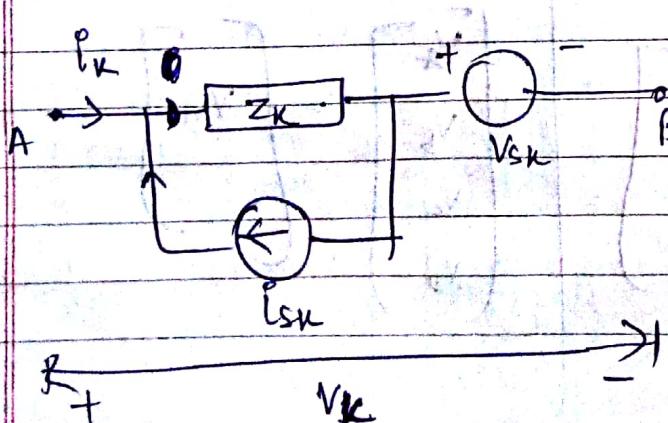

$$Y_K(V_K - V_{SK}) - l_{SK} = l_K$$

$$V_K = V_{SK} + Z_K(l_K + l_{SK})$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \left[\begin{array}{c|ccccc} \Sigma & 0 & 0 & 0 & 0 & 0 \\ 0 & z_1 & 0 & 0 & 0 & 0 \\ 0 & 0 & z_2 & 0 & 0 & 0 \\ \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \end{array} \right] \left(\begin{bmatrix} i_{e_1} \\ i_{e_2} \end{bmatrix} + \begin{bmatrix} i_{s_1} \\ i_{s_2} \end{bmatrix} \right) + \begin{bmatrix} v_{s_1} \\ v_{s_2} \end{bmatrix}$$

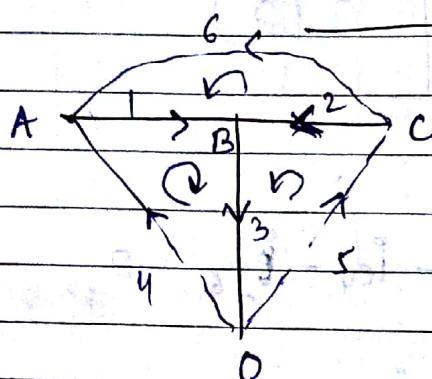

Tree : n -)

$$n = \# \text{nodes}$$

$$e = \# \text{ edges}$$

$$l = e - \# \text{twigs} = e - (n-1)$$

Nodal mtd give $n-1$ unknowns (~~as one = 0~~)
 $n-1$ eq \approx (KCL)


Mesh & unknowns

l KVL eq

The diagram illustrates a sequence of four nested loops, each representing a set. The first loop contains three elements: v_1 , v_2 , and v_3 . The second loop contains two elements: v_1 and v_2 . The third loop contains one element: v_1 . The fourth loop also contains one element: v_1 . Arrows indicate the progression from the first loop to the second, and from the second loop to the third.

Rules of

- ① KCL N
- ② KVL M
- ③ Branch eq^{ns} N, M .

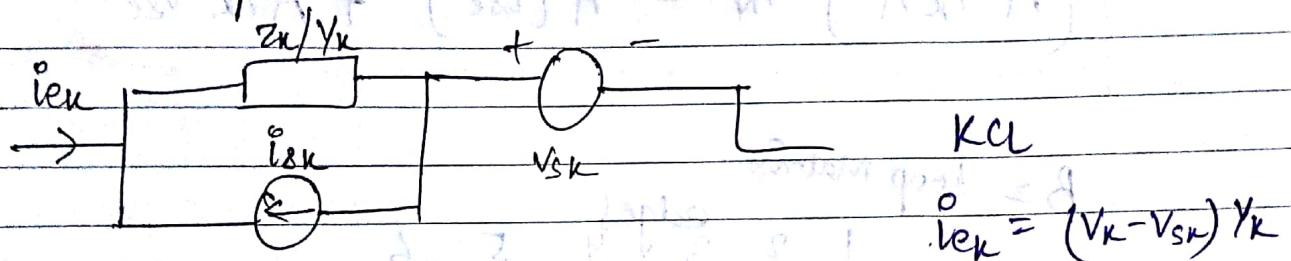Branch eq^{ns}

K

 $+ V_K -$ $- i_{8K}$

$$Y_K = \begin{bmatrix} Y_{e1} & 0 & 0 \\ 0 & Y_{e2} & 0 \\ 0 & 0 & Y_{ee} \end{bmatrix}$$

$$\begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{ee} \end{bmatrix} = \begin{bmatrix} Y_{e1} & Y_{e2} & Y_{ee} \end{bmatrix} \left(\begin{bmatrix} V_{e1} \\ V_{e2} \\ V_{ee} \end{bmatrix} - \begin{bmatrix} V_{8e1} \\ V_{8e2} \\ V_{8ee} \end{bmatrix} \right) - \begin{bmatrix} i_{8e1} \\ i_{8e2} \\ i_{8ee} \end{bmatrix}$$

~~KCL~~ $\boxed{i_e} = [Y_K] ([V_e] - [V_8]) - [i_{8e}]$

~~KVL~~ $\boxed{[A][i_e]} = A ([Y_K] ((V_e) - (V_8)) - (i_{8e})) = 0$

$$\text{As } [V_e] = A^T [V_N]$$

$$A Y_K \left(A^T [V_N] - [V_{8e}] \right) - A [I_{8e}] = 0$$


$$\boxed{[A Y_K A^T] V_N = A [I_{8e}] + A Y_K V_{8e}}$$

$B = \text{loop Matrix}$

	1	2	3	4	5	6
4	1	0	1	1	0	0
loop 5	0	1	1	0	1	0
6	1	-1	0	0	0	1

$$\begin{bmatrix} i_{k1} \\ i_{k2} \\ \vdots \\ i_{k6} \end{bmatrix} = 1 \begin{bmatrix} 1 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} i_{24} \\ i_{25} \\ i_{26} \end{bmatrix}$$


B^T

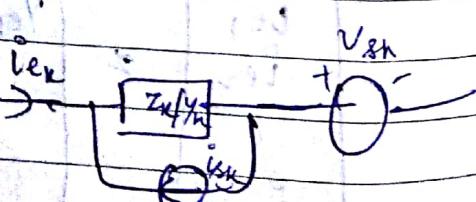


$$V_K = Z_K (I_k + I_{k2}) + V_{8K}$$

$$\begin{bmatrix} V_e \\ V_{8e} \\ 1 \\ V_{ec} \end{bmatrix} = \begin{bmatrix} Z_{e1} \\ Z_{e2} \\ \vdots \\ Z_{ec} \end{bmatrix} \left(\begin{bmatrix} i_{k1} \\ i_{k2} \\ \vdots \\ i_{k6} \end{bmatrix} + \begin{bmatrix} I_{81} \\ I_{82} \\ \vdots \\ I_{86} \end{bmatrix} \right) + \begin{bmatrix} V_{81} \\ V_{82} \\ \vdots \\ V_{86} \end{bmatrix}$$

* Two Port Networks.

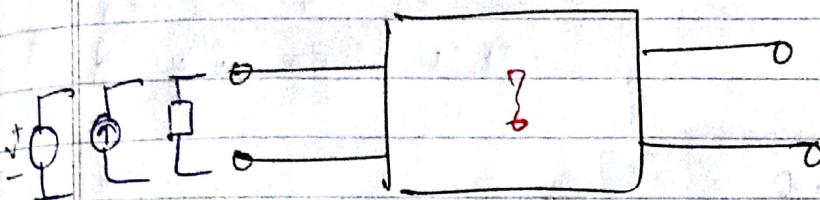

Inside sw No Independent sources.

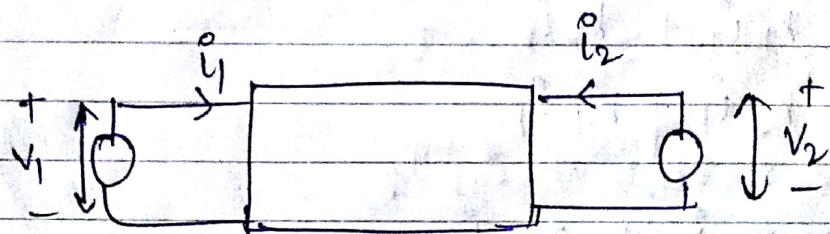

$$\overset{\circ}{i}_1 = k_1 v_1 + k_2 v_2 \quad (\text{By superposition theo.})$$

$$\overset{\circ}{i}_2 = k_3 v_1 + k_4 v_2$$

$$\begin{bmatrix} \overset{\circ}{i}_1 \\ \overset{\circ}{i}_2 \end{bmatrix} = \begin{bmatrix} k_1 & k_2 \\ k_3 & k_4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\overset{\circ}{i}_1 = \gamma_{11} v_1 + \gamma_{12} v_2$$

$$\overset{\circ}{i}_2 = \gamma_{21} v_1 + \gamma_{22} v_2$$

$$\begin{bmatrix} \overset{\circ}{i}_1 \\ \overset{\circ}{i}_2 \end{bmatrix} = \begin{bmatrix} \gamma_{11} & \gamma_{12} \\ \gamma_{21} & \gamma_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

Short ckt admittance parameters.

$$Y_{11} = \left(\frac{i_1}{v_1} \right)_{v_2=0}$$

$$Y_{12} = \left(\frac{i_1}{v_2} \right)_{v_1=0}$$

↑ Transfer admittance.

Now,

$$V_1 = k_1 i_1 + k_2 i_2$$

$$V_2 = k_3 i_1 + k_4 i_2$$

$$V_1 = z_{11} i_1 + z_{12} i_2$$

$$V_2 = z_{21} i_1 + z_{22} i_2$$

$$Z_{11} = \left(\frac{v_1}{i_1} \right)_{i_2=0}$$

| | |

* Also,


$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

↑ Primary

↑

↑ Secondary.

Transmission parameters

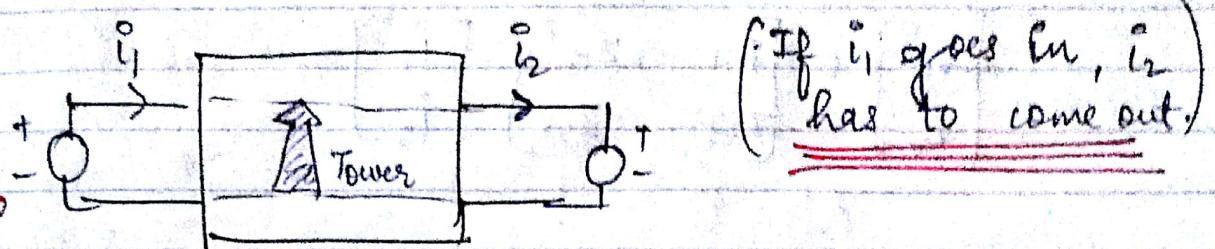

$$\star \begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ V_2 \end{bmatrix}$$

↑
hybrid parameters.

* Relation betⁿ the parameters.

① $Z \propto Y$

$$[V] = [Z] [I] \quad Z = Y^{-1}$$

$$[I] = [Y] [V]$$


$$② \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \quad \checkmark$$

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -i_2 \end{bmatrix}$$

H.W. 8

* Properties:
Reciprocity
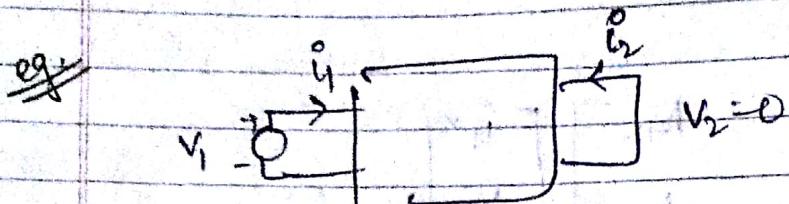
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$




when $V_2 = 0$; To find $\frac{V_1}{I_2}$

$$Z_{21} I_1 + Z_{22} I_2 = 0$$


$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$\frac{V_1}{I_2} = -Z_{11} \frac{Z_{22} I_2}{Z_{21}} + Z_{12}$$
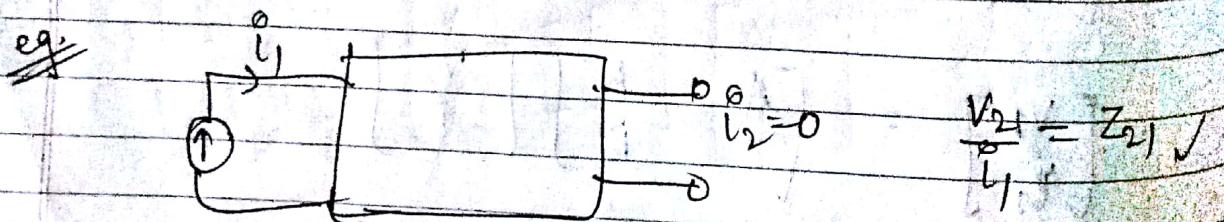
$$\frac{V_1}{I_2} = Z_{12} - \frac{Z_{11} Z_{22}}{Z_{21}}$$



$$\frac{V_2}{I_1} = Z_{21}$$

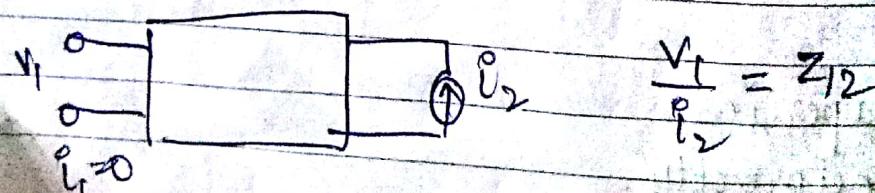

For reciprocity
 $Z_{21} = Z_{12}$

* Y & Reciprocity.

$$Y_{12} = Y_{21}$$

* ABCD & Reciprocity.

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & -B \\ C & -D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

Apply $I_2 = 0$ & current source on primary.

Apply $I_1 = 0$ & measure V_2

$$I_1 = CV_2 \Rightarrow \frac{V_2}{I_1} = \frac{1}{C}$$

Now,

Apply $I_2 = 0$ & measure V_1

$$I_1 = 0$$



$$0 = CV_2 - DI_2$$

$$V_1 = AV_2 - BI_2$$

$$V_1 = A \frac{DI_2}{C} - BI_2$$

$$\frac{V_1}{I_2} = \left(\frac{AD}{C} - B \right)$$


By Reciprocity $\frac{\text{Out/p}}{\text{Inp/p}} = \frac{\text{Out/p}}{\text{Inp/p}} \Rightarrow \frac{V_1}{I_1} = \frac{V_2}{I_2}$

$$\frac{1}{c} = \frac{AD}{c} - B$$

$$\underline{AD - BC = 1}$$

determinant.

* Symmetry

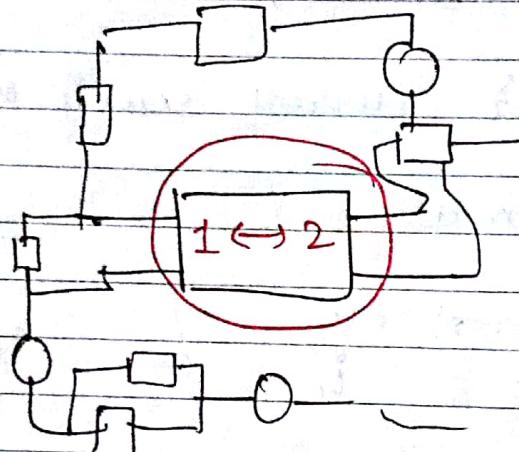

If we change 1 ↔ 2
no change occurs,
this is symmetry.

① Reciprocal

② If P Impedance of port 1 & 2 should be eq

eg $\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & -B \\ C & -D \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$ (given)

$$\begin{bmatrix} v_2 \\ i_2 \end{bmatrix} = \begin{bmatrix} A & -B \\ C & -D \end{bmatrix}^{-1} \begin{bmatrix} v_1 \\ i_1 \end{bmatrix}$$
 (to find)

$\xrightarrow{\text{X matrix}}$

Since, the network is symmetric

X matrix is $(ABCD)^{-1}$

$$\text{X matrix} \xrightarrow{\substack{\text{Divided by:} \\ \text{Determinant} = -1}} \begin{pmatrix} -D & B \\ -C & A \end{pmatrix} \quad \left(X = \frac{1}{\det(A)} \begin{pmatrix} -D & B \\ -C & A \end{pmatrix} \right)$$

As $A \neq 0$, X is symm.

$$\begin{pmatrix} A & -B \\ C & -D \end{pmatrix} = \begin{pmatrix} +D & -B \\ +C & -A \end{pmatrix}$$

$$\Rightarrow A = \underline{\bullet D}, \quad \underline{\oplus - - -}$$

- * Eigen vector of a matrix output vector whose direction is same as input

$$\begin{bmatrix} ? \\ ? \\ ? \end{bmatrix}_{3 \times 1} = \begin{bmatrix} 0 & 1 & 0 \\ 2 & 0 & 0 \\ 0 & 0 & 10 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}$$

$$\begin{bmatrix} 0 \\ 0 \\ 10 \end{bmatrix} = \underline{10} \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix} \quad \text{Eigen value}$$


Doubt

Eigen vector ??

Both of them can be considered as eigen vectors as only direction matters.

- * Eigen func. of a sys. Same pattern, magnitude may differ.

Eigen value = Multiplication factor.

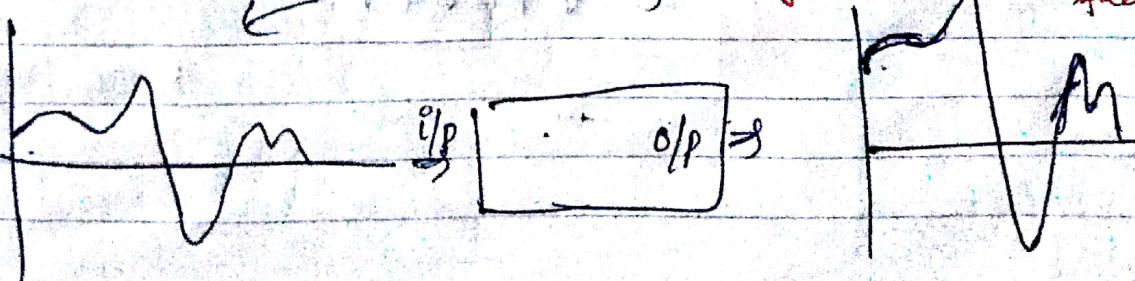

$$\text{eg: } 1 \cdot \frac{d^2y}{dt^2} + 2 \frac{dy}{dt} + 3y(t) = x(t) \quad \text{--- (1)}$$

Can we find the eigen fns?

Check whether the following are eigen fns.

- a) $x(t) = \delta(t)$ X
- b) $x(t) = u(t)$ X
- c) $= \sin \omega t$ X
- d) $= \cos \omega t$ X
- e) $= e^{at}$ ✓
- f) $= e^{-at}$ ✓
- g) $= e^{j\omega t}$ ✓

(b) Let $y = k u(t)$ If $x(t)$ is eigen fn

Put in (1)

$$k \delta + 2k \delta(t) + k u(t) = u(t) \quad \text{X Not possible}$$

$$(e) x(t) = e^{at}, y(t) = k e^{at}$$

$$k \sigma^2 e^{at} + 2k \sigma e^{at} + 3k e^{at} = e^{at}$$

$$k \sigma^2 + 2k \sigma + 3k - 1 = 0$$

$$k = \frac{1}{\sigma^2 + 2\sigma + 3}$$

Eigen value

$$(d) y = K \cos \omega t ; x(t) = \cos \omega t$$

--- X ---

~~***~~ for any LTI sys., exponential fns. are eigen fns.

Proof: for any LTI sys.

$$h(t) \rightarrow h(t)$$

valid only for LTI sys.

$$y(t) = x(t) * h(t)$$

$$= \int_{-\infty}^{\infty} h(\tau) x(t-\tau) d\tau$$

Choose $x(t) = e^{st}$; $s = \text{real/complex/anything.}$

$$= \int_{-\infty}^{\infty} h(\tau) e^{st} e^{-s\tau} d\tau$$

$$= e^{st} \int_{-\infty}^{\infty} h(\tau) e^{-s\tau} d\tau$$

Being a definite integral, it is a const

$$y(t) = k e^{st}$$

~~∴ PROOF~~ $\therefore e^{st}$ is eigen fns. ~~exp~~.

Eigen value

$$= \int_{-\infty}^{\infty} h(t) e^{-st} dt$$

~~***~~

$$e^{at} \rightarrow \boxed{\text{LTI}} \rightarrow k e^{at} \quad (k \text{ can be complex})$$

$$\text{Now } k = \delta \{ h(t) \}_{s=a}$$

(1)	I/P	O/P
$e^{j\omega t}$		$k_1 e^{j\omega t}$
$e^{-j\omega t}$		$k_2 e^{-j\omega t}$

$$k_1 = \int_{-\infty}^{\infty} h(t) e^{-j\omega t} dt \quad \Rightarrow k_1 = k_1^*$$

$$k_2 = \int_{-\infty}^{\infty} h(t) e^{j\omega t} dt \quad \text{for Real systems,}\\ \text{all } h(t) \text{ has to be Real.}$$

(2)	I/P	O/P
-----	-----	-----

$$\frac{e^{j\omega t} + e^{-j\omega t}}{2} \quad \left| \begin{array}{l} \text{Cos } \omega t \\ \frac{k_1 e^{j\omega t}}{2} + \frac{k_2 e^{-j\omega t}}{2} = R e^{j\theta} \frac{e^{j\omega t}}{2} + R e^{-j\theta} \frac{e^{-j\omega t}}{2} \\ = R \cos(\omega t + \theta) \end{array} \right.$$

$H(s) = \mathcal{L}\{x(t)\}$ = called Transfer func.



discrete

Date _____

Page _____

To know any LTI sys. \Rightarrow knowing all eig. value of exponential fns

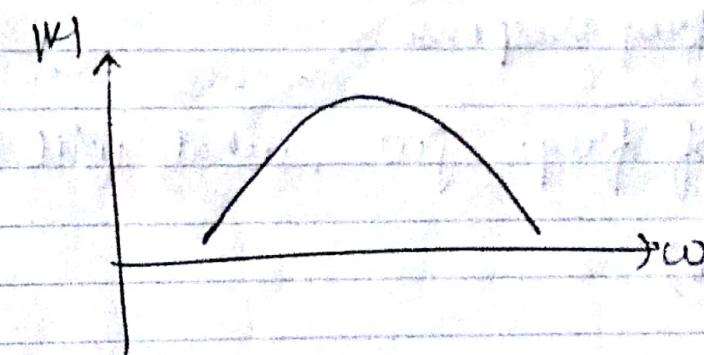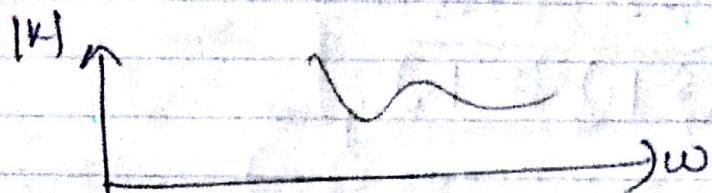Take all w 's f^w of sines & cosines ~~as~~ as input
& $k = \mathcal{R}e s_0$



$$Q. \quad a \frac{d^2y}{dt^2} + b \frac{dy}{dt} + c y(t) = x(t)$$

$$k = \mathcal{L}\{h(t)\}$$

To find $\mathcal{L}\{h(t)\}$

$$a \ddot{h} + b \dot{h} + c h(t) = g(t)$$

$$a s^2 H(s) + b s H(s) + c H(s) = 1$$

$(h(0) = h'(0) = 0)$
(as for LTI
initial condition = 0)

$$H(s) = \frac{1}{as^2 + bs + c}$$

$$ay'' + by' + cy = px(t) + q(x) + \sigma x^*$$

$$H(s) = \frac{as^2 + bs + c}{as^2 + bs + c}$$

where $x(t) = s(t)$

$$= \frac{(s - z_1)(s - z_2)}{(s - p_1)(s - p_2)}$$

zeros *poles*


Given $H(s) = \frac{(s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$

To find freq. response


If i/p $\stackrel{\alpha}{\sim}$ of freq. $j\omega$, what will be k(eigen value)

$$k = H(j\omega)$$
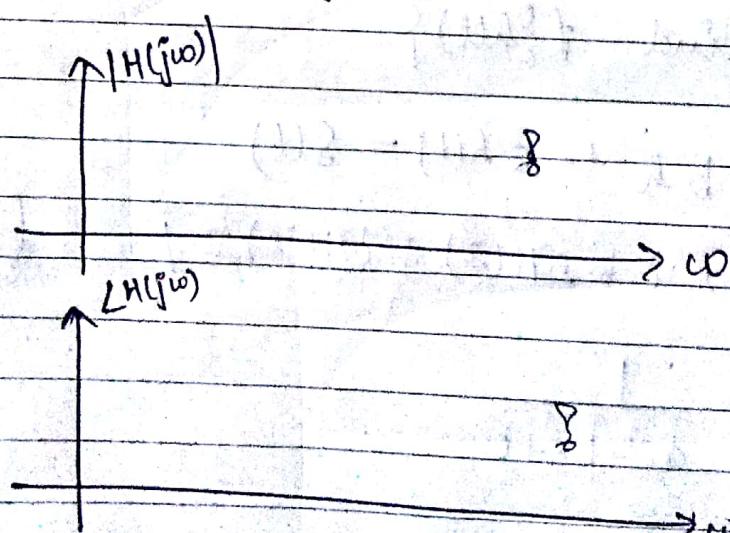
$$= \frac{(j\omega - z_1)(j\omega - z_2) \dots}{(j\omega - p_1)(j\omega - p_2) \dots}$$



Complex Plane


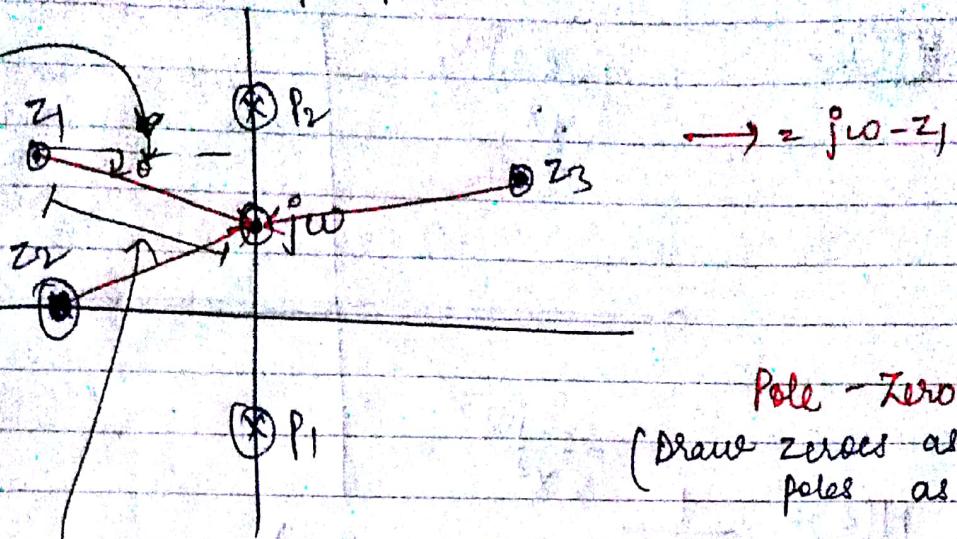


Pole - Zero diagram.

(Draw zeroes as dots & poles as cross)

$$|H(j\omega)| = \frac{|j\omega - z_1| |j\omega - z_2|}{|j\omega - p_1| |j\omega - p_2|} \dots$$
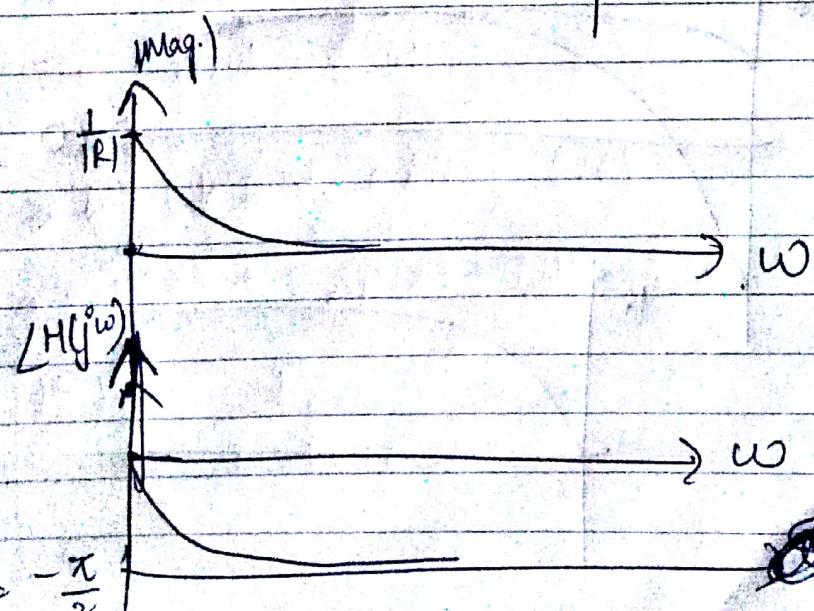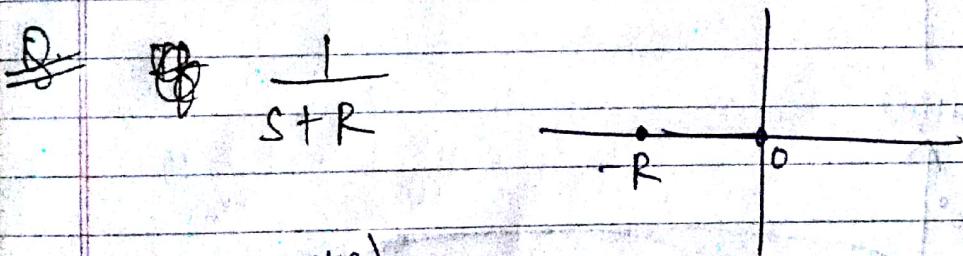
$$\angle H(j\omega) = \angle j\omega - z_1 + \angle j\omega - z_2 + \dots - (\angle j\omega - p_1 + \angle j\omega - p_2) + \dots$$





$$90^\circ = -\frac{\pi}{2}$$

Q. $H(s)$


Alone this pole cannot exist as then $H(s)$,

which cannot be complex as coeffs. $a_1, b_1, c_1, d_1, e_1, f_1$ are real so we need to have this.
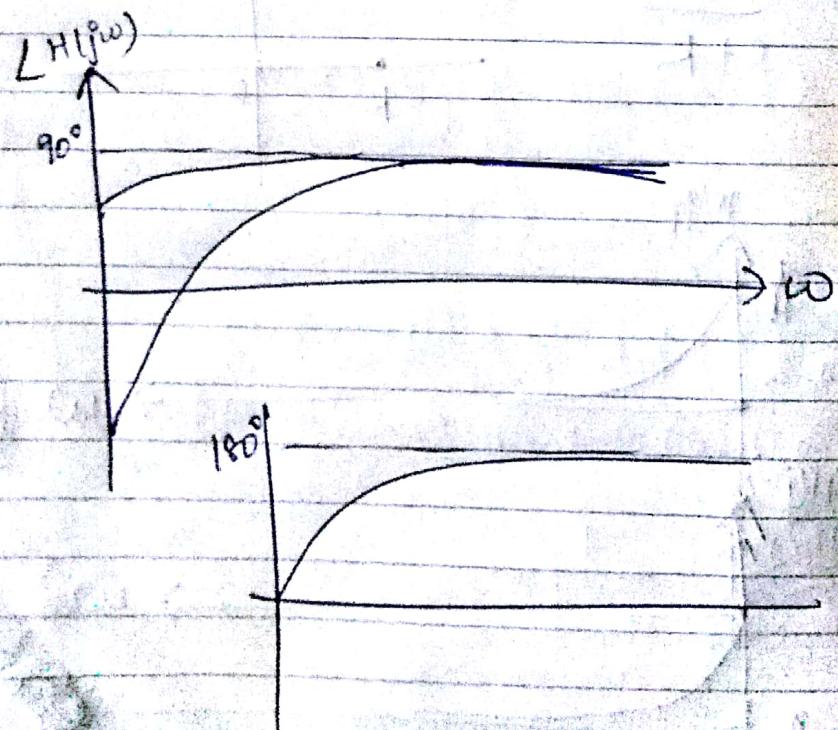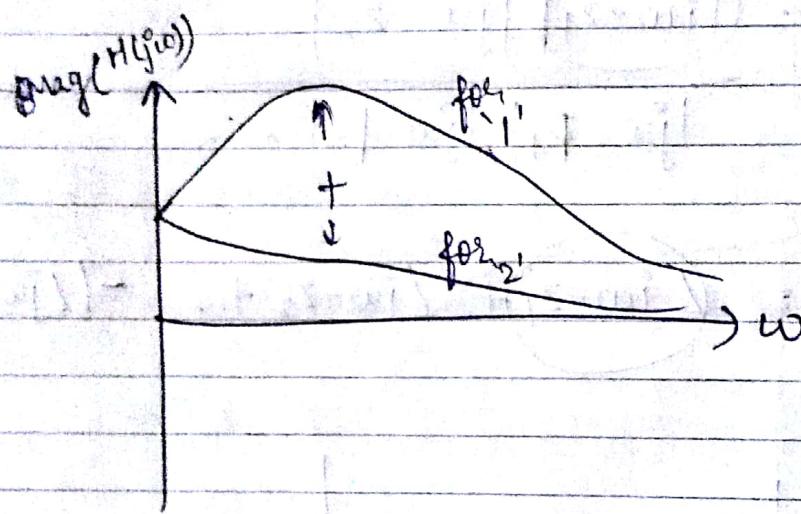
$$H(s) = \frac{1}{(s + 5 - j\omega)(s + 5 + j\omega)}$$



Ans

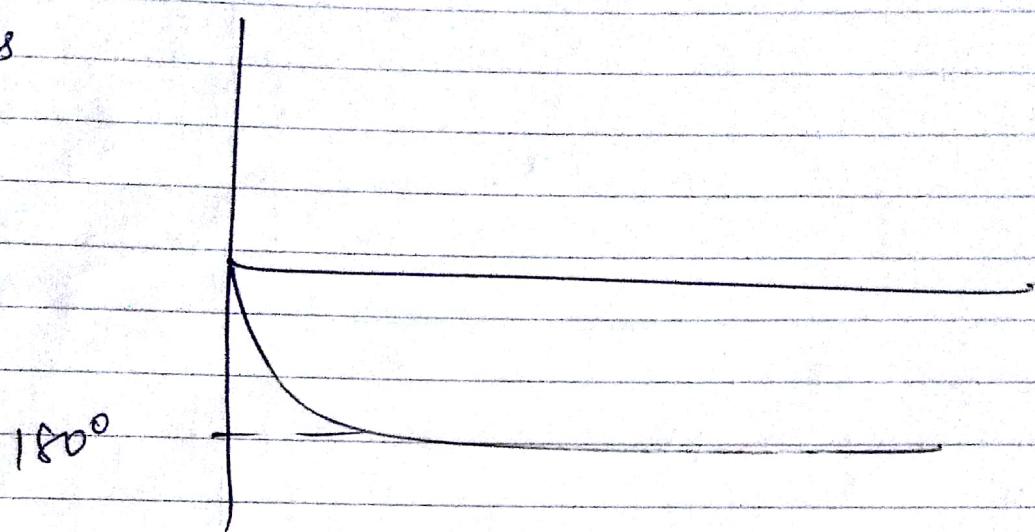

as we have the poles in denominators.

* Bode Plots.


$$O/P = e^{\alpha t}$$

$$O/P = k e^{\alpha t}$$


$$k = H(s) \Big|_{s=\alpha} \quad \text{where } H(s) = L[h(t)]$$

α = real / imag. / complex.
= complex freq.

$\text{mag}(H(j\omega))$

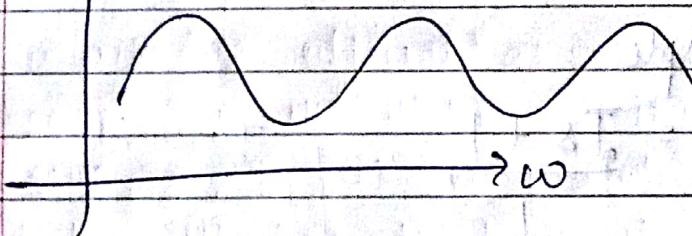

$|H(j\omega)|$

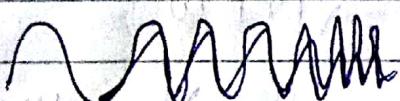

$\rightarrow \log \omega$

Magnitude gain $|H(j\omega)|$

Amplitude of o/p
u u i/p


Power / Energy = amplitude²

$$(2) H(s) = \frac{1}{sT + 1}$$

$$20 \log |H(j\omega)| = -20 \log (1 + j\omega T)$$

$$\omega = 1/T \quad \Rightarrow \quad 20 \log |H(j\omega)| = -20 \log (1 + j\omega T) \approx -3 \text{ dB}$$

$$\log \omega = -\log T$$

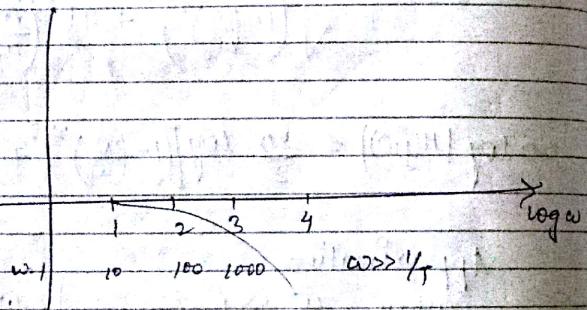

$$(3) H(s) = (s - (\alpha + j\beta)) \times (s - (\alpha - j\beta))$$

$$H(s) = (s - \alpha)^2 + \beta^2$$

$$= s^2 + \alpha^2 + \beta^2 - 2\alpha s$$

$\underbrace{\alpha^2}_{\omega_0^2} \quad \underbrace{\beta^2}_{j\omega_0^2}$

$$\text{o/p Power} = |H(j\omega)|^2$$

$$\text{i/p Power}$$

$$\log (") = 2 \log |H(j\omega)|$$

$$10 \log |H(j\omega)| \quad (\text{decibel})$$

$$20 \log |H(j\omega)| \quad (\text{power gain in decibel})$$

+ Examples:

$$(1) H(s) = \frac{1}{s + 1} \quad ; \quad T = \text{const.}$$


$$H(j\omega) = 1 + jT\omega$$

$$|H(j\omega)| = \sqrt{1 + T^2\omega^2}$$

$$M = 20 \log |H(j\omega)| \approx 10 \log (1 + T^2\omega^2)$$

Approximation
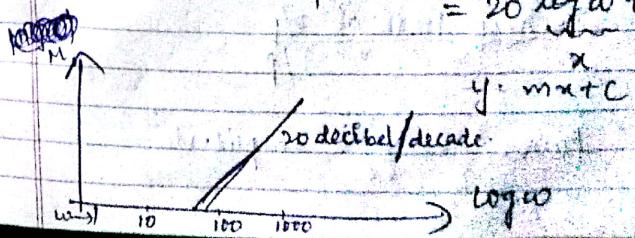
$$\text{when } \omega \gg \frac{1}{T} \Rightarrow M \approx 20 \log (T\omega) \\ = 20 \log \omega + 20 \log T$$



$$= s^2 - 2f\omega_0 s + \omega_0^2$$

$$= \omega_0^2 \left[1 - 2f \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2 \right]$$

$$|H(j\omega)| = \omega_0^2 \left[1 - 2f \left(\frac{j\omega}{\omega_0} \right) - \frac{\omega^2}{\omega_0^2} \right]$$

$$|H(j\omega)| = \sqrt{\left(1 - \left(\frac{\omega}{\omega_0} \right)^2 \right)^2 + 4f^2 \left(\frac{\omega}{\omega_0} \right)^2}$$

$$20 \log |H(j\omega)| = \frac{20}{2} \log \left[\left(1 - \left(\frac{\omega}{\omega_0} \right)^2 \right)^2 + 4f^2 \left(\frac{\omega}{\omega_0} \right)^2 \right]$$

Approximation

when $\frac{\omega}{\omega_0} \gg 1$

$$4 \times 10 \log \left(\frac{\omega}{\omega_0} \right)$$

$$= 40 \log \left(\frac{\omega}{\omega_0} \right)$$

$$= 40 \log \omega - 40 \log(\omega_0)$$

$20 \log |H(j\omega)|$

$f=1$

40 decibel/decade

$\log \omega$

$0 < f < \frac{1}{2}$

$f = \frac{1}{2}, M = 0$

$f = 1, M = \log 9 \times 10$

$0 < f < \frac{1}{2}$