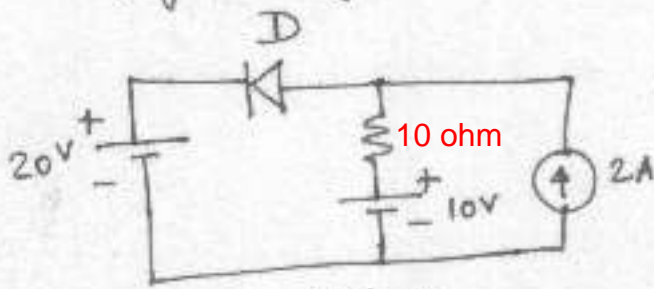



Tutorial-6

①

① Verify Tellegen's Theorem for the following networks.




ckt. A

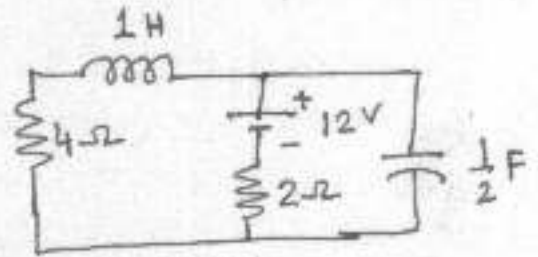


ckt. B

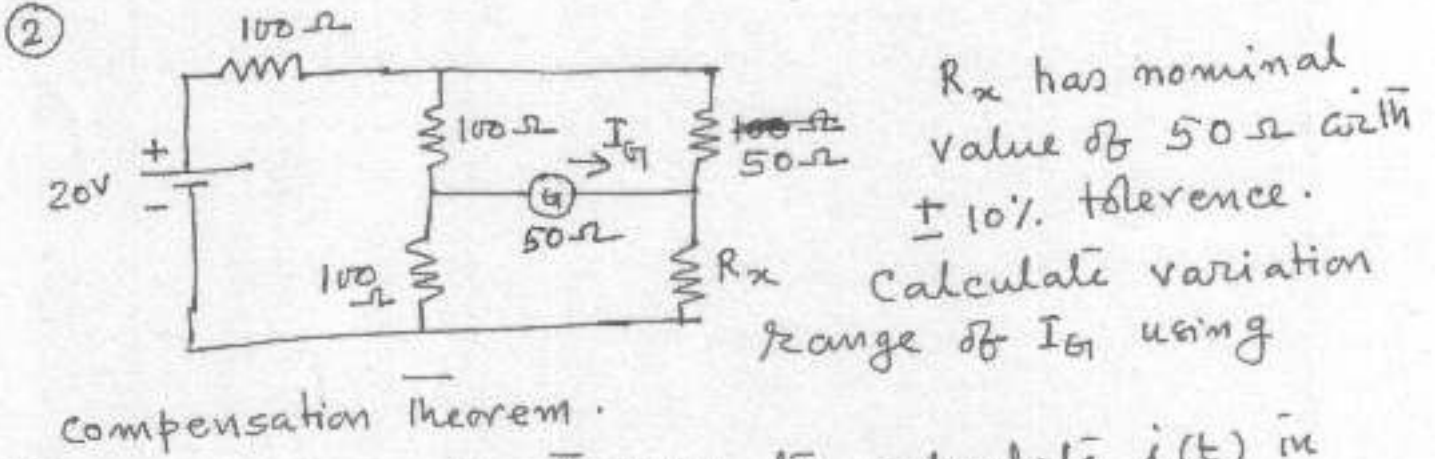
Assume both the ckt's to be in steady state and diode D to be ideal.



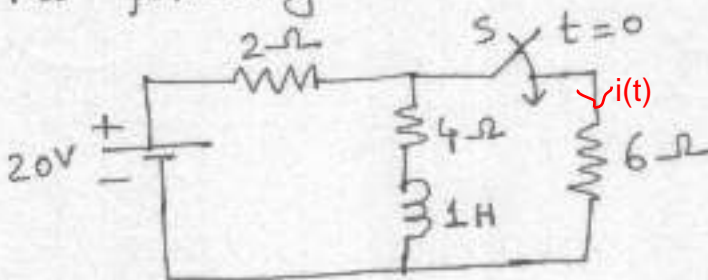③ Use compensation theorem to calculate $i(t)$ in the following network.




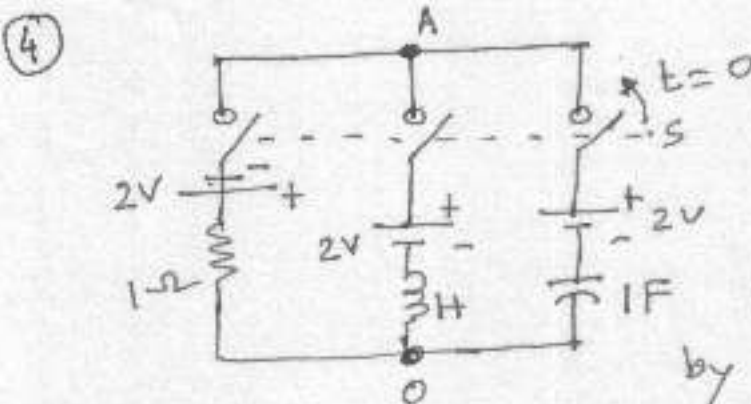ckt. was in steady state before switching. Verify your result by solving it using Thevenin Theorem.



Assume zero initial conditions. Tripple pole switch S is closed at $t=0$. Get $v_{AO}(t)$ for $t>0$ by using Millman's Theorem.


⑤

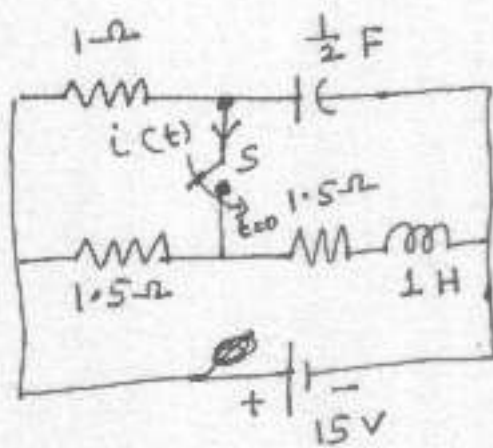

②
After s.s has been reached,
s is closed at $t=0$.
Calculate $i(t)$ for $t>0$
by using


- (a) Thevenin Theorem.
- (b) Mesh Analysis.

⑥

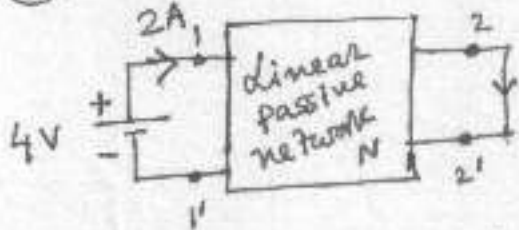

When 4v is applied at 1-1',
& current in 2-2' is 1 A
To the same network if

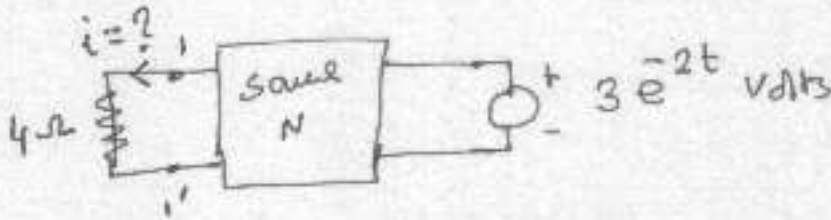
$3e^{-2t}$ v is applied what will be i in 1-1'?



Apply suitable
network theorems
to get the result.

Make necessary assumptions

⑦

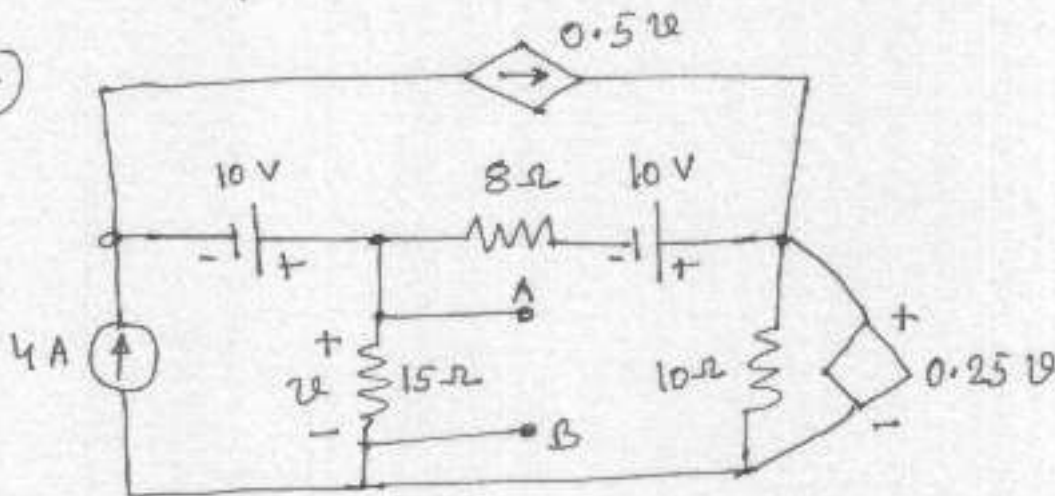

(a) use superposition Theorem to get v .

(b) Get Thevenin Equivalent ckt across AB.