
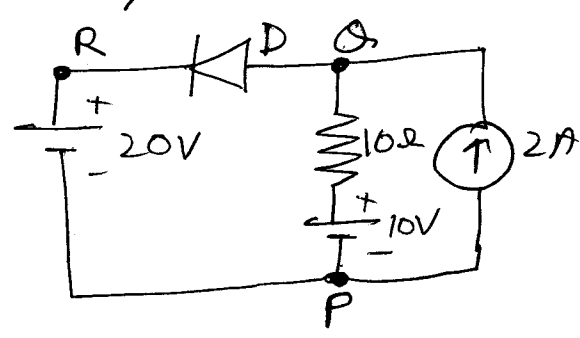


① Ckt A

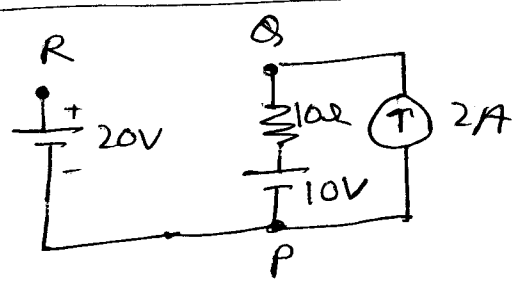We will first solve ckt ~~A~~ using Thevenin's equivalence theorem. Note that ckt A has only one non-linear branch QR. The rest of the ckt is linear. Therefore we will treat the branch QR as external to the ckt. And find the ~~th~~ Thevenin equivalence ckt for the rest of the ckt.




Thevenin Voltage (open ckt voltage) between Q, R




$$\begin{aligned} V_{QR} &= 10\Omega \times 2A + 10V - 20V \\ &= 20V + 10V - 20V \\ &= 10V \\ \therefore V_{th} &= 10V \end{aligned}$$

Thevenin resistance between Q, R

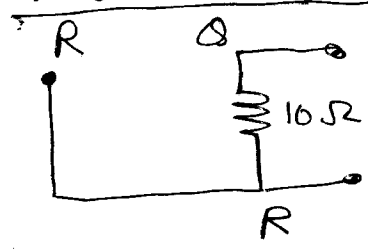

clearly $R_{th} = 10\Omega$


\therefore Thevenin's equivalent ckt

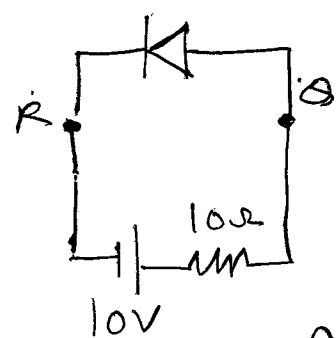

\therefore Current through the diode
 $= \frac{10V}{10\Omega} = 1A$ (From Q to R)

Notation:
 V_{xy} = Voltage drop from X to Y


\therefore Solution for ckt A

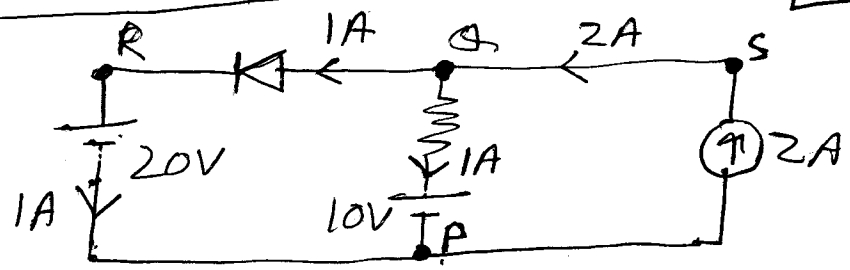


$$\begin{aligned} V_{QR} &= 0 \\ V_{RP} &= 20V \\ V_{QP} &= 20V \\ V_{QSP} &= 20V \end{aligned}$$

Ckt B

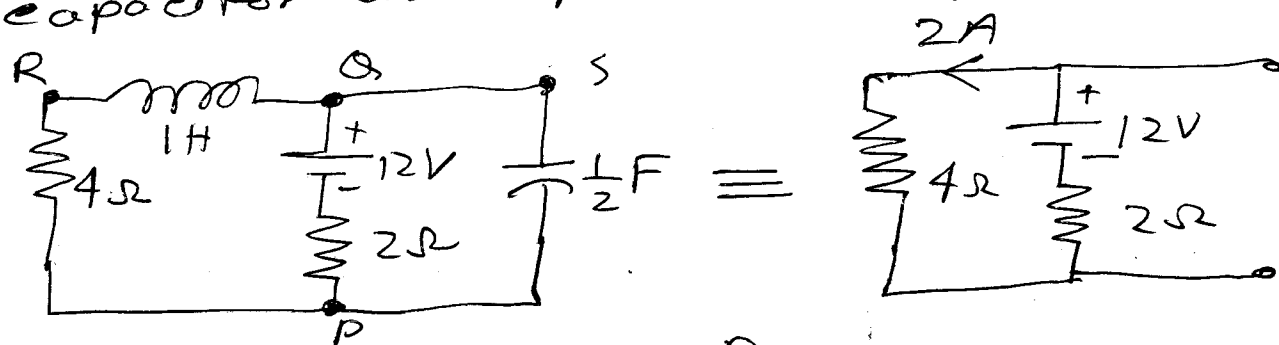Since the ckt has only DC sources therefore at steady state the inductor behaves like a short circuit & the capacitor as open circuit



∴ Solution of Ckt B.

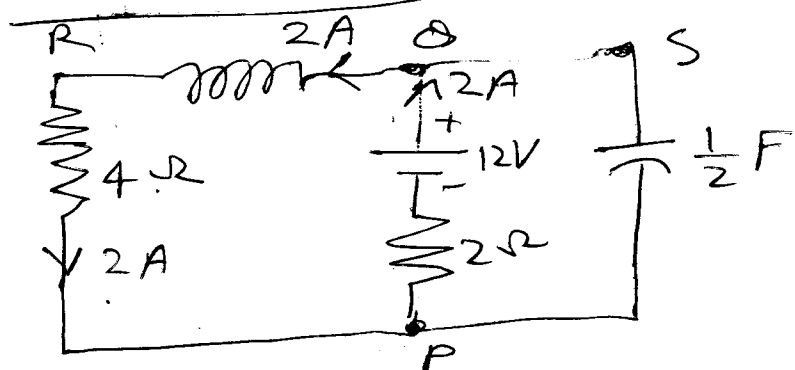

$$\begin{aligned} V_{QR} &= 0V \\ V_{RP} &= 8V \\ V_{QP} &= (12 - 4)V = 8V \\ V_{QSP} &= 8V \end{aligned}$$

VERIFICATION OF TELLEGN'S THEOREM

(i) Using Voltages from ckt A & currents from ckt B

$$V_{QR}^A I_{QR}^B + V_{RP}^A I_{RP}^B + V_{QP}^A I_{QP}^B + V_{QSP}^A I_{QSP}^B$$

(superscripts denote which ckt the quantities are taken from)

$$= (0 \times 2 + 20 \times 2 + 20 \times (-2) + 20 \times 0) \text{ VA}$$

$$= 0 \quad (\text{Tellegen's theorem obeyed})$$


(ii) Using Voltages from ckt B & currents from ckt A

$$V_{QR}^B I_{QR}^A + V_{RP}^B I_{RP}^A + V_{QP}^B I_{QP}^A + V_{QSP}^B I_{QSP}^A$$

$$(0 \times 1 + 8 \times 1 + 8 \times 1 + 8 \times (-2)) \text{ VA}$$

$$= 0 \quad (\text{Tellegen's theorem obeyed})$$

② Nominal Circuit

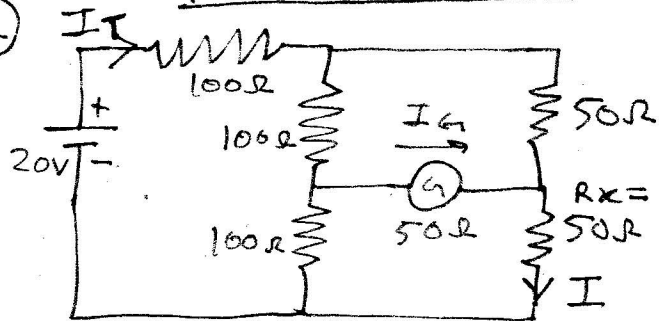

Let the current through R_x be $= I$. Lets find I .

One can find I using mesh, nodal analysis or Thevenin theorem etc.

But observe that I_G will be zero because G is ~~between~~ in a balanced Wheatstone bridge condition. So we can compute I easily

$$I = \cancel{I_G} + I_T \times \frac{200}{200+100}$$

$$= \frac{20}{100 + (200 \parallel 100)} \times \frac{2}{3} A$$


$$= \frac{20}{100 + \frac{200}{3}} \times \frac{2}{3} A$$

$$= \frac{40}{500} = \frac{4}{500} = 0.008 A$$


$$= 0.08 A$$

Circuit with $\pm 10\% = \pm 5\Omega$


tolerance for R_x

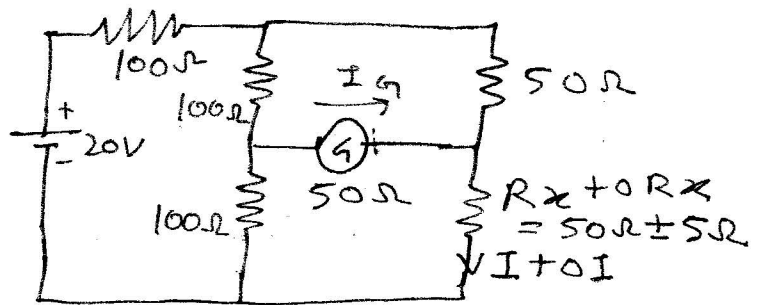

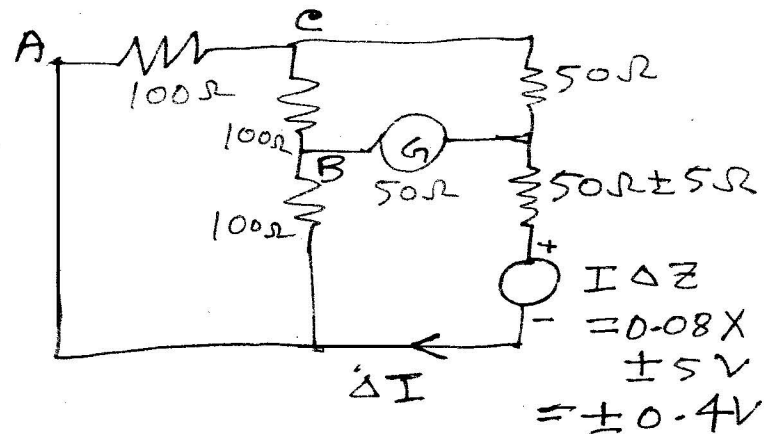Lets compute ΔI in this circuit using compensation theorem



Apply Δ -Y conversion for ΔABC

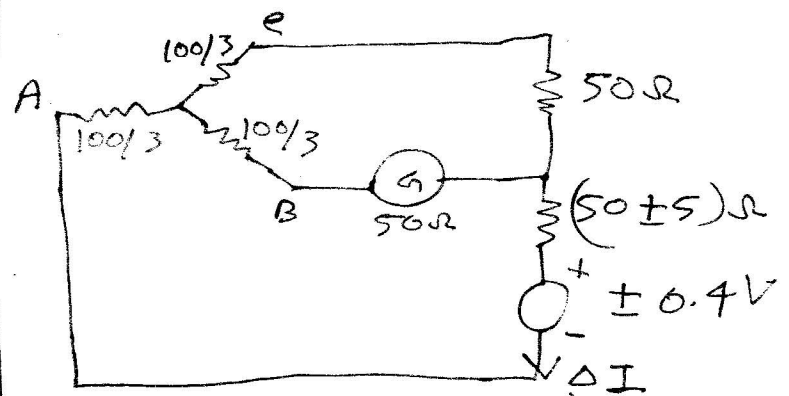


$$-\Delta I = \frac{\pm 0.4 V}{\frac{100}{3} + \frac{100}{3} + 50 + 50 \pm 5} A$$

$$= \frac{\pm 0.4}{\frac{100}{3} + \frac{250}{6} + 50 \pm 5} A$$

$$= \frac{\pm 0.4}{125 \pm 5} A = \frac{.4}{130} \text{ or } \frac{-.4}{120} A$$

$$\therefore \Delta I = -.4/130 \text{ or } .4/120 A$$

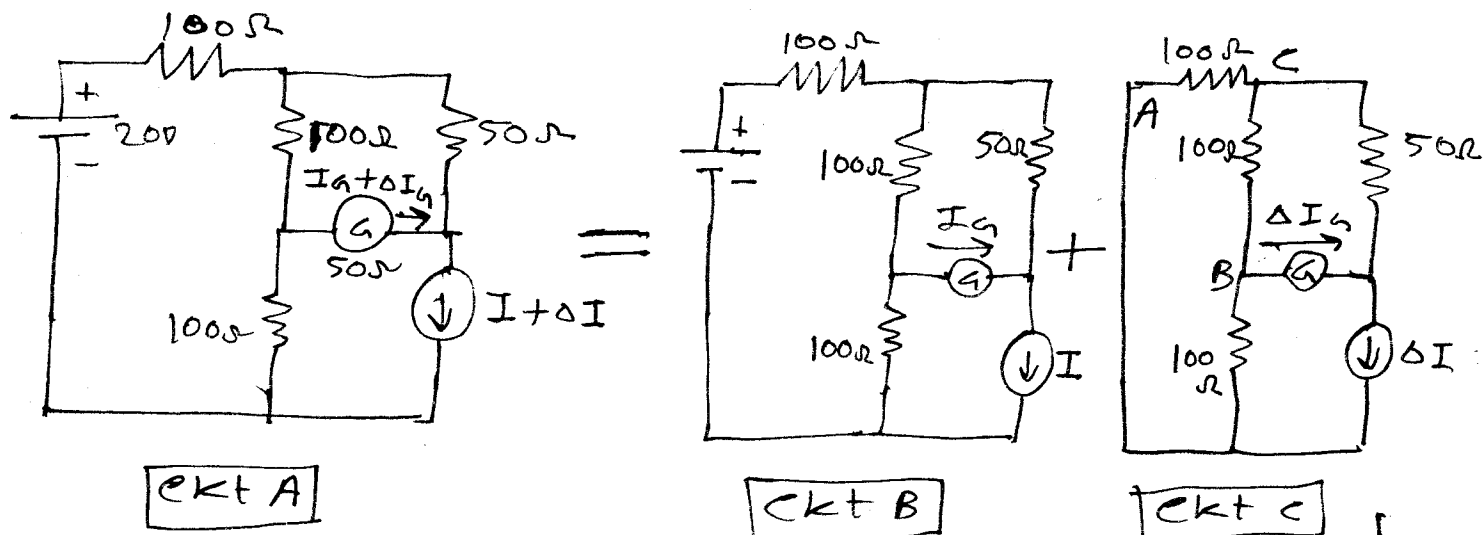Now apply substitution theorem to the circuit with 10% tolerance to get **ckt A**




ckt A is broken into **ckt B** + **ckt C** using superposition theorem.

Now **ckt B** is nothing but the nominal ckt with R_x substituted with a current source. Therefore, in **ckt B** galvanometer current will be equal to the nominal current I_G . Therefore, the galvanometer current in **ckt C** will be same as the error current ΔI_G .

So let us solve **ckt C** to get ΔI_G .

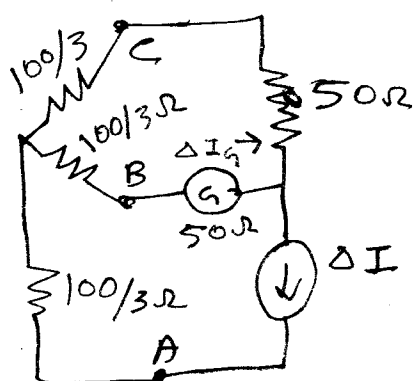
Apply Δ -Y conversion on ΔABC of **ckt C**



clearly from current divider rule $\Delta I_G = \frac{1}{2} \Delta I$

$$\therefore \Delta I_G = \frac{0.4}{130} \text{ or } +\frac{0.4}{120} \text{ A.}$$


3) Relevant theory

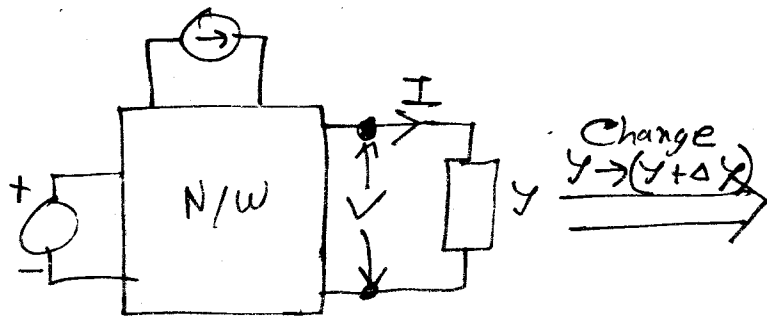

Y is the admittance

$$Y = \frac{1}{Z}$$


CKT 1

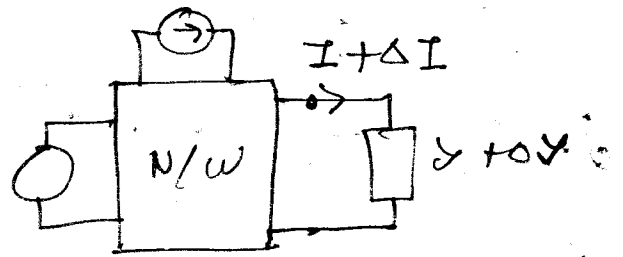

The current is changed from I to $I + \Delta I$

CKT 2

↓ Add a compensating current source I_s to bring the current to the previous value

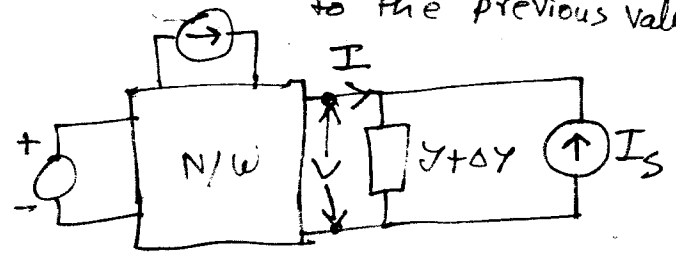

CKT 3

In CKT 3 we want to have same voltage V and current I as in CKT 1.

But under a increased admittance ΔY , the voltage V ~~show~~ would cause $V \Delta Y$ amount of more current to be drawn. I choose


$I_s = V \Delta Y$ so that the extra current drawn by the load ~~#~~ comes exactly from I_s .

$\therefore I_s = V \Delta Y$ which compensates the circuit.

Now,

I_s and N/w together supplies current I


(-) N/w alone	\gg	\gg	$I + \Delta I$
$\therefore I_s$ \gg	\gg	\gg	$-\Delta I$
$\Rightarrow (-) I_s$ \gg	\gg	\gg	$+\Delta I$

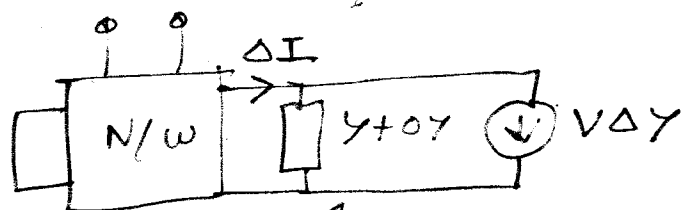


Ckt 4

To find ΔI we can use ckt 4.. where the N/w is inactive & a compensating ~~set~~ current source $V\Delta Y$ is connected as shown.

Before switching ON

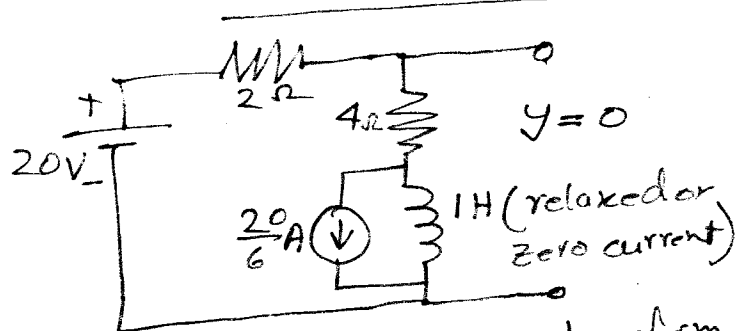


||| Laplace transform

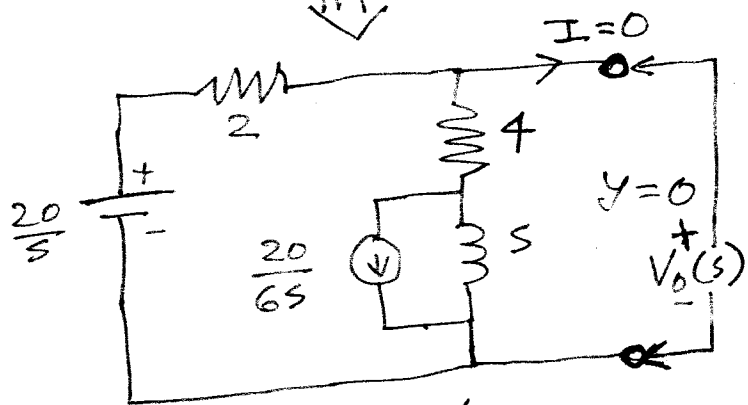


Ckt 1

After switching ON

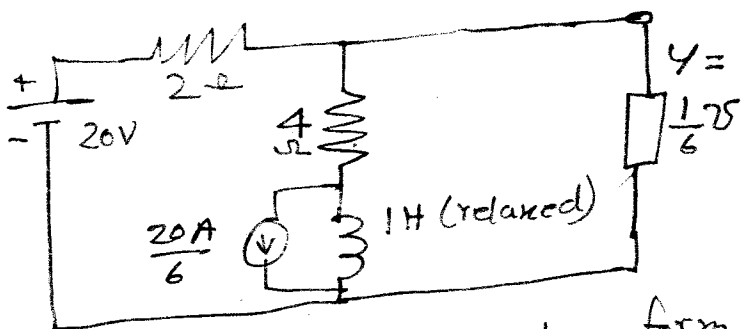

||| Laplace transform

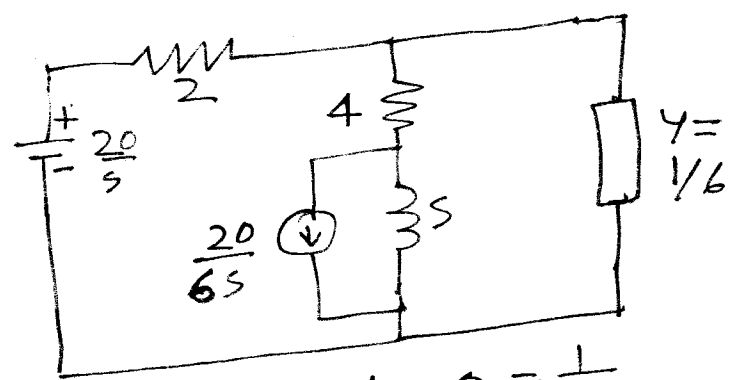


$$\Delta Y = \frac{1}{6} - 0 = \frac{1}{6}$$


~~A using compensation theorem we get.~~

Lets compute $V_0(s)$ first (see ckt 1)

$$\text{clearly } V_0(s) = \frac{20}{6s} \times 4$$

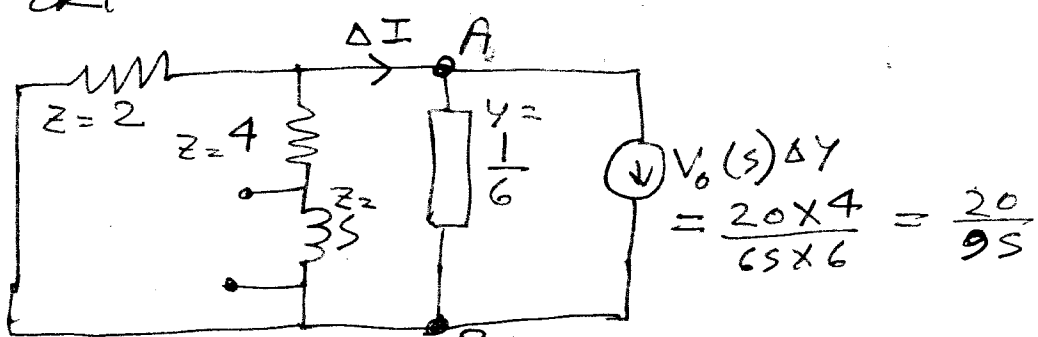∴ Using compensation theorem we can draw the following ckt



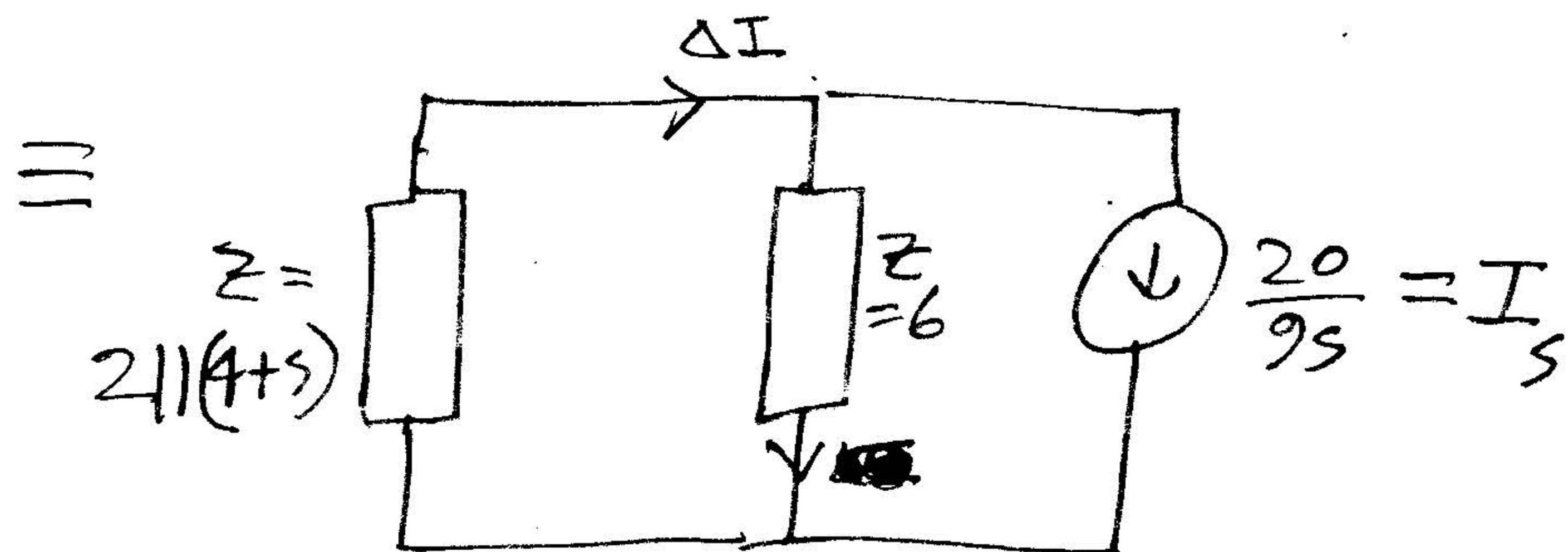

$$\Delta I = I_s \times \frac{6}{6 + (2||4+s)} = \frac{20}{9s} \times \frac{6}{6 + \frac{8+2s}{6+s}}$$

$$= \frac{20}{9s} \times \frac{6(6+s)}{44+8s} = \frac{20}{3s} \times \frac{6+s}{4s+22} = \frac{10}{3s} \times \frac{6+s}{2s+11}$$

$$= \frac{10}{3} \left(\frac{6}{s} + \frac{-1}{2s+11} \right) \cdot \frac{1}{11}$$

$$\therefore i(t) = \mathcal{L}^{-1}\{\Delta I\} = \frac{10}{33} \left[6u(t) - \frac{1}{2}e^{-11/2t}u(t) \right]$$

$$= \left(\frac{20}{11} - \frac{5}{33}e^{-\frac{11t}{2}} \right) u(t)$$


Verification: ① $\lim_{t \rightarrow \infty} i(t) = \frac{20}{11}$. From D.E.

Circuit analysis (by shorting the inductor) we also get $i(t) = \frac{20}{11}$ at steady state.

② Time constant: $\frac{L}{R} = \frac{1}{4 + 2||6} = \frac{1}{4 + \frac{12}{8}} = \frac{8}{44} = \frac{2}{11}$

This also matches with our answer.

④ Zero initial condition.

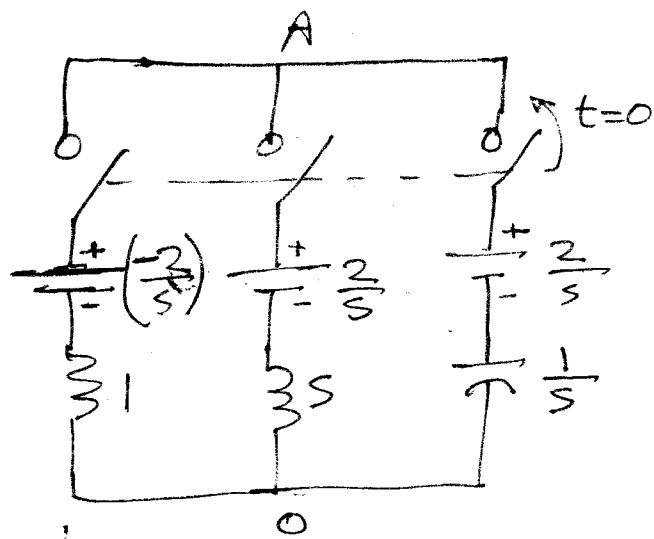

using Millman's Theorem

$$V_{AO}(s) = \frac{\left(-\frac{2}{s}\right) \times 1 + \left(\frac{2}{s}\right) \times \frac{1}{s} + \left(\frac{2}{s}\right) \times s}{1 + \frac{1}{s} + s}$$

$$= \frac{\frac{2}{s} \left(s + \frac{1}{s} - 1\right)}{\left(s + \frac{1}{s} + 1\right)} = \frac{\frac{2}{s} (s^2 - s + 1)}{(s^2 + s + 1)}$$

$$\therefore V_{AO}(s) = \frac{2(s^2 - s + 1)}{s(s^2 + s + 1)} = \frac{2(s^2 + s + 1 - 2s)}{s(s^2 + s + 1)}$$


$$= 2 \left[\frac{1}{s} - \frac{2}{s^2 + s + 1} \right]$$

$$= 2 \left[\frac{1}{s} - \frac{2}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} \right]$$

$$\therefore V_{AO}(t) = 2 \left[u(t) - 2 \times \frac{2}{\sqrt{3}} \sin \left(\frac{\sqrt{3}}{2} t \right) e^{-1/2 t} u(t) \right]$$

$$= 2 \left(1 - \frac{4}{\sqrt{3}} \sin \left(\frac{\sqrt{3}}{2} t \right) e^{-t/2} \right) u(t)$$



5

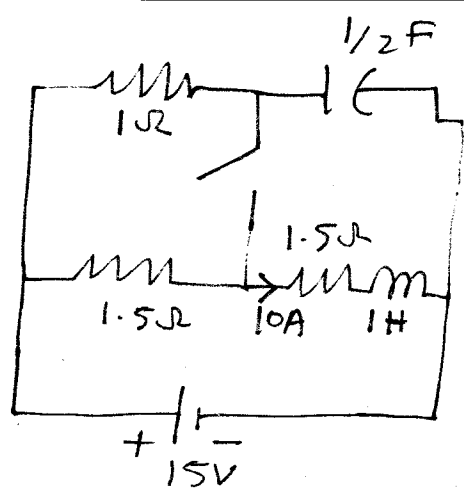

Before the switch is closed at steady state the capacitor behaves like a open circuit and the inductor as short ckt. Therefore, s.s current through the inductor $= \frac{15}{2 \times 1.5} A = 5 A = 5 A$ (left to right)

The capacitor voltage $e = 15V$

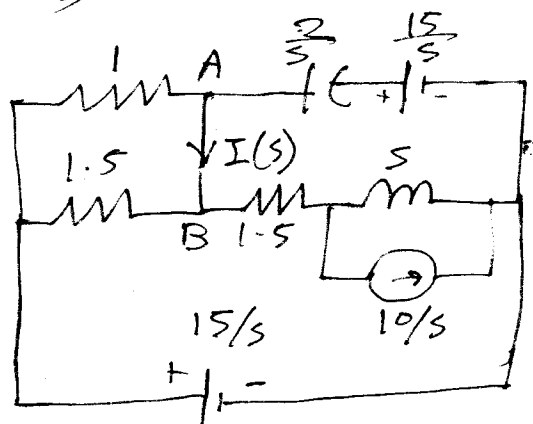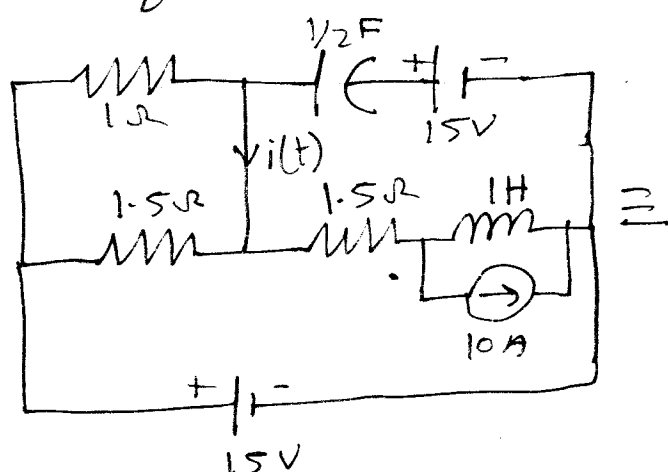\therefore Equivalent ckt after $t \geq 0$



a) Thevenin Theorem

Thevenin impedance between A and B

$$= (1.5 \parallel (1.5 + s)) + (1 \parallel (\frac{2}{s}))$$


$$= \frac{2 \cdot 2.5 + 1.5s}{3 + s} + \frac{\frac{2}{s}}{1 + \frac{2}{s}} = \frac{2 \cdot 2.5 + 1.5s}{3 + s} + \frac{2}{2 + s}$$

$$= \frac{4.5 + 3s + 2 \cdot 2.5s + 1.5s^2 + 6 + 2s}{(3 + s)(2 + s)}$$

$$= \frac{1.5s^2 + 7.25s + 10.5}{(3 + s)(2 + s)} = Z_{th} \text{ (say)}$$

Thevenin voltage between A and B

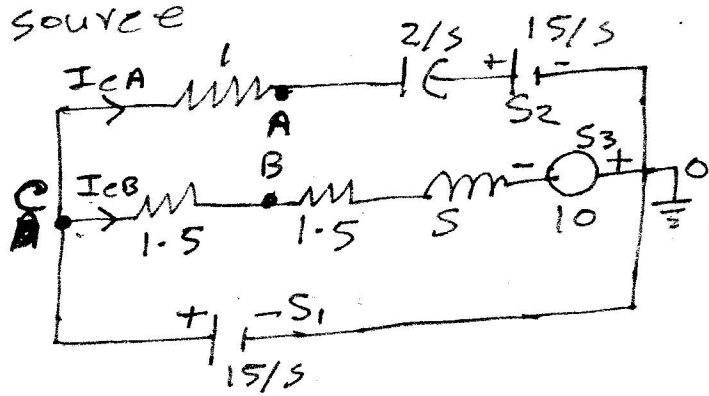Lets convert the current source into a voltage source



Clearly $V_C = \frac{15}{s}$

$$\therefore V_{AB} = V_A - V_B = -I_{CA} \times 1 + I_{CB} \times 1.5$$

$$= -\left(\frac{\frac{15}{s} - \frac{15}{s}}{1 + \frac{2}{s}}\right) \times 1 + \frac{\frac{15}{s} + 10}{3 + s} \times 1.5$$

$$= 0 + \frac{(3 + 2s) 7.5}{s(s + 3)} = 7.5 \left(\frac{1}{s + 3} + \frac{1}{s} \right)$$


$$\therefore V_{th}(s) = 7.5 \left(\frac{1}{s + 3} + \frac{1}{s} \right) = \frac{7.5(2s + 3)}{s(s + 3)}$$

$$\therefore I(s) = \frac{V_{th}(s)}{Z_{th} + 0} = \frac{7.5(2s + 3)}{s(s + 3)} \times \frac{(3 + s)(2 + s)}{1.5s^2 + 7.25s + 10.5}$$

$$= \frac{750(2s + 3)(2 + s)}{s(150s^2 + 725s + 1050)}$$

$$= \frac{30(2s + 3)(s + 2)}{s(6s^2 + 29s + 42)}$$

(b) Mesh ~~analysis~~ analysis

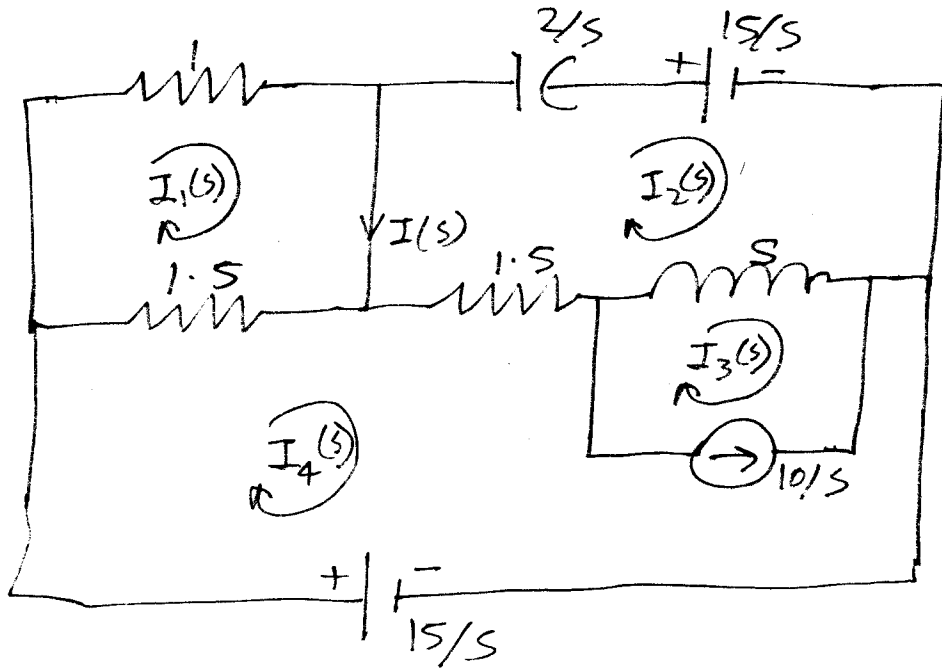

KVL on loop 1: $2.5 I_1(s) = 1.5 I_4(s)$
 $\Rightarrow I_4(s) = \frac{5}{3} I_1(s) \quad \text{--- (1)}$

Current source between loop 3 and 4:

$$I_4(s) - I_3(s) = \frac{10}{s}$$
$$\Rightarrow \frac{5}{3} I_1(s) - I_3(s) = \frac{10}{s} \quad (\text{using (i)})$$
$$\Rightarrow I_3(s) = \frac{5}{3} I_1(s) - \frac{10}{s} \quad \text{--- (ii)}$$

$$\begin{aligned} \text{KVL on loop 2:} \\ I_2(s) \left(\frac{2}{s} + s + 1.5 \right) - I_3(s) s - I_4(s) 1.5 &= -\frac{15}{s} \\ \Rightarrow I_2(s) \left(\frac{s^2 + 1.5s + 2}{s} \right) - \frac{ss}{3} I_1(s) + 10 - \frac{s}{2} I_1(s) &= -\frac{15}{s} \\ \Rightarrow I_2(s) \left(\frac{s^2 + 1.5s + 2}{s} \right) - I_1(s) \left(\frac{10s + 15}{6} \right) &= -\frac{15}{s} - 10 \\ &= -\frac{15 + 10s}{s} \end{aligned}$$

$$\Rightarrow I_1(s) = \left(I_2(s) \left(\frac{s^2 + 1.5s + 2}{s} \right) + \frac{15 + 10s}{s} \right) \times \frac{6}{(10s + 15)} \quad \dots \textcircled{iii}$$

KVL on combined loop 3 & 4:

$$\frac{15}{s} = -1.5 I_1(s) - I_2(s)(s+1.5) + I_3(s)s + I_4(s)(1.5+1.5)$$

$$= -1.5 I_1(s) - I_2(s)(s+1.5) + \left(\frac{5}{3} I_1(s) - \frac{10}{s}\right)s +$$

$$= 3.5 I_1(s) + \frac{5s}{3} I_1(s) - I_2(s)(s+1.5) - 10$$

$$\Rightarrow I_1(s) \left(\frac{10.5 + 5s}{3} \right) - I_2(s)(s+1.5) = \frac{15+10s}{s}$$

using the value of $I_1(s)$ from (iii)

$$\Rightarrow \frac{(10.5 + 5s)}{3} \times \left(I_2(s) \left(\frac{s^2 + 1.5s + 2}{s} \right) + \frac{15+10s}{s} \right) \times \frac{2}{(10s+15)} - I_2(s)(s+1.5) = \frac{10s+15}{s}$$

$$\Rightarrow \frac{2(10.5 + 5s)}{(15+10s)} \left(I_2(s) \left(\frac{s^2 + 1.5s + 2}{s} \right) \right) - I_2(s)(s+1.5) + \frac{2(10.5 + 5s)}{s} = \frac{10s+15}{s}$$

$$\Rightarrow I_2(s) \left(\frac{21+10s}{15+10s} \times \frac{s^2 + 1.5s + 2}{s} - \frac{s^2 + 1.5s}{s} \right) = \frac{-6}{s}$$

$$\Rightarrow I_2(s) \left(\frac{(21+10s)(s^2 + 1.5s) + 2(21+10s) - (s^2 + 1.5s)(15+10s)}{15+10s} \right) = -6$$

$$\Rightarrow I_2(s) \left(\frac{(s^2 + 1.5s)6 + 42 + 20s}{6s^2 + 29s + 42} \right) = -90 - 60s$$

$$\Rightarrow I_2(s) = \frac{-30(3+2s)}{6s^2 + 29s + 42} \quad \text{--- (iv)}$$

Now from (iii)

$$I_1(s) = I_2(s) \left(\frac{s^2 + 1.5s + 2}{s} \right) \frac{6}{(15 + 10s)} + \frac{6}{s}$$

$$\text{Now } I(s) = I_1(s) - I_2(s)$$

$$= I_2(s) \left(\frac{6(s^2 + 1.5s + 2)}{(15 + 10s)s} - 1 \right) + \frac{6}{s}$$

$$= \frac{-30(3+2s)}{6s^2 + 29s + 42} \left(\frac{6s^2 + 9s + 12 - 10s^2 - 15s}{s(15+10s)} \right) + \frac{6}{s}$$

[using equation (iv)]

$$= \frac{-30}{6s^2 + 29s + 42} \left(\frac{-4s^2 - 6s + 12}{5s} \right) + \frac{30}{5s}$$


$$= \frac{30}{6s^2 + 29s + 42} \left[\frac{4s^2 + 6s - 12}{5s} + \frac{6s^2 + 29s + 42}{5s} \right]$$

$$= \frac{30}{6s^2 + 29s + 42} \left[\frac{10s^2 + 35s + 30}{5s} \right]$$


$$= \frac{30(2s+3)(s+2)}{(6s^2 + 29s + 42)s}$$

Now $i(t)$ can be computed by taking a Laplace inverse of $I(s)$ using partial fraction method which is left for the students.

⑥

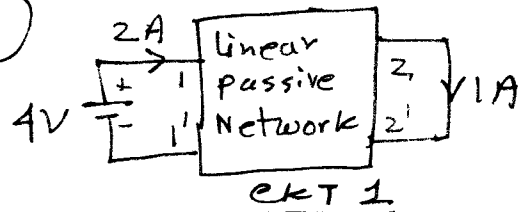

ckt 1

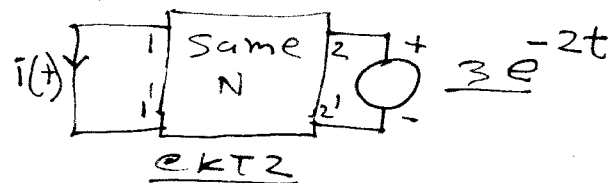

ckt 2

- Using compensation theorem, $i(t)$ in ckt 2 is given by $\frac{3}{4}e^{-2t}$.

- From ckt 1, the impedance as viewed from 1-1' port (i.e. input impedance of 1-1') is

$$Z_{th} = \frac{4V}{2A} = 2\Omega$$

- The short circuit current in 1-1' of ckt 2

$$I_{sc} = \frac{3}{4}e^{-2t} A$$

- The impedance of 1-1' of ckt 2 is same as the impedance of 1-1' of ckt 1 = $Z_{th} = 2\Omega$

- Now if we replace the short ckt at 1-1' in ckt 2 with a 4Ω resistance then the current in 1-1' of ckt can be found using Norton's theorem


$$i = I_{sc} \times \frac{Z_{th}}{Z_{th} + 4\Omega} = \frac{3}{4}e^{-2t} \times \frac{2}{2+4} A$$

$$= \frac{1}{4}e^{-2t} A.$$

Note

In this problem we have implicitly assumed that the network is instantaneous i.e. has no transient behaviour ~~or~~ i.e. - resistive in nature.

7

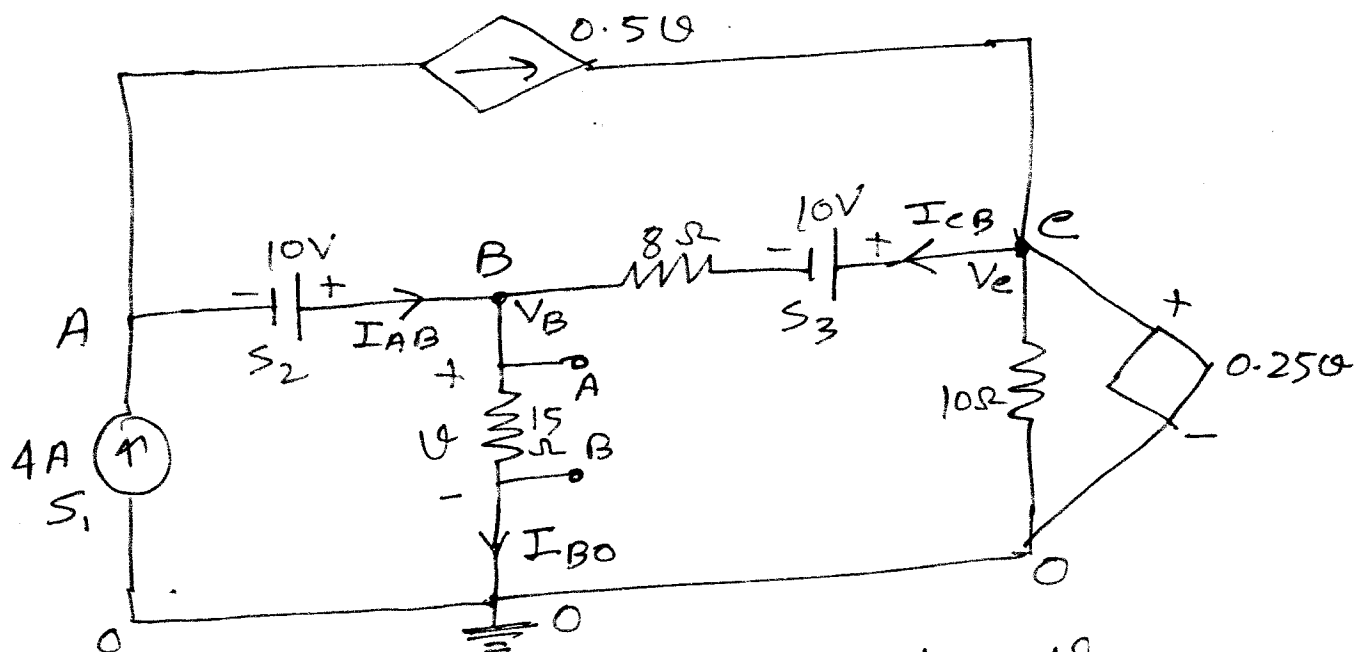

(a) Superposition theorem to compute V
Step 1: S_1 Active, S_2 & S_3 short circuited

$$I_{AB} = 4 - 0.5V$$

$$V_C = 0.25V \quad \text{and} \quad V_B = V$$

$$\therefore I_{CB} = \frac{V_C - V_B}{8} = \frac{0.25V - V}{8} = -\frac{3}{32}V$$

$$\therefore I_{BO} = I_{AB} + I_{CB} = 4 - 0.5V - \frac{3}{32}V$$

$$\therefore V_B = V = 15 \times I_{BO} = 15 \left(4 - \frac{1}{2}V - \frac{3}{32}V \right)$$

$$= 60 - \left(\frac{15 \times 16}{32} + \frac{45}{32} \right) V$$

$$\Rightarrow V \left(1 + \frac{15 \times 16}{32} + \frac{45}{32} \right) = 60$$

$$\Rightarrow V = \frac{60 \times 32}{317}$$

(b) Step 2: S_1 opened, S_2 active, S_3 shorted

$$I_{AB} = -\frac{1}{2}V$$

$$I_{CB} = -\frac{3}{32}V \quad (\text{as before})$$

$$\therefore V = 15 \times I_{BO} = 15 \left(I_{AB} + I_{CB} \right) = 15 \left(-\frac{1}{2} - \frac{3}{32} \right) V$$

$$\Rightarrow V = 0$$

Step 3: S_1 open, S_2 shorted, S_3 active

$$\therefore I_{AB} = -\frac{1}{2} V$$

from branch BC

$$V + 8 I_{CB} + 10 = \frac{V}{4}$$

$$\Rightarrow 8 I_{CB} = -10 - \frac{3}{4} V$$

$$\Rightarrow I_{CB} = -\frac{1}{8} \left(10 + \frac{3}{4} V \right)$$

$$\begin{aligned} \therefore V_{BO} = V &= 15 \times I_{BO} = 15 (I_{AB} + I_{CB}) \\ &= 15 \left(-\frac{1}{2} V - \frac{10}{8} - \frac{3}{32} V \right) \\ &= 15 \left(-\frac{10}{8} - \frac{19}{32} V \right) \end{aligned}$$

$$\Rightarrow V \left(1 + \frac{15 \times 19}{32} \right) = -\frac{150}{8}$$

$$\Rightarrow V \left(\frac{317}{32} \right) = -\frac{150}{8} \Rightarrow V = \frac{-150}{8} \times \frac{32}{317} = \frac{-600}{317}$$

\therefore By adding the results for individual sources
(superposition theorem)


$$V = \frac{60 \times 32}{317} + 0 - \frac{600}{317} = \frac{60 \times 22}{317} = \frac{1320}{317}$$

$$\therefore V_{AB} = V = \frac{1320}{317}$$

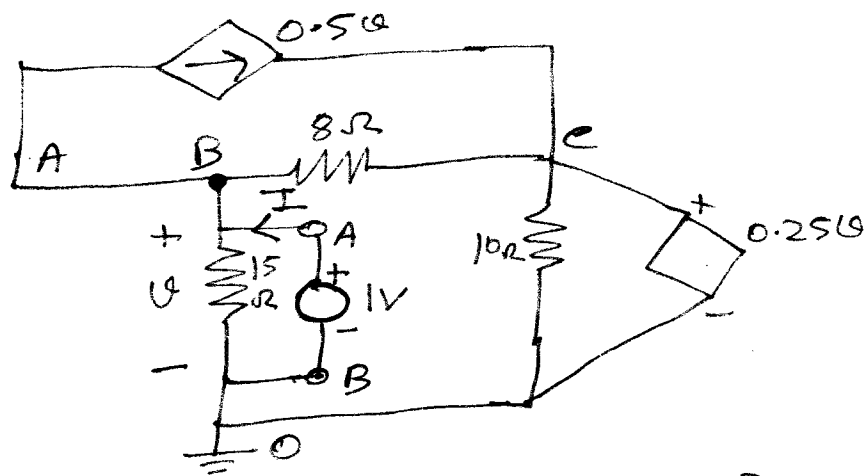(b) Thevenin voltage as computed in part (a)

$$= \frac{1320}{317} \text{ V}$$

To get thevenin impedance we connect a 1V source between A and B & deactivate all the internal ^{independent} sources



Clearly now
 $V = 1$
 we need to find
 the current I

Applying KCL at node B

$$I - 0.5V - (V - 0.25V)/8 - \frac{V}{15} = 0$$

$$\Rightarrow I = \frac{V}{15} + \frac{V}{8} + \frac{3}{32}V = \frac{1}{15} + \frac{1}{8} + \frac{3}{32} \quad [\because V=1]$$

$$= \frac{32 + 16 \times 15 + 3 \times 15}{32 \times 15} = \frac{32 + 240 + 45}{480}$$

$$= \frac{317}{480}$$

$$\therefore Z_{th} = \frac{1}{I} = \frac{480}{317}$$

\therefore Thevenin eqv. ckt between AB is

