

Tutorial Sheet-4 (Three Phase System)

1. A high-voltage generator is connected to a 3-phase wye connected load through a transmission line. Each phase of the line has impedance Z_l , and the load is a balanced wye with branch impedance Z . Line to line voltage, $|V_{ab}| = 45\text{kV}$, $Z_l = (0.5 + j3)\Omega$, $Z = (4.5 + j9)\Omega$. Find the line currents, power consumed by the load and line losses. Draw the phasor diagram.

[Ans. $I_a = 2\angle -67.38^\circ \text{ A}$, $I_b = 2\angle 172.62^\circ \text{ A}$, $I_c = 2\angle 52.62^\circ \text{ A}$, $P_{\text{Load}} = 53.99 \text{ MW}$, $P_{\text{Line}} = 6 \text{ MW}$]

2. A balanced 3-phase a-b-c system with line-to-line voltage $V_{ab} = 208\angle 0^\circ \text{ V}$ supplies to a balanced Δ connected load of 3 kW with a power factor of 0.8 (lag) through a lossless transmission line. Find the line currents. Draw the phasor diagram.

[Ans. $I_a = 10.41\angle -66.9^\circ \text{ A}$, $I_b = 10.41\angle 173.1^\circ \text{ A}$, $I_c = 10.41\angle 53.1^\circ \text{ A}$]

3. A balanced 3-phase delta connected load of 160 kW, connected to a line voltage of 1100 V, 50Hz, takes a leading current of 100 A. Find the circuit constants of the load per phase.

[Ans. $R_{\text{ph}} = 16 \Omega$, $C_{\text{ph}} = 307.87 \mu\text{F}$]

4. Calculate the value of X_C in Fig. 1 such that the combined circuit behaves as a three phase balanced resistive network.

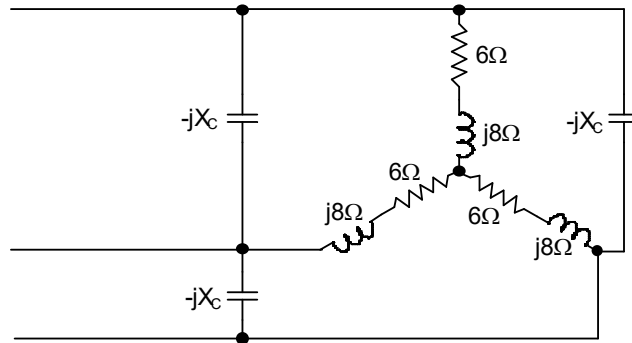


Fig.1

[Ans. 37.5Ω]

5. For the 3-phase balanced system of Fig.4 calculate the current phasors I_{R1} and I_{R2} as marked in the figure with R-phase supply voltage as reference (sequence be RYB). Each $Z = 10\angle 30^\circ \Omega$ and each $Z_1 = 30\angle -90^\circ \Omega$.

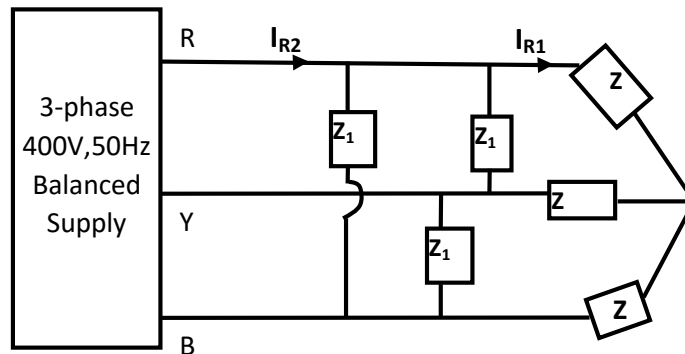


Fig.2

[Ans. $I_{R1} = 23.094\angle -30^\circ \text{ A}$, $I_{R2} = 23.094\angle 30^\circ \text{ A}$]

6. For the circuit shown in Fig. 2, calculate the branch currents of the Δ connected load and the active and reactive power consumed by it.



Fig.3

[Ans. $I_{RB} = 5.75 \angle -30^\circ$ A, $I_{BY} = 5.78 \angle 30^\circ$ A, $I_c = 5.78 \angle -90^\circ$ A, $P = 499$ W, $Q = 499$ VAR]

7. In the circuit of Fig. 3, A three phase balanced voltage source is supplying power to a three phase constant power load as shown in Fig. 3. Calculate the line currents.

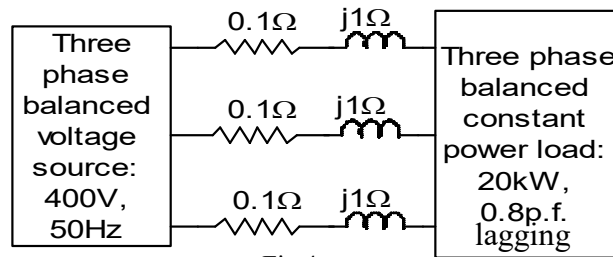


Fig.4

[Ans. $I_a = 41.55 \angle -44.86^\circ$ A, $I_b = 41.55 \angle -164.86^\circ$ A, $I_c = 41.55 \angle 75.14^\circ$ A]

8. A wattmeter reads 5.54 kW when its current coil is connected in R phase and its voltage coil connected between the neutral and the R phase of a symmetrical 3-phase system supplying a balanced load of 30 A at 400 V. What will be the reading on the instrument if the connections to the current coil remain unchanged and the voltage coil be connected between B and Y phases? Take phase sequence RYB. Draw the corresponding phasor diagram.

[Ans. 7.2 kW]

9. Calculate the readings of the two wattmeters (W1 and W2) connected to measure the total power for a balanced delta-connected load fed from a three-phase, 400 V balanced supply with phase sequence as R-Y-B as shown in Fig.5. The load impedance per phase contains capacitive reactance, $X_c = 14 \Omega$ and resistance, $R = 14 \Omega$.

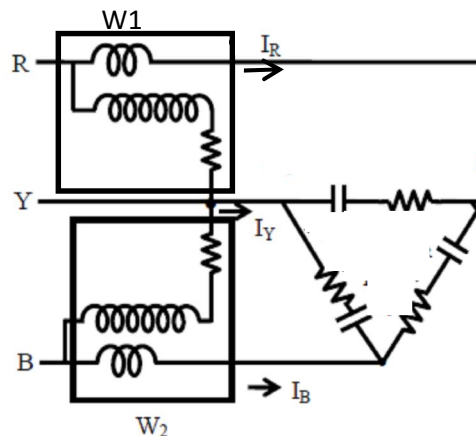


Fig.5

[Ans. $W1 = 13.52$ kW, $W2 = 3.623$ kW]