

# Signals & Networks Laboratory Experiment Manual

Department of Electrical Engineering, I.I.T. Kharagpur

## Experiment No. : 1

### Maximum power transfer and Reciprocity theory

**Objective:** Verification of Maximum Power Transfer theorem and Reciprocity theorem.

**Theory:** Maximum power is transfer from a source of given voltage and an initial impedance to the load impedance  $Z_L$  in a circuit (Fig: 1) under three different condition.

a) When only  $X_i$  is adjustable:

Under this condition the power consumed by the load ( $P_{R_L}$ ) is maximum, when  $I$  is maximum, since  $R_L$  is constant.

$$I = \frac{V_S}{R_i + jX_i + R_L + jX_L} \dots\dots\dots(1)$$

$$\Rightarrow |I|_{\max} = \frac{V_S}{R_i + R_L} \dots\dots\dots(2)$$

Where,  $X_i = -X_L$

This means that if the Load reactance  $X_L$  is made equal in magnitude and opposite in sign to the internal reactance  $X_i$ , the power is transferred maximum.

b) When only  $R_L$  are adjustable:

From equation (1) in section (a), one may write,

$$\begin{aligned} P &= |I|^2 R_L \\ &= \frac{V_S^2}{(R_i + R_L)^2 + (X_i + X_L)^2} * R_L \dots\dots\dots(3) \end{aligned}$$

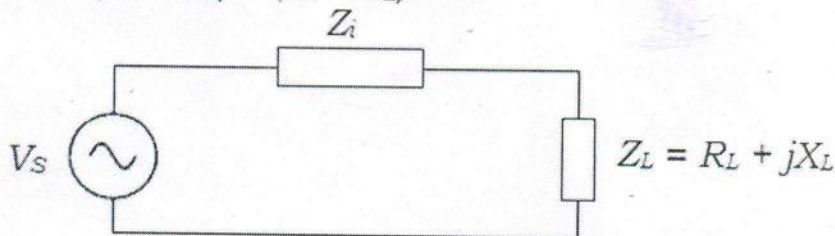


Fig. 1

Differentiating equation (3) w.r.t.  $R_L$  and equating to zero, one obtains,

$$R_L = \sqrt{R_i^2 + (X_i + X_L)^2} \dots\dots\dots(4)$$

c) When both  $R_L$  and  $X_L$  are adjustable:

Under this condition both equation (2) and (4) are valid simultaneously and one obtains,

$$R_L = R_i, \quad X_L = -X_i$$

**Procedure: (A)**

- i) Take a suitable set of values of  $V_S$ ,  $R_i$  and  $X_i$  as shown in fig. (2). You can choose  $X_i$  to be inductive (assume the resistive loss of the coil to be negligible).
- ii) Next choose a suitable load resistance  $R_L$  and a variable capacitance  $C$  such that the critical value of  $C$ , ( $C_0 = \frac{1}{4\pi^2 f^2 L}$ ) falls within the range of the values of  $C$ , available (decade box) in steps. This is to ensure that for a particular frequency, we can obtain the condition;

$$|X_C| = |X_L| \quad \text{or,} \quad \frac{1}{\omega C} = \omega L, \quad \text{for some value of } C \text{ within the range provided.}$$

Now for different value of  $C$  note down  $V_3$  and  $V_1$ ,

$$P_L = I^2 R_L = I \cdot I R_L = \frac{V_1}{100} \cdot V_3 = K \cdot V_1 V_3 \quad \text{where } K = \frac{1}{100} = \frac{1}{R_i}$$

Enter the values of the voltage for different values of  $C$  and obtain the set corresponding to the maximum value of  $(V_1 V_3)$ . Verify that for this set

$$V_2 = V_4.$$

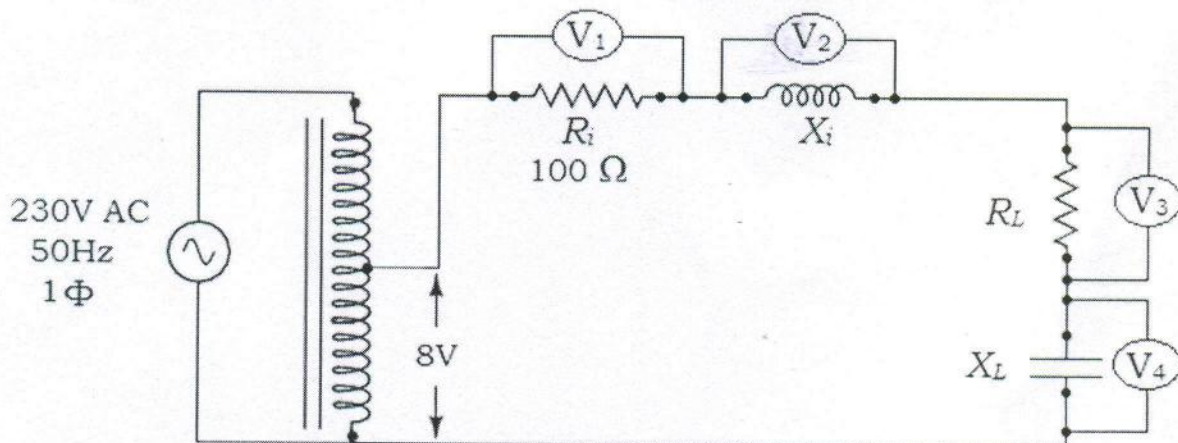


Fig. 2



Enter the data in the following table:

| SL. No. | C | V <sub>1</sub> | V <sub>3</sub> | (V <sub>1</sub> .V <sub>3</sub> ) | Max. value (V <sub>1</sub> .V <sub>3</sub> ) |
|---------|---|----------------|----------------|-----------------------------------|--|
| 1       |   |                |                |                                   |  |
| 2       |   |                |                |                                   |  |
| 3       |   |                |                |                                   |  |
| 4       |   |                |                |                                   |  |
| 5       |   |                |                |                                   |  |

(B) Repeat the procedure of part (A), with  $C$  fixed and  $R_L$  varied. At the point of maximum power, check

$$R_L = \sqrt{R_i^2 + (X_i + X_L)^2} \dots\dots\dots(4)$$

(C) Repeat the procedure of part (B), varying  $C$  and obtain the maximum power condition. Check under this condition;

$$\begin{array}{lll} & V_{RL} = V_{Ri} & \text{i.e. } V_1 = V_3 \\ \text{and} & V_{XL} = V_{Xi} & \text{i.e. } V_2 = V_4 \end{array}$$





## RECIPROCITY THEOREM

**Theory:** Consider 2-Port (4-terminal) linear bilateral passive networks as shown in Fig.3. Apply a voltage  $V_S$  across terminals 1-1' and  $I_3$  flows through the ammeter connecting terminals 2-2'. Next interchange the positions of the ammeter and the source voltage. The magnitude of the source voltage in this new position is set to  $V'_s$ . Measure the corresponding current  $I'_1$ . The reciprocity theorem states that for passive bilateral network;

$$\frac{V_S}{I_3} = \frac{V'_s}{I'_1}$$

**Procedure:** Connect the given resistive network. Apply 220V, single phase 50 Hz AC voltage at 1-1' and measure the ammeter current  $I_3$  through 2-2'. Check the ratio  $V_S/I_3$ . Now apply the AC voltage across 2-2' with  $V'_s=110$  V and measure the current  $I'_1$  through 1-1' by ammeter. Find the ratio  $V'_s/I'_1$ . These two ratio should be identical and calculate branch currents and node voltages for two circuit configurations.

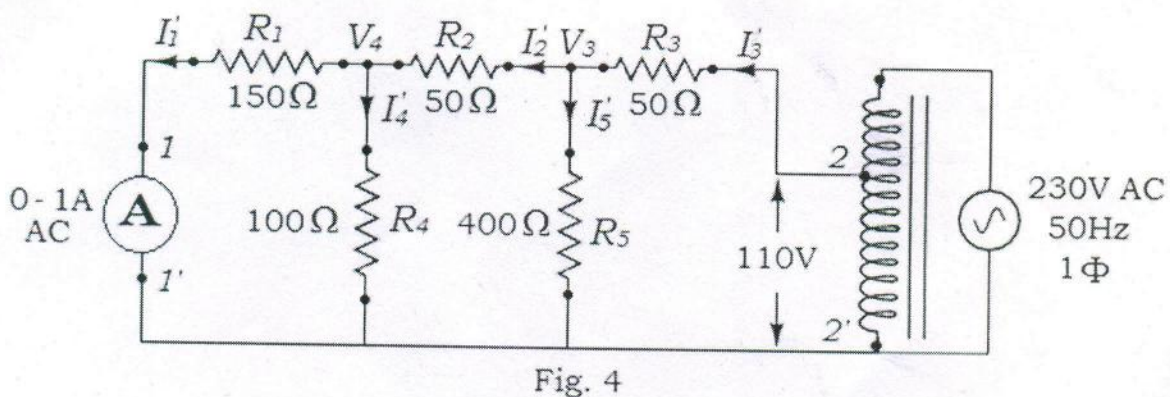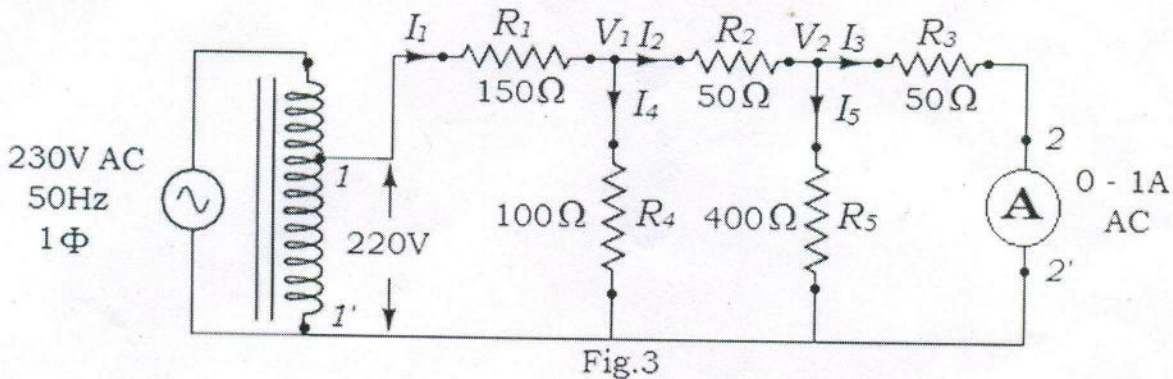

Enter the data in the following table:

| $V_S$ | $I_3$ | $V_S/I_3$ | $V'_s$ | $I'_1$ | $V'_s/I'_1$ |
|-------|-------|-----------|--------|--------|-------------|
|       |       |           |        |        |             |