
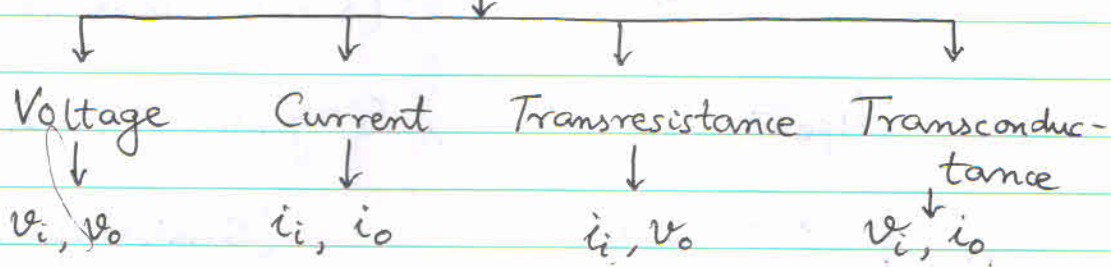


19. Types of Amplifiers:

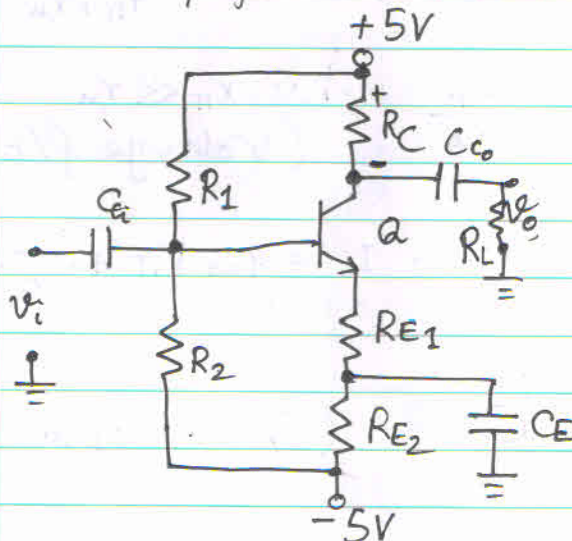

20. CE amplifier with Emitter Bypass Capacitor:




w/o C_E $\{ R_E \uparrow, A_v \downarrow$

with $\left\{ \begin{array}{l} X_C \downarrow_{(ac)}^{HF} R_E \downarrow \\ I_E \uparrow I_C \uparrow A_v \uparrow \end{array} \right.$

$$\left[X_{C_E} = \frac{1}{2\pi f C_E} \right]$$






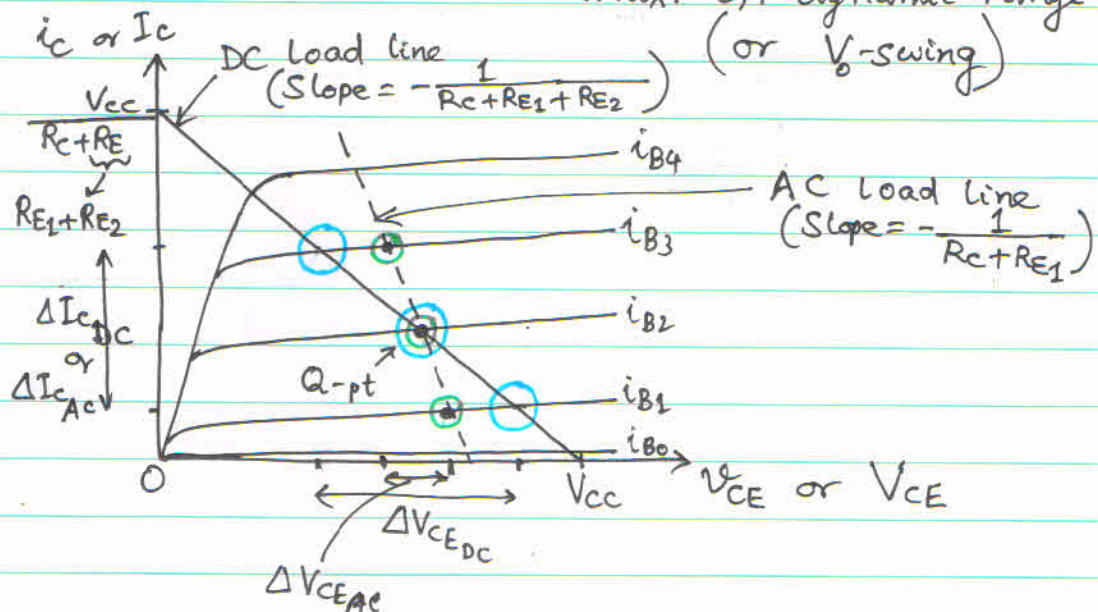
21. AC Load Line Analysis: & its relation with max. O/P dynamic range (or V_o -swing)




Due to $C_E // R_{E2}$, at high frequencies, R_{E2} is bypassed/shorted through C_E , thereby increases/compensates gain at high frequencies.

Due to C_E & AC load line, max. O/P V-swing/range changes for a particular I/P V-swing/range, provided the amp. works in forward-active region (or linear mode/region).

22. Frequency response analysis.

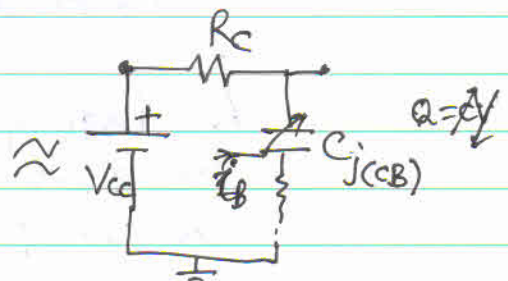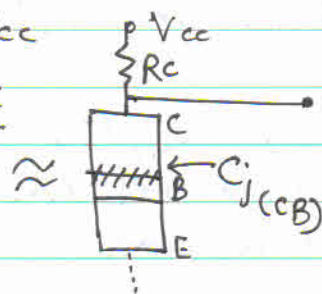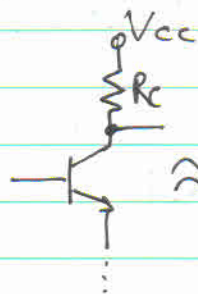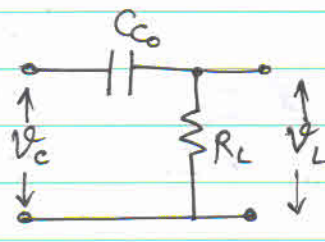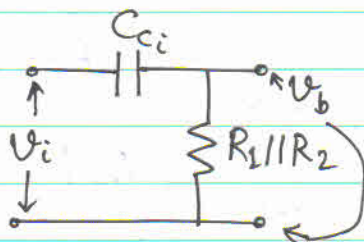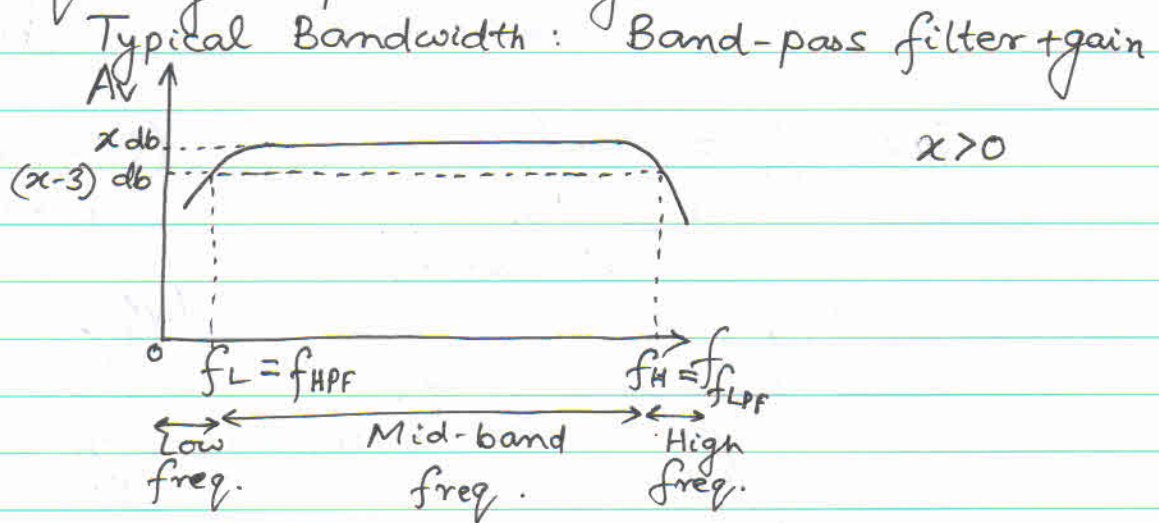

Hybrid- π eqv. ckt. (high freq.)


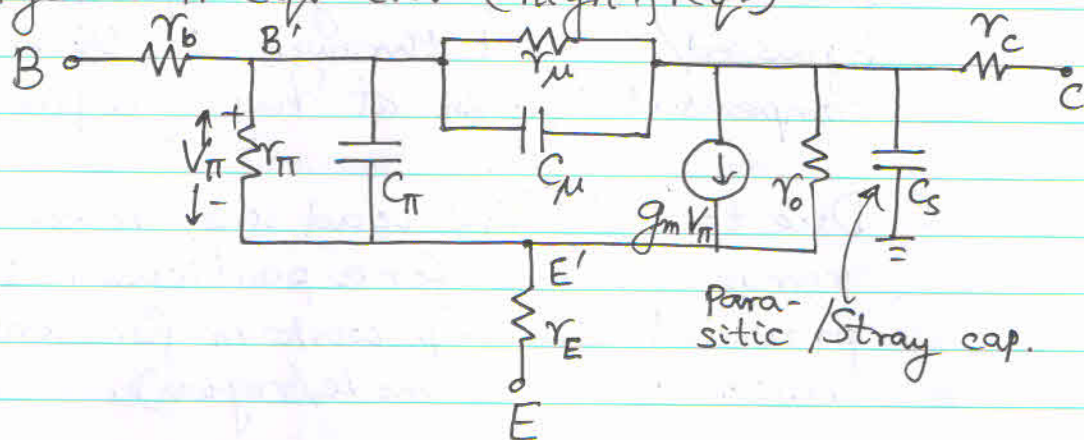


$$f_{\beta} = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_{\mu})} \quad (3 \text{ db cut-off})$$

↑
LPF

GBW $\rightarrow f_T = \beta_o \cdot f_{\beta}$ (Gain-bandwidth product)
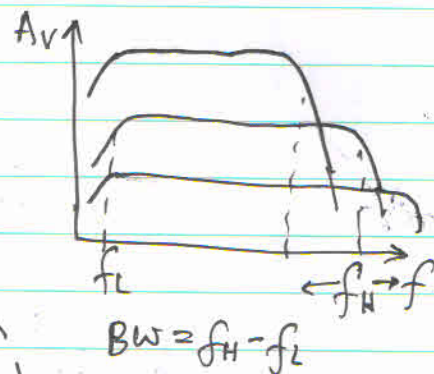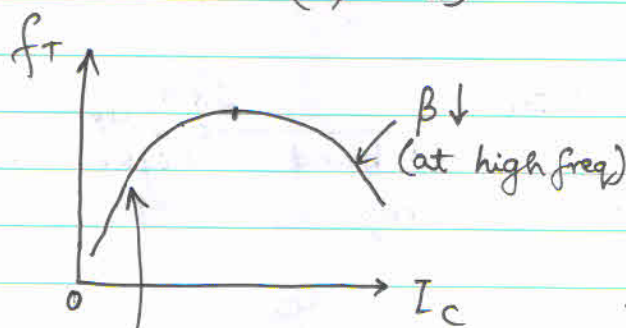
$$= \frac{g_m}{2\pi (C_{\mu} + C_{\pi})}$$



$$g_m \propto I_C \quad \left(\because g_m = \frac{I_{CQ}}{V_T} \right)$$

$$r_{\pi} \& C_{\pi} \rightarrow I_C \quad \left(\because r_{\pi} = \frac{V_T}{I_{BQ}} \right)$$




$A_v \uparrow \quad BW \downarrow$

23. Miller effect

\rightarrow Feedback multiplication.

At high freq, C_{c_i} , C_{c_o} & C_E are considered to be short-circuited. And, C_{μ} connects O/P to I/P.
 $C_{\mu} \rightarrow$ 2-port network.

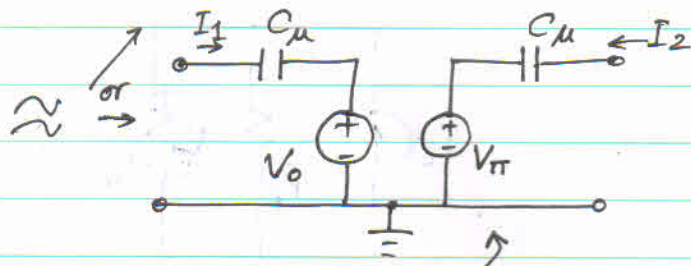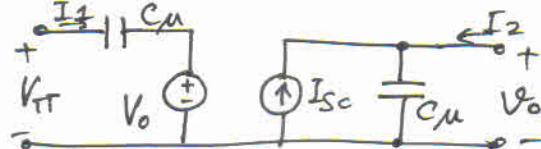
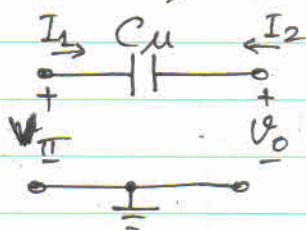
Norton's equivalent $\rightarrow I_{sc} = \frac{V_{\pi}}{(j\omega C_{\mu})}$




$$C_{\mu} = \frac{g_m}{\omega} \leftarrow \text{Angular freq}$$

Thevenin's equivalent.
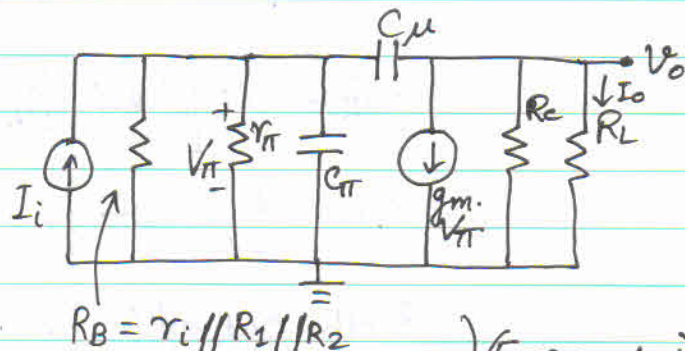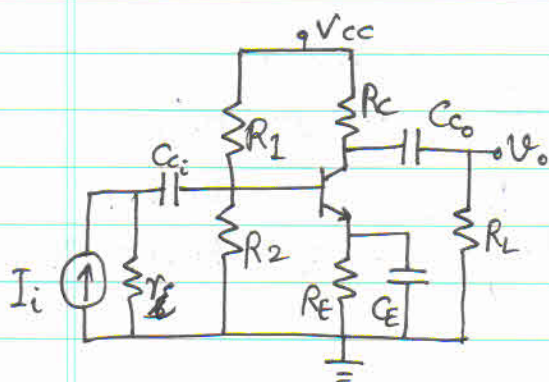
$$\Rightarrow f = \frac{g_m}{2\pi C_{\mu}} \quad (\text{freq. at which } V_o = V_{\pi})$$



(Expanded into)

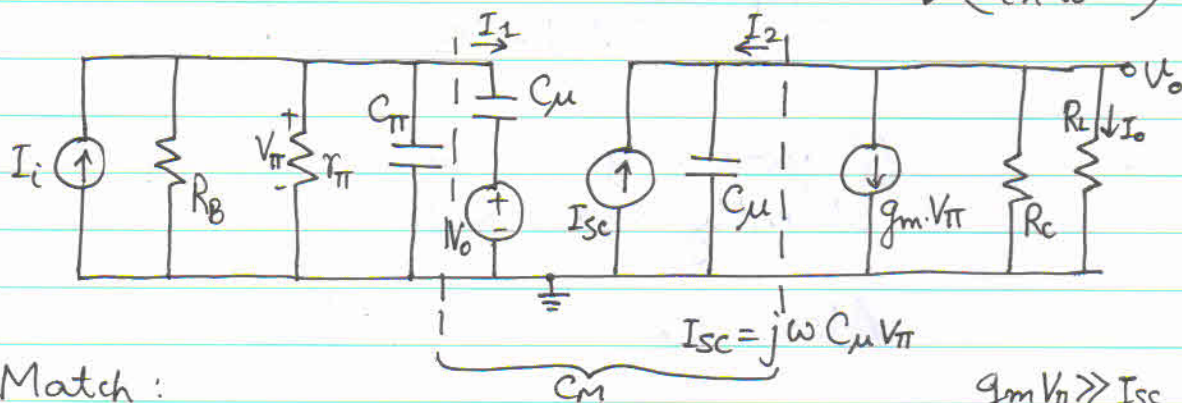

Match:

$$Z_{C_{\mu}} = Z_{(R_C // R_L)}$$

$$\Rightarrow \frac{1}{\omega C_{\mu}} = R_C // R_L$$


$$\therefore f = \frac{1}{2\pi C_{\mu} (R_C // R_L)}$$

$$V_o = -g_m V_{\pi} (R_C // R_L)$$

$$I_o = -g_m V_{\pi} \frac{R_C}{R_C + R_L}$$

Ckt. segment in between the dotted lines can be replaced by C_M
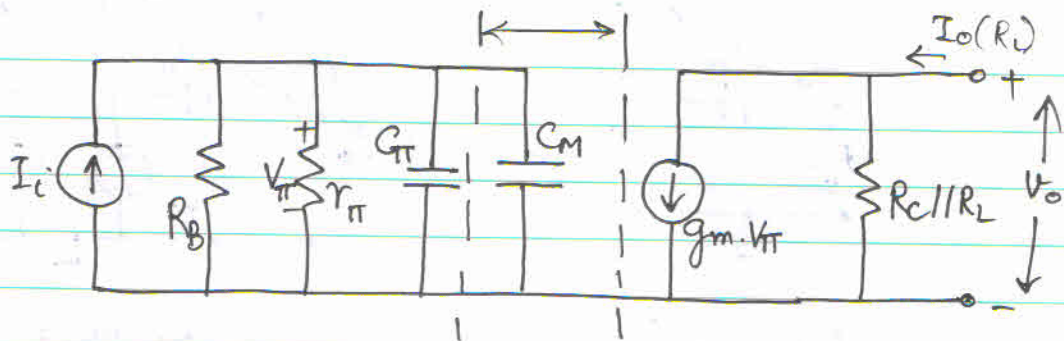
$$C_M = C_{\mu} [1 + g_m (R_C // R_L)] \quad (\text{Miller Capacitance})$$



Simplified hybrid- π eqv. ckt. with C_M

I/P capacitance ^{is} increased $\Rightarrow C_\pi + C_M$.

$$V_\pi = I_i \left[(R_B \parallel r_\pi) \parallel \left(\frac{1}{j\omega C_\pi} \right) \parallel \left(\frac{1}{j\omega C_M} \right) \right]$$

$$A_i = \frac{I_o}{I_i} = -g_m \left(\frac{R_C}{R_C + R_L} \right) \left[\frac{R_B \parallel r_\pi}{1 + j\omega (R_B \parallel r_\pi) (C_\pi + C_M)} \right]$$

3 db cut-off freq.

$$\hookrightarrow f_{3db} = \frac{1}{2\pi (R_B \parallel r_\pi) (C_\pi + C_M)}$$

If you neglect C_M (or $C_M = 0$), the result is slightly inaccurate

$$\text{Also, } C_M = C_\mu (1 + |A_v|)$$