
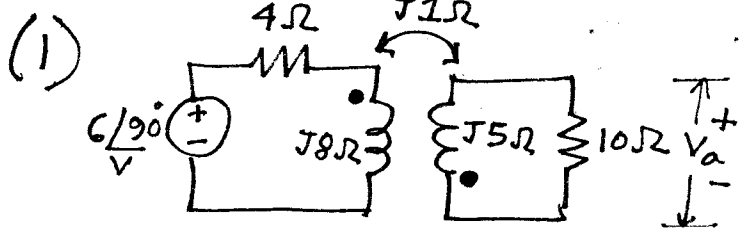


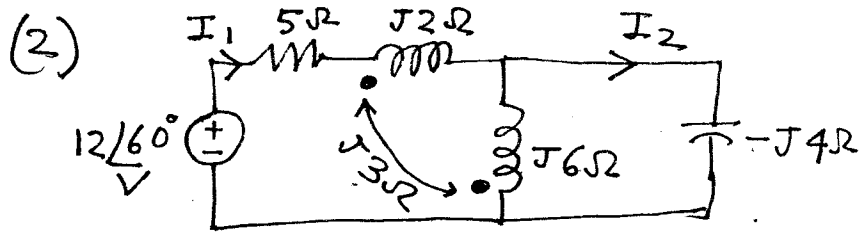Tutorial 7: MAGNETICALLY COUPLED CIRCUITS






Determine the voltage V_a across the 10Ω resistance




Determine the phasor currents I_1 and I_2

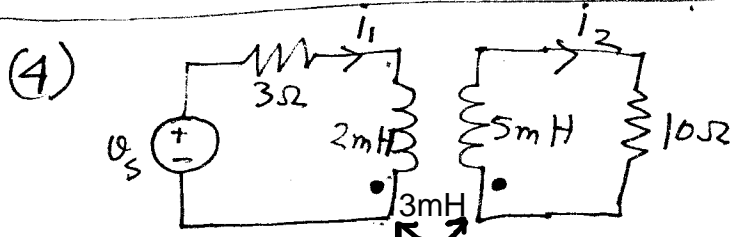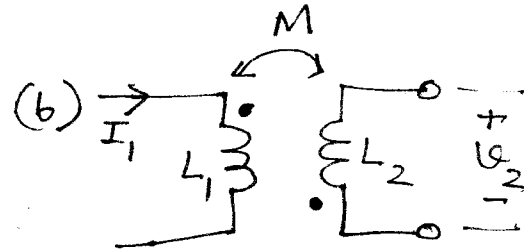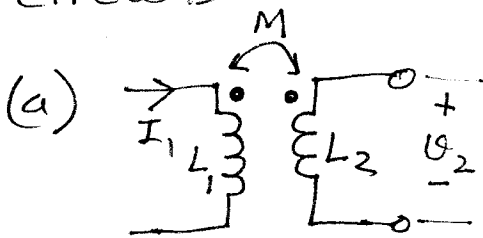(3) Assuming $M=10H$, coil L_2 is open-circuited, and $i_1 = -2e^{-5t} A$, Find the voltage V_2 for the following circuits




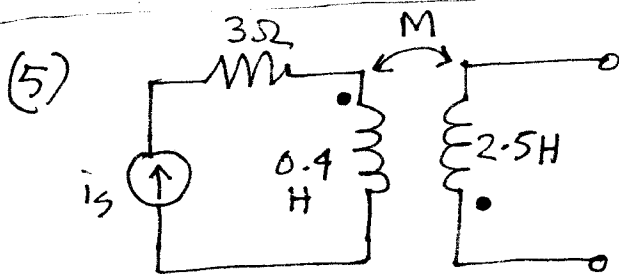Write the appropriate mesh equations for the given circuit.



Let $i_s = 2\cos(10t) A$. $k=0.6$. Find the total energy stored in the passive network at $t=0$ if (a) secondary is open-circuited (b) secondary is shorted.


(6)

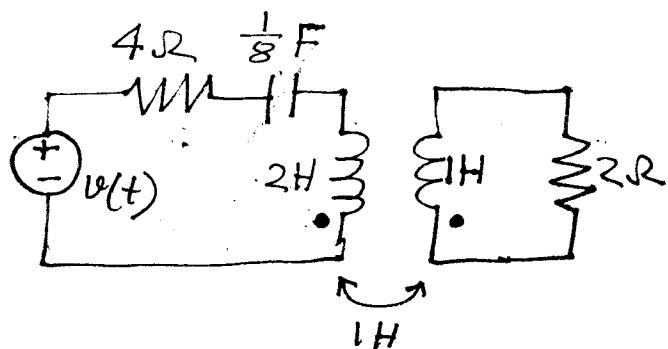

$$v(t) = 20 \cos(2t) \text{ V.}$$

Determine the coupling coefficient and the energy stored in the coupled inductors at $t = 1.55$.

(7)

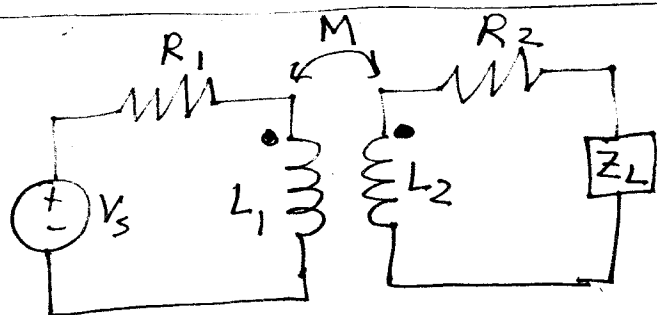

$$R_1 = 3\Omega, R_2 = 6\Omega,$$

$$L_1 = 2\text{ mH}, L_2 = 10\text{ mH}$$

$$M = 4\text{ mH}. \text{ If } \omega = 5000 \text{ rad/s, Find}$$


Z_{in} (input impedance)

as seen from the primary side) for Z_L

equal to (a) 10Ω (b) $j20\Omega$ (c) $10 + j20\Omega$

(d) $-j20\Omega$


(8)

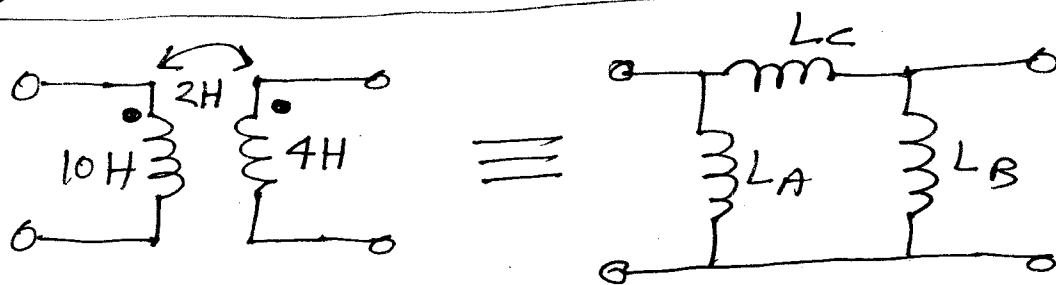

For the transformer shown on the left find the parameters of its π equivalent circuit (shown on the right), i.e. find L_A , L_B & L_C .

(9) Solve the problem in question 1, using the T equivalent of the coupled inductors.


(10)

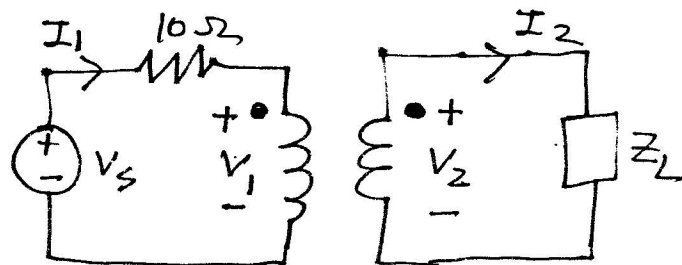

Let $N_1 = 1000$ turns
 $N_2 = 5000$ turns. in the
 ideal transformer
 shown in the figure.

If $Z_L = 500 - j400 \Omega$ find the average power
 delivered to Z_L for (a) $I_2 = 1.4 \angle 20^\circ \text{ A rms}$
 (b) $V_2 = 900 \angle 40^\circ \text{ V rms}$ (c) $V_1 = 80 \angle 100^\circ \text{ V rms}$ (d) $I_1 =$
 $6 \angle 45^\circ \text{ A rms}$ (e) $V_s = 200 \angle 0^\circ \text{ V rms}$.

(11)

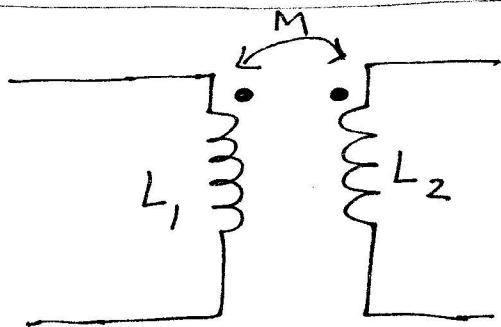

$$L_1 = 3 \text{ H}$$

$$L_2 = 12 \text{ H}$$

$$M = 5 \text{ H}$$

number of primary turns = 1000

number of secondary turns = 4000

primary coil resistance = 1Ω


secondary coil resistance = 4Ω

Draw the equivalent circuit of the transformer

(a) referring to primary side

(b) referring to the secondary side

(12)

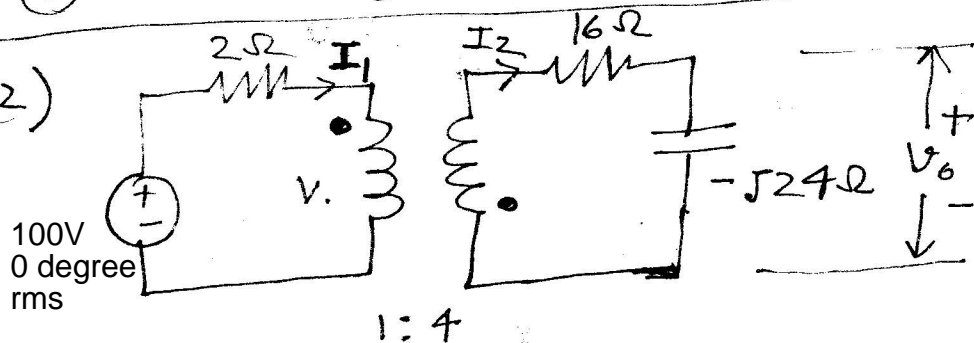

Find V_o .
 Calculate the
 complex power
 supplied by the
 source.

Assume the transformer to be ideal.