

**DEPARTMENT OF ELECTRICAL ENGINEERING**  
**EE 19001 FIRST YEAR E.T. LAB**  
**Experiment No. – 5**


**SINGLE PHASE TRANSFORMER**

**OBJECT:**

To determine the efficiency and regulation of a single phase transformer by conducting:

- (a) Open Circuit test;
- (b) Short Circuit test;

**(a) OPEN CIRCUIT TEST:**

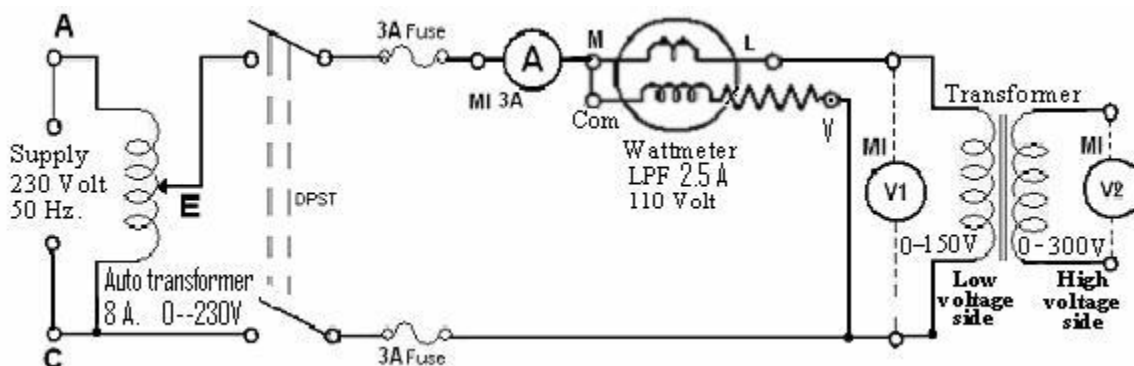

**Fig. 1 Circuit diagram for Open Circuit test of a transformer**

**INDIVIDUALLY** note the **complete** name-plate data/information of the motor/transformer that is/are required for the experiment and **obtain the signature of the teacher before the start of the experiment**. It must also be confirmed that the fuse/meter ratings being used are suitable.

**PROCEDURE:**

- i) Note the transformer ratings;
- ii) Connect the circuit as shown in Fig- 1 choosing suitable instruments;
- iii) Note: supply is connected to the Low-Voltage side of the transformer-under-test;
- iv) Set the autotransformer output to zero. Switch on the supply. Increase the voltage, in steps, up to rated voltage of the LV side and tabulate in Table no. 1 the no load current, (Primary Current,  $I_1$ ), input power,  $P_1$  and the primary & secondary voltages,  $V_1$  and  $V_2$ , corresponding to each value of the applied voltage.

**Table no. 1      Open Circuit test**

Sl. No.	Primary Voltage $V_1$ L. V. side (V)	Primary Current $I_1$ (I)	Input Power $P_1$ (W)	Secondary Voltage $V_2$ H. V. side (V)

## (b) SHORT CIRCUIT TEST:

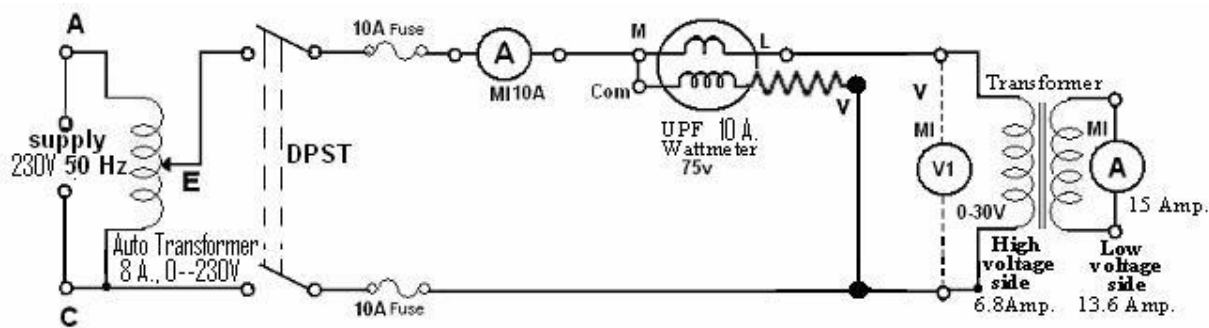


Fig. 2 Circuit diagram for Short Circuit test of a transformer

### PROCEDURE:

- Connect the circuit as shown in Fig- 2, choosing instruments of ranges suitable to go up to the rated current.
- Set the autotransformer output to zero. Switch on the supply. Increase the voltage, in steps, **slowly**, and observe the primary and secondary currents. (Note: The current flowing through the any of the windings must not exceed their rated levels.)
- Adjust the output voltage of the autotransformer to get secondary short circuit current of 25%, 50%, 75% and 100% of the rated current of the LV side. Note down in Table no. 2 the value of the input voltage,  $V_1$ , primary current (HV side)  $I_1$ , input power,  $P_1$  and the secondary current,  $I_2$  (LV side).

Table no. 2 Short Circuit test

Sl. No.	Primary Voltage $V_1$ H. V. side (v)	Primary Current $I_1$ (I)	Input Power $P_1$ (w)	Secondary Current $I_2$ L. V. side

## **RESULTS:**

### **From the observations of the open circuit test:**

- i) Plot no load current (refer to L.V side) and power input Vs applied voltage on a graph paper.
- ii) Calculate the parallel branch parameters of the equivalent circuit of the transformer referred to L.V side.

### **From the observations of the short circuit test:**

- iii) Calculate the equivalent circuit series parameters of the transformer with respect to **H.V.** side.

### **Finally determine the following:**

- i) Complete equivalent circuits of the transformer referred to both H.V. & L.V. side.
- ii) Efficiency of the Transformer at 25%, 50%, 75%, & 100% of the full load current at unity p.f.
- iii) Full load regulation at power factor of (a) 1.0 (b) 0.8 lagging and (c) 0.8 leading.
- iv) A graph showing efficiency at unity p.f. against load current at rated voltage.
- v) The maximum efficiency at the load (at unity p.f.) at which the maximum efficiency has occurred from the graph.

## **Discussion:**

- 1). Why is OC test carried out by energising LV side?
- 2). Why is SC test carried by energising side?
- 3). When is the efficiency maximum for a transformer?
- 4). Why does no-load losses arise in a transformer?

## **References:**

*HUGHES: Electrical Technology.*

*NAGARTH & KOTHARI: Electrical Machines.*

*M.G.Say: AC Machine.*

*A.S.Langsdorf: Theory of Alternating Current Machinery.*