

Module 3: Design of Synchronous Sequential Circuits

Assignment 7 Date: 18.03.2019

8. a. Design a circuit that will take a serial bit stream as input in synchronism with a clock, and will output a 1 whenever the pattern (possibly overlapping) 1001 is encountered.
- b. Design a modulo-10 synchronous binary counter using JK flip-flops.