
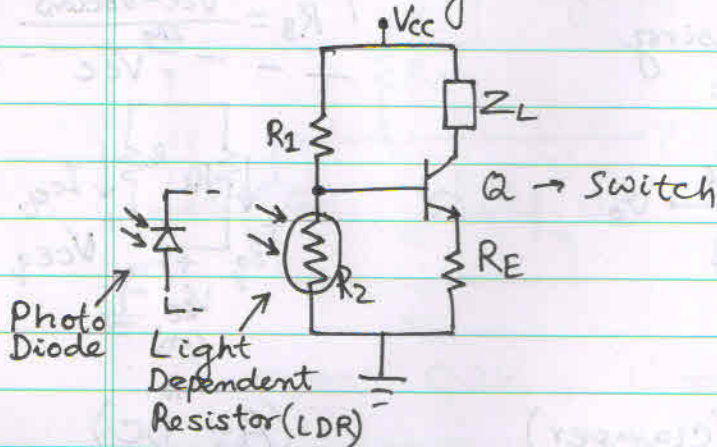


14. BJT as a Light controlled switch

→ Digital

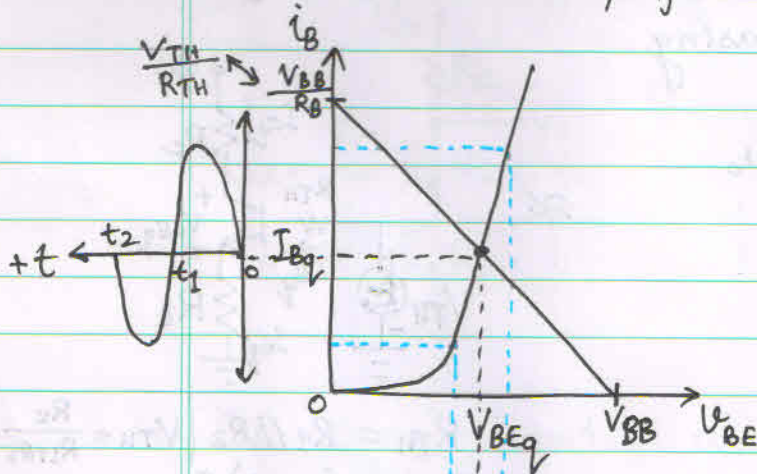


15. BJT as an amplifier: CE config.



$$i_B = \frac{I_S}{B} \cdot e^{\left(\frac{V_{BE}}{V_T}\right)}$$


$$= \frac{I_{BQ}}{V_T} \cdot V_{BE}$$

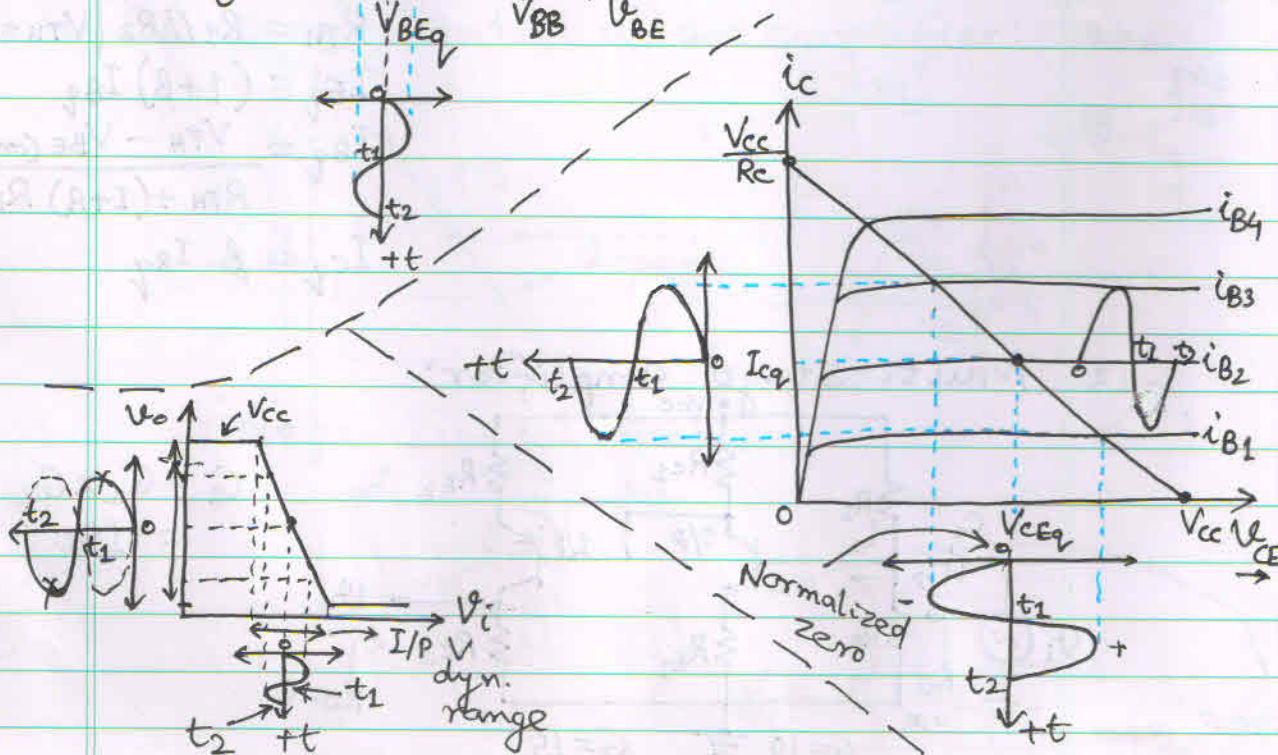

npn
BC548 / BC549

CE amp.

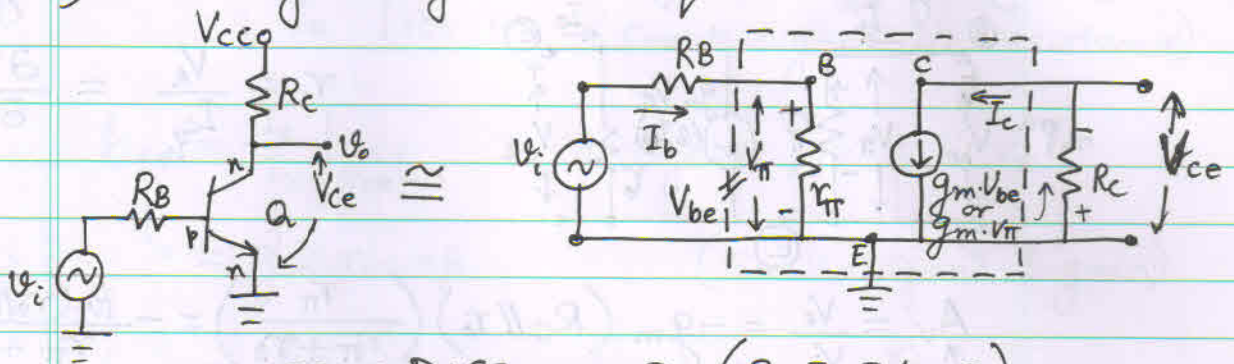16. a) Small signal hybrid- π equivalent circuit: AC + DC



$r_{\pi} \Rightarrow$ Diffusion R (B-E I/P R)

$g_m \Rightarrow$ Transconductance

$V_{\pi} \Rightarrow$ V across B-E junction.

$$r_{\pi} = \frac{V_{be}}{i_b} = \frac{V_T}{I_{BQ}} = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{\beta}{g_m}$$

$$V_{\pi} = \left(\frac{r_{\pi}}{r_{\pi} + R_B} \right) V_i$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$V_o = V_{ce} = -[g_m \cdot V_{\pi}] \cdot R_c$$

$$\text{Gain} \rightarrow A_v = \frac{V_o}{V_i} = -(g_m \cdot R_c) \cdot \left(\frac{r_{\pi}}{r_{\pi} + R_B} \right)$$

↑
V-gain of an amplifier (BJT in CE config.)
(Small-signal)


$$i_b = \frac{V_i}{r_{\pi} + R_B} ; i_c = \beta \cdot i_b = I_s \cdot e^{\left(\frac{V_{BE}}{V_T} \right)}$$

$$V_{ce} = -i_c \cdot R_c$$

↓
 V_o

Time Varying characteristics

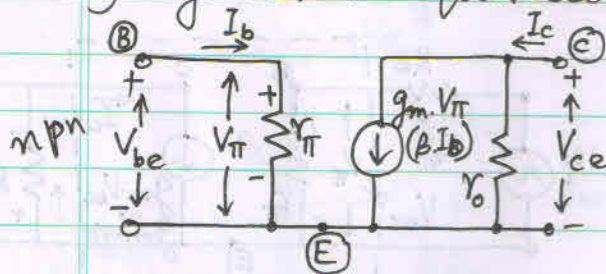b) Hybrid- π equivalent circuit with Early Effect:





$$r_o = \frac{V_A}{I_{CQ}} = \left. \frac{\partial V_{CE}}{\partial I_C} \right|_{Q\text{-pt}}$$

$$A_V = \frac{V_o}{V_i} = -g_m (R_C \parallel r_o) \left(\frac{r_{\pi}}{r_{\pi} + r_B} \right) = -\frac{\beta \cdot (r_o \parallel R_C)}{r_{\pi} + R_B}$$

V-Gain

$$V_o = g_m \cdot V_{\pi} (r_o \parallel R_C)$$

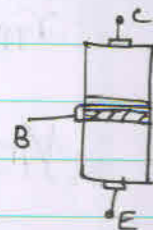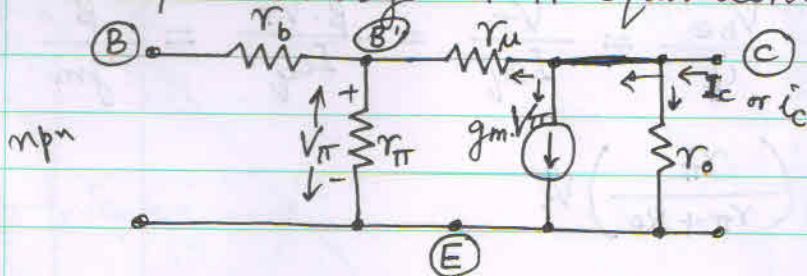c) Expanded hybrid- π equivalent circuit:



r_b : Series resistance in 'Base' region of S-C (10s Ω)
 $r_b \ll r_{\pi}$ $r_b \approx 0$ at low frequencies.


r_{μ} : Reverse-biased diffusion resistance (C-B juncⁿ)
 (M Ω normally).

Feedback is realized. $\rightarrow I_b \rightarrow f(V_{ce})$
 (O/P \rightarrow I/P) \rightarrow 'f/b' in short $\rightarrow f(i_c)$

17. h-parameters:

$$V_{be} = h_{ie} I_b + h_{re} V_{ce}$$

$$I_c = h_{fe} I_b + h_{oe} V_{ce}$$

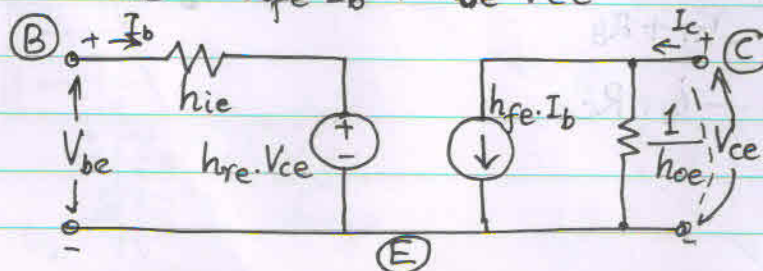

$$h_{ie} = \left. \frac{V_{be}}{I_b} \right|_{V_{ce}=0} = r_b + (r_{\pi} \parallel r_{\mu}) \quad ; \quad h_{ie} \approx r_{\pi}$$

(Small-signal I/P resistance)

$$h_{fe} = \left. \frac{I_c}{I_b} \right|_{V_{ce}=0} \quad ; \quad I_c = g_m \cdot V_{\pi} \quad ; \quad V_{\pi} = I_b \cdot r_{\pi}$$

$$\rightarrow = g_m \cdot r_{\pi} = \beta \quad (\text{Small-signal I-gain})$$

$$h_{re} = \left. \frac{V_{be}}{V_{ce}} \right|_{I_b=0} \quad ; \quad V_{be} = V_{\pi} = \frac{r_{\pi}}{r_{\pi} + r_{\mu}} \cdot V_{ce}$$

$$\rightarrow = \frac{r_{\pi}}{r_{\pi} + r_{\mu}} \approx \frac{r_{\pi}}{r_{\mu}} \quad ; \quad \because r_{\pi} \ll r_{\mu}$$

(Voltage f/b ratio)

$$h_{oe} = \left. \frac{I_c}{V_{ce}} \right|_{I_b=0} \quad ; \quad I_c = g_m \cdot V_{\pi} + \frac{V_{ce}}{r_o} + \frac{V_{ce}}{r_{\pi} + r_{\mu}}$$

$$\rightarrow = \frac{1+\beta}{r_{\mu}} + \frac{1}{r_o}$$

(Small-signal O/P admittance)

$\hookrightarrow \frac{1}{Z}$

18. T-model

