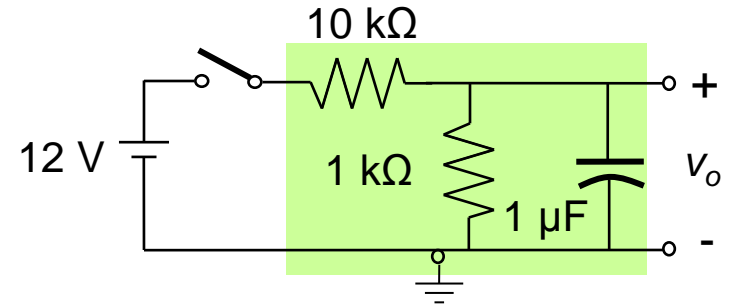


Tutorial - 1

Q1. (i) What type of filter is it? Calculate the cutoff frequency of the filter.

(ii) The switch is closed at $t = 0$, calculate the output voltage at $t = 0$ and at $t = 10$ mS.



(i) Lowpass filter.

Cutoff frequency = 175.1 Hz.


(ii) At $t = 0$, the capacitor is shorted.

$\rightarrow V_o = 0$ V.

Now, time constant = $R_{eq} \times C = 0.909$ mS.

$\rightarrow t \geq 5\tau$


$\rightarrow V_o = 1.09$ V.

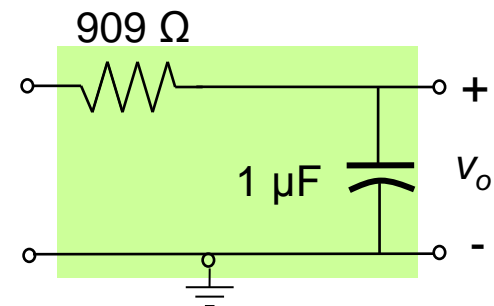

- Calculate the time constant of the following circuit.

The output is open-circuited.

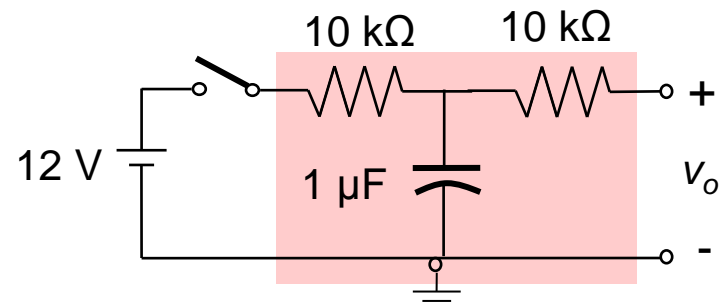
\rightarrow time constant = $R \times C = 10$ mS.




Questions

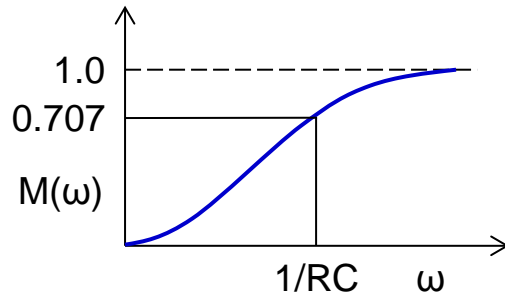Q2. A Series RC circuit is excited by a voltage source of variable frequency. The output is taken across the R . Sketch the variation of the steady state transfer function with angular frequency ω .

Hints: Obtain $H(j\omega)$ and represent in magnitude and phase form.




Magnitude response

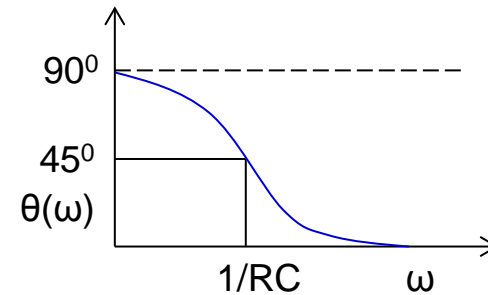

Phase response

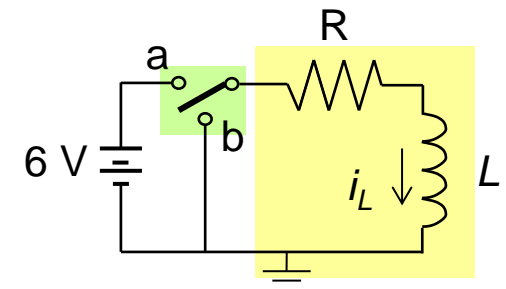Q3. Initially the switch is connected to a and the circuit is in steady state. The switch is moved from a to b at $t = 0$. Find the current in the inductor. What is the power dissipated in R at $t = 0$ and $t = \infty$?


Answer: $i = -6/R e^{-Rt/L}$ A, $t \geq 0$ $P_R = 36/R$ W,
 $= 6/R$ A, $t < 0$ $= 0$ W.



Tutorial - 1

Q4. In the circuit, the capacitors are fully charged at $t = 0_-$ so that $v_i = 12 \text{ V}$ ($C = 47 \text{ } \mu\text{F}$, and $R = 1 \text{ k}\Omega$).

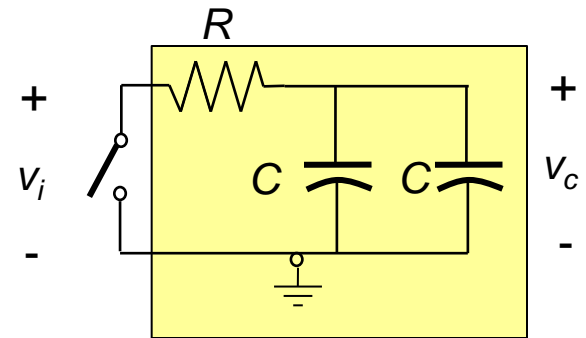- (i) The switch is closed at $t = 0$, calculate the time when $v_c = 6 \text{ V}$.
- (ii) Calculate the minimum power rating of the resistor.



(i) $C_{eq} = 94 \text{ } \mu\text{F}$.

$$v_c = V_o e^{-t/RC_{eq}}$$

$$\Rightarrow \ln \frac{v_c}{V_o} = -t/RC_{eq}$$

$$\Rightarrow t = 65.2 \text{ mS}.$$


(ii). Power rating $= (i_{peak})^2 R$

$$= \left(\frac{12}{1k} \right)^2 1k$$

$$= 144 \text{ mW}.$$

Tutorial - 1

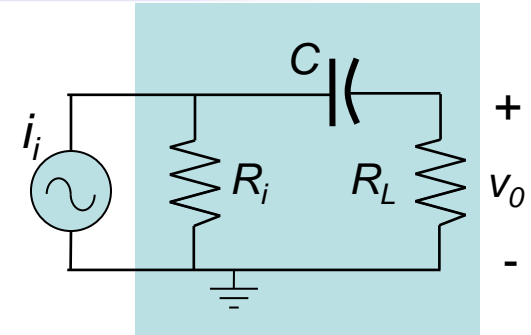Q5. In the following circuit, a current source $i_i = \sin(2\pi ft)$ mA with internal resistance $R_i = 10 \text{ k}\Omega$ is connected to a RC circuit. Calculate the output voltages (magnitudes) at $f = 10 \text{ kHz}$ and 100 kHz . Given that $C = 2.2 \text{ nF}$, and $R_L = 10 \text{ k}\Omega$.



Transform the current source into a voltage source v_i .

$$\therefore v_i = i_i R_i = 10 \sin(2\pi ft) \text{ V.}$$

$$\text{Now, } \left| \frac{v_{R_L}}{v_i} \right| = \frac{\omega C R_L}{\sqrt{1 + \omega^2 C^2 (R_i + R_L)^2}}$$


$$\therefore \text{at } 10 \text{ kHz, } \omega C R_L = 1.382, \quad \omega^2 C^2 (R_i + R_L)^2 = 7.643 \quad \Rightarrow \left| \frac{v_{R_L}}{v_i} \right| = 0.47$$

$$\therefore v_{R_L} \Big|_{10 \text{ kHz}} = 4.7 \sin(20 \times 10^3 \pi t) \text{ V.}$$

$$\therefore \text{at } 100 \text{ kHz, } \left| \frac{v_{R_L}}{v_i} \right| = \frac{13.82}{\sqrt{1 + 764.3}} = 0.4996 \quad \Rightarrow v_{R_L} \Big|_{100 \text{ kHz}} = 5 \sin(20 \times 10^4 \pi t) \text{ V.}$$

Tutorial - 1

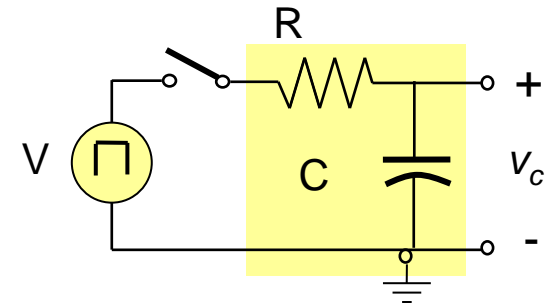Q6. In the following circuit, a pulse of height V and width a is applied at $t = 0$. Find an expression for the current.



$$\therefore v_{in}(t) = V[U(t) - U(t-a)].$$

$$\text{Now, applying KVL, } v_c(0_-) + \frac{1}{C} \int_{0_-}^t i \, dt + Ri = V[U(t) - U(t-a)]$$

\therefore Taking Laplace transform,

$$\frac{v_c(0_-)}{s} + \frac{I(s)}{Cs} + RI(s) = \frac{V}{s} [1 - e^{-as}]$$

$$\text{Assuming } v_c(0_-) = 0, I(s) = VC \frac{1 - e^{-as}}{1 + CRs} = \frac{V}{R} \left[\frac{1}{s + 1/CR} - \frac{e^{-as}}{s + 1/CR} \right]$$

\therefore Taking inverse Laplace transform,

$$i(t) = \frac{V}{R} \left[e^{-t/CR} U(t) - e^{-(t-a)/CR} U(t-a) \right].$$

Tutorial - 1

Q7. In the following circuit, charge on the capacitor is zero for $t < 0$. $R_1 = 10 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_3 = 1 \text{ k}\Omega$, $C = 10 \text{ }\mu\text{F}$.

- (i) At $t = 0 \text{ Sec}$, the switch is closed. Find I_1 and I_2 at $t = 0$ and at $t = 1 \text{ Sec}$.
(ii) The switch is reopened at $t = 2 \text{ Sec}$. Find I_1 and I_2 at $t = 2 \text{ Sec}$.

Answer:

(i) At $t = 0$, the capacitor is shorted.

$$\therefore I_1(0) = 9 / (R_1 + R_2 \parallel R_3) = 0.825 \text{ mA. and}$$


$$I_2(0) = R_3 \times 0.825 / (R_2 + R_3) = 0.075 \text{ mA.}$$

$\tau = R_{eq} C = 60 \text{ mS} \ll 1 \text{ Sec} \Rightarrow$ the capacitor is fully charged.

$$\therefore I_1(1 \text{ Sec}) = I_2(1 \text{ Sec}) = 9 / (R_1 + R_2) = 0.45 \text{ mA.}$$

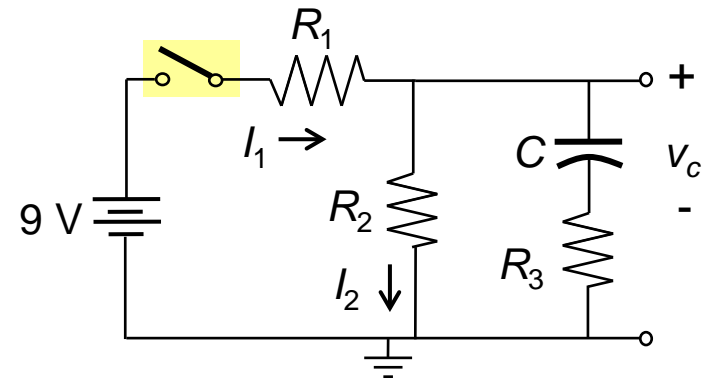(ii) At $t = 2 \text{ Sec}$, left-hand part is open.

$$\therefore I_1(2 \text{ Sec}) = 0 \text{ and } I_2(2 \text{ Sec}) = 4.5 / (R_2 + R_3) = 0.409 \text{ mA.}$$



Tutorial - 1

Q8. The circuit is in steady state. The switch is closed at $t = 0$. Find an expression for the v_c .

$$\therefore v_c(0_-) = \frac{2}{3}V.$$

But, for $t > 0$, looking from the capacitor terminal, the Thevenin's voltage = $\frac{V}{2}$.



Now, applying KVL,
$$\frac{R}{2}i + v_c(0_-) + \frac{1}{C} \int_{0_-}^t i dt = \frac{V}{2}$$

Taking Laplace transform,

$$\frac{R}{2}I(s) + \frac{v_c(0_-)}{s} + \frac{I(s)}{Cs} = \frac{V}{2s},$$

$$\Rightarrow \frac{R}{2}I(s) + \frac{2V}{3s} + \frac{I(s)}{Cs} = \frac{V}{2s},$$
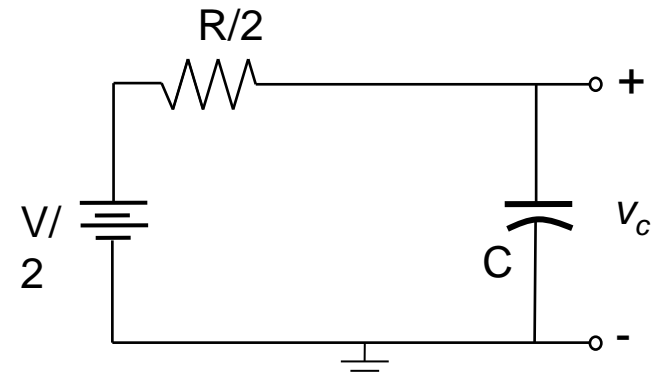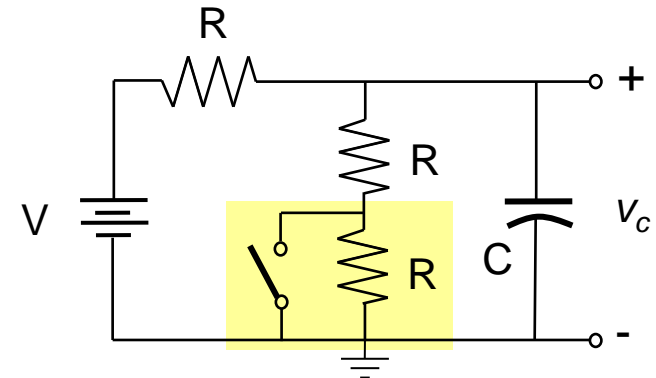
$$\Rightarrow I(s) = -\frac{V/(3R)}{s + 2/(CR)}.$$



Equivalent circuit for $t > 0$.

Tutorial - 1

∴ Capacitor voltage for $t > 0$,

$$V_c(s) = \frac{v_c(0_-)}{s} + \frac{I(s)}{Cs} = \frac{2V}{3s} - \frac{V/(3RC)}{s[s + 2/(CR)]},$$

$$= \frac{(2/3)V s + V/(RC)}{s[s + 2/(CR)]} = \frac{A}{s} + \frac{B}{s + 2/(CR)}.$$

Now, expanding into partial fractions,


$$A = \left. \frac{(2/3)V s + V/(RC)}{[s + 2/(CR)]} \right|_{s=0} = \frac{V}{2}$$

$$B = \left. \frac{(2/3)V s + V/(RC)}{s} \right|_{s=-2/CR} = \frac{V}{6}.$$

$$\therefore V_c(s) = \frac{V}{2s} + \frac{V}{6[s + 2/(CR)]}.$$

∴ Taking inverse Laplace transform,
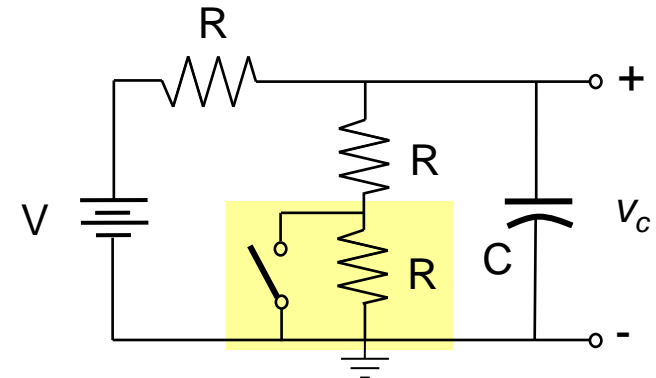
$$v_c(t) = \frac{V}{2} + \frac{V}{6} e^{-2t/CR}, \quad (\text{for } t > 0).$$



Tutorial - 1

∴ Capacitor voltage for $t > 0$,

$$V_c(s) = \frac{v_c(0_-)}{s} + \frac{I(s)}{Cs} = \frac{2V}{3s} - \frac{V/(3RC)}{s[s + 2/(CR)]},$$

$$= \frac{(2/3)V s + V/(RC)}{s[s + 2/(CR)]} = \frac{A}{s} + \frac{B}{s + 2/(CR)}.$$

Now, expanding into partial fractions,

$$A = \left. \frac{(2/3)V s + V/(RC)}{[s + 2/(CR)]} \right|_{s=0} = \frac{V}{2}$$

$$B = \left. \frac{(2/3)V s + V/(RC)}{s} \right|_{s=-2/CR} = \frac{V}{6}.$$

$$\therefore V_c(s) = \frac{V}{2s} + \frac{V}{6[s + 2/(CR)]}.$$

∴ Taking inverse Laplace transform,

$$v_c(t) = \frac{V}{2} + \frac{V}{6} e^{-2t/CR}, \quad (\text{for } t > 0).$$

