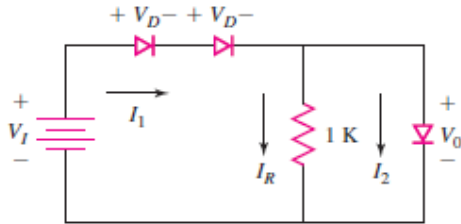


TUTORIAL QUESTIONS AND SOLUTIONS (Introduction to Electronics):

1. If reverse saturation current of the diodes shown below is $2 \times 10^{-13} \text{ A}$ and output is 0.6V DC, find the input voltage.



$$I_S = 2 \times 10^{-13} \text{ A}$$

$$V_0 = 0.60 \text{ V}$$

$$I_2 = I_S \exp\left(\frac{V_0}{V_T}\right) = (2 \times 10^{-13}) \exp\left(\frac{0.60}{0.026}\right)$$

$$= 2.105 \text{ mA}$$

$$I_R = \frac{0.6}{1 \text{ K}} = 0.60 \text{ mA}$$

$$I_1 = I_2 + I_R = 2.705 \text{ mA}$$

$$V_D = V_T \ln\left(\frac{I_1}{I_S}\right) = (0.026) \ln\left(\frac{2.705 \times 10^{-3}}{2 \times 10^{-13}}\right)$$

$$= 0.6065$$

$$V_I = 2V_D + V_0 \Rightarrow \underline{V_I = 1.81 \text{ V}}$$

2. Consider a Si diode is applied with a forward bias voltage 0.6V. Determine the ratio of diode current at 100°C and 55°C .

$$\frac{I_S(T)}{I_S(-55)} = 2^{\Delta T/5}, \quad \Delta T = 155^\circ \text{ C}$$

$$\frac{I_S(100)}{I_S(-55)} = 2^{155/5} = 2.147 \times 10^9$$

$$V_T @ 100^\circ\text{C} \Rightarrow 373^\circ\text{K} \Rightarrow V_T = 0.03220$$

$$V_T @ -55^\circ\text{C} \Rightarrow 216^\circ\text{K} \Rightarrow V_T = 0.01865$$

$$\frac{I_D(100)}{I_D(-55)} = (2.147 \times 10^9) \times \frac{\exp\left(\frac{0.6}{0.0322}\right)}{\exp\left(\frac{0.6}{0.01865}\right)}$$

$$= \frac{(2.147 \times 10^9)(1.237 \times 10^8)}{(9.374 \times 10^{13})}$$

$$\underline{\frac{I_D(100)}{I_D(-55)} = 2.83 \times 10^3}$$

3. Consider a Si P-N diode with $N_a = 10^{18} \text{ cm}^{-3}$, $N_d = 10^{15} \text{ cm}^{-3}$ and $C_{j0} = 0.25 \text{ pF}$. If a 2.2 mH inductor is connected in parallel with the PN diode, calculate the resonant frequency f_0 for reverse biased voltages of 1 V and 10 V .

$$V_{bi} = (0.026) \ln\left[\frac{(10^{18})(10^{15})}{(1.5 \times 10^{10})^2}\right] = 0.757 \text{ V}$$

$$\text{a. } V_R = 1 \text{ V}$$

$$C_j = (0.25) \left(1 + \frac{1}{0.757}\right)^{-1/2} = 0.164 \text{ pF}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(2.2 \times 10^{-3})(0.164 \times 10^{-12})}}$$

$$\underline{f_0 = 8.38 \text{ MHz}}$$

b. $V_R = 10 \text{ V}$

$$C_j = (0.25) \left(1 + \frac{10}{0.757} \right)^{-1/2} = 0.0663 \text{ pF}$$

$$f_0 = \frac{1}{2\pi\sqrt{(2.2 \times 10^{-3})(0.0663 \times 10^{-12})}}$$

$$\underline{f_0 = 13.2 \text{ MHz}}$$

4. Hole concentration is expressed as: $p(x) = 10^4 + 10^{15} e^{(-x/L_p)}$, for $x \geq 0$, for a Si slab. If, $D_p = 15 \text{ cm}^2/\text{s}$ and $L_p = 10 \text{ }\mu\text{m}$, find hole diffusion current density at $x = 0, 10 \text{ }\mu\text{m}$ and $30 \text{ }\mu\text{m}$.

$$\begin{aligned} J_p &= -eD_p \frac{dp}{dx} \\ &= -eD_p (10^{15}) \left(\frac{-1}{L_p} \right) \exp \left(\frac{-x}{L_p} \right) \\ J_p &= \frac{(1.6 \times 10^{-19})(15)(10^{15})}{10 \times 10^{-4}} \exp \left(\frac{-x}{L_p} \right) \end{aligned}$$

$$J_p = 2.4 e^{-x/L_p}$$

(a) $x = 0 \quad J_p = 2.4 \text{ A/cm}^2$

(b) $x = 10 \text{ }\mu\text{m} \quad J_p = 2.4 e^{-1} = 0.883 \text{ A/cm}^2$

(c) $x = 30 \text{ }\mu\text{m} \quad J_p = 2.4 e^{-3} = 0.119 \text{ A/cm}^2$

5. Calculate the concentrations of electrons and holes in silicon and germanium if the concentration of acceptor atoms is 10^{16} cm^{-3} . Also, determine the type of semiconductor.

a. $N_a = 10^{16} \text{ cm}^{-3} \Rightarrow \underline{p\text{-type}}$

$$\underline{p_0 = N_a = 10^{16} \text{ cm}^{-3}}$$

$$n_0 = \frac{n_i^2}{p_0} = \frac{(1.5 \times 10^{10})^2}{10^{16}} \Rightarrow \underline{n_0 = 2.25 \times 10^4 \text{ cm}^{-3}}$$

b. **Germanium**

$N_a = 10^{16} \text{ cm}^{-3} \Rightarrow \underline{p\text{-type}}$

$$\underline{p_0 = N_a = 10^{16} \text{ cm}^{-3}}$$


$$n_i = (1.66 \times 10^{15})(300)^{3/2} \exp \left(\frac{-0.66}{2(86 \times 10^{-6})(300)} \right)$$

$$= (1.66 \times 10^{15})(300)^{3/2} (2.79 \times 10^{-6})$$

$$= 2.4 \times 10^{13} \text{ cm}^{-3}$$

$$n_0 = \frac{n_i^2}{p_0} = \frac{(2.4 \times 10^{13})^2}{10^{16}} \Rightarrow \underline{n_0 = 5.76 \times 10^{10} \text{ cm}^{-3}}$$

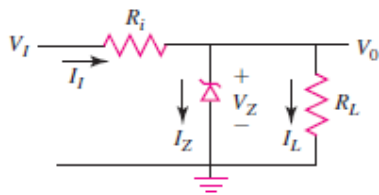6. In a zener regulator circuit, consider $V_i = 6.3 \text{ V}$, $R_i = 12 \text{ }\Omega$, $V_z = 4.8 \text{ V}$, $I_{z\min} = 5 \text{ mA}$, $I_{z\max} = 100 \text{ mA}$. Determine the ranges for load current and load resistance. Also find the power ratings of the regulator and the load.



a.

$$I_I = \frac{6.3 - 4.8}{12} \Rightarrow 125 \text{ mA}$$

$$I_L = I_I - I_Z = 125 - I_Z$$



$$25 \leq I_L \leq 120 \text{ mA} \Rightarrow 40 \leq R_L \leq 192 \Omega$$

b.

$$P_Z = I_Z V_Z = (100)(4.8) \Rightarrow P_Z = 480 \text{ mW}$$

$$P_I = I_I V_O = (120)(4.8) \Rightarrow P_I = 576 \text{ mW}$$

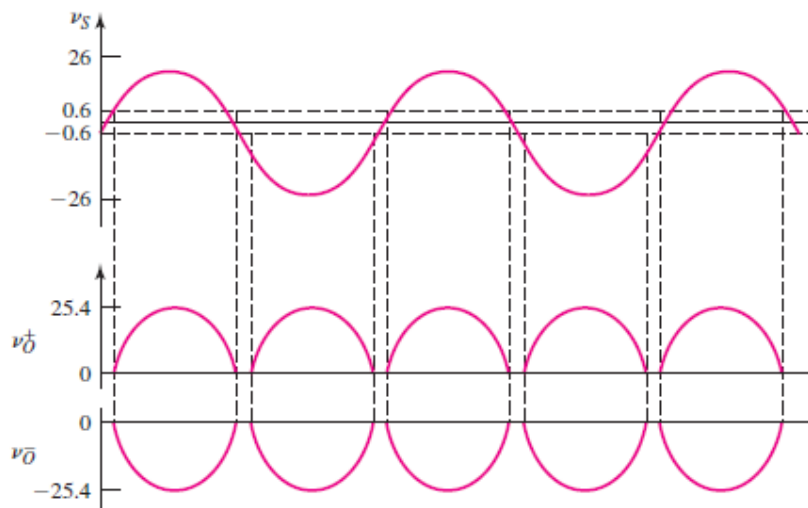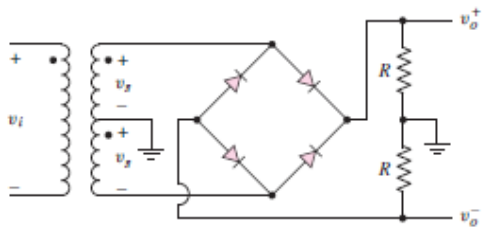7. <SOLVED Example 2.6 from Neamen book; pg. 84 or equivalent> Line (source) and load regulation for a zener diode based voltage regulator.
8. Draw the output waveforms of the following circuit if $v_s = 26 \sin(2\pi 60t)$ V.



9. Consider the figure below and draw the output waveforms if RC time constant is large and cut-in voltage of the diode is 0.

