

STUDIES ON LOGIC GATES:

AIM: To study logic gates

APPARATUS REQUIRED:

- Cathode Ray Oscilloscope
- Multimeter
- Connecting wires
- AC signal generator
- Printed circuit board
- DC power supply (5V)

THEORY:

Logic gates are elementary building blocks of digital circuits. They can be binary (takes in two inputs) or unary (only one input, eg: NOT gate). Input can be • Low • High.

These are available in TTL (Transistor-Transistor Logic) or CMOS (Complementary Metal-Oxide Silicon). TTL uses NPN and PNP BJTs and are utilised in this experiment for realising various logic gates.

A	B	AND $A \cdot B$	OR $A + B$	NAND $\overline{A \cdot B}$	NOR $\overline{A + B}$	XOR $A \cdot \overline{B} + \overline{A} \cdot B$	XNOR $\overline{A \cdot B} + A \cdot B$
0	0	0	0	1	1	0	1
0	1	0	1	1	0	1	0
1	0	0	1	1	0	1	0
1	1	1	1	0	0	0	1

Teacher's Signature : _____

I. LOGIC GATES USING ONLY NANDGATES :

All figures are in volts (V).

*) AND :

A		B		$Y = A \cdot B$	
0	0	0	0	0.16	0
0	0	4.93	1	0.17	0
4.93	1	0	0	0.17	0
4.93	1	4.93	1	3.12	1

*) OR :

A		B		$Y = A + B$	
0	0	0	0	0.18	0
0	0	4.93	1	3.23	1
4.93	1	0	0	3.23	1
4.93	1	4.93	1	3.12	1

*) NOT : (Unary)

A		$Y = \bar{A}$	
0	0	3.12	1
4.93	1	0.12	0

Teacher's Signature : _____

*) NOR gate :

A		B		$Y = \overline{A+B}$	
0	0	0	0	2.98	1
0	0	4.93	1	0.08	0
4.93	1	0	0	0.05	0
4.93	1	4.93	1	0.05	0

*) XOR gate :

A		B		$Y = \bar{A} \cdot B + A \cdot \bar{B}$	
0	0	0	0	0.08	0
0	0	4.90	1	2.96	1
4.90	1	0	0	2.98	1
4.90	1	4.90	1	0.08	0

XOR as controlled inverter :

1 KHz square waveform is applied to one of the inputs and the input is low (0V) or Invert. In this next table Invert input is kept high. Thus, the controlled inversion feature is realised.


i) Invert = Low :

A		B		Y	
0	0	0	0	0	0
1	1	0	0	0.84	1


ii) Invert = High :

A		B		Y	
0	0	4.93	1	0.82	1
1	1	4.93	1	0	0


Teacher's Signature : _____

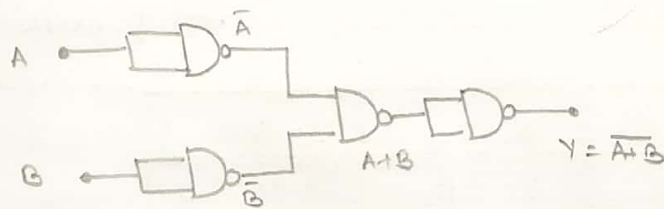

NAND gate

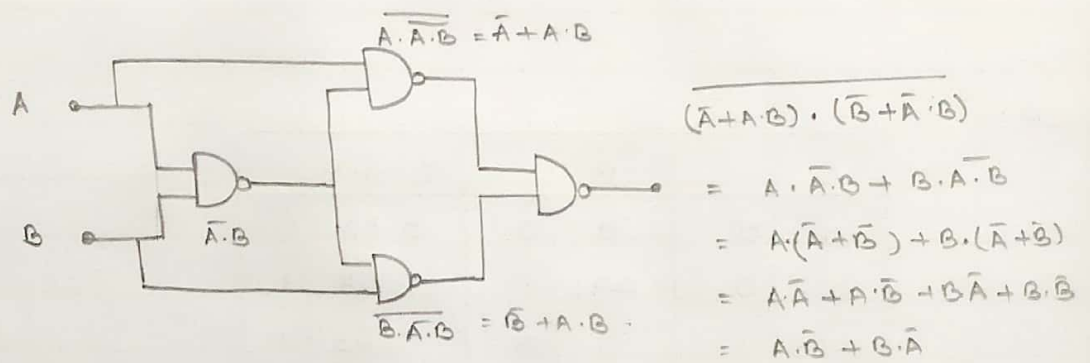

XOR gate

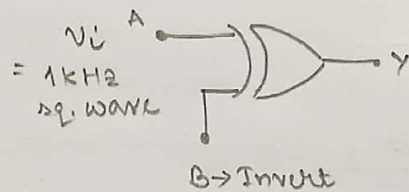

XOR as controlled inverter

Invert = low

TIP

O/P

Invert = high

TIP


O/P

II) Different logic gates using only NOR gates:


$f = 300\text{Hz}$

$V/\text{div} = 1\text{V}/\text{div}$


$T/\text{div} = 0.5\text{ms}/\text{div}$

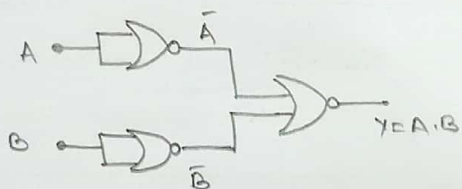


And gate

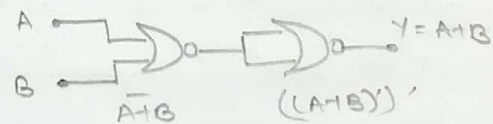

OR gate

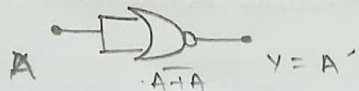

NOT gate

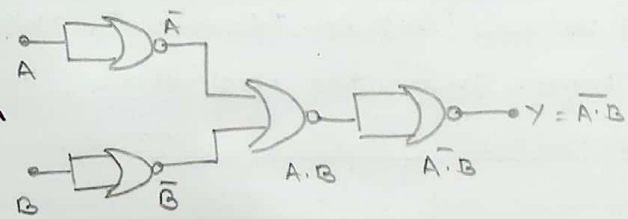

NAND gate



II) LOGIC GATES USING ONLY NOR GATES:

*) AND:

A		B		$Y = A \cdot B$	
0	0	0	0	0.16	0
0	0	4.93	1	0.17	0
4.93	1	0	0	0.17	0
4.93	1	4.94	1	3.13	1

*) OR:

A		B		$Y = A + B$	
0	0	0	0	0.19	0
0	0	4.93	1	2.93	1
4.93	1	0	0	2.93	1
4.93	1	4.93	1	2.88	1


*) NOT:

A		$Y = \bar{A}$	
0	0	2.93	1
4.93	1	0.17	0

*) NAND:

A		B		$Y = \overline{A \cdot B}$	
0	0	0	0	2.92	1
0	0	4.92	1	2.90	1
4.92	1	0	0	2.90	1
4.93	1	4.92	1	0.13	0

Teacher's Signature : _____

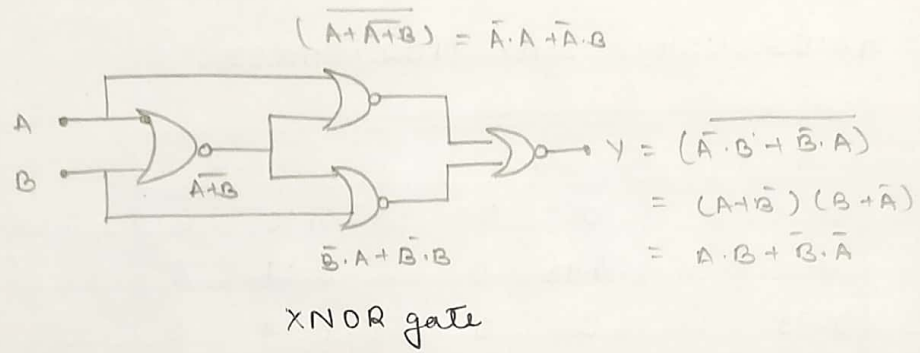


III. Verification of De-morgan's Theorem:

a)




$$F = (X + Y)'$$

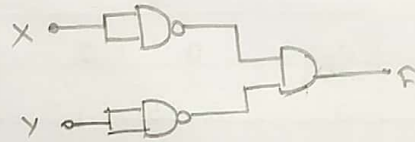


$$F = X' \cdot Y'$$

b)

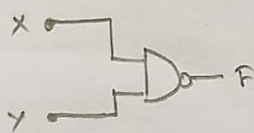

$$F = (X \cdot Y)'$$

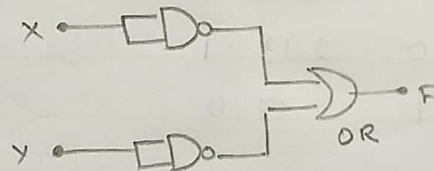

$$F = X' + Y'$$



*) XNOR :

A		B		$Y = A \cdot \bar{B} + \bar{A} \cdot B$	
0	0	0	0	2.98	1
0	0	4.93	0	0.16	0
4.92	1	0	0	0.16	0
4.92	1	4.92	1	2.89	1

III. VERIFICATION OF DE-MORGAN'S THEOREM :

a) $(X+Y)' = X' \cdot Y'$

$(X+Y)'$ is realised with IC7402 and $X' \cdot Y'$ using IC7400 and IC7408.

$F = (X+Y)'$						$F = X' \cdot Y'$					
X		Y		C1 $(X+Y)'$		X		Y		C2 $X' \cdot Y'$	
0	0	0	0	3.10	1	0	0	0	0	2.41	1
0	0	4.91	1	0.16	0	0	0	4.82	1	0.27	0
4.90	1	0	0	0.17	0	4.90	1	0	0	0.21	0
4.93	1	4.93	1	0.17	0	4.91	1	4.89	1	0.23	0

Thus, comparing C1 and C2, we conclude

$$(X+Y)' = X' \cdot Y'$$


$F = (X \cdot Y)'$						$F = X' + Y'$					
X		Y		C3 $(X \cdot Y)'$		X		Y		C4 $X' + Y'$	
0	0	0	0	2.73	1	0	0	0	0	2.41	1
0	0	4.89	1	2.86	1	0	0	4.71	1	2.83	1
4.85	1	0	0	2.85	1	4.70	1	0	0	2.83	0
4.92	1	4.93	1	0.16	0	4.70	1	4.70	1	0.21	0

Comparing C3 and C4, $(X \cdot Y)' = X' + Y'$


Teacher's Signature : _____

IV Verification of Theorems in Switching Algebra:


a)

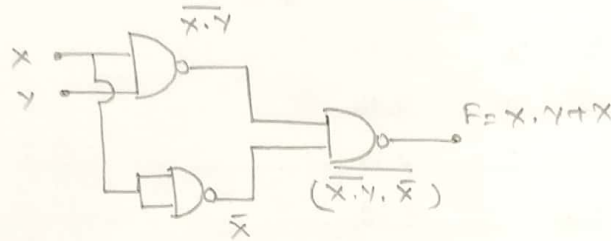

b)


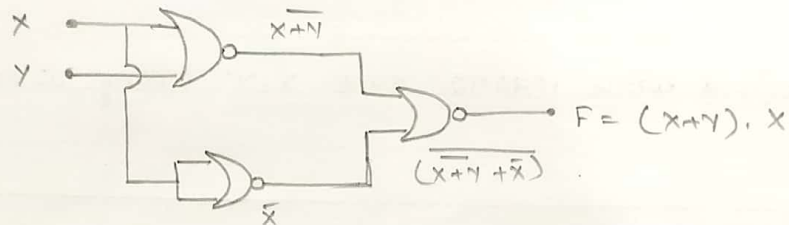


c)

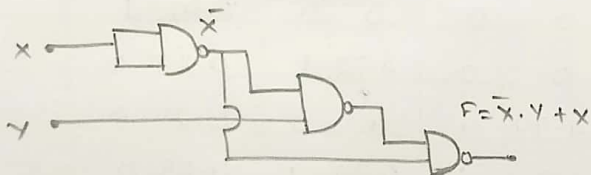

$$[(\bar{X}.Y).\bar{X}]$$
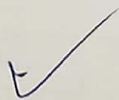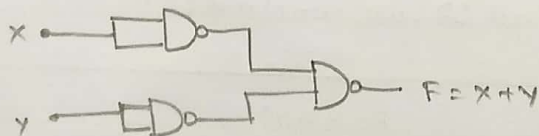
$$= \bar{X}.Y + X \quad (\text{De Morgan's law})$$



IV VERIFICATION OF THEOREMS IN SWITCHING ALGEBRA:

a) $F = X + X \cdot Y$ and $F = X$

X		Y		C ₁ $F = X + X \cdot Y$		C ₂ $F = X$	
0	0	0	0	0.26	0	0	0
0	0	4.89	1	0.35	0	0	0
4.89	1	0	0	3.87	1	4.88	1
4.89	1	4.88	1	3.89	1	4.88	1

Comparing C₁ and C₂, we conclude $X + X \cdot Y = X$.

b) $F = X \cdot (X + Y)$ and $F = X$

X		Y		C ₃ $F = (X + Y) \cdot X$		C ₄ $F = X$	
0	0	0	0	0.32	0	0	0
0	0	4.72	1	0.29	0	0	0
4.89	1	0	0	3.91	1	4.92	1
4.89	1	4.94	1	4.24	1	4.93	1

comparing C₃ and C₄ we conclude $X \cdot (X + Y) = X$.



c) $F = X + X' \cdot Y$ and $F = X + Y$

X		Y		C ₅ $F = X + X' \cdot Y$		C ₆ $F = X + Y$	
0	0	0	0	0.16	0	0.19	0
0	0	4.92	1	2.92	1	3.23	1
4.92	1	0	0	2.93	1	3.23	1
4.93	1	4.92	1	2.99	1	3.12	1

Comparing C₅ and C₆ we conclude $X + X' \cdot Y = X + Y$

Teacher's Signature : _____

d)

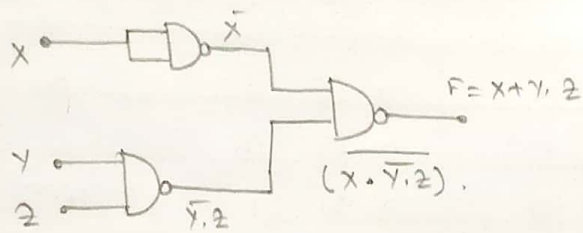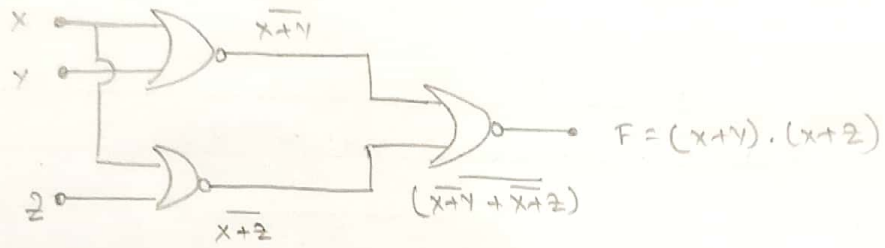

✓

Expt. No.

Page No.

d) $F = (x+y) \cdot (x+z)$ and $F = x+y \cdot z$

X		Y		Z		C1 $(x+y) \cdot (x+z)$	
0	0	0	0	0	0	0.45	0
0	0	0	0	4.92	1	0.20	0
0	0	4.93	1	0	0	0.25	0
0	0	4.94	1	4.92	1	3.39	1
4.94	1	0	0	0	0	3.12	1
4.93	1	0	0	4.93	1	3.32	1
4.94	1	4.92	1	0	0	3.01	1
4.94	1	4.92	1	4.92	1	3.02	1

X		Y		Z		C2 $x+y \cdot z$	
0	0	0	0	0	0	0.40	0
0	0	0	0	4.92	1	0.31	0
0	0	4.93	1	0	0	0.29	0
0	0	4.93	1	4.92	1	2.60	1
4.91	1	0	0	0	0	2.83	1
4.92	1	0	0	4.92	1	2.49	1
4.92	1	4.88	1	0	0	2.12	1
4.92	1	4.93	1	4.93	1	3.43	1

Comparing C1 and C2, we conclude that $(x+y) \cdot (x+z) = x+y \cdot z$.



Teacher's Signature : _____

DISCUSSION:

Different logic gates were realised and verified in the circuit board using NAND and NOR gates. Representative logic gate diagrams were drawn. Since all other gates can be realised using NOR and NAND gates, they are also called 'universal gates'.


Then we observed function of XOR gate as controlled inverter. We get non-inverted O/P if invert is kept low and inverted O/P if invert is kept high.

We verified De-morgan's Theorems and we state the generalised theorem:

$$(A_1 + A_2 + \dots + A_n)' = A_1' \cdot A_2' \cdot \dots \cdot A_n'$$

$$(A_1 \cdot A_2 \cdot \dots \cdot A_n)' = A_1' + A_2' + \dots + A_n'$$

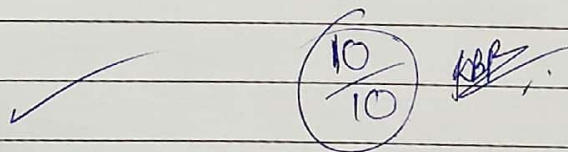Lastly, various Theorems in switching algebra were proved using logic gates.




Teacher's Signature : _____

Discussion :-

By Chelsi Rakeja
16CS10013

1. Logic Gates are building blocks of digital circuits made by transistor-transistor logic (TTL) or complementary metal-oxide silicon (CMOS).
2. NAND and NOR gates are known as universal gates because gates like OR, AND, XOR can be obtained by combination of several NAND gates and NOR gates. This was realised during the experiment.
3. XOR was observed and used to as controlled inverter. by using the input at B to be 0 as inversion disabled and 1 as inversion enabled.

4.

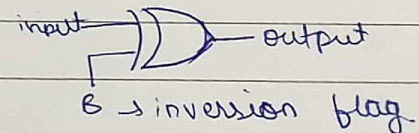

4. De Morgan's Theorem was verified using 7408 (AND), 7432 (OR), 7400 (NAND), 7402 (NOR). Inversion was done using NAND gate $x \rightarrow \square \rightarrow x'$

$$(A_1 + A_2 + A_3 + \dots + A_n)' = A_1' \cdot A_2' \cdot A_3' \cdot \dots \cdot A_n'$$

$$(A_1 \cdot A_2 \cdot \dots \cdot A_n)' = A_1' + A_2' + A_3' + \dots + A_n'$$

5. Verification of theorems in switching algebra was proved and it can be concluded that complicated circuit giving ~~same~~ output can be deduced to much simpler circuit with same output like one of the input can be derived from combination of that input with another one. It can be used to derive an input out of their combination.

Teacher's Signature : _____