
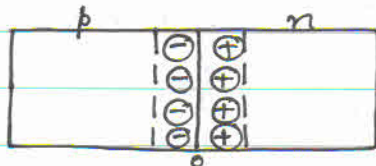
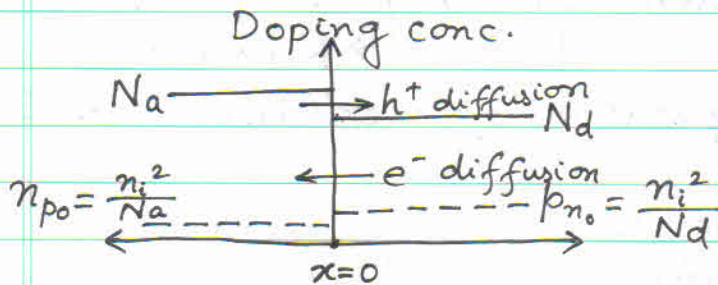
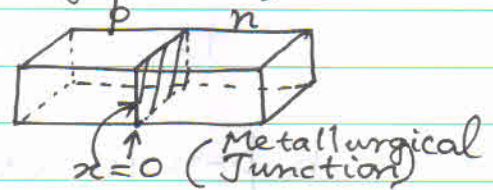
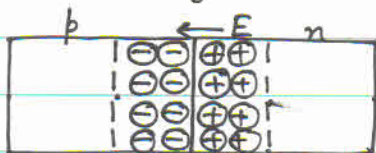


Diode (p-n junction)


a.  (Formation)



← a) Immediately after joining p & n



← b) Sometime later

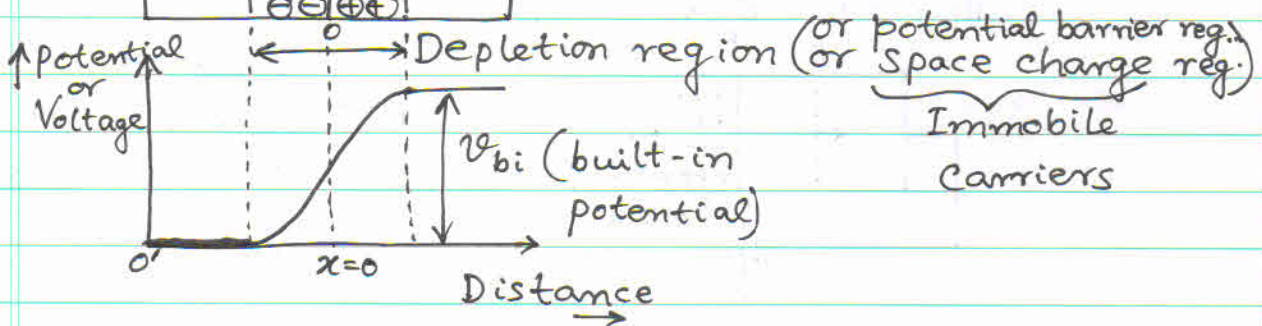

$$V_{bi} = \frac{kT}{e} \ln \left(\frac{N_a N_d}{n_i^2} \right) \quad ; \text{ where, } V_T = \frac{kT}{e}$$

Built-in potential forms due to the electric field around the junction without any external applied V.

Thermal voltage ($\sim 26\text{mV}$ @ 300°K)


Thermal equilibrium occurs while the force due to E-field & force due to density gradient equalizes.
(Transport of carriers due to drift \approx Transport due to diffusion)

$$V_{bi}(\text{Si}) \approx 0.7\text{V} \quad \& \quad V_{bi}(\text{Ge}) \approx 0.3\text{V}$$

b. p-n junction biasing $\begin{matrix} \rightarrow \text{Forward} \\ \downarrow \\ \rightarrow \text{Reverse} \end{matrix}$


Application of an external V or E-field.

i) Forward (FB) biasing:

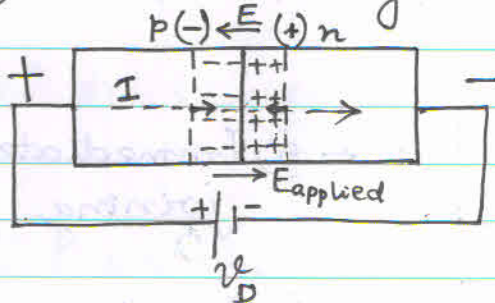

1. Depletion width reduces
2. FB junction allows passage of current.

ii) Reverse (RB) biasing:

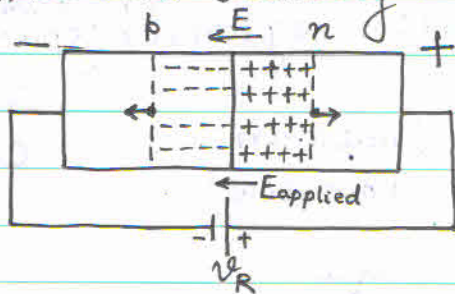

1. Depletion width increases
2. RB junction forms a capacitance
3. RB junction restricts/stops flow of current.

$$C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}}\right)^{-\frac{1}{2}}$$

Capacitance at zero voltage (applied)

c. Diode equation:

$$I_D = I_S \left[e^{\frac{V_D}{nV_T}} - 1 \right]$$


I_S : RB saturation I ($I_{S(\text{Si})} \approx 10^{-15}$ to 10^{-13})

n : Emission co-efficient (1 to 2)


V_T : Thermal voltage

V_D : Applied forward voltage across a diode.

d. Diode symbol:

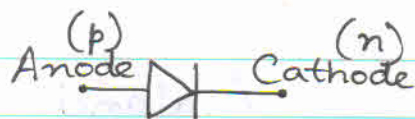


e. V-I characteristics:

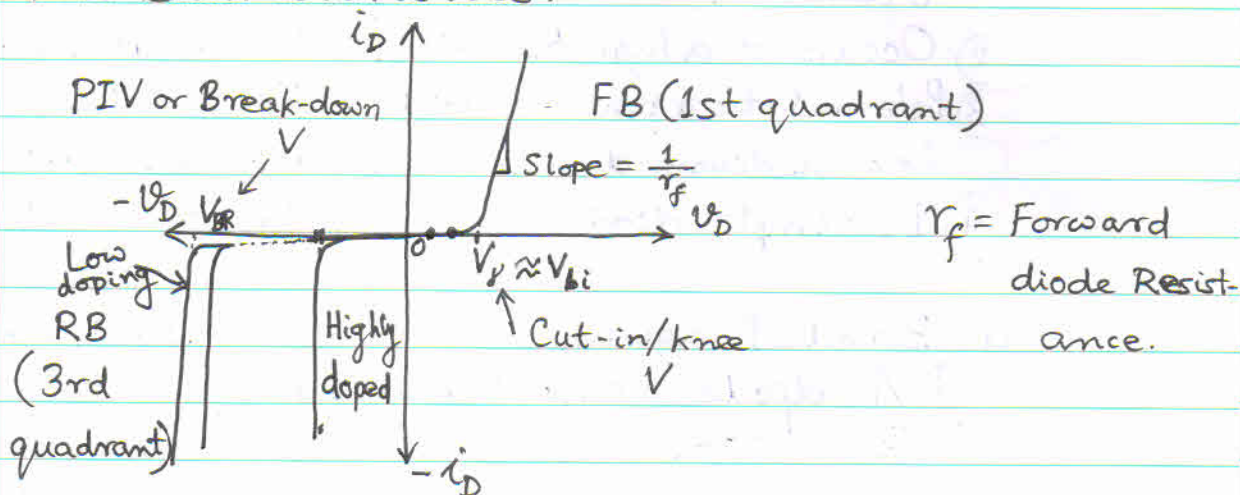

PIV: Peak Inverse Voltage (break-down V)
 \uparrow In RB only

f.

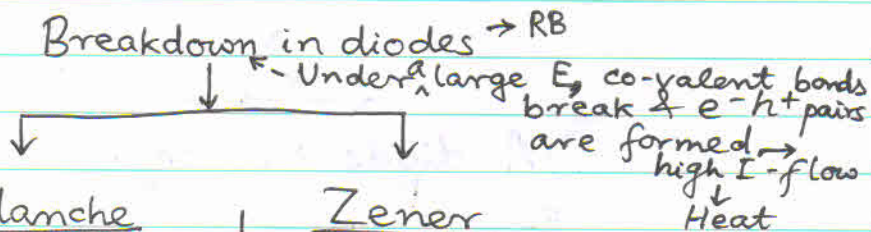

Avalanche
 A large RB Voltage causes carriers (e^- or h^+) to cross the depletion region with a high kinetic energy, which results in breaking of co-valent bonds & collision. Additional bonds are broken & more collision occurs.

Zener
 Due to sufficiently doped p-n diode & adequate RB voltage, tunneling of carriers occurs across the junction

PIV: Max. reverse bias (RB) voltage that may be applied across a diode safely without causing breakdown.

Avalanche


- 1) Permanent/unrecoverable breakdown
- 2) Occurs at a high RB voltage
- 3) Relevant to a p-n junction with low/medium doping
- 4) In simple diodes

Zener

- 1) Temporary/recoverable breakdown.
- 2) Occurs at a lower RB voltage.
- 3) For p-n junction with very high doping only.
- 4) In zener diodes.


g) Band Diagram

i) A diode without biasing:


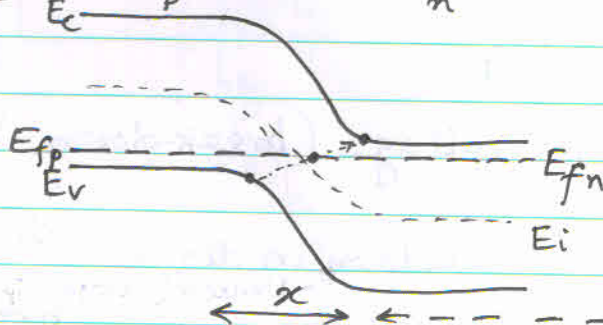


E_f : Fermi energy level \rightarrow Highest energy state of a carrier in a material at 0 Kelvin (Work done to add an e^- to a sys.)

ii) A diode in forward biased mode:

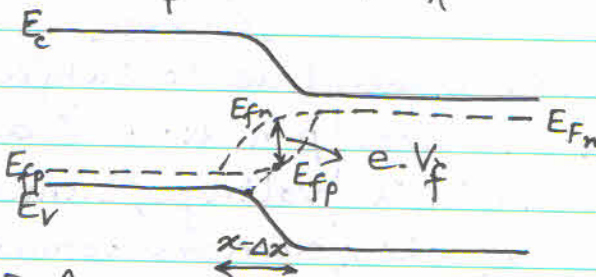


iii) A diode in reverse biased mode:

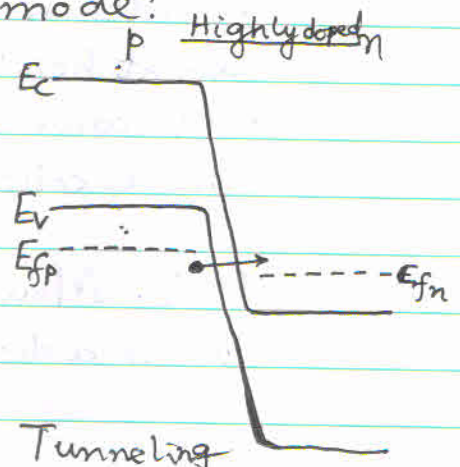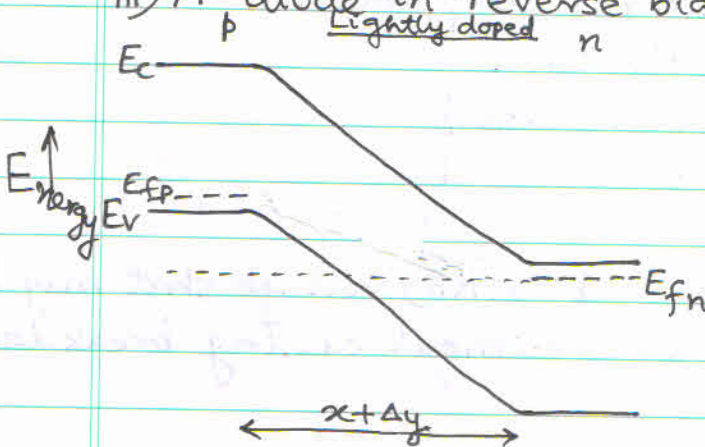


h. Diode as a switch:


i) Forward Bias: (FB)

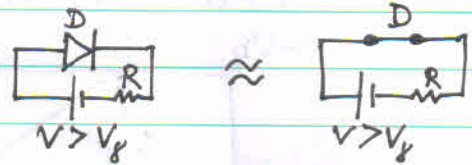



Reverse Bias: (Case 1) (RB)

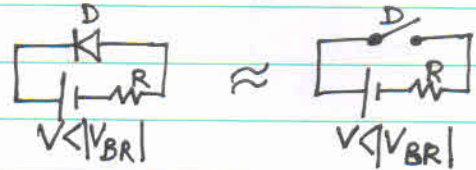



(Case 2)

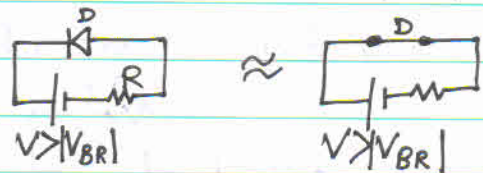

ii) FB & RB switching:

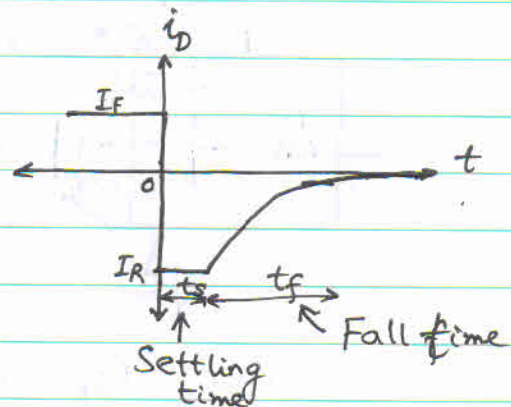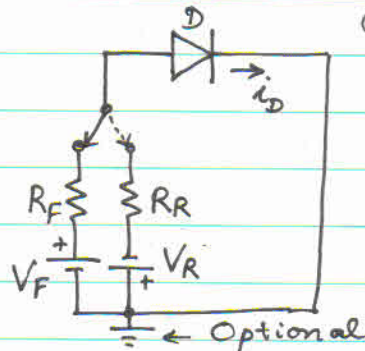


i) Load line concept \rightarrow DC & AC

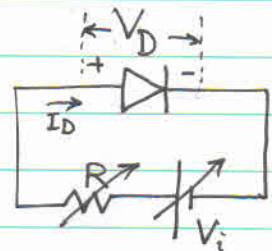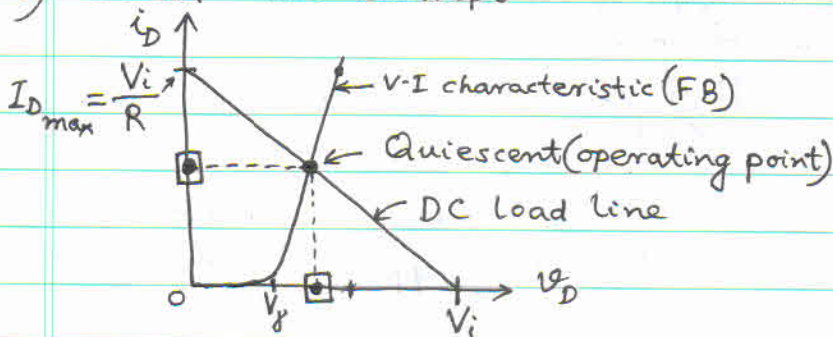


Load line equation: $V_i = I_D \cdot R + V_D$

where, $V_D = V_F + I_D \cdot r_f$
(power) $P_D = I_D \cdot V_D$

Load line in RB

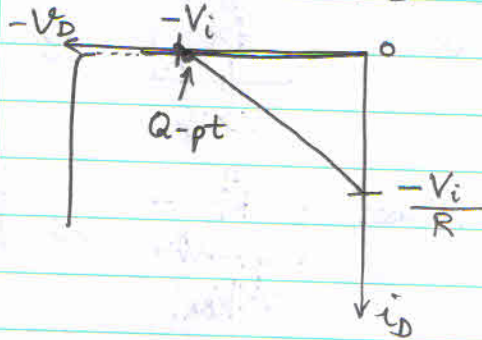

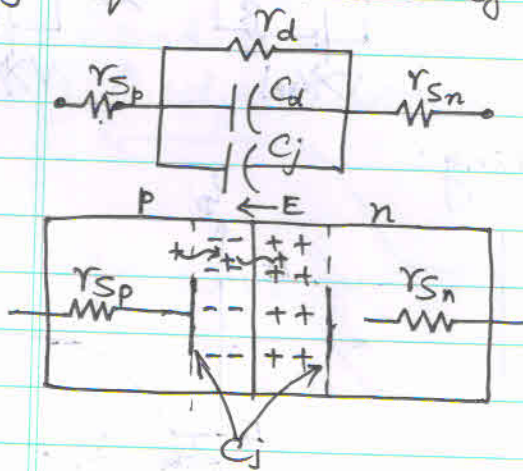j. Equivalent ckt. of a diode: Small signal



$$C_d = \frac{dQ}{dV_D} \quad (\text{Diffusion C})$$

r_{sx} = S-C resistance

C_j = Junction C

r_d = Diffusion R (junction)

$$r_f \approx r_{sp} + r_{sn} + r_d$$

k. Rectifiers: \rightarrow AC to DC converter


Half wave
(1-diode)


Full wave

2-diodes
(Center-tapped)

4-diodes
(Bridge)

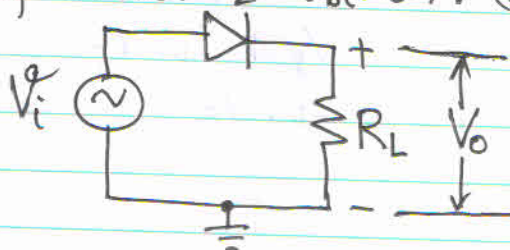
Half wave! $\leftarrow V_{bi} = 0.7V$ (Si)



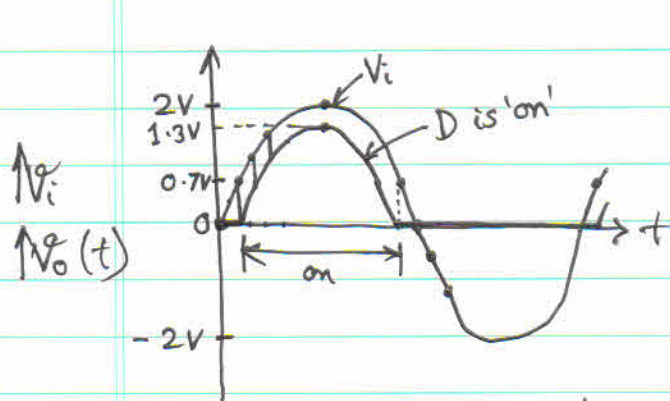

$$V_i = V_R + V_D \quad \rightarrow I_D \cdot R_D$$

$$V_i = V_o + V_D$$

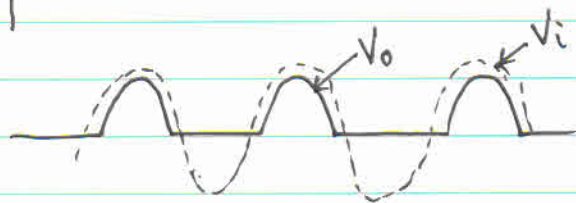

Transfer funcⁿ
curve

