

STUDIES ON SMALL SIGNAL CE AMPLIFIER

Trace the circuit of the CE-amplifier given in Part-1 of the board (see bottom side). Note down the component values and match them against Fig.1.

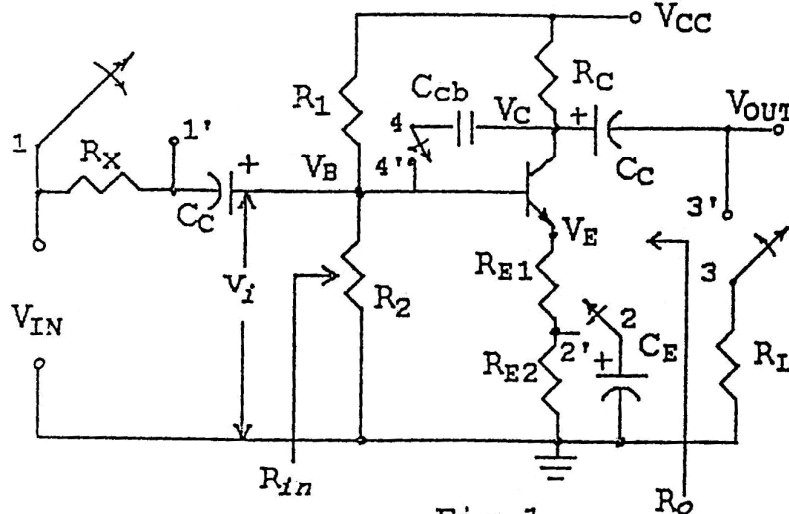


Fig.1

$R_1 = 47K$   
 $R_2 = 4.7K$   
 $R_C = 6.8K$   
 $R_{E1} = 0.33K$   
 $R_{E2} = 0.33K$   
 $R_X = 1K$   
 $R_L = 1K$   
 $C_C = 10mF$   
 $C_E = 100mF$   
 $C_{Cb} = 33pF$

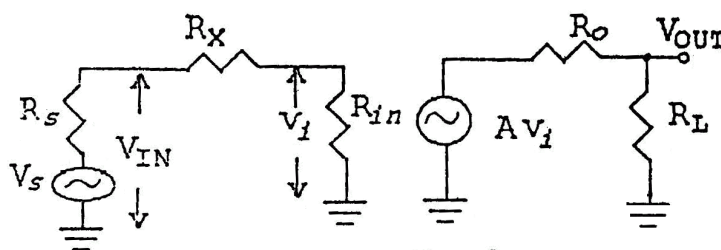


Fig.2

Measurement of DC conditions:

Supply +12 Volts  $V_{CC}$  to the amplifier circuit from the dc power supply. Remember to connect the power supply ground to the circuit ground! Measure  $V_B$ ,  $V_C$ , and  $V_E$ . Remember these voltages are measured with respect to the circuit ground. Knowing these and the resistance values calculate  $V_{BE}$ ,  $V_{CE}$ ,  $I_C$  and  $I_E$ . Determine whether the amplifier is biased in the active region and whether the Q-point is suitably located.

Measurement of Signal Handling Capacity:

- (i) Short the resistor  $R_X$  (by connecting a jumper wire across it; i.e. by joining the points 1 – 1' in Fig.1. Bypass  $R_{E2}$  by joining points 2 – 2' (thereby connecting  $C_E$  across  $R_{E2}$ ). Apply a mid-band frequency (say 4 KHz) sinusoidal voltage of about 100 mV p-p amplitude at  $V_{IN}$  and observe the output waveform on the CRO. Measure the gain. Increase the input voltage in steps and measure

the corresponding output voltages. Note the maximum input voltage  $V_{SM}$  for which the gain remains constant (or beyond which the  $V_{OUT}$  vs  $V_{IN}$  curve deviates from a straight line). This is the signal handling capacity. A quick (but crude) way of determining  $V_{SM}$  is to note the maximum input voltage for which the CRO displayed output voltage remains undistorted. Note when using CRO, it is convenient to measure the peak to peak voltage.

- (ii) Now connect the load  $R_L$  by joining points 3 – 3'. Measure  $V_{SM}$ . Compare this result with that of (i).

#### Measurement of Frequency Response:

- (i) Keep  $R_X$  shorted, load  $R_L$  and capacitor  $C_E$  connected. Choose a convenient sinusoidal  $V_{IN}$  (amplitude well below  $V_{SM}$ ). Vary the frequency over the range of your signal generator (say 100 Hz – 1000 KHz) in convenient steps. Record the corresponding  $V_{OUT}$  at each step. It is convenient to choose a constant amplitude  $V_{IN}$ . This may be ensured by noting the peak-to-peak amplitude in the CRO at each frequency step. Increase the number of steps in regions where change in  $V_{OUT}$  is large. Plot the frequency response of the amplifier (i.e. plot  $20\log(V_{OUT}/V_{IN})$  vs frequency). From the plot determine the lower and upper cutoff frequencies. These are the frequencies at which the ratio  $20\log(V_{OUT}/V_{IN})$  falls 3-dB below its maximum value.
- (ii) Now disconnect load  $R_L$  by removing the connection between the points 3-3'. Obtain the frequency response as in (i) above.
- (iii) Effect of  $C_E$ : Keep 1 – 1', 3 – 3' connected. Remove the connection between 2 – 2'. Measure the frequency response. Compare with (i) above. Finally, consider the case when point 2' is instead connected to the emitter (i.e.  $R_{E1}$  &  $R_{E2}$  are fully bypassed) and measure the frequency response. Compare this response with those above.
- (iv) Miller effect due to  $C_{cb}$ : Disconnect 1 – 1'. Connect 2 – 2' and 3 – 3'. Now measure the frequency response when  
 (a) terminals 4 – 4' are connected,  
 (b) terminals 4 – 4' are disconnected.  
 Compare the results of (a) and (b) above.

#### Measurement of Input Resistance in the Mid-Frequency Range:

Connect 1 – 1', 2 – 2' and disconnect 3 – 3', 4 – 4'. For a  $V_{IN}$  having amplitude well below the signal capacity  $V_{SM}$  and frequency well within the midfrequency range, measure the output voltage  $V_{OUT}|_O$ . [From Fig.2:  $V_{OUT}|_O = A \cdot V_S \cdot R_{IN} / (R_{IN} + R_S)$ ]. Now disconnect 1 – 1' and measure the output voltage  $V_{OUT}|_{R_X}$ . [From Fig.2:  $V_{OUT}|_{R_X} = A \cdot V_S \cdot R_{IN} / (R_{IN} + R_S + R_X)$ ].

$$\text{Then the input resistance is given by: } R_{IN} = \frac{R_X \cdot V_{out}|_{R_X}}{V_{out}|_O - V_{out}|_{R_X}} - R_S$$

#### Measurement of Output Resistance in the Mid-Frequency Range.

Connect 1 – 1', 2 – 2', 3 – 3' and disconnect 4 – 4'. Then for a  $V_{IN}$  well below the signal handling capacity  $V_{SM}$  and frequency well within the midfrequency range let the measured output voltage be  $V_{OUT}|_{R_L}$ . [From Fig.2:  $V_{OUT}|_{R_L} = A \cdot V_{IN} \cdot R_L / (R_O + R_S)$ ].

Now disconnect 3 – 3'. Then the measured output voltage is  $V_{OUT}|_{\infty}$ . [From Fig.2:  $V_{OUT}|_{\infty} = A \cdot V_{IN}$ ]. Then the output resistance is given by

$$R_{OUT} = R_L \cdot \frac{V_{OUT}|_{\infty} - V_{OUT}|_{R_L}}{V_{OUT}|_{R_L}}$$

