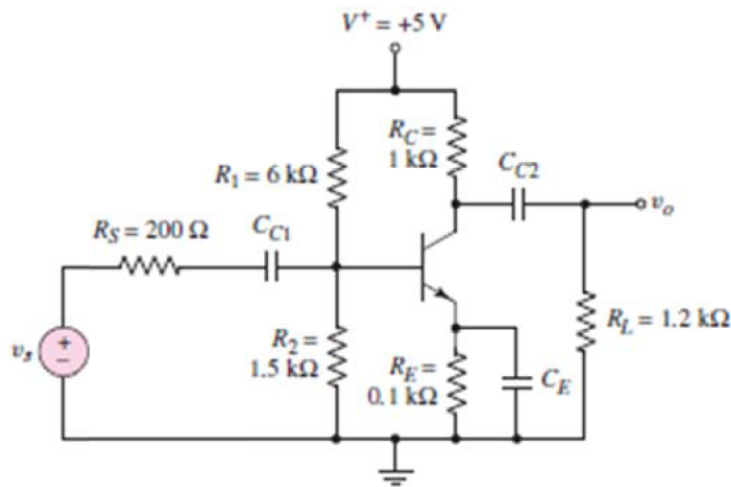


14. Refer to the BJT amplifier below. Determine the q-point values, small signal hybrid- π parameters and small signal voltage gain ($A_v = v_o/v_i$), if $\beta = 180$ and $r_o = \infty$.



a.

$$R_{TH} = R_1 \parallel R_2 = 6 \parallel 1.5 = 1.2 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V^+ = \left(\frac{1.5}{1.5 + 6} \right) (5) = 1.0 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE}(\text{on})}{R_{TH} + (1 + \beta) R_E} = \frac{1.0 - 0.7}{1.2 + (181)(0.1)} = 0.0155 \text{ mA}$$

$$I_{CQ} = 2.80 \text{ mA}, I_{EQ} = 2.81$$

$$V_{CEQ} = V^+ - I_{CQ} R_C - I_{EQ} R_E \\ = 5 - (2.8)(1) - (2.81)(0.1) \Rightarrow V_{CEQ} = 1.92 \text{ V}$$

b.

$$r_p = \frac{(180)(0.026)}{2.80} \Rightarrow r_p = 1.67 \text{ k}\Omega$$

$$g_m = \frac{2.80}{0.026} \Rightarrow g_m = 108 \text{ mA/V}, r_o = \infty$$


(c)

$$A_v = 2 g_m \left(\frac{R_1 \parallel R_2 \parallel r_p}{R_1 \parallel R_2 \parallel r_p + R_S} \right) (R_C \parallel R_L)$$

$$R_1 \parallel R_2 \parallel r_p = 6 \parallel 1.5 \parallel 1.67 = 0.698 \text{ k}\Omega$$

$$A_v = \blacksquare (108) \left(\frac{0.698}{0.698 + 0.2} \right) (1 \parallel 1.2) \Rightarrow A_v = \blacksquare 45.8$$

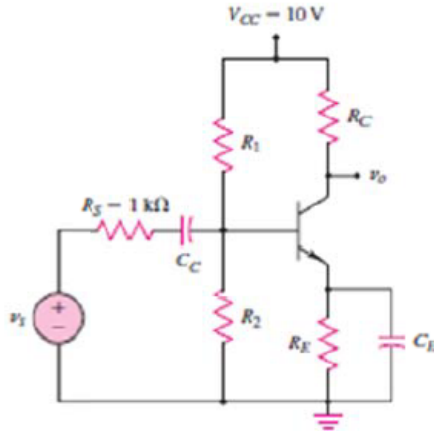15. Design a single stage BJT amplifier for a microphone of $1\text{k}\Omega$ series resistance. The microphone produces 10 mV (rms) and the required output voltage is 0.5V (rms) . Calculate the component values that are used in the circuit while assuming suitable device parameters (eg. β).



Assume an npn transistor with $\beta = 100$ and $V_A = \infty$. Let $V_{CC} = 10\text{ V}$.

$$|A_v| = \frac{0.5}{0.01} = 50$$

Bias at $I_{CQ} = 1\text{ mA}$ and let $R_E = 1\text{ k}\Omega$

For a bias stable circuit

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(1) = 10.1\text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1}(10.1)(10) = \frac{101}{R_1}$$

$$I_{BQ} = \frac{1}{100} = 0.01\text{ mA}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E$$

$$\frac{101}{R_1} = (0.01)(10.1) + 0.7 + (101)(0.01)(1)$$

which yields $R_1 = 55.8\text{ k}\Omega$ and $R_2 = 12.3\text{ k}\Omega$

Now

$$r_p = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$g_m = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

$$V_o = -g_m V_p R_c$$

$$\text{where } V_p = \left(\frac{R_1 R_2 r_p}{R_1 R_2 r_p + R_s} \right) V_i = \left(\frac{10.1 \cdot 2.6}{10.1 \cdot 2.6 + 1} \right) V_i$$

$$\text{or } V_p = 0.674 V_i$$

$$\text{Then } A_v = \frac{V_o}{V_i} = -(0.674) g_m R_c = -(0.674)(38.46) R_c = -50$$

$$\text{which yields } R_c = 1.93 \text{ k}\Omega$$

With this R_c , the dc bias is OK.

Finish Design, Set $R_c = 2 \text{ K}$ $R_g = 1 \text{ K}$

$$R_1 = 56 \text{ K}$$

$$R_2 = 12 \text{ K}$$

$$R_{TH} = R_1 \parallel R_2 = 9.88 \text{ K}$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{12}{12 + 56} \right) (10) = 1.765 \text{ V}$$

$$I_{BQ} = \frac{1.765 - 0.7}{9.88 + (101)(1)} = 9.60 \text{ }\mu\text{A}$$

$$I_{CQ} = 0.9605 \text{ mA}$$

$$r_\pi = \frac{(100)(0.026)}{0.9605} = 2.707 \text{ K} \quad g_m = \frac{0.9605}{0.026} = 36.94$$


$$R_{TH} \parallel r_\pi = 2.125 \text{ K}$$

$$V_x = \left(\frac{R_{TH} \parallel r_\pi}{R_{TH} \parallel r_\pi + R_s} \right) V_i = \left(\frac{2.125}{2.125 + 1} \right) V_i = (0.680) V_i$$


$$A_v = -(0.680) g_m R_c = -(0.680)(36.94)(2) = -50.2$$

This meets the design specifications.

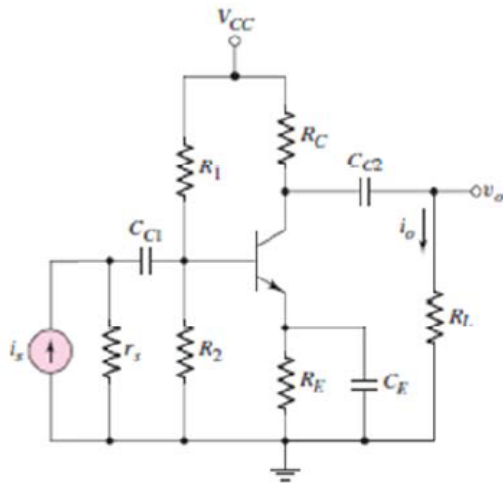16. Consider the circuit shown below. Let, $R_1//R_2=5k$, $r_s=\infty$, $R_C=R_L=1k\Omega$, $I_{CQ}=5mA$, $\beta_o=200$, $V_A=\infty$, $C_\mu=5pF$ and $f_T=250$ MHz. Find the upper cut-off frequency for a small signal current gain.



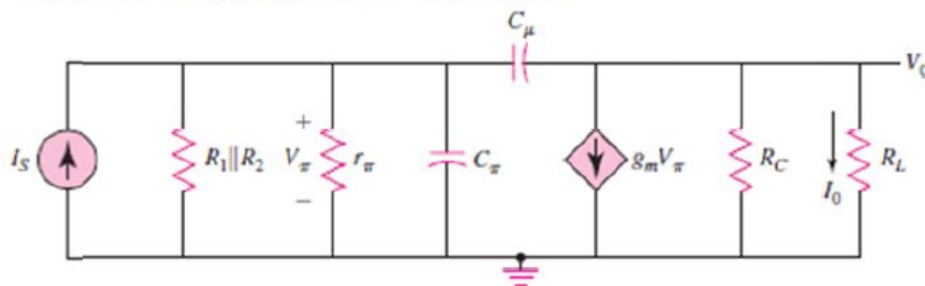High Freq. $\Rightarrow C_{C1}, C_{C2}, C_E \rightarrow$ short circuits



$$g_m = \frac{I_{CQ}}{V_T} = \frac{5}{0.026} = 192.3 \text{ mA/V}$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} \Rightarrow 250 \times 10^6 = \frac{192 \times 10^{-3}}{2\pi(C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = 122.4 \text{ pF} \Rightarrow C_\mu = 5 \text{ pF}, C_\pi = 117.4 \text{ pF}$$

$$C_M = C_\mu(1 + g_m(R_C \parallel R_L))$$

$$= 5[1 + (192.3)(1 \parallel 1)] \Rightarrow C_M = 485.8 \text{ pF}$$

$$C_i = C_\pi + C_M = 117 + 485 = 603 \text{ pF}$$

$$r_\pi = \frac{(200)(0.026)}{5} = 1.04 \text{ k}\Omega$$

$$R_{eq} = R_1 \parallel R_2 \parallel r_\pi = 5 \parallel 1.04 = 0.861 \text{ k}\Omega$$

$$\tau = R_{eq} \cdot C_i = (0.861 \times 10^3)(603 \times 10^{-12})$$

$$= 5.19 \times 10^{-7} \text{ s}$$

$$f = \frac{1}{2\pi\tau} = \frac{1}{2\pi(5.19 \times 10^{-7})} \Rightarrow f = 307 \text{ kHz}$$